

# Noise

*David Johns and Ken Martin  
University of Toronto  
(johns@eecg.toronto.edu)  
(martin@eecg.toronto.edu)*



## Interference Noise

- Unwanted interaction between circuit and outside world
- May or may not be random
- Examples: power supply noise, capacitive coupling

### Improvement by ...

- Reduced by careful wiring or layout
  
- These notes do not deal with interference noise.



## Inherent Noise


- Random noise — can be reduced but NEVER eliminated
- Examples: thermal, shot, and flicker

### Improvement by ...

- Not strongly affected by wiring or layout
  - Reduced by proper circuit DESIGN.
- 
- These notes discuss noise analysis and inherent noise sources.



## Time-Domain Analysis

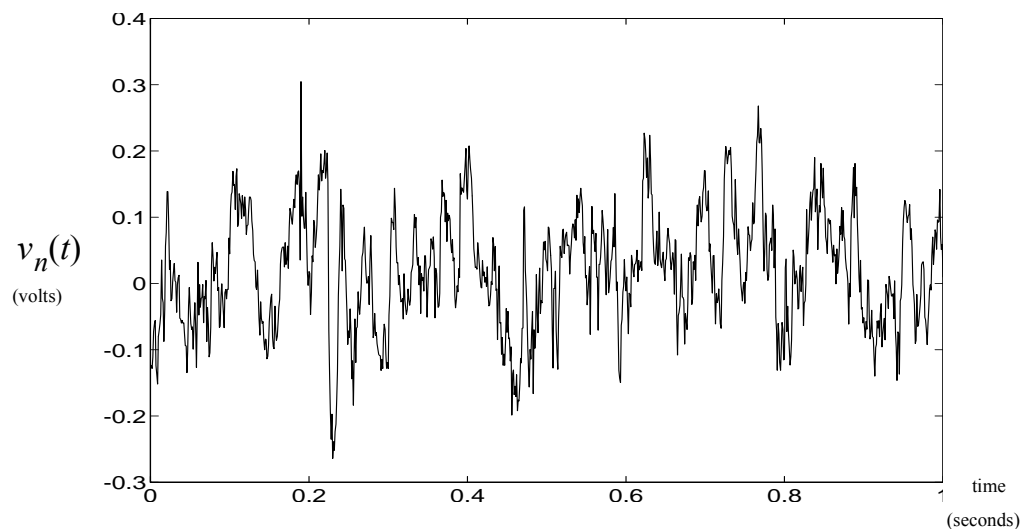

- ***Assume all noise signals have zero mean***



## RMS Value

$$V_{n(rms)} \equiv \left[ \frac{1}{T} \int_0^T v_n^2(t) dt \right]^{1/2} \quad (1)$$

- $T$  — suitable averaging time interval
- Indicates **normalized noise power**.
- If  $v_n(t)$  applied to  $1\Omega$  resistor, average power dissipated,  $P_{diss}$ ,

$$P_{diss} = \frac{V_{n(rms)}^2}{1\Omega} = V_{n(rms)}^2 \quad (2)$$



## SNR

$$\text{SNR} \equiv 10 \log \left[ \frac{\text{signal power}}{\text{noise power}} \right] \quad (3)$$

- If signal node has normalized signal power of  $V_{x(rms)}^2$ , and noise power of  $V_{n(rms)}^2$ ,

$$\text{SNR} = 10 \log \left[ \frac{V_{x(rms)}^2}{V_{n(rms)}^2} \right] = 20 \log \left[ \frac{V_{x(rms)}}{V_{n(rms)}} \right] \quad (4)$$

- When mean-squared values of noise and signal are same,  $\text{SNR} = 0\text{dB}$ .



## Units of dBm

- Often useful to know signal's power in dB on absolute scale.
- With dBm, all power levels referenced 1mW.
- 1mW signal corresponds to 0 dBm
- $1\mu\text{W}$  signal corresponds to -30dBm

### What if only voltage measured (not power)?

- If voltage measured — reference level to equiv power dissipated if voltage applied to  $50\ \Omega$  resistor
- Also, can reference it to  $75\ \Omega$  resistor



## dBm Example

- Find rms voltage of 0 dBm signal ( $50\ \Omega$  reference)
- What is level in dBm of a 2 volt rms signal?
- 0 dBm signal ( $50\ \Omega$  reference) implies

$$V_{(rms)} = \sqrt{(50\ \Omega) \times 1\text{mW}} = 0.2236 \quad (5)$$


- Thus, a 2 volt (rms) signal corresponds to

$$20 \times \log\left(\frac{2.0}{0.2236}\right) = 19\ \text{dBm} \quad (6)$$


- Would dissipate  $2^2/50 = 80\ \text{mW}$  across a  $50\ \Omega$  resistor
- 80 mW corresponds to  $10\log(80) = 19\ \text{dBm}$



## Noise Summation

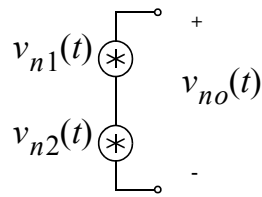

**Voltage**

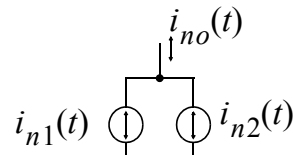

**Current**

$$v_{no}(t) = v_{n1}(t) + v_{n2}(t) \quad (7)$$

$$V_{no(rms)}^2 = \frac{1}{T} \int_0^T [v_{n1}(t) + v_{n2}(t)]^2 dt \quad (8)$$

$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2 + \frac{2}{T} \int_0^T v_{n1}(t)v_{n2}(t) dt \quad (9)$$



## Correlation

- Last term relates correlation between two signals
- Define correlation coefficient,  $C$ ,

$$C \equiv \frac{\frac{1}{T} \int_0^T v_{n1}(t)v_{n2}(t) dt}{V_{n1(rms)}V_{n2(rms)}} \quad (10)$$

$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2 + 2CV_{n1(rms)}V_{n2(rms)} \quad (11)$$

- Correlation always satisfies  $-1 \leq C \leq 1$
- $C = +1$  — fully-correlated in-phase (0 degrees)
- $C = -1$  — fully-correlated out-of-phase (180 degrees)
- $C = 0$  — uncorrelated (90 degrees)



## Uncorrelated Signals

- ***In case of two uncorrelated signals, mean-squared value of sum given by***

$$V_{no(rms)}^2 = V_{n1(rms)}^2 + V_{n2(rms)}^2 \quad (12)$$

- Two rms values add as though they were vectors at right angles

### When fully correlated

$$V_{no(rms)}^2 = (V_{n1(rms)} \pm V_{n2(rms)})^2 \quad (13)$$

- sign is determined by whether signals are in or out of phase
- Here, rms values add linearly (aligned vectors)



## Noise Summation Example

- $V_{n1(rms)} = 10\mu V$ ,  $V_{n2(rms)} = 5\mu V$ , then

$$V_{no(rms)}^2 = (10^2 + 5^2) = 125 \quad (14)$$

which results in  $V_{no(rms)} = 11.2\mu V$ .

- Note that ***eliminating***  $V_{n2(rms)}$  noise source same as ***reducing***  $V_{n1(rms)} = 8.7\mu V$  (i.e. ***reducing by 13%***)!

### Important Moral

- ***To reduce overall noise, concentrate on large noise signals.***




## Frequency-Domain Analysis

- With deterministic signals, frequency-domain techniques are useful.
- Same true for dealing with random signals like noise.
- This section presents frequency-domain techniques for dealing with noise (or random) signals.



## Spectral Density

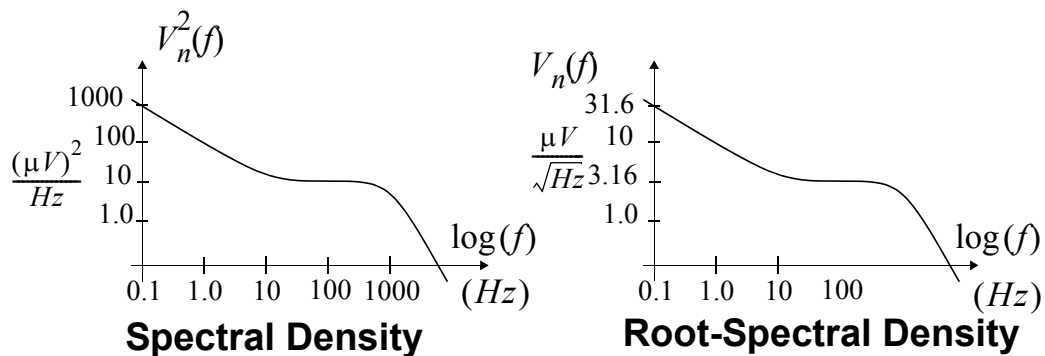

- Periodic waveforms have their power at distinct frequencies.
- Random signals have their power spread out over the frequency spectrum.



## Spectral Density

### Spectral Density $V_n^2(f)$

- Average normalized power over a 1 hertz bandwidth
- Units are volts-squared/hertz

### Root-Spectral Density $V_n(f)$

- Square root of vertical axis (freq axis unchanged)
- Units are volts/root-hertz (i.e.  $V/\sqrt{\text{Hz}}$ ).


### Total Power

$$V_{n(rms)}^2 = \int_0^{\infty} V_n^2(f) df \quad (15)$$

- Above is a one-sided definition (i.e. all power at positive frequencies)



## Root-Spectral Density Example

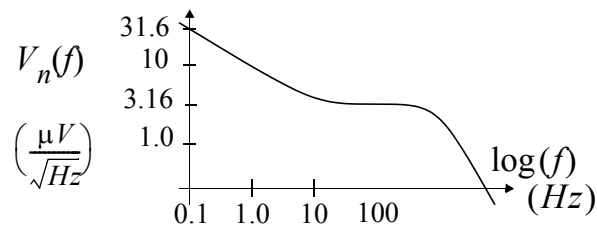

- Around 100 Hz,  $V_n(f) = \sqrt{10} \mu\text{V}/\sqrt{\text{Hz}}$
- If measurement used RBW = 30 Hz, measured rms

$$\sqrt{10} \times \sqrt{30} = \sqrt{300} \mu\text{V} \quad (16)$$


- If measurement used RBW = 0.1 Hz, measured rms

$$\sqrt{10} \times \sqrt{0.1} = 1 \mu\text{V} \quad (17)$$





## White Noise

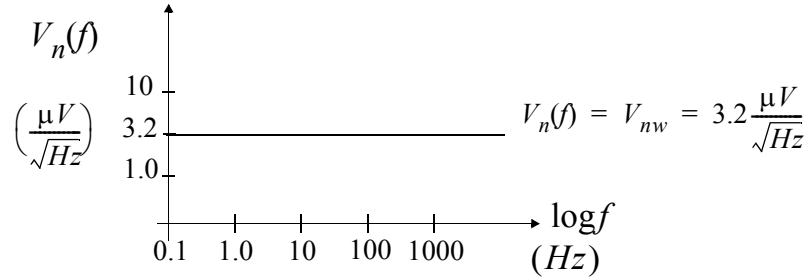


- Noise signal is “white” if a constant spectral density

$$V_n(f) = V_{nw} \quad (18)$$

where  $V_{nw}$  is a constant value



## 1/f Noise

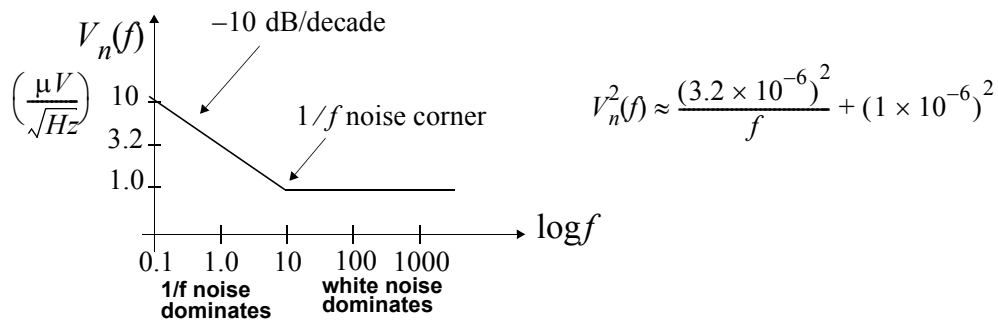

$$V_n^2(f) = k_v^2 / f \quad (k_v \text{ is a constant}) \quad (19)$$

- In terms of root-spectral density


$$V_n(f) = k_v / \sqrt{f} \quad (20)$$

Falls off at -10 db/decade due to  $\sqrt{f}$

- Also called **flicker** or **pink** noise.



## Filtered Noise




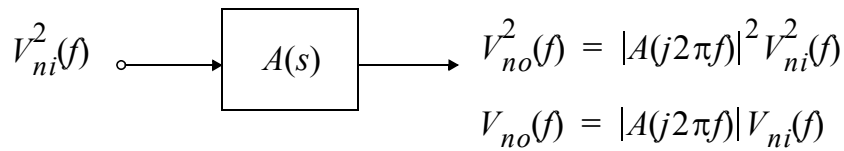


- Output only a function of magnitude of transfer-function **and not its phase**
- Can always apply an allpass filter without affecting noise performance.
- Total output mean-squared value is

$$V_{no(rms)}^2 = \int_0^{\infty} |A(j2\pi f)|^2 V_{ni}^2(f) df \quad (21)$$



## Noise Example

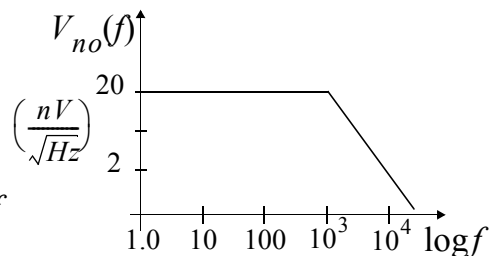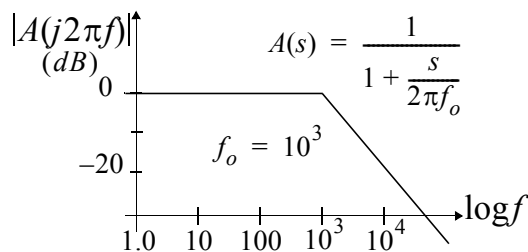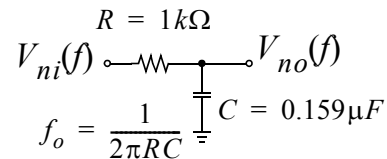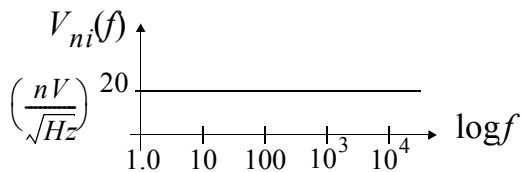

## Noise Example

- From dc to 100 kHz of input signal

$$V_{ni(rms)}^2 = \int_0^{10^5} 20^2 df = 4 \times 10^7 (nV)^2 = (6.3 \mu V \text{ rms})^2 \quad (22)$$

- Note: for this simple case,

$$V_{ni(rms)}^2 = 20 \text{ nV} / \sqrt{\text{Hz}} \times \sqrt{100\text{kHz}} = (6.3 \mu V \text{ rms})^2 \quad (23)$$

- For the filtered signal,  $V_{no}(f)$ ,

$$V_{no}(f) = \frac{20 \times 10^{-9}}{\sqrt{1 + \left(\frac{f}{f_o}\right)^2}} \quad (24)$$



## Noise Example


- Between dc and 100kHz

$$\begin{aligned} V_{no(rms)}^2 &= \int_0^{10^5} \frac{20^2}{1 + \left(\frac{f}{f_o}\right)^2} df = 20^2 f_o \operatorname{atan}\left(\frac{f}{f_o}\right) \Big|_0^{10^5} \\ &= 6.24 \times 10^5 (nV)^2 = (0.79 \mu V \text{ rms})^2 \end{aligned} \quad (25)$$

- Noise rms value of  $V_{no}(f)$  is almost 1/10 that of  $V_{ni}(f)$  since high frequency noise above 1kHz was filtered.
- ***Don't design for larger bandwidths than required otherwise noise performance suffers.***



## Sum of Filtered Noise

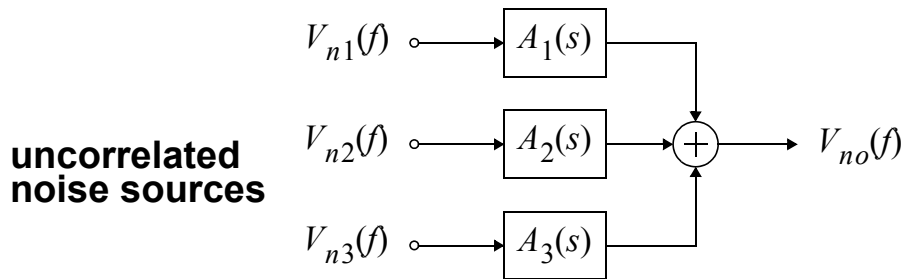

- If filter inputs are uncorrelated, filter outputs are also uncorrelated
- Can show


$$V_{no}^2(f) = \sum_{i=1,2,3} |A_i(j2\pi f)|^2 V_{ni}^2(f) \quad (26)$$



## Noise Bandwidth

- Equal to the frequency span of a brickwall filter having the same output noise rms value when white noise is applied to each

### Example

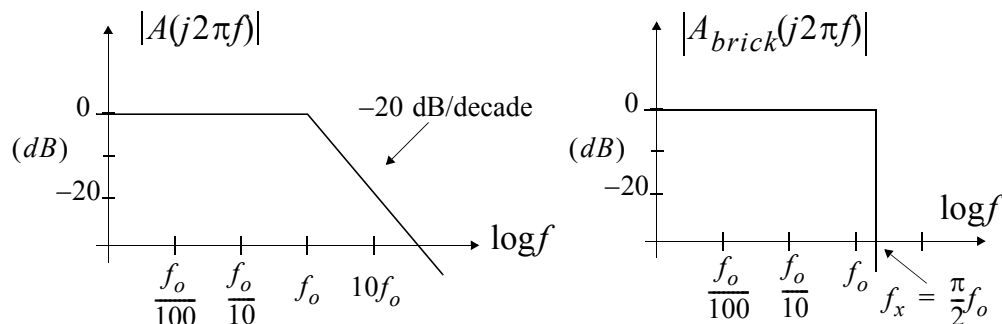

- Noise bandwidth of a 1<sup>st</sup>-order filter is  $\frac{\pi}{2}f_o$



## Noise Bandwidth

- Advantage — total output noise is easily calculated for white noise input.
- If spectral density is  $V_{nw}$  volts/root-Hz and noise bandwidth is  $f_x$ , then

$$V_{no(rms)}^2 = V_{nw}^2 f_x \quad (27)$$

### Example

- A white noise input of  $100 \text{ nV}/\sqrt{\text{Hz}}$  applied to a 1'st order filter with 3 dB frequency of 1 MHz

$$V_{no(rms)} = 100 \times 10^{-9} \times \sqrt{\frac{\pi}{2}} \times 10^6$$
$$V_{no(rms)} = 125 \text{ } \mu\text{V} \quad (28)$$




## 1/f Noise Tangent Principle

- Method to determine the frequency region(s) that contributes the dominant noise
- Lower a 1/f noise line until it touches the spectral density curve
- The total noise can be approximated by the noise in the vicinity of the 1/f line
- Works because a curve proportional to  $1/x$  results in equal power over each decade of frequency



## 1/f Tangent Example

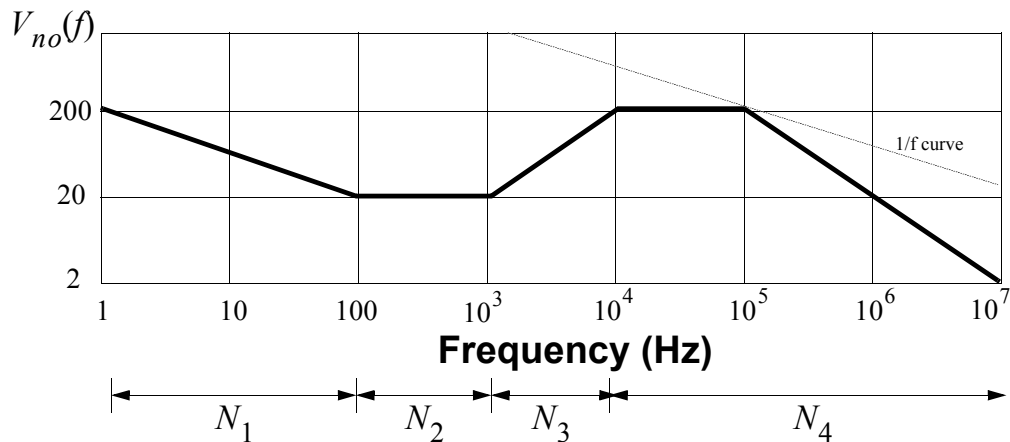

- Consider root-spectral noise density shown above



## 1/f Tangent Example

$$N_1^2 = \int_1^{100} \frac{200^2}{f} df = 200^2 \ln(f) \Big|_1^{100} = 1.84 \times 10^5 (nV)^2 \quad (29)$$

$$N_2^2 = \int_{100}^{10^3} 20^2 df = 20^2 f \Big|_{100}^{10^3} = 3.6 \times 10^5 (nV)^2 \quad (30)$$

$$N_3^2 = \int_{10^3}^{10^4} \frac{20^2 f^2}{(10^3)^2} df = \left(\frac{20}{10^3}\right)^2 \left[ \frac{1}{3} f^3 \Big|_{10^3}^{10^4} \right] = 1.33 \times 10^8 (nV)^2 \quad (31)$$

$$N_4^2 = \int_{10^4}^{\infty} \frac{200^2}{10^4 \left(1 + \left(\frac{f}{10^5}\right)^2\right)} df = \int_0^{\infty} \frac{200^2}{1 + \left(\frac{f}{10^5}\right)^2} df - \int_0^{10^4} 200^2 df \quad (32)$$

$$= 200^2 \left(\frac{\pi}{2}\right) 10^5 - (200^2)(10^4) = 5.88 \times 10^9 (nV)^2$$



## 1/f Tangent Example

- The total output noise is estimated to be

$$V_{no(rms)} = (N_1^2 + N_2^2 + N_3^2 + N_4^2)^{1/2} = 77.5 \mu V \text{ rms} \quad (33)$$

- But ...

$$N_4 = 76.7 \mu V \text{ rms} \quad (34)$$

- Need only have found the noise in the vicinity where the 1/f tangent touches noise curve.
- **Note:** if noise curve is parallel to 1/f tangent for a wide range of frequencies, then also sum that region.



## Noise Models for Circuit Elements

- Three main sources of noise:

### Thermal Noise

- Due to thermal excitation of charge carriers.
- Appears as white spectral density

### Shot Noise

- Due to dc bias current being pulses of carriers
- Dependent of dc bias current and is white.


### Flicker Noise

- Due to traps in semiconductors
- Has a 1/f spectral density
- Significant in MOS transistors at low frequencies.



## Resistor Noise

- Thermal noise — white spectral density

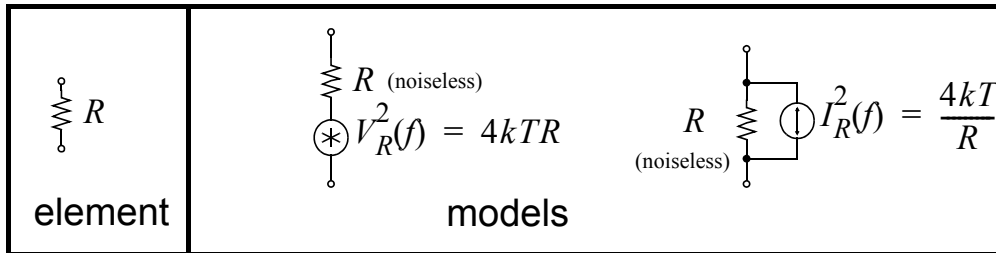


- $k$  is Boltzmann's constant =  $1.38 \times 10^{-23} \text{ JK}^{-1}$
- $T$  is the temperature in degrees Kelvin
- Can also write

$$V_R(f) = \sqrt{\frac{R}{1k}} \times 4.06 \text{ nV}/\sqrt{\text{Hz}} \quad \text{for } 27^\circ\text{C} \quad (35)$$



## Diodes

- Shot noise — white spectral density

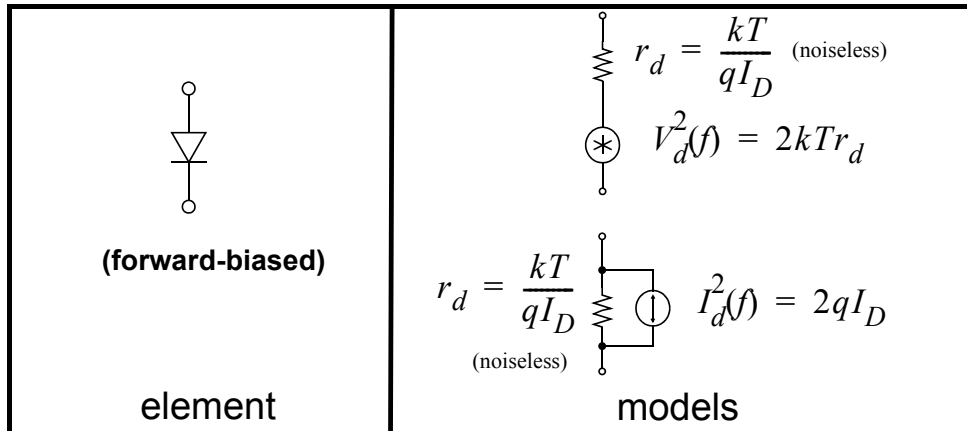


- $q$  is one electronic charge =  $1.6 \times 10^{-19} \text{ C}$
- $I_D$  is the dc bias current through the diode




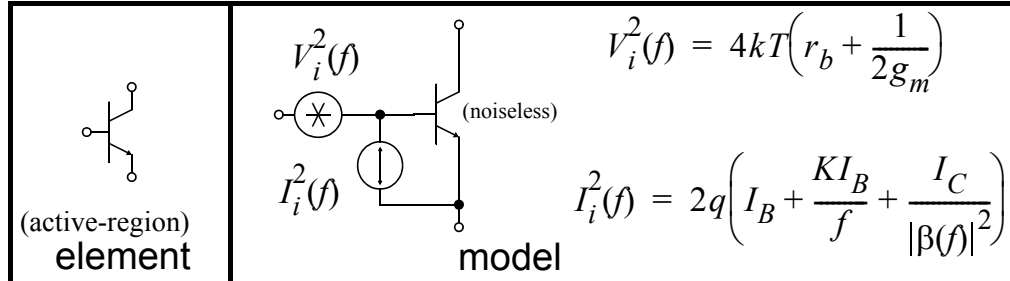
## Bipolar Transistors

- Shot noise of collector and base currents
- Flicker noise due to base current
- Thermal noise due to base resistance




- $V_i(f)$  has base resistance thermal noise plus collector shot noise referred back
- $I_i(f)$  has base shot noise, base flicker noise plus collector shot noise referred back


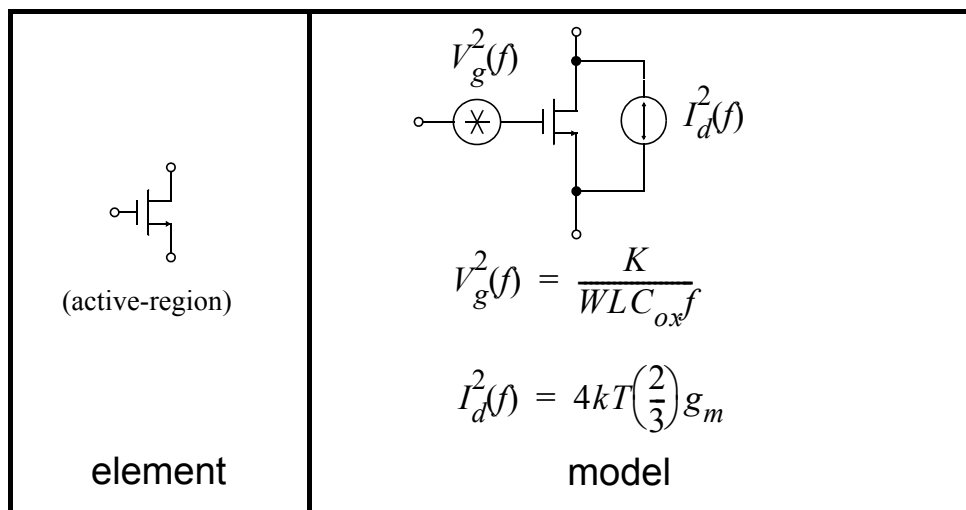
## MOSFETS

- Flicker noise at gate
- Thermal noise in channel



## MOSFET Flicker (1/f) Noise

$$V_g^2(f) = \frac{K}{WLC_{ox}f} \quad (36)$$

- $K$  dependent on device characteristics, varies widely.
- $W$  &  $L$  — Transistor's width and length
- $C_{ox}$  — gate-capacitance/unit area
- **Flicker noise is inversely proportional to the transistor area,  $WL$ .**
- 1/f noise is extremely important in MOSFET circuits as it can dominate at low-frequencies
- Typically p-channel transistors have less noise since holes are less likely to be trapped.



## MOSFET Thermal Noise



- Due to resistive nature of channel
- In triode region, noise would be  $I_d^2(f) = (4kT)/r_{ds}$  where  $r_{ds}$  is the channel resistance
- In active region, channel is not homogeneous and total noise is found by integration

$$I_d^2(f) = 4kT\left(\frac{2}{3}\right)g_m \quad (37)$$

for the case  $V_{DS} = V_{GS} - V_T$





## Low-Moderate Frequency MOSFET Model

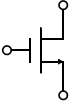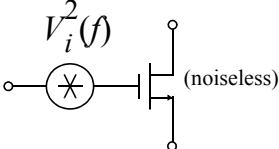 (active-region)  element	 $V_i^2(f) = 4kT \left( \frac{2}{3} \right) \frac{1}{g_m} + \frac{K}{WLC_{ox}f}$ model
---	--

- Can lump thermal noise plus flicker noise as an input voltage noise source at low to moderate frequencies.
- At high frequencies, gate current can be appreciable due to capacitive coupling.




## Opamps

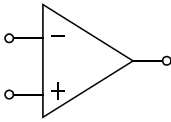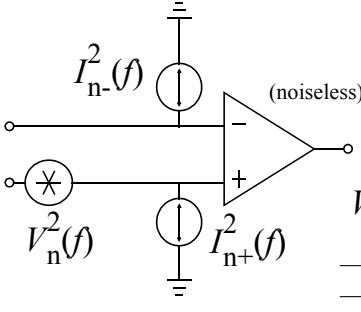  element	 $V_n(f), I_{n-}(f), I_{n+}(f)$ <p>— values depend on opamp — typically, all uncorrelated.</p> model
--	---

- Modelled as 3 uncorrelated input-referred noise sources.
- Current sources often ignored in MOSFET opamps




## Why 3 Noise Sources?

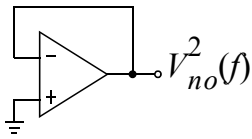


$$V_n(f) \text{ ignored} \Rightarrow V_{no}^2 = 0$$

$$\text{Actual } V_{no}^2 = V_n^2$$

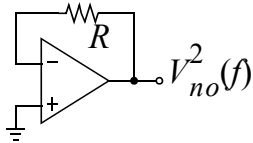

$$I_{n-}(f) \text{ ignored} \Rightarrow V_{no}^2 = V_n^2$$
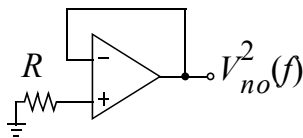
$$\text{Actual } V_{no}^2 = V_n^2 + (I_{n-}R)^2$$




$$I_{n+}(f) \text{ ignored} \Rightarrow V_{no}^2 = V_n^2$$

$$\text{Actual } V_{no}^2 = V_n^2 + (I_{n+}R)^2$$


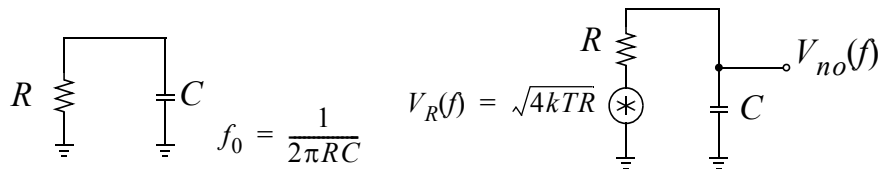
## Capacitors

- Capacitors and inductors do not generate any noise but ... they accumulate noise.
- Capacitor noise mean-squared value equals  $kT/C$  when connected to an arbitrary resistor value.



- Noise bandwidth equals  $(\pi/2)f_o$

$$V_{no(rms)}^2 = V_R^2(f) \left(\frac{\pi}{2}\right) f_o = (4kTR) \left(\frac{\pi}{2}\right) \left(\frac{1}{2\pi RC}\right)$$

$$V_{no(rms)}^2 = \frac{kT}{C} \tag{38}$$



## Capacitor Noise Example

- At 300 °K, what capacitor size is needed to have 96dB dynamic range with 1 V<sub>rms</sub> signal levels.
- Noise allowed:

$$V_{n(rms)} = \frac{1V}{10^{96/20}} = 15.8 \mu V_{rms} \quad (39)$$

- Therefore


$$C = \frac{kT}{V_{n(rms)}^2} = 16.6pF \quad (40)$$

- This min capacitor size determines max resistance size to achieve a given time-constant.



## Sampled Signal Noise


- Consider basic sample-and-hold circuit

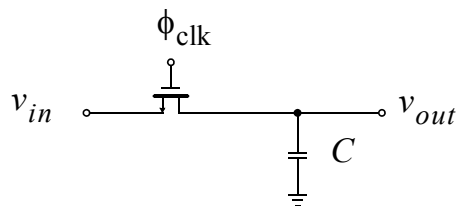


- 
- When  $\phi_{clk}$  goes low, noise as well as signal is held on  $C$ . — an rms noise voltage of  $\sqrt{kT/C}$ .
- Does not depend on sampling rate and is independent from sample to sample.
- Can use “oversampling” to reduce effective noise.
- Sample, say 1000 times, and average results.



## Opamp Example

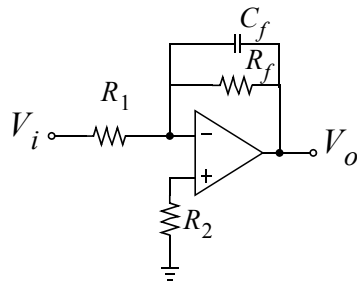

circuit

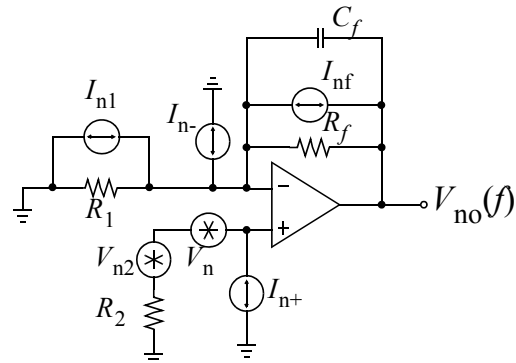

equivalent noise circuit

- Use superposition — noise sources uncorrelated
- Consider  $I_{n1}$ ,  $I_{nf}$  and  $I_{n-}$  causing  $V_{no1}^2(f)$

$$V_{no1}^2(f) = (I_{n1}^2(f) + I_{nf}^2(f) + I_{n-}^2(f)) \left| \frac{R_f}{1 + j2\pi f R_f C_f} \right|^2 \quad (41)$$



## Opamp Example

- Consider  $I_{n+}$ ,  $V_{n2}$  and  $V_n$  causing  $V_{no2}^2(f)$

$$V_{no2}^2(f) = (I_{n+}^2(f) R_2^2 + V_{n2}^2(f) + V_n^2(f)) \left| 1 + \frac{R_f / R_1}{1 + j2\pi f C_f R_f} \right|^2 \quad (42)$$

- If  $R_f \ll R_1$  then gain  $\cong 1$  for all freq and ideal opamp would result in infinite noise — practical opamp will lowpass filter noise at opamp  $f_t$ .
- If  $R_f \gg R_1$ , low freq gain  $\cong R_f / R_1$  and  $f_{3dB} = 1 / (2\pi R_f C_f)$  similar to noise at negative input — however, gain falls to unity until opamp  $f_t$ .

$$\text{Total noise: } V_{no(\text{rms})}^2 = V_{no1(\text{rms})}^2 + V_{no2(\text{rms})}^2 \quad (43)$$



## Numerical Example

- Estimate total output noise rms value for a 10kHz lowpass filter when  $C_f = 160\text{pF}$ ,  $R_f = 100\text{k}$ ,  $R_1 = 10\text{k}$ , and  $R_2 = 9.1\text{k}$ .
- Assume  $V_n(f) = 20\text{ nV}/\sqrt{\text{Hz}}$ ,  $I_n(f) = 0.6\text{ pA}/\sqrt{\text{Hz}}$  opamp's  $f_t = 5\text{ MHz}$ .
- Assuming room temperature,

$$I_{\text{nf}} = 0.406\text{ pA}/\sqrt{\text{Hz}} \quad (44)$$

$$I_{\text{n1}} = 1.28\text{ pA}/\sqrt{\text{Hz}} \quad (45)$$

$$V_{\text{n2}} = 12.2\text{ nV}/\sqrt{\text{Hz}} \quad (46)$$



## Numerical Example

- The low freq value of  $V_{\text{no1}}^2(f)$  is found by  $f = 0$ , in (41).

$$\begin{aligned} V_{\text{no1}}^2(0) &= (I_{\text{n1}}^2(0) + I_{\text{nf}}^2(0) + I_{\text{n-}}^2(0))R_f^2 \\ &= (0.406^2 + 1.28^2 + 0.6^2)(1 \times 10^9)^2 (100\text{k})^2 \\ &= (147\text{ nV}/\sqrt{\text{Hz}})^2 \end{aligned} \quad (47)$$

- Since (41) indicates noise is first-order lowpass filtered,

$$\begin{aligned} V_{\text{no1(rms)}}^2 &= (147\text{ nV}/\sqrt{\text{Hz}})^2 \times \frac{\pi/2}{2\pi(100\text{k}\Omega)(160\text{pF})} \\ &= (18.4\text{ }\mu\text{V})^2 \end{aligned} \quad (48)$$



## Numerical Example

- For  $V_{no2}^2(0)$

$$\begin{aligned} V_{no2}^2(0) &= (I_{n+}^2(f)R_2^2 + V_{n2}^2(f) + V_n^2(f))(1 + R_f/R_1)^2 \\ &= (24.1 \text{ nV}/\sqrt{\text{Hz}})^2 \times 11^2 \\ &= (265 \text{ nV}/\sqrt{\text{Hz}})^2 \end{aligned} \quad (49)$$

- Noise is lowpass filtered at  $f_o$  until  $f_1 = (R_f/R_1)f_o$  where the noise gain reaches unity until  $f_t = 5 \text{ MHz}$
- Breaking noise into two portions, we have

$$\begin{aligned} V_{no2(\text{rms})}^2 &= (265 \times 10^{-9})^2 \left( \frac{\pi/2}{2\pi R_f C_f} \right)^2 + (24.1 \times 10^{-9})^2 \left( \frac{\pi}{2} \right)^2 (f_t - f_1) \\ &= (74.6 \text{ } \mu\text{V})^2 \end{aligned} \quad (50)$$



## Numerical Example

- Total output noise is estimated to be

$$V_{no(\text{rms})} = \sqrt{V_{no1(\text{rms})}^2 + V_{no2(\text{rms})}^2} = 77 \text{ } \mu\text{V rms} \quad (51)$$


- Note: major noise source is opamp's voltage noise.
- To reduce total output noise
  - use a lower speed opamp
  - choose an opamp with a lower voltage noise.
- Note:  $R_2$  contributes to output noise with its thermal noise AND amplifying opamp's positive noise current.
- If dc offset can be tolerated, it should be eliminated in a low-noise circuit.




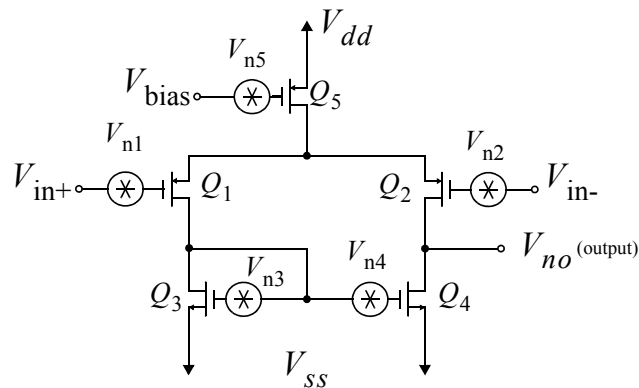
## CMOS Example

- Look at noise in input stage of 2-stage CMOS opamp



- Equivalent voltage noise sources used since example addresses low-moderate frequency.



## CMOS Example

$$\left| \frac{V_{no}}{V_{n1}} \right| = \left| \frac{V_{no}}{V_{n2}} \right| = g_{m1} R_o \quad (52)$$

where  $R_o$  is the output impedance seen at  $V_{no}$ .

$$\left| \frac{V_{no}}{V_{n3}} \right| = \left| \frac{V_{no}}{V_{n4}} \right| = g_{m3} R_o \quad (53)$$

$$\left| \frac{V_{no}}{V_{n5}} \right| = \frac{g_{m5}}{2g_{m3}} \quad (54)$$

- Found by noting that  $V_{n5}$  modulates bias current and drain of  $Q_2$  tracks that of  $Q_1$  due to symmetry — this gain is small (compared to others) and is ignored.



## CMOS Example

$$V_{no}^2(f) = 2(g_{m1}R_o)^2 V_{n1}^2(f) + 2(g_{m3}R_o)^2 V_{n3}^2(f) \quad (55)$$

- Find equiv input noise by dividing by  $g_{m1}R_o$

$$V_{neq}^2(f) = 2V_{n1}^2(f) + 2V_{n3}^2(f) \left( \frac{g_{m3}}{g_{m1}} \right)^2 \quad (56)$$

### Thermal Noise Portion

- For white noise portion, substitute

$$V_{ni}^2(f) = 4kT \left( \frac{2}{3} \right) \left( \frac{1}{g_{mi}} \right) \quad (57)$$

$$V_{neq}(f) = \left( \frac{16}{3} \right) kT \left( \frac{1}{g_{m1}} \right) + \left( \frac{16}{3} \right) kT \left( \frac{g_{m3}}{g_{m1}} \right) \left( \frac{1}{g_{m1}} \right) \quad (58)$$



## CMOS Example

- Assuming  $g_{m3}/g_{m1}$  is near unity, near equal contribution of noise from the two pairs of transistors which is inversely proportional to  $g_{m1}$ .
- ***In other words,  $g_{m1}$  should be made as large as possible to minimize thermal noise contribution.***

### 1/f Noise Portion

- We make the following substitution into (56),

$$g_{mi} = \sqrt{2\mu_i C_{ox} \left( \frac{W}{L} \right)_i I_{Di}} \quad (59)$$

$$V_{ni}^2(f) = 2V_{n1}^2(f) + 2V_{n3}^2(f) \left( \frac{(W/L)_3 \mu_n}{(W/L)_1 \mu_p} \right) \quad (60)$$



## CMOS Example

- Now, letting each of the noise sources have a spectral density

$$V_{ni}^2(f) = \frac{K_i}{W_i L_i C_{ox} f} \quad (61)$$

we have

$$V_{ni}^2(f) = \frac{2}{C_{ox} f} \left( \frac{K_1}{W_1 L_1} + \left( \frac{\mu_n}{\mu_p} \right) \left( \frac{K_3 L_1}{W_1 L_3^2} \right) \right) \quad (62)$$

- Recall first term is due to p-channel input transistors, while second term is due to the n-channel loads



## CMOS Example

### Some points for low 1/f noise

- For  $L_1 = L_3$ , the noise of the n-channel loads dominate since  $\mu_n > \mu_p$  and typically n-channel transistors have larger 1/f noise than p-channels (i.e.  $K_3 > K_1$ ).
- Taking  $L_3$  longer greatly helps due to the inverse squared relationship — this will limit the signal swings somewhat
- The input noise is independent of  $W_3$  and therefore one can make it large to maximize signal swing at the output.



## CMOS Example

### Some points for low 1/f noise

- Taking  $W_1$  wider also helps to minimize 1/f noise (recall it helps white noise as well).
- Taking  $L_1$  longer increases the noise due to the second term being dominant.

