

Continuous-Time Filters

*David Johns and Ken Martin
University of Toronto
(johns@eecg.toronto.edu)
(martin@eecg.toronto.edu)*



University of Toronto

1 of 89

© D. Johns, K. Martin, 1997

Motivation

Switched-capacitor filters

- + Accurate transfer-functions
- + High linearity, good noise performance
- Limited in speed
- Requires anti-aliasing filters

Continuous-time filters

- Moderate transfer-function accuracy (requires tuning circuitry)
- Moderate linearity
- + High-speed
- + Good noise performance




University of Toronto

2 of 89

© D. Johns, K. Martin, 1997

G_m-C Integrators

 


$$V_o = \frac{I_o}{sC_1} = \frac{G_m V_i}{sC_1} \equiv \left(\frac{\omega_{ti}}{s}\right) V_i$$

$$\omega_{ti} = \frac{G_m}{C_1}$$

- Use a transconductor to build an integrator
- Output current is linearly related to input voltage
- Output impedance is ideally infinite
- Note — an OTA (operational transconductance amplifier) has a high G_m value but not usually linear.



Multiple-Input G_m-C Integrator

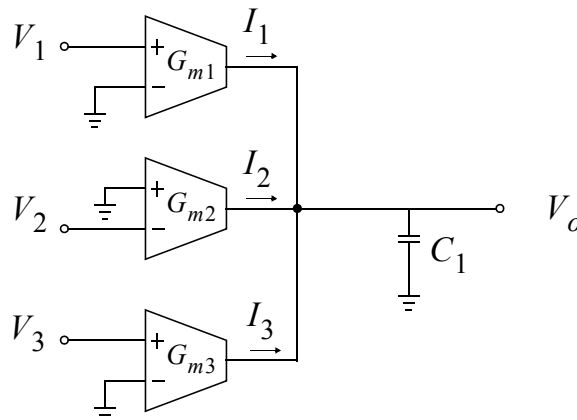

$$V_o = \frac{1}{sC_1} (G_{m1}V_1 - G_{m2}V_2 + G_{m3}V_3)$$



Example

- What G_m is needed for an integrator having a unity-gain frequency of $\omega_{ti} = 20 \text{ MHz}$ when $C = 2 \text{ pF}$?

$$G_m = \frac{2\pi \times 20 \text{ MHz} \times 2 \text{ pF}}{1} = 0.251 \text{ mA/V} \quad (1)$$

or equivalently,

$$G_m = 1/3.98 \text{ k}\Omega \quad (2)$$


- which is related to unity-gain frequency by

$$2\pi \times 20 \text{ MHz} = \frac{1}{3.98 \text{ k}\Omega \times 2 \text{ pF}} \quad (3)$$



Fully-Differential Integrators

 - Better noise and linearity than single-ended.




$$V_o = \frac{I_o}{sC_1} = \frac{G_m V_i}{sC_1} \quad \omega_{ti} = \frac{G_m}{C_1}$$

- Use a single capacitor between differential outputs
- Requires some sort of common-mode feedback to set output common-mode voltage
- Needs some extra caps for compensating common-mode feedback loop.



Fully-Differential Integrators

 


$$V_o = \frac{2I_o}{s(2C_1)} = \frac{G_m V_i}{sC_1} \quad \omega_{ti} = \frac{G_m}{C_1} \quad \begin{aligned} v_o &= v_o^+ - v_o^- \\ i_o &= G_m v_i \end{aligned}$$

- Use 2 grounded capacitors
- Still requires common-mode feedback but compensation caps for common-mode feedback can be the same grounded capacitors



Fully-Differential Integrators

 


$$V_o = \frac{G_m V_i}{s(C_1 + C_p/2)} \quad \omega_{ti} = \frac{G_m}{(C_1 + C_p/2)}$$

- Integrated capacitors have top and bottom plate parasitic capacitances.
- To maintain symmetry, usually 2 parallel caps used as shown above
- Note that parasitic capacitance affects time-constant



G_m-C Opamp Integrator

 

$$V_o = \frac{2I_o}{s(2C_1)} = \frac{G_m V_i}{sC_1} \quad \omega_{ti} = \frac{G_m}{C_1}$$

- Use an extra opamp to improve linearity and noise performance
- Also known as a “Miller Integrator”



G_m-C Opamp Integrator

Advantages


- Effect of parasitic caps reduced by opamp gain — more accurate time-constant and better linearity.
- Less sensitive to noise since transconductor output is low impedance (due to opamp feedback).
- G_m cell drives virtual gnd — output-impedance of G_m cell can be lower and smaller voltage swing needed.

Disadvantages

- Lower operating speed because it now relies on feedback
- Larger power dissipation
- Larger silicon area




Example G_m -C Opamp Integrator

 

- A low input impedance on the order of $2/(g_{m2}^2 r_{ds})$ due to common-gate input impedance and feedback.



First-Order Filter

 


- General first-order transfer-function

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{k_1 s + k_0}{s + \omega_0} \quad (4)$$

- Built with a single integrator and two feedins branches.
- ω_0 sets the pole frequency



First-Order Filter

 


$$C_X = \left(\frac{k_1}{1 - k_1} \right) C_A \text{ where } (0 \leq k_1 < 1) \quad G_{m1} = k_0(C_A + C_X) \quad G_{m2} = \omega_o(C_A + C_X)$$

- Can show that the transfer function is given by

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{sC_X + G_{m1}}{s(C_A + C_X) + G_{m2}} = \frac{s \left(\frac{C_X}{C_A + C_X} \right) + \left(\frac{G_{m1}}{C_A + C_X} \right)}{s + \left(\frac{G_{m2}}{C_A + C_X} \right)} \quad (5)$$



Fully-Differential First-Order Filter

 

$$C_X = C_A \left(\frac{k_1}{1 - k_1} \right) \text{ where } (0 \leq k_1 < 1) \quad G_{m1} = k_0(C_A + C_X) \quad G_{m2} = \omega_o(C_A + C_X)$$

- Same eqns as single-ended case but cap sizes doubled
- Can realize $k_1 < 0$ by cross-coupling wires at C_x .



Example

- Find fully-diff values when dc gain = 0.5, a pole at 20MHz and a zero at 40MHz. Assume $C_A = 2pF$.

$$H(s) = \frac{0.25(s + 2\pi \times 40MHz)}{(s + 2\pi \times 20MHz)} = \frac{0.25s + 2\pi \times 10MHz}{s + 2\pi \times 20MHz} \quad (6)$$

$$k_1 = 0.25, k_0 = 2\pi \times 10^7, \omega_o = 4\pi \times 10^7 \quad (7)$$

- We find


$$C_X = 2pF \times \frac{0.25}{1 - 0.25} = 0.667pF \quad (8)$$

$$G_{m1} = 2\pi \times 10^7 \times 2.667pF = 0.168 \text{ mA/V} \quad (9)$$

$$G_{m2} = 4\pi \times 10^7 \times 2.667pF = 0.335 \text{ mA/V} \quad (10)$$




Second-Order Filter

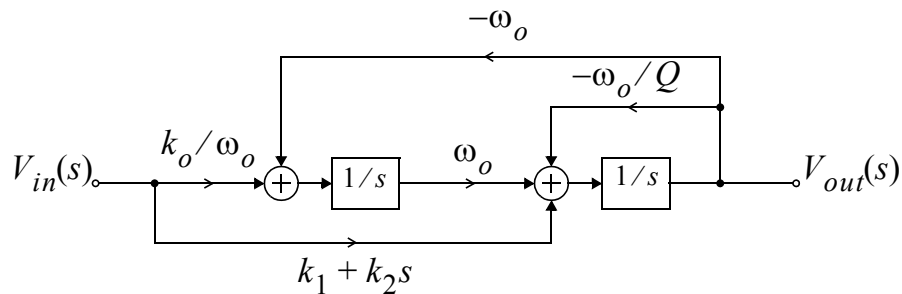

$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = \frac{k_2s^2 + k_1s + k_o}{s^2 + \left(\frac{\omega_o}{Q}\right)s + \omega_o^2} \quad (11)$$



Second-Order Filter

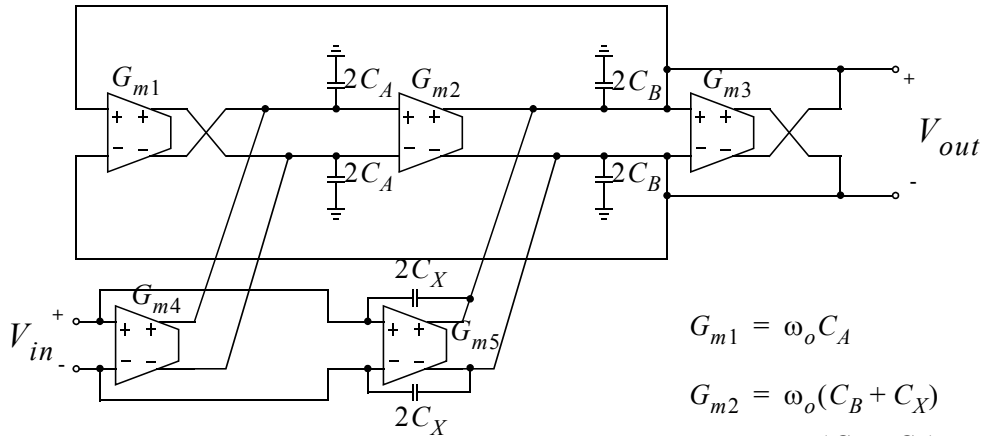

$$C_X = C_B \left(\frac{k_2}{1 - k_2} \right) \text{ where } (0 \leq k_2 < 1)$$

$$G_{m1} = \omega_o C_A$$

$$G_{m2} = \omega_o (C_B + C_X)$$

$$G_{m3} = \frac{\omega_o (C_B + C_X)}{Q}$$

$$G_{m4} = (k_o C_A) / \omega_o$$

$$G_{m5} = k_1 (C_B + C_X)$$



Second-Order Filter

$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = \frac{s^2 \left(\frac{C_X}{C_X + C_B} \right) + s \left(\frac{G_{m5}}{C_X + C_B} \right) + \left(\frac{G_{m2} G_{m4}}{C_A (C_X + C_B)} \right)}{s^2 + s \left(\frac{G_{m3}}{C_X + C_B} \right) + \left(\frac{G_{m1} G_{m2}}{C_A (C_X + C_B)} \right)} \quad (12)$$

- Note that there is a restriction on the high-frequency gain coeff k_2 as in the first-order case.
- Note that G_{m3} sets the damping of this biquad
- G_{m1} and G_{m2} form two integrators with unity-gain frequencies of ω_o/s .



Example

- Find values for a bandpass filter with a center frequency of 20MHz , a Q value of 5, and a center frequency gain of 1.
- Assume $C_A = C_B = 2\text{pF}$

$$H(s) \equiv \frac{V_{out}(s)}{V_{in}(s)} = \frac{Gs \frac{\omega_o}{Q}}{s^2 + s \frac{\omega_o}{Q} + \omega_o^2} \quad (13)$$

where $G = 1$ is the gain at the center frequency.



Example

- Since, $\omega_o = 2\pi \times 20\text{MHz}$ and $Q = 5$, we find

$$k_1 = G \frac{\omega_o}{Q} = 2.513 \times 10^7 \text{ rad/s} \quad (14)$$

- Since k_0 and k_2 are zero, we have $C_x = G_{m4} = 0$
- The transconductance values are:

$$G_{m1} = \omega_o C_A = 0.2513 \text{ mA/V} \quad (15)$$

$$G_{m2} = \omega_o (C_B + C_X) = 0.2513 \text{ mA/V} \quad (16)$$

$$G_{m3} = G_{m5} = k_1 C_B = 50.27 \mu\text{A/V} \quad (17)$$



Bipolar Transconductors

- 2 main methods

Fixed Transconductor with Gain Cell


- Larger input range, lower transconductance
- Create a transconductor with a fixed G_m value using a resistor
- Tune the transconductance using a gain cell

Multiple Differential Pairs

- Smaller input range, higher transconductance
- Use 2 diff pairs to extend linear input range
- Tuning done by adjusting bias current



Fixed Transconductors using Resistors

 

- Left circuit needs higher common-mode voltage



Max Differential Input Range

- Determine when one of diff transistors turns off
- For example, find when Q_2 turns off in right circuit
- If Q_2 off, then all of I_1 flows through R_E resulting in

$$V_{i,max} = I_1 R_E \quad (18)$$

- However, there is significant distortion at this point since V_{be} is not constant
- Maximum input range might be half that resulting in

$$V_{i,max} = (I_1/2)R_E \quad (19)$$



Distortion

- So far, have assumed V_{be} voltages remain constant which is reasonable if $r_e \ll R_E$

$$r_e \equiv \frac{V_T}{I_E} \quad (20)$$

implying

$$r_{e,max} = \frac{V_T}{I_{E,min}} \ll R_E \quad (21)$$

or equivalently,

$$I_{E,min} \gg \frac{V_T}{R_E} \quad (22)$$



Distortion

Example

- If $R_E = 20k\Omega$ and $V_T = 25mV$, then $I_{E, min} \gg 1.25 \mu A$

How much is “much greater than”?

- Depends on how much distortion can be tolerated
- If $r_{e, max} = 0.1R_E$ when $V_{i, max} = (I_1/2)R_E$, the actual output current is 3% from ideal linear response.
- Results in about a 1% THD (3 times better than peak linearity error)
- Can use smaller input signals but then noise might dominate



Transconductance

- Use small-signal T-model for bipolar transistors

$$i_{o1} = \frac{v_i}{r_{e1} + R_E + r_{e2}} = \frac{v_i}{2r_e + R_E} \quad (23)$$

where r_e is small-signal emitter resist ($r_e = \alpha/g_m$)

$$r_e = \frac{V_T}{I_E} = \frac{V_T}{I_1} \quad (24)$$

- Leading to

$$G_m = \frac{i_{o1}}{v_i} = \frac{1}{2r_e + R_E} \quad (25)$$



Example

- Given $R_E = 3k\Omega$ (i.e. $G_m \approx 0.333 \text{ mA/V}$),
 $V_{i,\max} = \pm 500 \text{ mV}$, find I_1 so $r_{e,\max} < 0.1R_E$

- We have $r_{e,\max} < 0.1R_E = 300\Omega$ which occurs when

$$I_{E2,\min} = \frac{V_T}{r_{e,\max}} = \frac{26 \text{ mV}}{300\Omega} = 86.7 \mu\text{A} \quad (26)$$

- For this same input voltage of 500 mV

$$I_{RE} \approx \frac{500 \text{ mV}}{3k\Omega} = 167 \mu\text{A} \quad (27)$$



Example

- Since $I_1 = I_{RE} + I_{E2}$

$$I_1 = 167 + 86.7 = 253 \mu\text{A} \quad (28)$$

- Thus, a minimum bias current of $253 \mu\text{A}$ should be chosen resulting in a nominal r_e and G_m given by


$$r_e = \frac{V_T}{I_1} = 103\Omega \quad (29)$$

$$G_m = \frac{1}{(2r_e + R_E)} = 0.312 \text{ mA/V} \quad (30)$$

- A 4 times increase in I_1 would improve distortion by about 10 times but use more power.




Linear Transconductor — Opamps

 

- Feedback keeps input voltage across R_E
- Simple opamps used (typically single stage)




Linear Transconductor — Constant Current

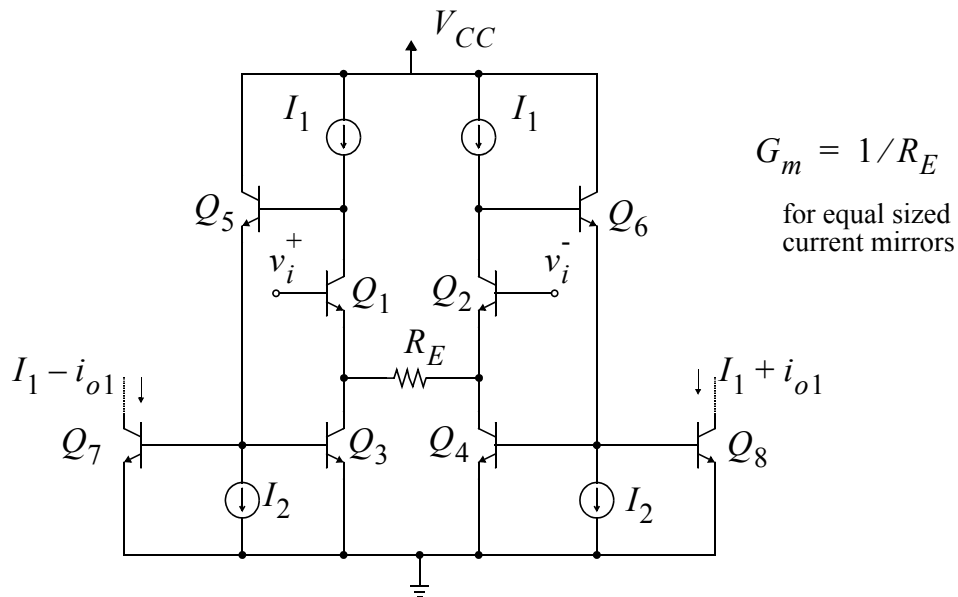

- Fix collector currents through diff pair using feedback



Differential Pair

 

$$i_{C2} = \frac{I_1}{1 + e^{v_i/V_T}} \quad (31)$$

- Relatively linear near $v_i = 0$

$$G_m = \frac{1}{2r_e} = \frac{I_1}{4V_T} \quad (32)$$




Differential Pair


- G_m proportional to I_1
- However, limited input range — when $v_i > 32\text{mVpp}$, THD > 1%.
- Use multiple diff pairs to increase linear input range
- Conceptual — use 2 diff pairs with dc offset
- Actual — replace dc offsets by resizing transistors in differential pairs
- Increases input range to $v_i > 96\text{mVpp}$ for 1% THD



Multiple Diff-Pairs

 

Multiple Diff-Pairs

 

$$G_m = \frac{8I_1}{25V_T}$$



Multiple Diff-Pair

- When $v_i = 0$, I through Q_1 and Q_2 are $0.8I_1$ and $0.2I_1$.

$$G_m = \frac{1}{r_{e1} + r_{e2}} + \frac{1}{r_{e3} + r_{e4}} \quad (33)$$

$$r_{e1} = r_{e4} = \frac{V_T}{0.8I_1} \quad (34)$$

$$r_{e2} = r_{e3} = \frac{V_T}{0.2I_1} \quad (35)$$

$$G_m = \frac{8I_1}{25V_T} \quad (36)$$

- which is 28% larger than diff pair but uses twice the current — same current results in 36% less G_m



CMOS Transconductors

- A large variety of methods
- Best approach depends on application
- 2 main classifications — triode or active transistor based

Triode vs. Active

- Triode based tends to have better linearity
- Active tend to have faster speed for the same operating current



Triode Transconductors

- Recall n-channel triode equation

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left((V_{GS} - V_{tn}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (37)$$

where to remain in triode

$$V_{DS} < V_{eff} \quad \text{where} \quad V_{eff} = V_{GS} - V_{tn} \quad (38)$$

or equivalently, $V_{GS} > V_{DS} + V_{tn}$

- Above models are only reasonably accurate (
- Not nearly as accurate as exponential model in BJTs
- Use fully-differential architectures to reduce even-order distortion terms — also improves common-mode noise rejection



Fixed-Bias Triode Transconductor

- Use a small V_{DS} voltage so V_{DS}^2 term goes to zero

$$r_{DS} \equiv \left. \left(\frac{\partial i_D}{\partial v_{DS}} \right)^{-1} \right|_{v_{DS} = 0} \quad (39)$$


which results in

$$r_{DS} = \left(\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_{tn}) \right)^{-1} \quad (40)$$


- Can use a triode transistor where a resistor would normally be used — resistance value is tunable



Fixed-Bias Triode Transconductor

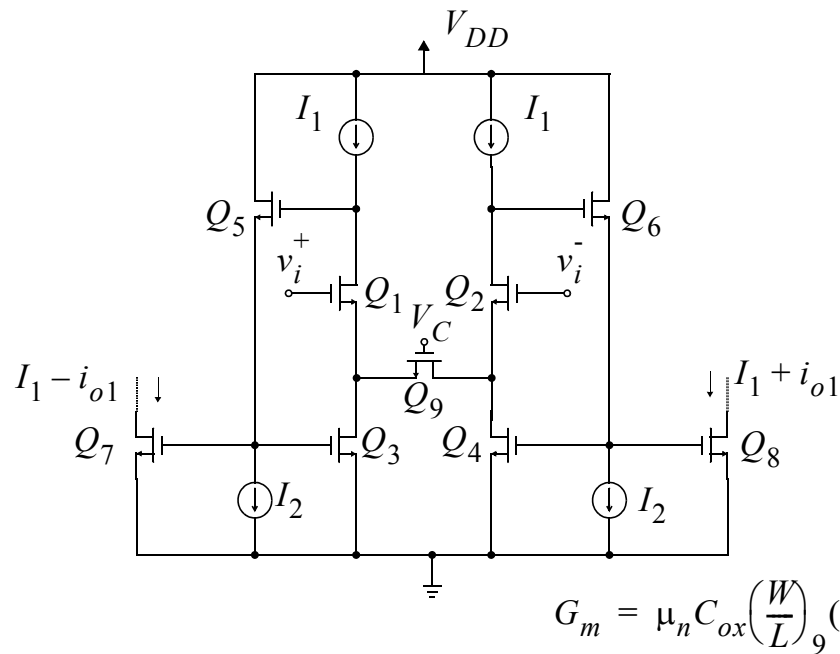


Biquad using Multiple Outputs

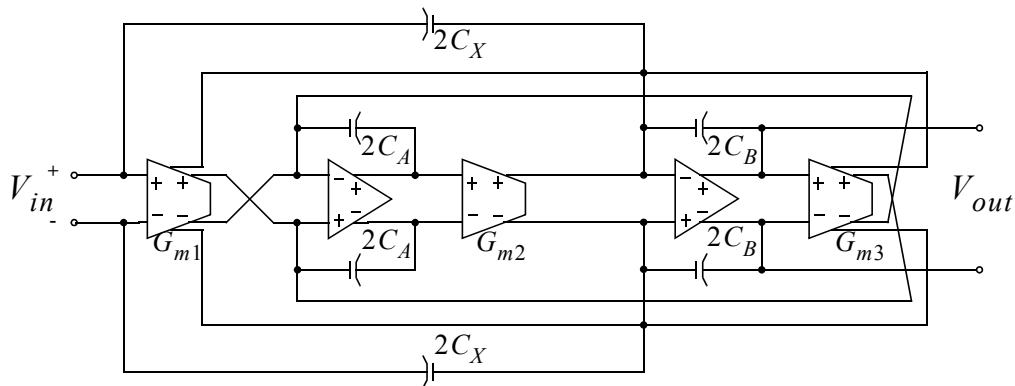

- Can make use of multiple outputs to build a biquad filter — scale extra outputs to desired ratio
- Reduces the number of transconductors — saves power and die area
- Above makes use of Miller integrators



Varying-Bias Triode Transconductor

 

$$G_m = \frac{4k_1k_3\sqrt{I_1}}{(k_1 + 4k_3)\sqrt{k_1}}$$



Varying-Bias Transconductor

- gates of Q_3, Q_4 connected to the differential input
- Q_3 and Q_4 undergo varying bias conditions to improve linearity
- Can show

$$G_m = \frac{4k_1k_3\sqrt{I_1}}{(k_1 + 4k_3)\sqrt{k_1}} \quad (41)$$

where

$$k_i = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_i \quad (42)$$


- Note, G_m proportional to square-root of I_1 as opposed to linear relation for a BJT transconductor.



Drain-Source Fixed-Bias Transconductor

$$i_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left((V_{GS} - V_{tn}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad (43)$$

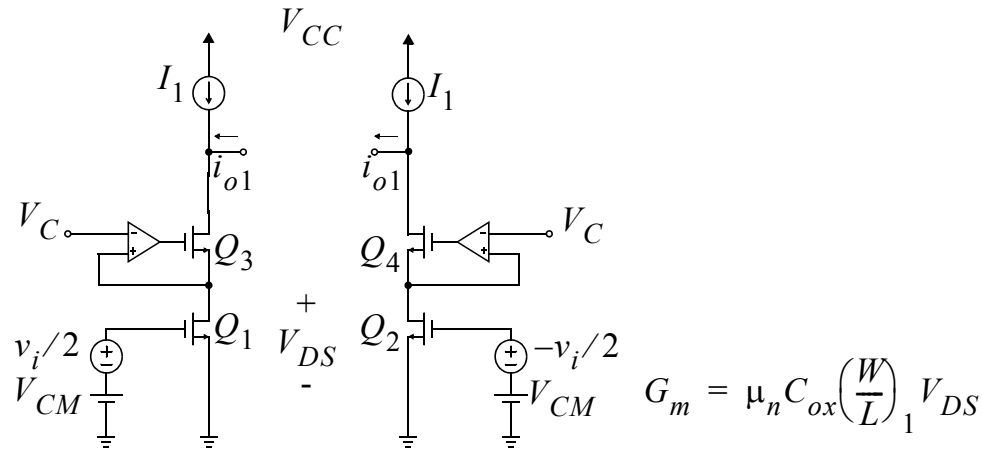- If V_{DS} kept constant, then i_D linear wrt V_{GS}



$$G_m = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 V_{DS}$$



Drain-Source Fixed-Bias Transconductor

- Can realize around 50 dB linearity (not much better since model is not that accurate)
- Requires a fully-differential structure to cancel even-order terms
- V_C sets V_{DS} voltage — rather than opamp with feedback can use BJTs in a BiCMOS technology
- Requires a non-zero common-mode voltage on input
- Transconductance given by

$$G_m = \mu_n C_{ox} \left(\frac{W}{L} \right)_1 V_{DS} \quad (44)$$

- Note that G_m roughly proportional to bias current since current roughly proportional to V_{DS}



Example

- $\mu_n C_{ox} = 96 \mu A/V^2$, $(W/L)_1 = (W/L)_2 = 10$, $V_{tn} = 0.8V$,
and $V_{CM} = 2V$

— $V_C = 0.2V$ **Case**

$$G_m = 96 \mu A/V^2 \times 10 \times 0.2V = 0.192 mA/V \quad (45)$$

$$I_1 = 96 \mu A/V^2 \times 10 \left((2 - 0.8)0.2 - \frac{0.2^2}{2} \right) = 0.211 mA \quad (46)$$

- **Max v_i** — $V_{eff1} > V_{DS} = 0.2V$ or $V_{G1} > V_{DS} + V_{tn} = 1.0V$.
Since $V_{CM} = 2V$, $\max v_i = 2V$.

— $V_C = 0.4V$ **Case**

- $G_m = 0.384 mA/V$, $I_1 = 0.384 mA$ and max input signal swing is $v_i = 1.6V$ (loss of signal swing)



Active-Based Transconductors

- Active transistors are those operating in the active region
- Active region also referred to as pinch-off or saturation region
- In active region


$$I_D = K_i (V_{GS} - V_{tn})^2 \quad (47)$$

when $V_{DS} \geq V_{GS} - V_{tn} = V_{eff}$ and $V_{GS} \geq V_{tn}$

- Here, $K_i \equiv (\mu_n C_{ox}/2)(W/L)_i$



CMOS Pair

 


$$K_{eq} = \frac{K_n K_p}{(\sqrt{K_n} + \sqrt{K_p})^2} \quad V_{teq} = V_{tn} - V_{tp} \quad (\text{where } V_{tn} > 0 \text{ and } V_{tp} < 0)$$

- Above circuit acts as a single transistor with threshold V_{teq} and parameter K_{eq}



Constant Sum of Gate-Source Voltages

 


$$(i_{D1} - i_{D2}) = K(v_{GS1} + v_{GS2} - 2V_{tn})(v_{GS1} - v_{GS2}) \quad (48)$$

$$K = (\mu_n/2)C_{ox}\left(\frac{W}{L}\right) \quad (49)$$

- If $V_{GS1} + V_{GS2} = \text{constant}$ then linear transconductor
- Note — Differential output current linear but single-ended currents have large second-order distortion.



Source-Connected Differential Pair

 

$$(i_{D1} - i_{D2}) = 2K(V_{CM} - V_{SS} - V_{tn})(v_i)$$

$$G_m = 2K(V_{CM} - V_{SS} - V_{tn})$$




Source-Connected Differential Pair

- Input signal varies symmetrically around a common-mode voltage
- Linearity limited due to square-law model being inaccurate
- In addition, even-order harmonics occur if the difference between two drain currents not exact.
- Limited to less than 50 dB linearity
- Adjust G_m by varying V_{CM}
- In a short channel process, velocity saturation limits transconductance variation




Inverter-Based

 

$$G_m = 4K_{eq}(V_{C1} - V_{teq})$$



Diff-Pair with Floating Voltage Sources

 

- Writing a voltage equation around the loop

$$v_{GS1} - (V_x + V_{tn}) + v_{GS2} - (V_x + V_{tn}) = 0 \quad (50)$$

implying

$$v_{GS1} + v_{GS2} = 2(V_x + V_{tn}) \quad (51)$$

- Thus, a constant sum of gate-source voltages occurs — even if input signal is not balanced



Diff-Pair with Floating Voltage Sources

$$v_1 - v_{GS1} + V_x + V_{tn} = v_2 \quad (52)$$

$$v_2 - v_{GS2} + V_x + V_{tn} = v_1 \quad (53)$$

- Subtracting (52) from (53), we obtain


$$v_{GS1} - v_{GS2} = 2(v_1 - v_2) \quad (54)$$

- Finally, output diff current found from (48)

$$(i_{D1} - i_{D2}) = 4KV_x(v_1 - v_2) \quad (55)$$



Approach #1

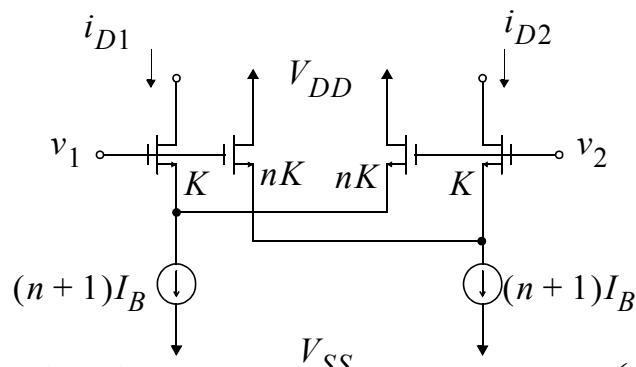


$$(i_{D1} - i_{D2}) = \left(\frac{n}{n+1}\right) 4\sqrt{KI_B}(v_1 - v_2) \quad G_m = \left(\frac{n}{n+1}\right) 4\sqrt{KI_B}$$

- Floating voltage sources built using large transistors (n times larger with n typically greater than 5)
- Disadvantage — large bias current and moderate linearity




BiCMOS Transconductors

Tunable MOS in Triode

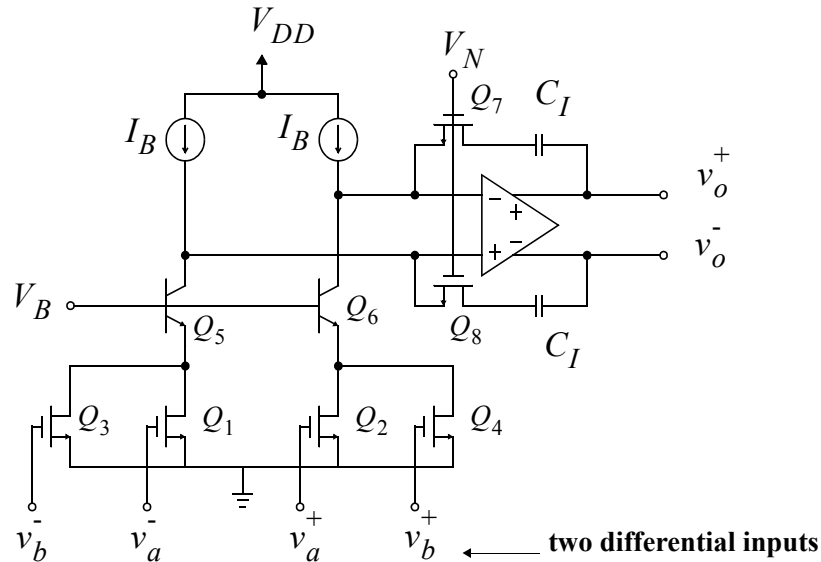

BiCMOS Transconductors

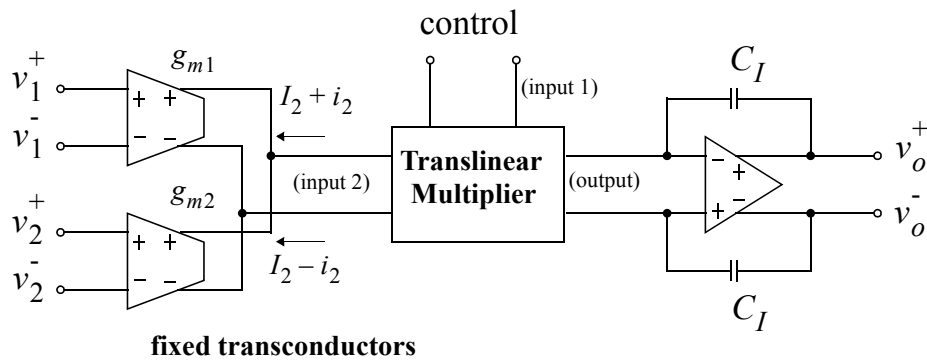Fixed-Transconductor with Translinear Multiplier




- Translinear multiplier used to tune transconductance
- Miller integrator used to maintain high linearity




BiCMOS Transconductors

Circuit GM Implementation

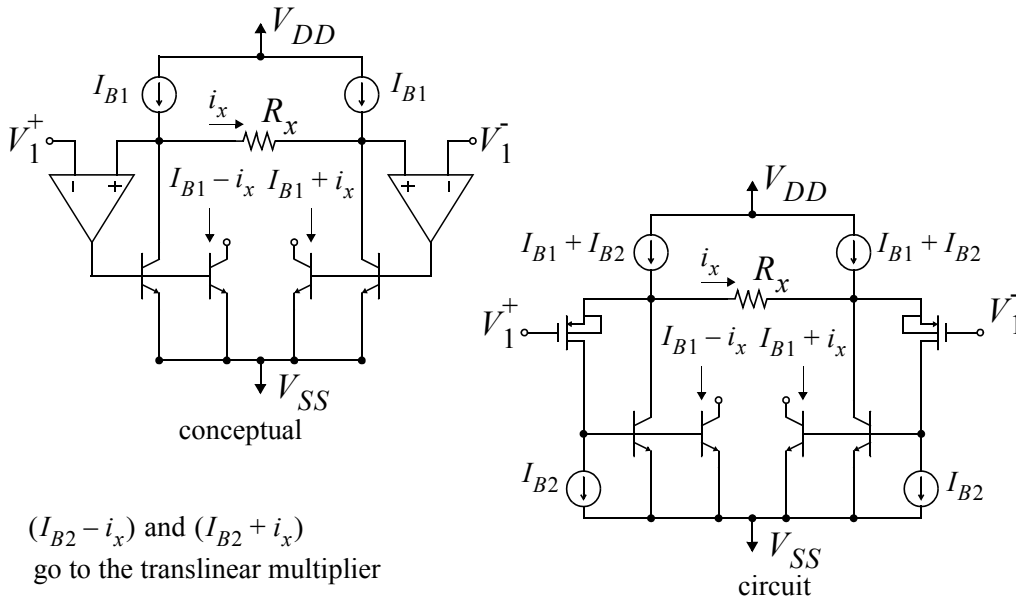

BiCMOS Transconductors

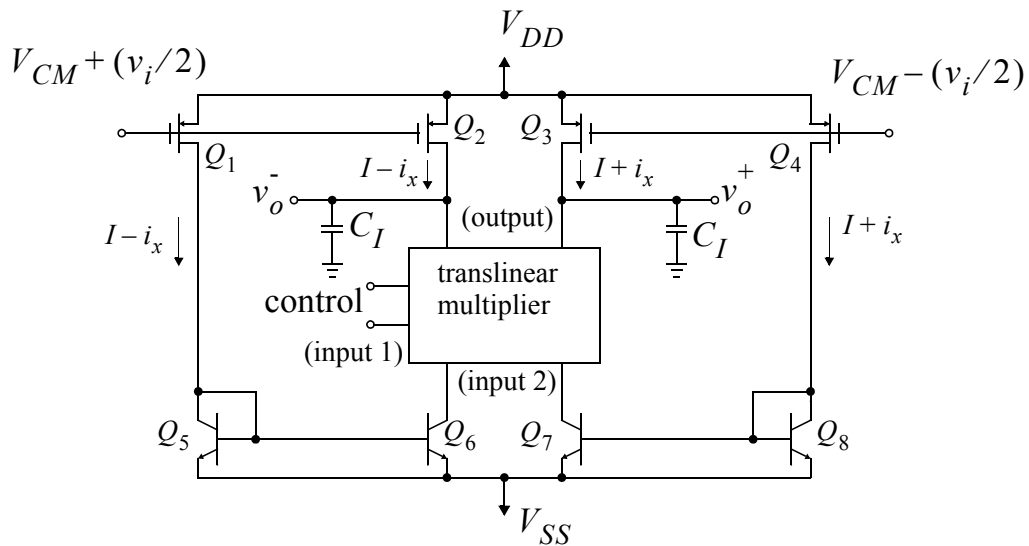Fixed MOS Gm with a Translinear Multiplier



Two-Transistor Integrators

- For resistor integrator

$$v_{\text{diff}} = \frac{1}{sR_1C_I}(v_{p1} - v_{n1}) + \frac{1}{sR_2C_I}(v_{p2} - v_{n2}) \quad (59)$$

- Negative integration — cross-couple wires
- For MOSFET-C integrator

$$r_{DS} = \left(\mu_n C_{ox} \left(\frac{W}{L} \right) (v_{GS} - V_{tn}) \right)^{-1} \quad (60)$$


leading to

$$v_{\text{diff}} = \frac{1}{sr_{DS1}C_I}(v_{p1} - v_{n1}) + \frac{1}{sr_{DS2}C_I}(v_{p2} - v_{n2}) \quad (61)$$

$$r_{DSi} = \left(\mu_n C_{ox} \left(\frac{W}{L} \right)_i (V_C - V_x - V_{tn}) \right)^{-1} \quad (62)$$




MOSFET-C Biquad Filter

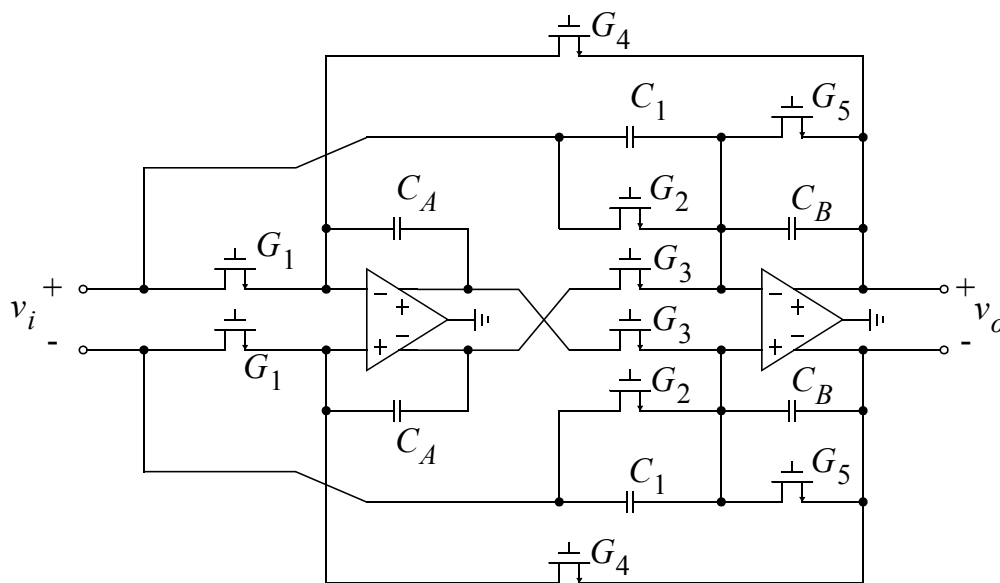

Four-Transistor Integrator

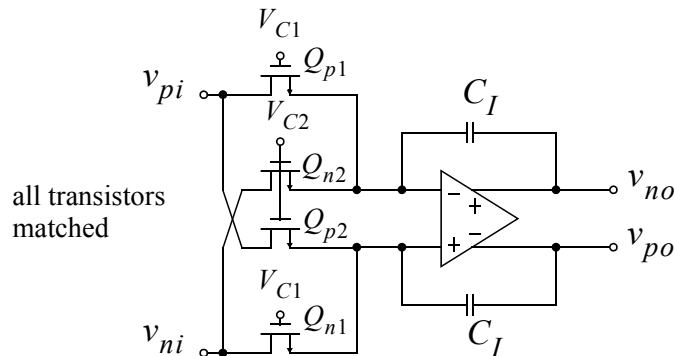- Can improve linearity of MOSFET-C integrators by using 4 transistors rather than 2



- Analyzed by treating it as a two-input integrator with inputs $(v_{pi} - v_{ni})$ and $(v_{ni} - v_{pi})$.



Four-Transistor Integrator

- If all four transistor matched,

$$v_{\text{diff}} = v_{po} - v_{no} = \frac{1}{sr_{DS}C_I}(v_{pi} - v_{ni}) \quad (63)$$

$$r_{DS} = \left(\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{C1} - V_{C2}) \right)^{-1} \quad (64)$$

Distortion

- Model for drain-source current shows non-linear terms not dependent on controlling gate-voltage
- All even and odd distortion products will cancel
- Model only valid for older long-channel length technologies
- In practice, about a 10 dB linearity improvement




Tuning Circuitry

- Tuning can often be the MOST difficult part of a continuous-time integrated filter design
- Tuning required for cont-time integrated filters to account for capacitance and transconductance variations — 30 percent time-constant variations
- Must account for process, temperature, aging, etc.
- While absolute tolerances high, ratio of two like components can be matched to under 1 percent
- Note that SC filters do not need tuning as their transfer-function accuracy set by ratio of capacitors and a clock-frequency




Indirect Tuning

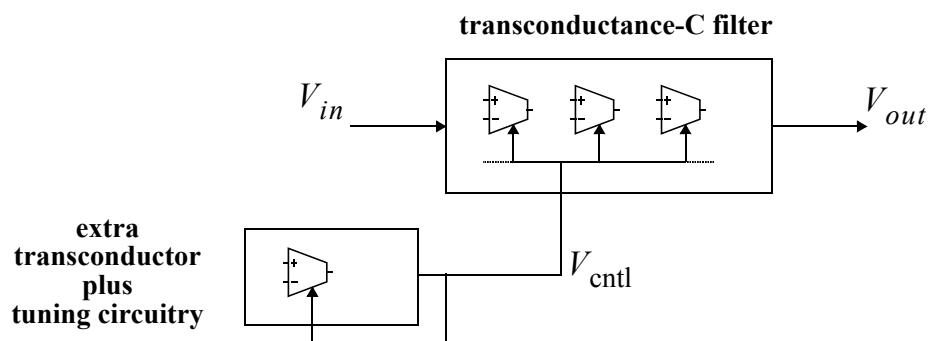


- Most common method — build an extra transconductor and tune it
- Same control signal is sent to filter's transconductors which are scaled versions of tuned extra
- Indirect since actual filter's output not measured



Constant Transconductance

 


$$G_m = \frac{1}{R_{\text{ext}}}$$

 

- Can tune G_m to off-chip resistance and rely on capacitor absolute tolerance to be around 10 percent



Frequency Tuning

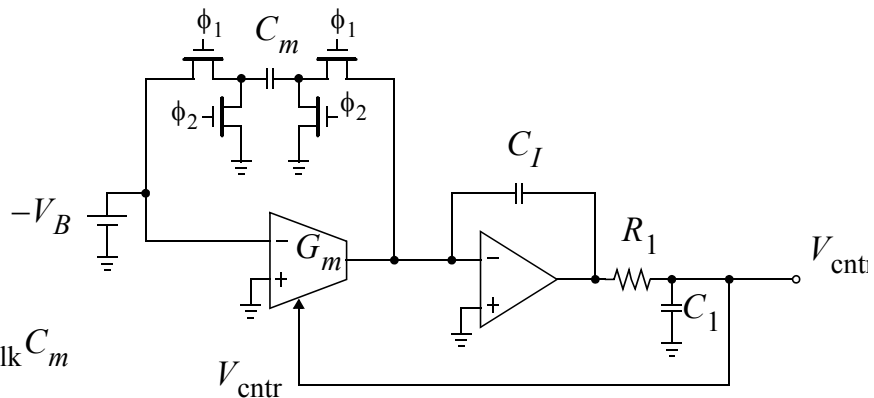


$$G_m = f_{\text{clk}} C_m$$

- A precise G_m/C ratio set — time period needed
- External resistance replaced by SC equivalent



Frequency Tuning

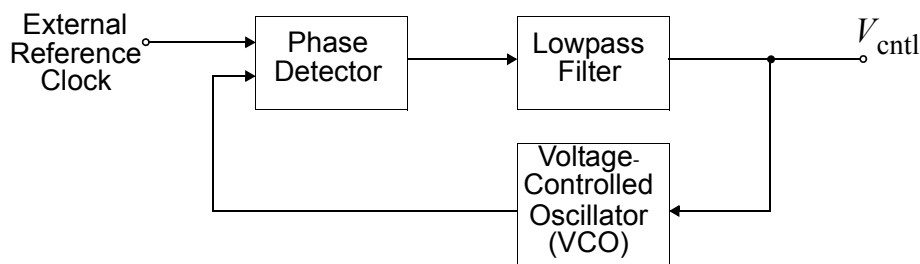

- Use a PLL to tune 2 integrators which realize a VCO
- Once VCO set to external freq, then G_m/C of VCO is set to correct value
- Choice of external clock freq is difficult.
 - Leaks into filter if within passband
 - Poor matching if too far from passband



Q-Factor Tuning

- Most industrial applications do not presently use Q-tuning and rely on matching
- For very high-performance circuits, may have to also tune Q-factor as well as G_m/C ratio
- Can use a magnitude locked-loop
- Can use adaptive filtering techniques where filter output is directly observed
- Example: look at step response for a square-wave type input (i.e. digital transmission signal)
 - slope determined by time-constant
 - peak determined by Q-factor



Dynamic Range Performance

- Linearity limits the value of the largest useful signals
- Noise limits the value of the smallest useful signals
- Linearity and noise together determine dynamic range of a filter
- Integrated continuous-time filters are often seriously impaired by their dynamic range performance

Measures

- Total Harmonic Distortion (THD)
- Third-order intercept point (IP3)
- Spurious-Free Dynamic Range (SFDR)



Total-Harmonic-Distortion (THD)

$$\text{THD} = 10 \log \left(\frac{V_{h2}^2 + V_{h3}^2 + V_{h4}^2 + \dots}{V_f^2} \right) \text{ in dB} \quad (65)$$

- V_f — amplitude of the fundamental
- V_{hi} — amplitude of the i 'th harmonic component.

$$\text{THD} = \frac{\sqrt{V_{h2}^2 + V_{h3}^2 + V_{h4}^2 + \dots}}{V_f} \times 100 \text{ in \%} \quad (66)$$

- Typically, only power of first few harmonics used since distortion components usually fall off quickly



THD Limits

- THD will give be optimistic if harmonics fall in stopband
- However, if a lower fundamental frequency is used, then THD is optimistic as distortion often degrades with high input frequencies
- Would like to measure distortion with input signals near the upper passband edge.
- Need an intermodulation test!

Example

- A 21MHz lowpass filter is being tested
- A 5MHz input signal has harmonics at 10, 15 and 20 but then fall in the stopband
- Want to test the filter with a 20MHz input



Third-Order Intercept Point (IP3)

- Here IP3 is described as third-order distortion often dominates in fully-diff circuits — can also define IP2
- Consider

$$v_o(t) = a_1 v_{in}(t) + a_2 v_{in}^2(t) + a_3 v_{in}^3(t) + a_4 v_{in}^4(t) + \dots \quad (67)$$

- The linear term is a_1
- a_2 , a_3 , and a_4 determine second, third and fourth order distortion terms.
- In fully-differential circuits, all even terms small and typically a_3 dominates

$$v_o(t) \approx a_1 v_{in}(t) + a_3 v_{in}^3(t) \quad (68)$$



Third-Order Intercept Point (IP3)

- If $v_{in}(t)$ is a sinusoidal

$$v_{in}(t) = A \cos(\omega t) \quad (69)$$

$$v_o(t) \approx a_1 A \cos(\omega t) + \frac{a_3}{4} A^3 (3 \cos(\omega t) + \cos(3\omega t)) \quad (70)$$

- Define H_{D1} and H_{D3} to be the amplitudes of the fundamental and third-harmonic terms

$$v_o(t) \equiv H_{D1} \cos(\omega t) + H_{D3} \cos(3\omega t) \quad (71)$$

- Since typically, $(3/4)a_3 A^3 \ll a_1 A$, then approximate

$$H_{D1} = a_1 A \quad (72)$$



Third-Order Intercept Point (IP3)

- Amplitude of third-order term is

$$H_{D3} = \frac{a_3}{4} A^3 \quad (73)$$

- Unfortunately, distortion term lies at $3\omega t$ for a single sinusoidal input and thus we resort to an intermodulation test
- Consider now

$$v_{in}(t) = A \cos(\omega_1 t) + A \cos(\omega_2 t) \quad (74)$$

- Can show that

$$I_{D1} = a_1 A \quad (75)$$

$$I_{D3} = \frac{3a_3}{4} A^3 \quad (76)$$




Third-Order Intercept Point (IP3)

- The fundamental appears at ω_1 and ω_2
- The third-order term appears at $2\omega_2 - \omega_1$ and $2\omega_1 - \omega_2$
- As A increased, fundamental rises linearly while third-order term rises as a cubic.
- Every 1dB increase in signal level increases the fundamental by 1dB but the intermod term by 3dB.
- **There is a 2dB worse intermod ratio for every 1dB increase in signal level.**
- Third-order intercept defined to be the point where third-order term will equal fundamental term
- Not physically possible (but an extrapolation) since other distortion terms will start to become important



Third-Order Intercept Point (IP3)

 

Third-Order Intercept Point (IP3)


- Knowing IP3 is useful to determine what signal level should be used for a certain intermodulation-ratio

Example

- If $OIP_3 = 20dBm$, what output signal level should be used such that the third-order intermodulation products are $60dB$ below the fundamental?
- Since we obtain a $2dB$ improvement for every dB drop in output signal level and we want a $60dB$ improvement from the intercept point, we need to lower the output by $60/2 = 30dB$
- The output level should be $-10dBm$



Spurious-Free Dynamic Range (SFDR)

 

SFDR

- Spurious-free dynamic range (SFDR) is the SNR when the power of the third-order intermodulation products equals the noise power.
- If the signal is larger, the distortion dominates
- If the signal is smaller, the noise dominates
- Actual dynamic range is 3dB lower since noise and distortion are equal



Example

- At an input signal level of 0dBm, an intermodulation ratio $-40dB$ was measured in an filter with a gain of 2dB.
- Since performance worsens by 2dB for each 1dB increase in signal level, the intermodulation ratio will be 0dB at an input level of 20dBm. Therefore, $IIP3=20dBm$ and $OIP3=22dBm$
- If one desires an intermodulation ratio of $-45dB$ then the input should be lowered by 2.5dB or equivalently, it should be at a level of $-2.5dBm$
- If the noise power at the output is measured to be $-50dBm$, the expected SFDR is found by

$$SFDR = \frac{2}{3}(22 + 50) = 48dB \quad (77)$$



Example

- In other words, the intermod ratio should be 48dB for the distortion power to equal the noise power.
- In intermod of 48dB is obtained for an input signal value of -4dBm and an output signal value of -2dBm
- A higher level implies that the distortion dominates while a lower signal level implies that the noise dominates.
- Signal-to-noise+distortion (SNDR) equals 45dB.

