


EXAMPLE DESIGN

Trevor Caldwell
trevor.caldwell@analog.com

Highlights (i.e. What you will learn today)

- 1 MOD2 implementation**
- 2 Switched-capacitor integrator**
Switched-C summer & DAC too
- 3 Dynamic-range scaling**
- 4 kT/C noise**
- 5 Verification strategy**



Review: A $\Delta\Sigma$ ADC System

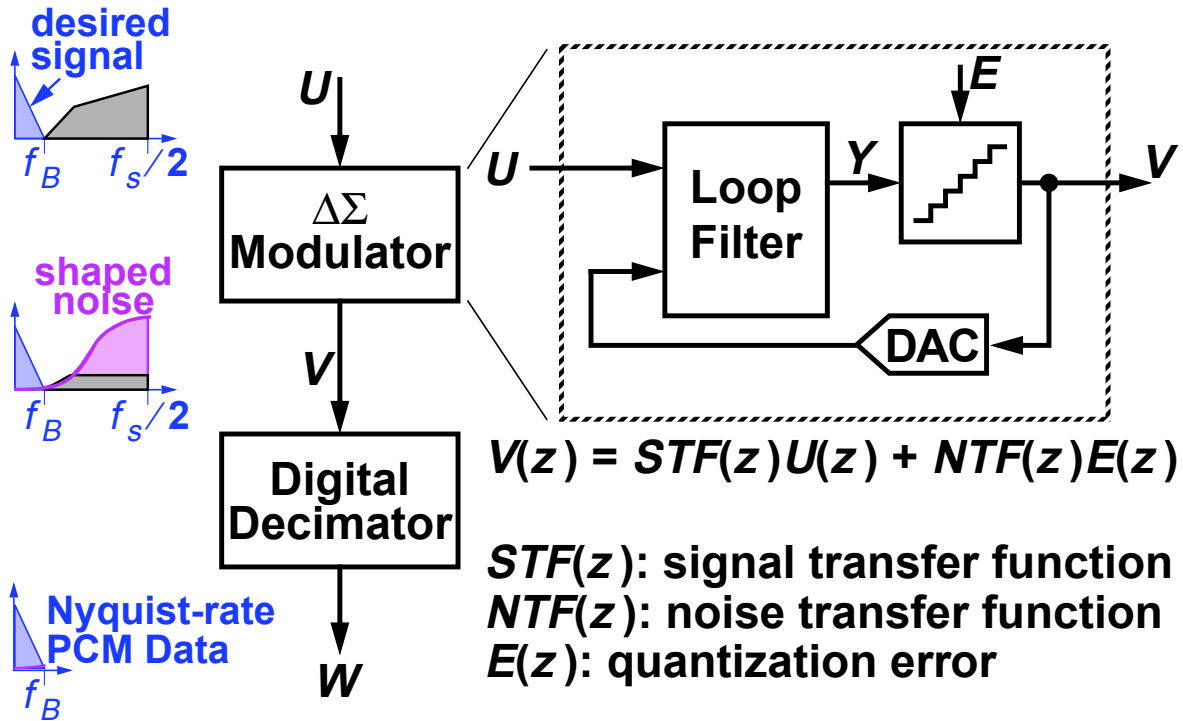

ECE1371

3

Review: MOD1

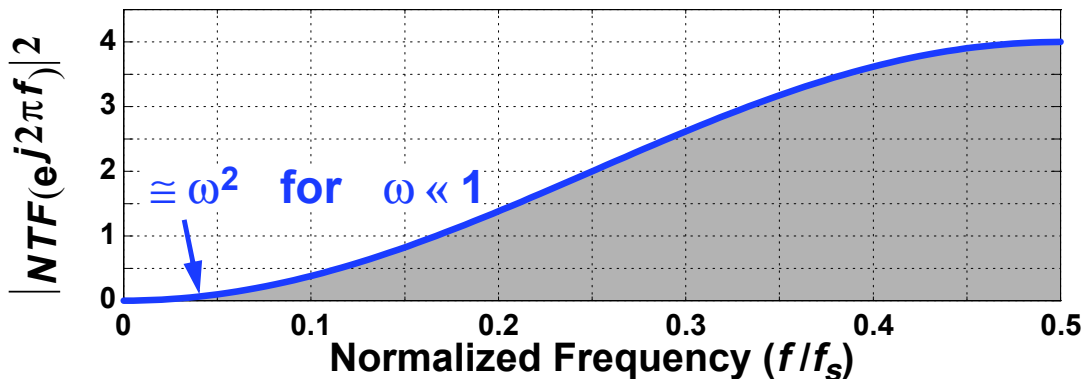
 


- Doubling OSR improves SQNR by 9 dB**
 Peak SQNR $\approx \text{dbp}(9 \cdot \text{OSR}^3 / (2\pi^2))$; $\text{dbp}(x) \equiv 10\log_{10}(x)$

ECE1371


4

Review: MOD2

  

- Doubling OSR improves SQNR by 15 dB
 Peak SQNR $\approx \text{dbp}((15 \cdot OSR^5)/(4\pi^4))$

 Review: Simulated MOD2 PSD Input at 50% of FullScale



Review: Advantages of $\Delta\Sigma$

- **ADC: Simplified Anti-Alias Filter**
Since the input is oversampled, only very high frequencies alias to the passband.
A simple RC section often suffices
If a continuous-time loop filter is used, the anti-alias filter can often be eliminated altogether.
- **DAC: Simplified Reconstruction Filter**
The nearby images present in Nyquist-rate reconstruction can be removed digitally.
- + **Inherent Linearity**
Simple structures can yield very high SNR.
- + **Robust Implementation**
 $\Delta\Sigma$ tolerates sizable component errors.

ECE1371

7


Let's Try Making One!

- **Clock at $f_s = 1$ MHz.**
Assume $BW = 1$ kHz.
- $\Rightarrow OSR = f_s / (2 \cdot BW) = 500 \approx 2^9$
- **MOD1: SQNR ≈ 9 dB/octave $\cdot 9$ octaves = 81 dB**
 - **MOD2: SQNR ≈ 15 dB/octave $\cdot 9$ octaves = 135 dB**
Actually more like 120 dB.
 - **SQNR of MOD1 is not bad, but SQNR of MOD2 is awesome!**
In addition to MOD2's SQNR advantage, MOD2 is usually preferred over MOD1 because MOD2's quantization noise is more well-behaved.

ECE1371

8

What Do We Need?

 


- 1 Summation blocks
 - 2 Delaying and non-delaying discrete-time integrators
 - 3 Quantizer (1-bit)
 - 4 Feedback DACs (1-bit)
 - 5 Decimation filter (not shown)
- Digital and therefore “easy.”

ECE1371


9

Switched-Capacitor Integrator

Single-ended circuit:

 


Timing:

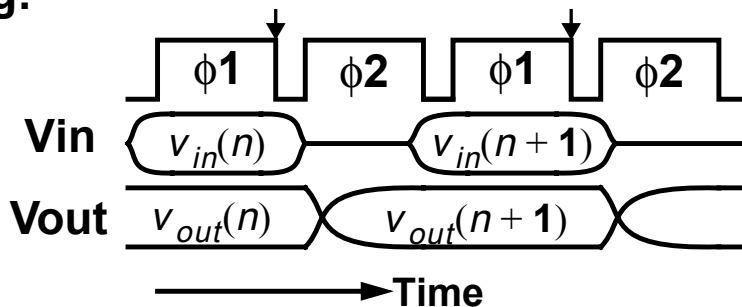


ECE1371

10

$\phi 1:$

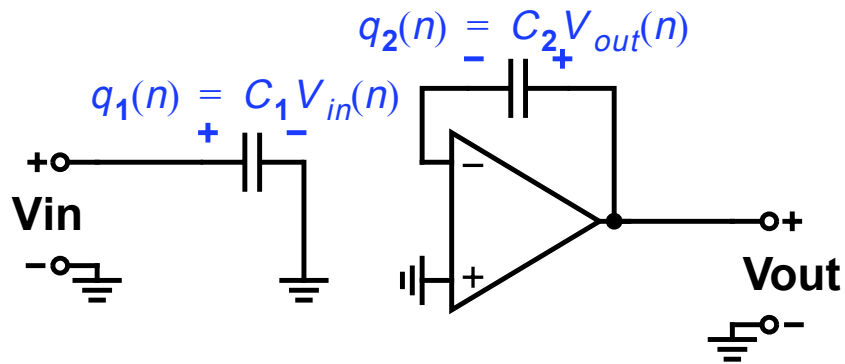

$\phi 2:$

 

ECE1371

11

$$q_2(n+1) = q_2(n) + q_1(n)$$

$$zQ_2(z) = Q_2(z) + Q_1(z)$$

$$Q_2(z) = \frac{Q_1(z)}{z-1}$$

- **This circuit integrates charge**
- **Since $Q_1 = C_1 V_{in}$ and $Q_2 = C_2 V_{out}$**

$$\frac{V_{out}(z)}{V_{in}(z)} = \frac{C_1/C_2}{z-1}$$


- **Note that the voltage gain is controlled by a *ratio* of capacitors**

With careful layout, 0.1% accuracy is possible.

ECE1371


12

Summation + Integration

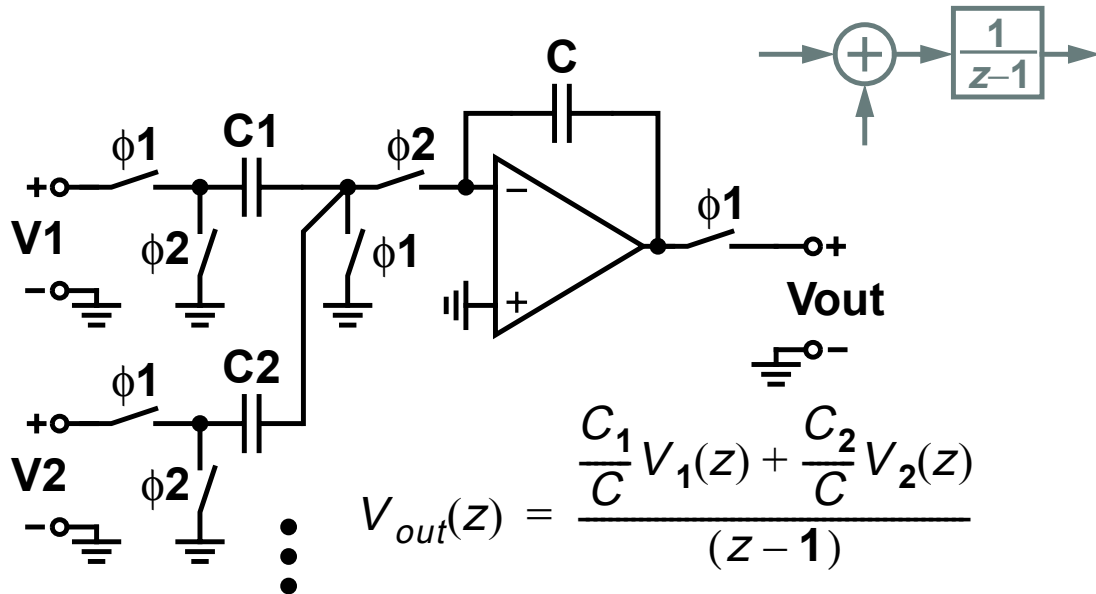


⇒ Adding an extra input branch accomplishes addition, with weighting

1b DAC + Summation + Integration

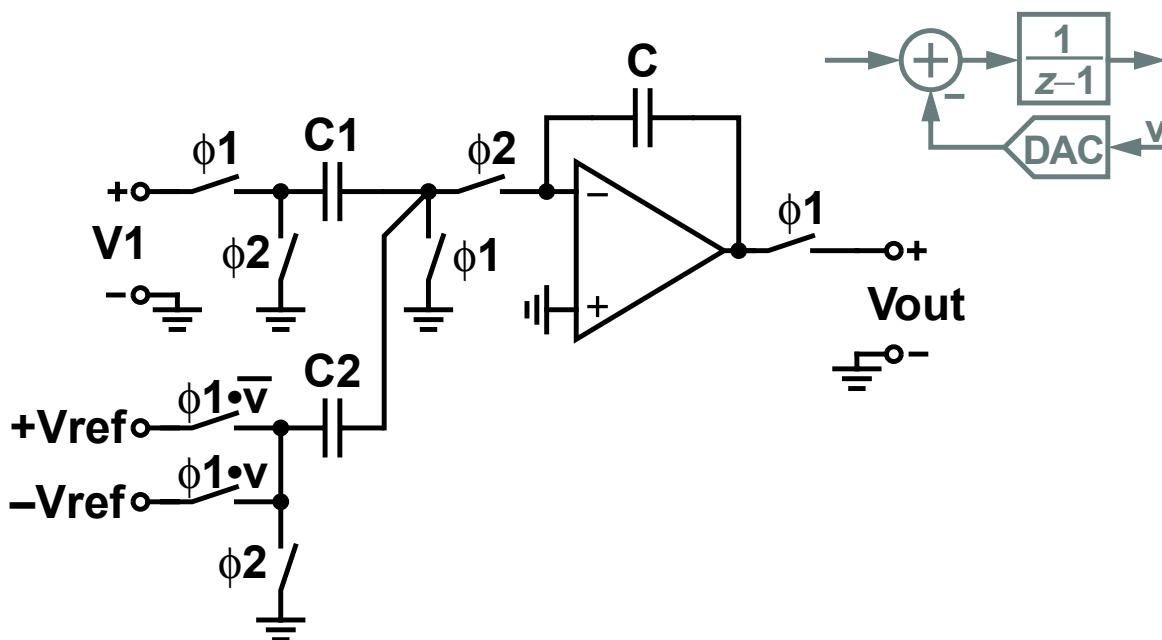

Differential Integrator

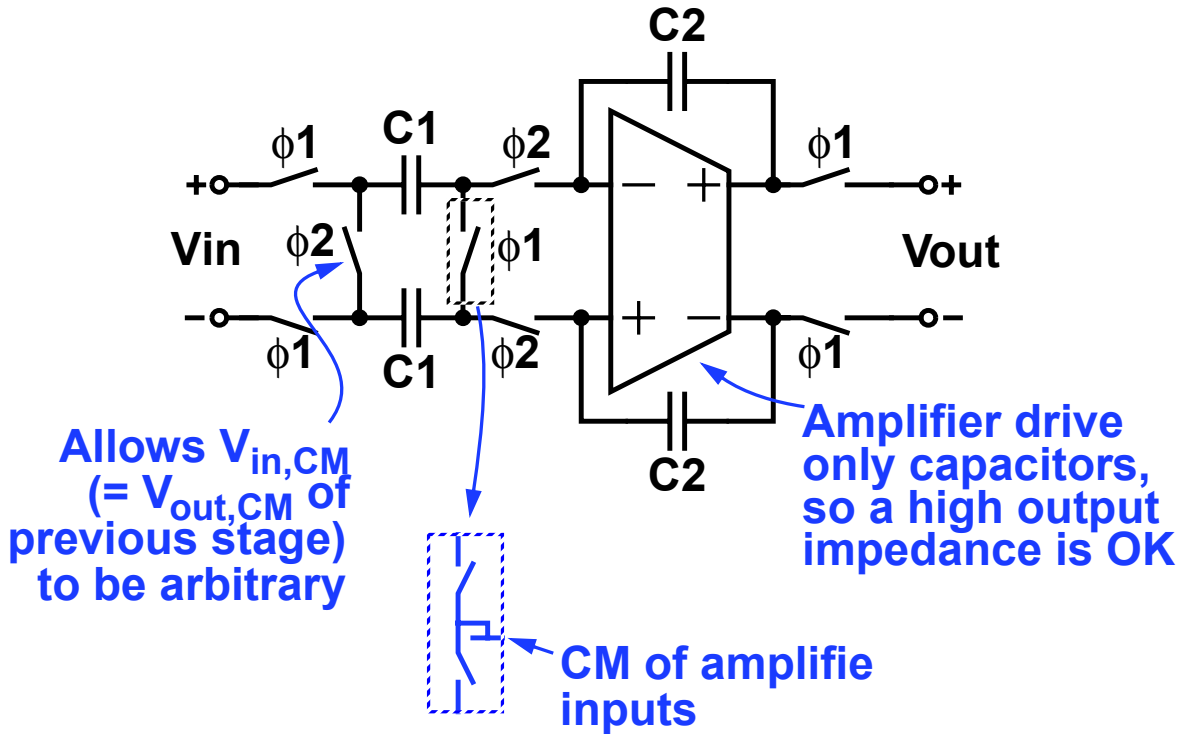


ECE1371


15

Non-Delaying Integrator

Single-ended circuit:

 


Timing:

 


ECE1371

16

$\phi 2:$

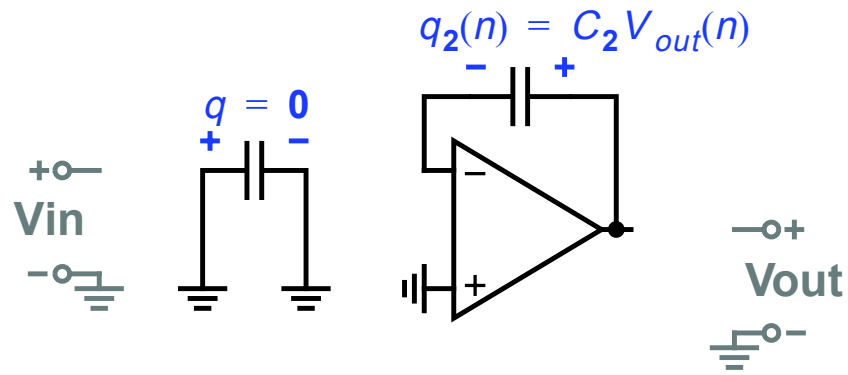

$\phi 1:$

 

ECE1371

17

$$q_2(n+1) = q_2(n) - q_1(n+1)$$

$$zQ_2(z) = Q_2(z) - zQ_1(z)$$

$$\frac{Q_2(z)}{Q_1(z)} = -\frac{z}{z-1}$$

$$\frac{V_{out}(z)}{V_{in}(z)} = -\left(\frac{C_1}{C_2}\right)\frac{z}{z-1}$$


- **Delay-free integrator (inverting)**

ECE1371


18

“Half-Delay” Integrator

Single-ended circuit:

 

Timing:

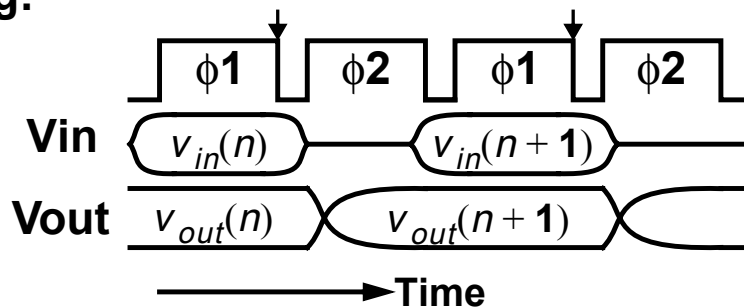

ECE1371

19

Half-Delay Integrator


- Output is sampled on a different phase than the input
 - Some use the notation $H(z) = \frac{z^{-1/2}}{z-1}$ to denote the shift in sampling time
I consider this an abuse of notation.
 - An alternative method is to declare that the border between time n and $n+1$ occurs at the end of a specific phase, say ϕ_2
- ⇒ A circuit which samples on ϕ_1 and updates on ϕ_2 is non-delaying, i.e. $H(z) = z/(z-1)$, whereas a circuit which samples on ϕ_2 and updates on ϕ_1 is delaying, i.e. $H(z) = 1/(z-1)$.

ECE1371

20

Timing in a $\Delta\Sigma$ ADC

 - The safest way to deal with timing is to construct a timing diagram and verify that the circuit implements the desired difference equations
- E.g. MOD2:




Difference Equations:

$$v(n) = Q(x_2(n)) \quad (0)$$


$$x_1(n+1) = x_1(n) - v(n) + u(n) \quad (1)$$

$$x_2(n+1) = x_2(n) - v(n) + x_1(n+1) \quad (2)$$

Switched-Capacitor Realization

 

Timing

 

Timing looks OK!

Signal Swing

- So far, we have not paid any attention to how much swing the op amps can support, or to the magnitudes of u , V_{ref} , x_1 and x_2
- For simplicity, assume:
 - the full-scale range of u is ± 1 V,
 - the op-amp swing is also ± 1 V and
 - $V_{\text{ref}} = 1$ V
- We still need to know the ranges of x_1 and x_2 in order to accomplish *dynamic-range scaling*


ECE1371

23


Dynamic-Range Scaling

- In a linear system with known state bounds, the states can be scaled to occupy any desired range

e.g. one state of original system:

 

state scaled by $1/k$:

 


ECE1371


24

Scaled MOD2

- Take $\|x_1\|_\infty = 3$ and $\|x_2\|_\infty = 9$
 The first integrator should not saturate.
 The second integrator will not saturate for dc inputs up to -3 dBFS and possibly as high as -1 dBFS.
- Our scaled version of MOD2 is thus

 


 First Integrator (INT1) Shared Input/Reference Caps



- How do we determine C?

Differential Noise

 

- Twice as many switched caps
⇒ twice as much noise power
- The input-referred noise power in our differential integrator is

$$\overline{v_n^2} = 4kT/C_1$$

ECE1371

27

INT1 Absolute Capacitor Sizes For SNR = 100 dB @ -3-dBFS input

- The signal power is

$$\overline{v_s^2} = \frac{1}{2} \cdot \frac{(1 \text{ V})^2}{2} = 0.25 \text{ V}^2$$

-3 dBFS $\frac{A^2}{2}$

- Therefore we want $\overline{v_{n, \text{in-band}}^2} = 0.25 \times 10^{-10} \text{ V}^2$
- Since $\overline{v_{n, \text{in-band}}^2} = \overline{v_n^2} / \text{OSR}$

$$C_1 = \frac{4kT}{\overline{v_n^2}} = 1.33 \text{ pF}$$


- If we want 10 dB more SNR, we need 10x caps

ECE1371

28

Second Integrator (INT2)

Separate Input and Feedback Caps

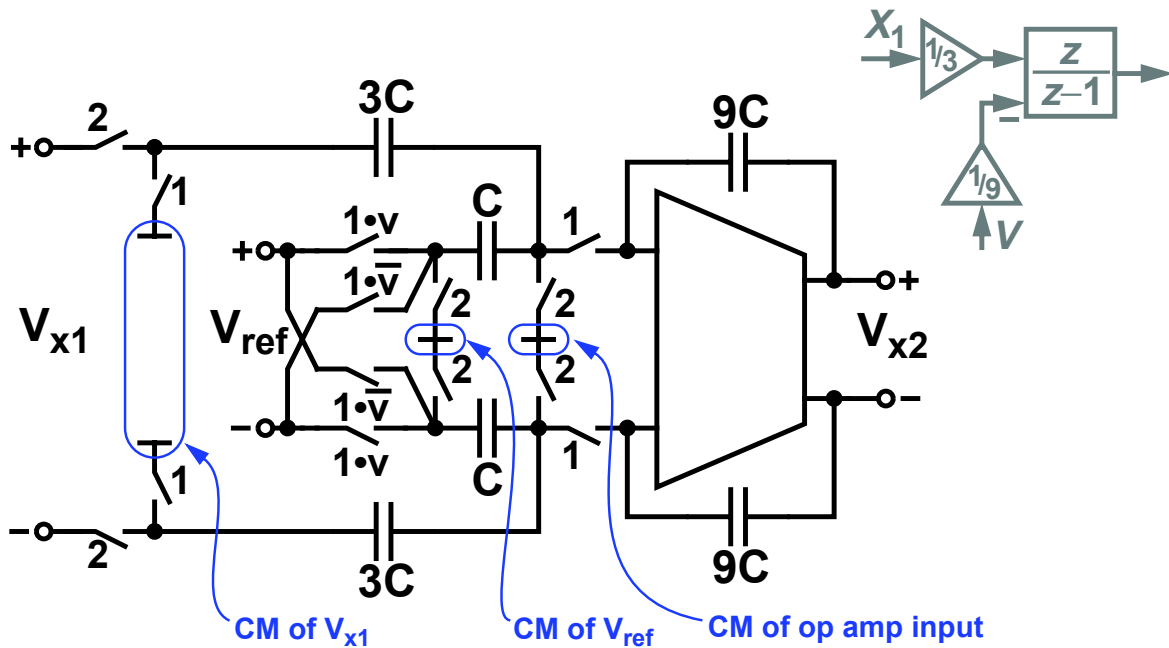


ECE1371

29

INT2 Absolute Capacitor Sizes

 - In-band noise of second integrator is greatly attenuated



$$\omega_B = \frac{\pi}{OSR}$$

$$\text{INT1 gain @ pb edge: } A = \frac{1/3}{\omega_B} = \frac{OSR}{3\pi}$$

$$\text{INT2 noise attenuation: } > OSR \cdot A^2 \approx 10^6$$

⇒ Capacitor sizes not dictated by thermal noise


- Charge injection errors and desired ratio accuracy set absolute size

A reasonable size for a small cap is currently ~10 fF.

ECE1371

30

Behavioral Schematic

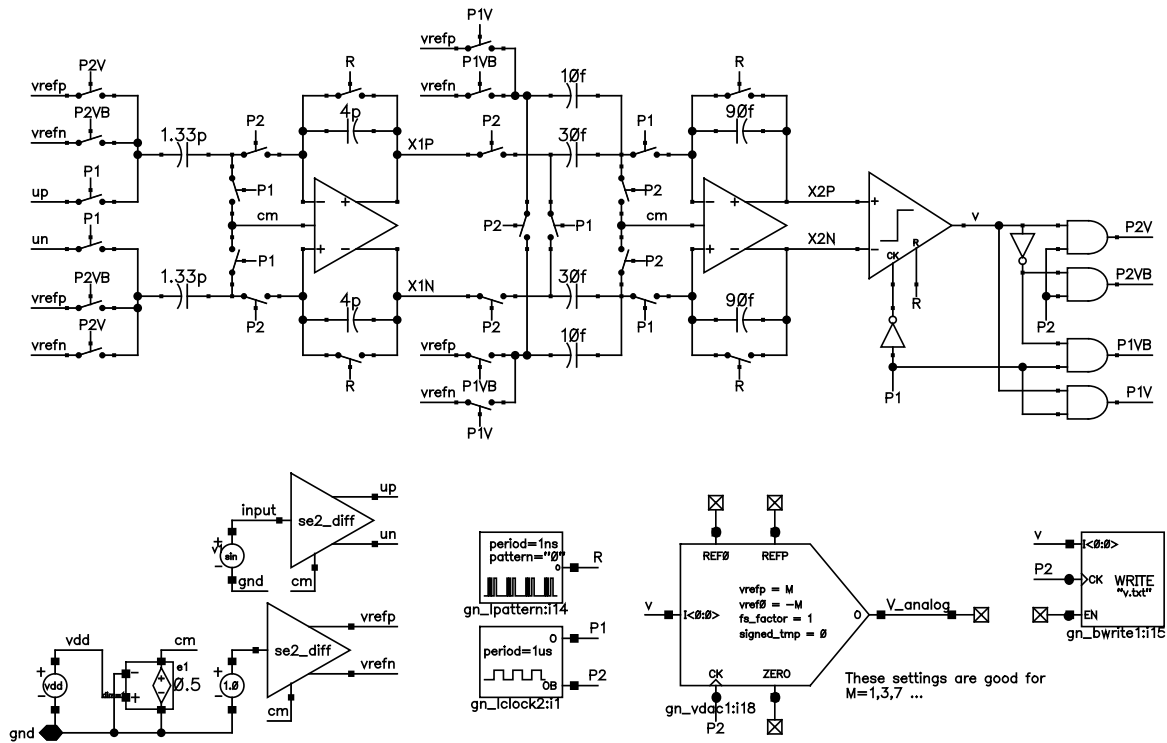

ECE1371

31

Verification

Open-loop verification

- 1 Loop filter
- 2 Comparator

Since MOD2 is a 1-bit system, all that can go wrong is the polarity and the timing. Usually the timing is checked by (1), so this verification step is not needed.

Closed-loop verification


- 3 Swing of internal states
- 4 Spectrum: SQNR, STF gain
- 5 Sensitivity, start-up, overload recovery, ...

ECE1371

32

Loop-Filter Check— Theory

 - Open the feedback loop, set $u = 0$ and drive an impulse through the feedback path




$$X_2 = \frac{-1}{z-1} \left(1 + \frac{z}{z-1} \right) Y$$

$$\therefore y(n) = \{1, 0, 0, \dots\} \Rightarrow x_2(n) = \{-2, -3, -4, \dots\}$$

- If x_2 is as predicted then the loop filter is correct
At least for the feedback signal, which implies that the NTF will be as designed.

Loop Filter Check— Practice*

 

*. "In theory there is no difference between theory and practice.
But in practice there is."

Hey! You Cheated!

- An impulse is $\{1,0,0,\dots\}$, but a binary DAC can only output ± 1 , i.e. it cannot produce a 0

Q: So how can we determine the impulse response of the loop filter through simulation?


A: Do two simulations: one with $v = \{-1,-1,-1,\dots\}$ and one with $v = \{+1,-1,-1,\dots\}$.

Then take the difference.


According to superposition, the result is the response to $v = \{2,0,0,\dots\}$, so divide by 2.

To keep the integrator states from growing too quickly, you could also use $v = \{-1,-1,+1,-1,\dots\}$ and then $v = \{+1,-1,+1,-1,\dots\}$.

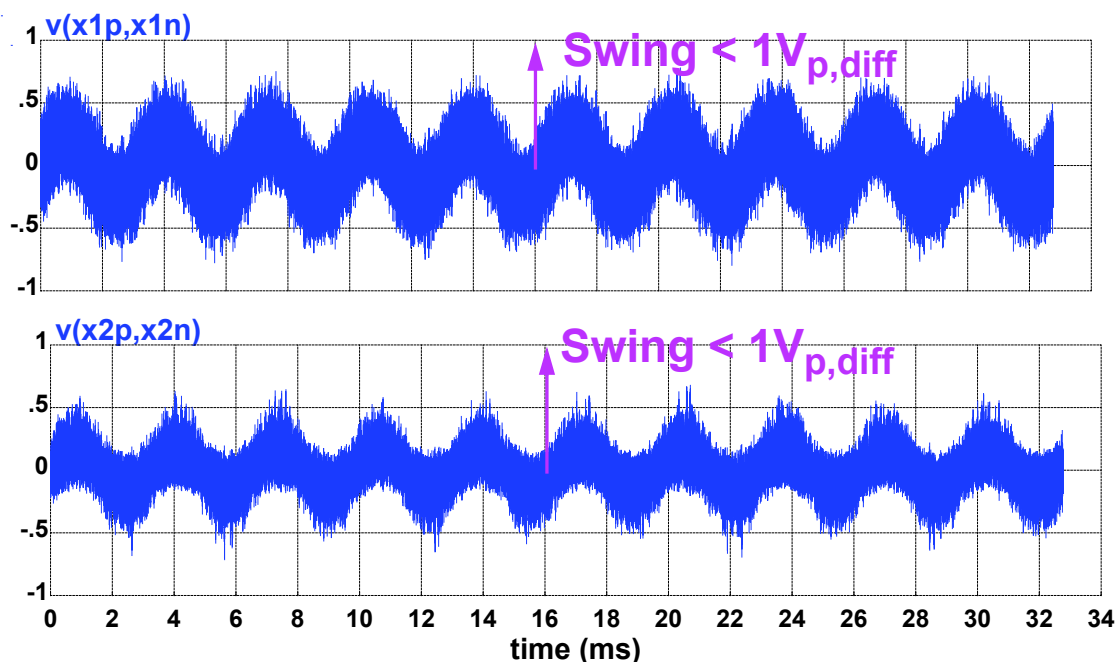Simulated State Swings -3-dBFS ~300-Hz sine wave




Unclear Spectrum

 

ECE1371

37

Professional Spectrum

 

- SQNR dominated by -109 -dBFS 3rd harmonic

ECE1371

38

Implementation Summary


- 1 Choose a viable SC topology and manually verify timing
- 2 Do dynamic-range scaling
You now have a set of capacitor ratios.
Verify operation: loop filter, timing, swing, spectrum.
- 3 Determine absolute capacitor sizes
Verify noise.
- 4 Determine op-amp specs and construct a transistor-level schematic
Verify everything.

ECE1371


39

Differential vs. Single-Ended

 - Differential is more complicated and has more caps and more noise \Rightarrow single-ended is better?


 
$$SNR = \frac{(2V)^2/2}{4kT/(C/2)} = \frac{CV^2}{4kT}$$




$$SNR = \frac{V^2/2}{2kT/C} = \frac{CV^2}{4kT}$$

- Same capacitor area \Rightarrow same SNR
Differential is generally preferred due to rejection of even-order distortion and common-mode noise/interference.

ECE1371

40

Double-Sampled Input

 


- Doubles the effective input signal
- Allows C_1 to be 1/4 the size for the same SNR
- Doubles the sampling rate of the signal, thereby easing AAF further

ECE1371

41

Shared vs. Separate Input Caps

- Separate caps \Rightarrow More noise:

 

$$V_1 \text{ input: } \overline{v_{n1}^2} = 2kT/C_1$$

$$V_2 \text{ input: } \overline{v_{n2}^2} = 2kT/C_2$$

$$V_2 \text{ gain} / V_1 \text{ gain: } C_2/C_1$$

$$v_{n2} \text{ referred to } V_1: v_{n2}C_2/C_1$$

$$\text{Total noise referred to } V_1: (2kT/C_1)(1 + C_2/C_1)$$


- But using separate caps allows input CM to be different from reference CM, and so is often preferred in a general-purpose ADC

ECE1371

42

Signal-Dependent Ref. Loading

 
- Another practical concern is the current draw from the reference



$$\text{ADC Output} \propto \frac{V_{in}}{V_{ref}(1 - \epsilon \sin \omega t)} \approx \frac{V_{in}}{V_{ref}} (1 + \epsilon \sin \omega t)$$

- If the reference current is signal-related, harmonic distortion can result

Shared Caps and Ref. Loading

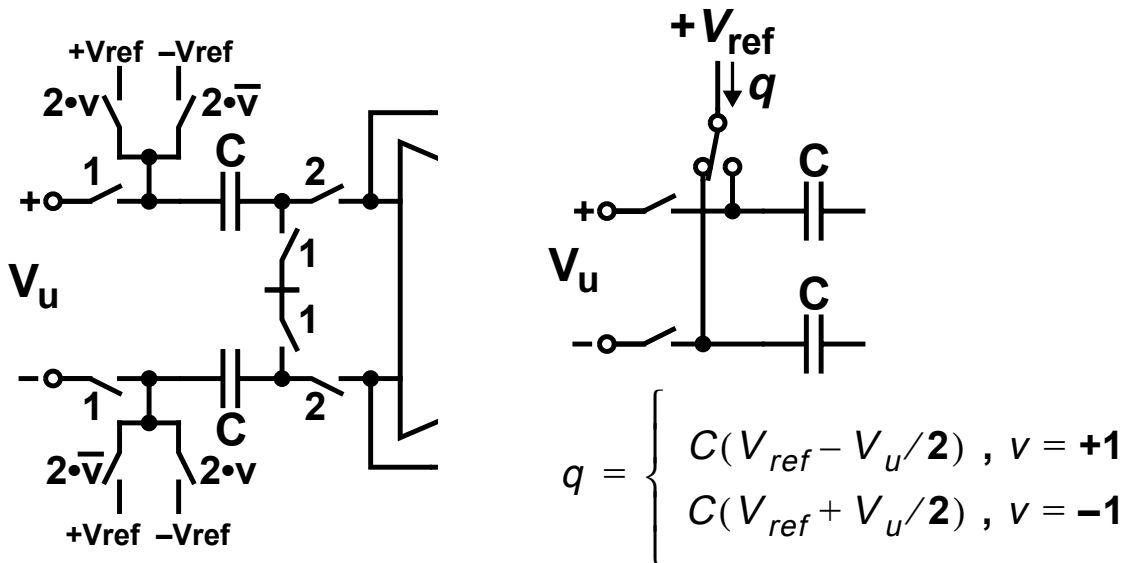

Thus

$$\bar{i} = \frac{C}{T}(V_{ref} - v \cdot V_u/2)$$


- If $u = A\sin\omega_u t$, then $v = u + error$ also contains a component at ω_u and thus I contains a component at $\omega = 2\omega_u$.
- Since ADC Output $\propto V_{in}(1 + \varepsilon \sin\omega t)$, the signal-dependent reference current in our circuit can produce 3rd-harmonic distortion

Also, the load presented to the driving circuit is dependent on v and this noisy load can cause trouble.

- With separate caps, the reference current is signal-independent


Yet another reason for using separate caps.

Unipolar Reference

 

- Be careful of the timing of v relative to the integration phase!


Single-Ended Input Shared Caps

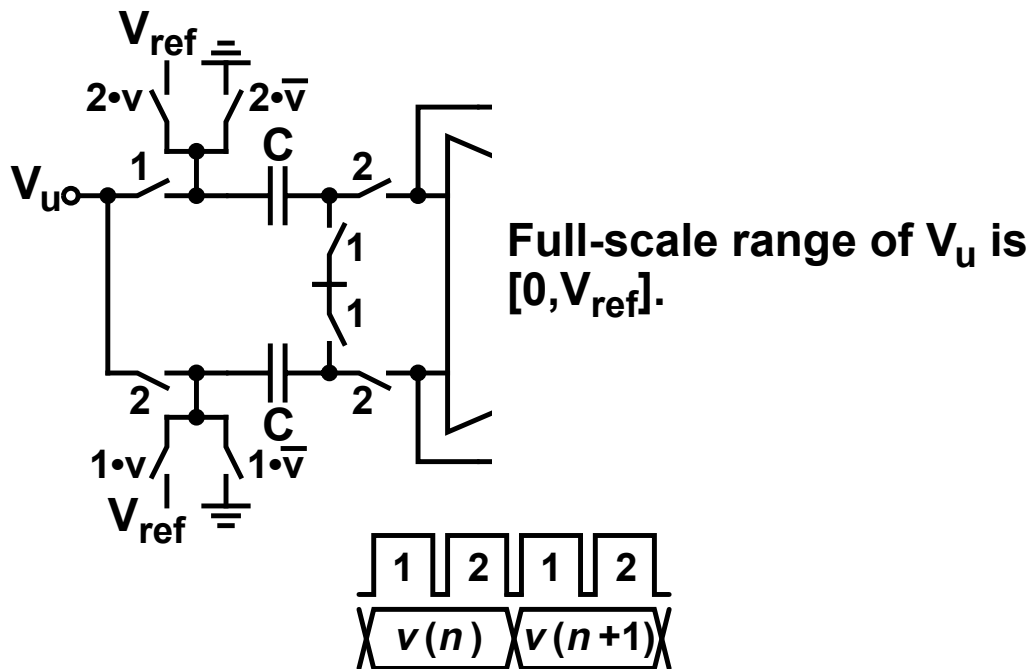

ECE1371

47

Topological Variant– Feed-Forward

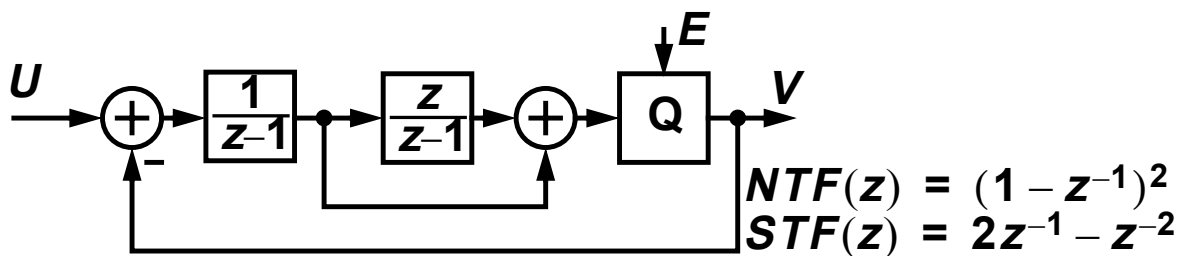


- + Output of first integrator has no DC component
Dynamic range requirements of this integrator are relaxed.
- Although $|STF| \approx 1$ near $\omega = 0$,
 $|STF| = 3$ for $\omega = \pi$
Instability is more likely.

ECE1371

48

 Topological Variant– Feed-Forward with Extra Feed-In




- + No DC component in either integrator's output
Reduced dynamic range requirements in both integrators, esp. for multi-bit modulators.
- + Perfectly flat STF
No increased risk of instability.
- Timing is tricky

ECE1371

49

Topological Variant– Error Feedback

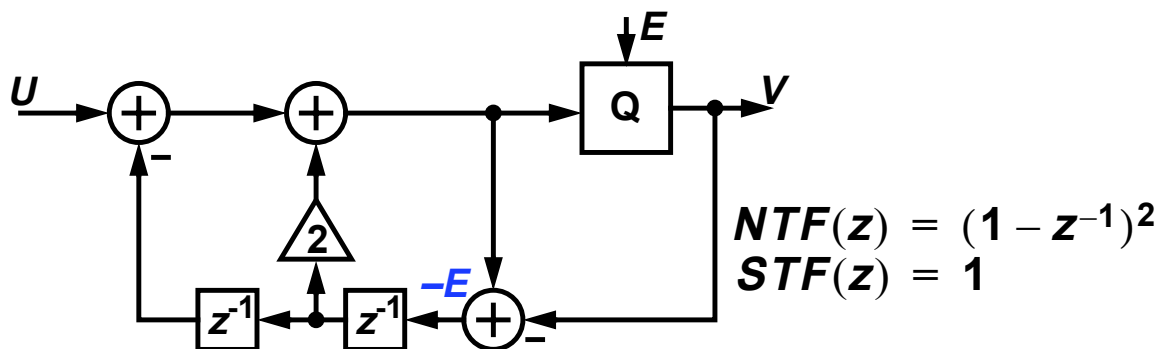

- + Simple
- Very sensitive to gain errors
Only suitable for digital implementations.

ECE1371

50

Is MOD2 The Only 2nd-Order Modulator?

- Except for the filtering provided by the STF, any modulator with the same NTF as MOD2 has the same input-output behavior as MOD2
 - SQNR curve is the same.
 - Tonality of the quantization noise is unchanged.
- Internal states, sensitivity, thermal noise etc. can differ from realization to realization


BUT, in terms of input-output behavior,

- A 2nd-order modulator is truly different only if it possesses a truly different (2nd-order) NTF

ECE1371

51


A Better 2nd-Order NTF

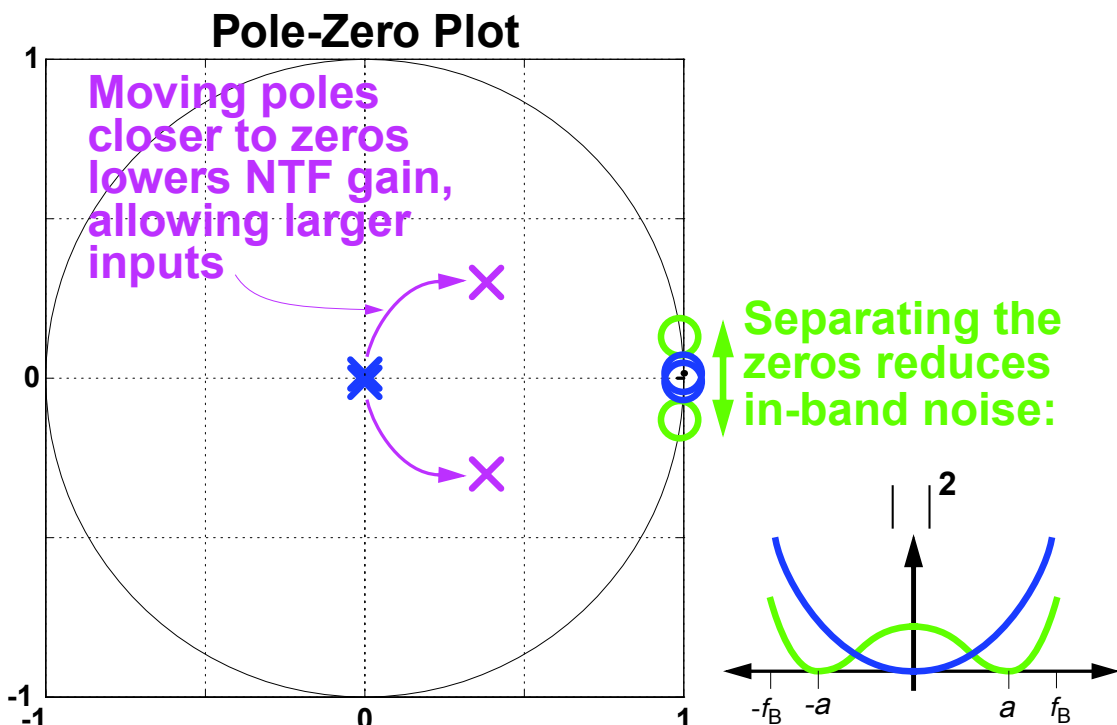

ECE1371

52


NTF Comparison

 

ECE1371

53

SNR vs. Amp Comparison

 


ECE1371

54

MOD2 Internal Waveforms

Input @ 75% of FS

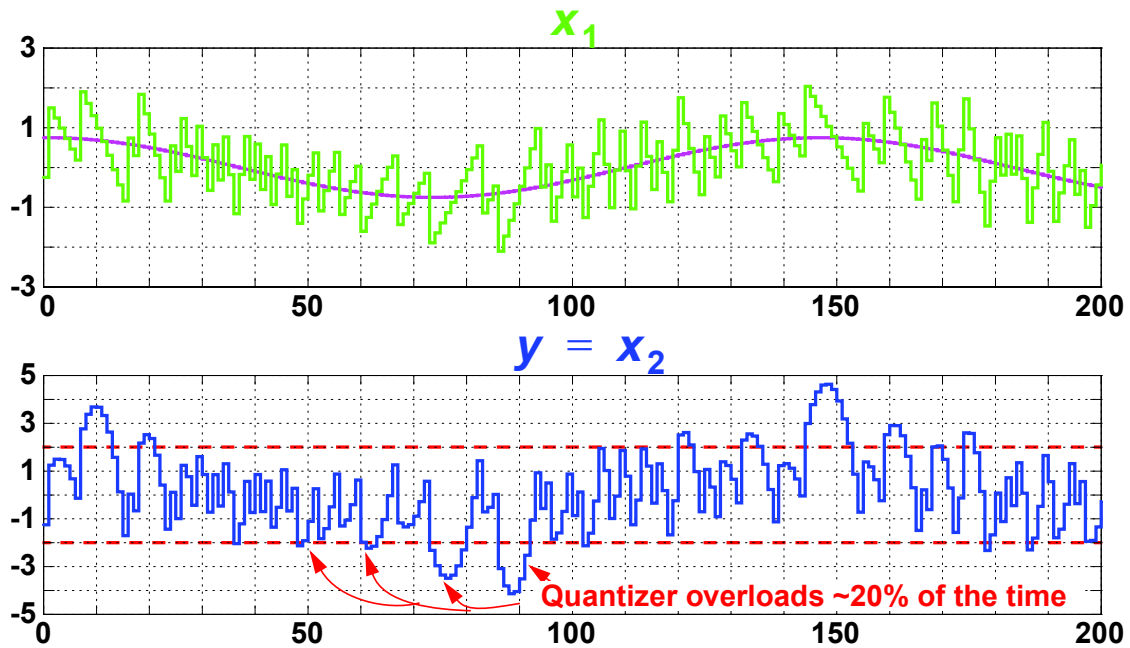


ECE1371

55

MOD2b Internal Waveforms


Input @ 75% of FS

 

ECE1371

56

Gain of a Binary Quantizer

 

- The effective gain of a binary quantizer is not known a priori
- The gain (k) depends on the statistics of the quantizer's input
 - Halving the signal doubles the gain.

ECE1371

57


Gain of the Quantizer in MOD2

- The effective gain of a binary quantizer can be computed from the simulation data using

$$k = \frac{E[|y|]}{E[y^2]} \text{ [S\&T Eq. 2.5]}$$

- For the simulation of 2-14, $k = 0.63$
- $k \neq 1$ alters the NTF:


$$NTF_k(z) = \frac{NTF_1(z)}{k + (1 - k)NTF_1(z)}$$

 

ECE1371

58

Revised PSD Prediction

 

- Agreement is now excellent

Variable Quantizer Gain

- When the input is small (below -12 dBFS), the effective gain of MOD2's quantizer is $k = 0.75$
- MOD2's "small-signal NTF" is thus

$$NTF(z) = \frac{(z - 1)^2}{z^2 - 0.5z + 0.25}$$
- This NTF has 2.5 dB less quantization noise suppression than the $(1 - z^{-1})^2$ NTF derived from the assumption that $k = 1$

Thus the SQNR should be about 2.5 dB lower than ✖.

- As the input signal increases, k decreases and the suppression of quantization noise degrades. SQNR increases less quickly than the signal power. Eventually the SQNR saturates and then decreases as the signal power reaches full-scale.