

University of Toronto

Final Exam

Date — Dec 12, 2016

Duration — 2.5 hrs

ECE 331 — Analog Electronics

Lecturer — D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

- Equation sheet is on the last page of this test.
 - Unless otherwise stated, use transistor parameters on equation sheet and assume $g_m r_o \gg 1$
 - Non-programmable calculator is allowed; No other aids are allowed
 - Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.
-

Last Name: SOLUTIONS


First Name: _____

Student #: _____

Question	1	2	3	4	5	6	Total
Points:	6	6	6	6	6	6	36
Score:							

Grading Table (do not write in above table)

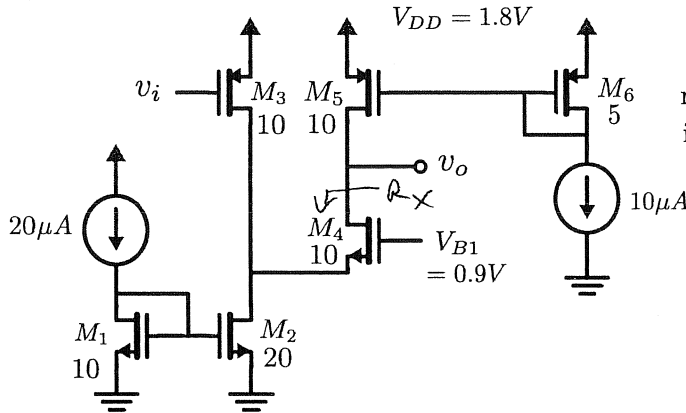Q1. Consider the amplifier shown below where all transistor lengths are $0.18 \mu m$.



numbers under transistor name indicate W/L

n-channel

$$V_{OV} = \sqrt{\frac{2I_D}{\mu_n C_{ox} (\frac{W}{L})}}$$

$$V_{OV} = 0.0913 \sqrt{I_D} (\frac{W}{L})^{-1/2}$$

[2]

(a) Calculate the drain currents, overdrive voltages and r_o for all the transistors.

$$I_{D1} = \underline{20 \mu A} \quad I_{D2} = \underline{40 \mu A} \quad I_{D6} = \underline{10 \mu A}$$

$$I_{D5} = \underline{20 \mu A} \quad I_{D4} = \underline{20 \mu A} \quad I_{D3} = I_{D2} - I_{D4} = \underline{20 \mu A}$$

$$V_{OV1} = V_{OV2} = \underline{0.129 V}$$

$$V_{OV4} = \underline{0.129 V}$$

$$V_{OV5} = V_{OV6} = \underline{0.2582}$$

$$V_{OV3} = \underline{0.2582}$$

p-channel

$$V_{OV} = 0.1826 \sqrt{I_D} (\frac{W}{L})^{-1/2}$$

$$\lambda = \frac{\lambda'}{L} = \frac{0.05}{0.18} = 0.278$$

$$r_o = \frac{1}{\lambda I_D} = \frac{3.6}{I_D}$$

$$r_{o1} = r_{o3} = r_{o4} = r_{o5} = \underline{180 k}$$

$$r_{o2} = \underline{90 k} \quad r_{o6} = \underline{360 k}$$

- [2] (b) Find the maximum V_{omax} and minimum V_{omin} DC voltage at the output while keeping all transistors in the active region.

$$V_{OMAX} = V_{DD} - V_{OV5} = \underline{\underline{1.54V}}$$

$$V_{OMIN} = V_{BI} - V_{EN} = 0.9 - 0.4 = \underline{\underline{0.5V}}$$

- [2] (c) Estimate the small-signal gain v_o/v_i . (CAN IGNORE)

$$\underline{R_{out}} \quad R_{out} = R_x \parallel r_{o5}$$

$$R_x \cong (1 + g_{m4} (r_{o2} \parallel r_{o3})) r_{o4} \cong g_{m4} (r_{o2} \parallel r_{o3}) r_{o4}$$

$$g_m = \frac{2I_D}{V_{OV}} \Rightarrow g_{m4} = 0.31 \text{ mA/V}$$

$$g_{m3} = 0.155 \text{ mA/V}$$

$$R_x \cong (0.31 \text{ mA/V}) (60k) (180k) \cong 3.35 \text{ M}\Omega$$

$$R_{out} = (3.35 \text{ M}) \parallel 180k = 170k \cong \underline{\underline{180k}}$$

$$I_{sc} = g_{m3} v_i = (0.155 \text{ e-3}) v_i$$

$$v_o = -I_{sc} R_{out} = (0.155 \text{ e-3}) (180k) v_i$$

$$\frac{v_o}{v_i} \cong 28 \frac{V}{V}$$

Q2. Using the transistor parameters on the equation sheet, consider a transistor of size $W = 2\mu\text{m}$ and $L = 0.18\mu\text{m}$.

- [2] (a) Assuming the transistor is biased in the active region and assuming $V_{sb} = 0$, find the values of C_{gs} , C_{gd} , and C_{db} for the transistor (all in fF).

$$C_{gp} = \left(\frac{2}{3}\right)WL C_{ox} + W L_{ov} C_{ox} = 2.04 + 0.68 = \underline{\underline{2.72 \text{ fF}}}$$

$$C_{gd} = W L_{ov} C_{ox} = \underline{\underline{0.68 \text{ fF}}}$$

$$C_{db} = \frac{C_{db0}}{W} \times W = 0.3 \times 2 = \underline{\underline{0.6 \text{ fF}}}$$

- [2] (b) If $V_{ov} = 0.2\text{V}$, find the unity gain freq of the transistor in Hz (do not ignore C_{gd}).

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov} = (240 \text{e-}6) \left(\frac{2}{0.18}\right) 0.2 = 5.33 \text{e-}4 \text{ A/V}$$

$$f_t = \frac{g_m}{2\pi(C_{gp} + C_{gd})} = \underline{\underline{24.97 \text{ GHz}}}$$


- [2] (c) Besides noise, give 2 reasons why bias voltages for current mirrors are NOT sent a long distance in a microchip. (Explain clearly).

= CURRENT MISMATCH - CAUSED BY EITHER

⇒ TRANSISTOR V_E MISMATCH DUE TO TRANSISTORS BEING FAR AWAY

⇒ SOURCE VOLTAGE OF TRANSISTORS BEING DIFFERENT DUE TO CURRENT IN GROUND OR POWER SUPPLIES LINES LINES

Q3. Consider the amplifier shown below.

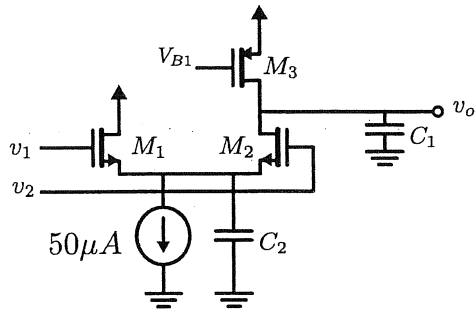

$$V_{ov1} = V_{ov2} = 0.1V$$

$$V_{ov3} = 0.4V$$

$$\text{All } r_o = 100k$$

$$C_1 = 1pF$$

$$C_2 = 2pF$$

$$g_{m1} = g_{m2} = \frac{2I_D}{V_{ov}} = \frac{0.5 \text{ mA/V}}{0.1V} = \frac{1}{2k}$$

[2] (a) Defining $v_i = v_1 - v_2$, find the dc gain v_o/v_i .

$$R_{out} = r_{o3} \parallel \left[\left(1 + g_{m2} \left(\frac{1}{g_{m1}} \right) \right) r_{o2} \right] = r_{o3} \parallel 2r_{o2} = 67k\Omega$$

$$I_{sc} = \frac{v_i}{r_{s1} + r_{s2}} = \frac{v_i}{4k}$$

$$v_o = I_{sc} R_{out} = \frac{67k}{4k} v_i = 16.7 v_i$$

$$\frac{v_o}{v_i} = \underline{\underline{16.7 \text{ V/V}}}$$

[2] (b) Find the poles due to C_1 and C_2 in Hz.

$$C_1 \Rightarrow \omega_{p1} = \frac{1}{25 \text{ nA} (R_{out} C_1)} = \frac{1}{25 \text{ nA} (67k)(1pF)} = \underline{\underline{2.37 \text{ MHz}}}$$

$$C_2 \Rightarrow \omega_{p2} = \frac{1}{25 \text{ nA} C_2 (r_{s1} \parallel \left[\frac{1}{g_{m2}} + \frac{r_{o3}}{g_{m2} r_{o2}} \right])} = \frac{1}{25 \text{ nA} C_2 (r_{s1} \parallel 2r_{s2})}$$

$$\omega_{p2} = \underline{\underline{60 \text{ MHz}}}$$

ESTIMATE


[2] (c) For the case where v_o is connected to v_2 , find the dc gain and 3dB freq for v_o/v_1 .

$$\beta = 1 \Rightarrow A_{cl} = \frac{A_o}{1 + A_o \beta} = \frac{16.7}{1 + 16.7} = \underline{\underline{0.94 \text{ V/V}}}$$


$$3\text{dB FREQ} \Rightarrow f_{3dB} \hat{=} f_{3dB} \times A_o = (2.37 \text{ MHz})(17)$$

$$\hat{=} \underline{\underline{40 \text{ MHz}}}$$

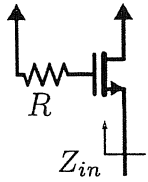Q4. Consider the input impedance looking into the source of the circuit below. Let $r_o \rightarrow \infty$ and only consider capacitance C_{gs} .



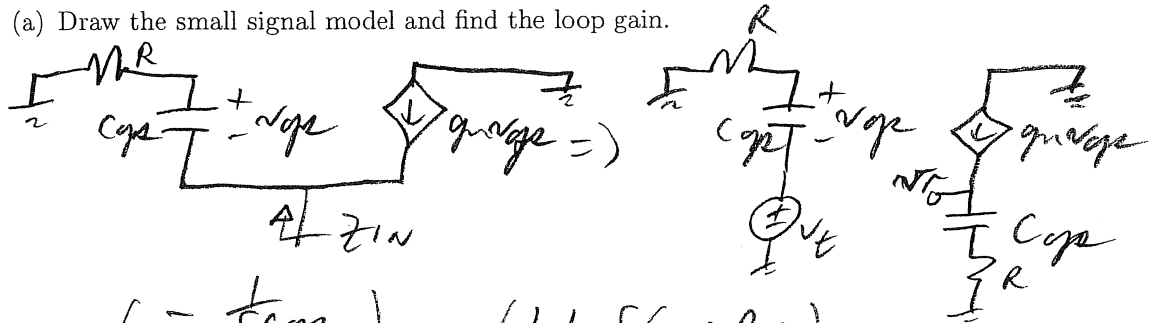[3] (a) Draw the small signal model and find the loop gain.



$$L_o = - \left(\frac{-\frac{1}{sC_{gs}}}{\frac{1}{sC_{gs}} + R} \right) g_m \left(\frac{1 + sC_{gs}R}{sC_{gs}} \right)$$

$$L_o = \frac{g_m}{sC_{gs}} \quad L_s = 0$$


[3] (b) Using the loop gain found above, find Z_{in} .

$$Z_{po} = R + \frac{1}{sC_{gs}} = \frac{1 + sC_{gs}R}{sC_{gs}}$$

$$Z_{in} = Z_{po} \left[\frac{1 + L_s}{1 + L_o} \right] = \left(\frac{1 + sC_{gs}R}{sC_{gs}} \right) \left(\frac{1}{1 + \frac{g_m}{sC_{gs}}} \right)$$

$$Z_{in} = \left(\frac{1 + sC_{gs}R}{g_m + sC_{gs}} \right) = \left(\frac{1}{g_m} \right) \left(\frac{1 + sC_{gs}R}{1 + \frac{sC_{gs}}{g_m}} \right)$$

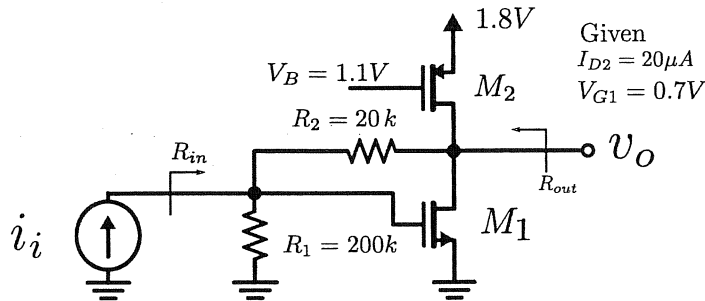Q5. Consider the current to voltage amplifier shown below where i_i is nominally zero.



- [2] (a) Find the dc operating points V_{D1} , g_{m1} , g_{m2} , r_{o1} , r_{o2} . (note I_{D2} and V_{G1} given)

$$I_{R1} = \frac{V_{G1}}{R1} = 3.5 \mu A \Rightarrow V_{D1} = V_{G1} + I_{R1} R1 = \underline{\underline{0.77V}}$$

$$I_{D1} = I_{D2} - I_{R1} = 16.5 \mu A$$

$$V_{ov1} = 0.7 - V_{G1} = 0.3V \quad V_{ov2} = (V_{DD} - V_B) - |V_{G1}| = 0.3V$$

$$g_{m1} = \frac{2I_{D1}}{V_{ov1}} = \underline{\underline{0.11 \text{ mA/V}}} \quad g_{m2} = \frac{2I_{D2}}{V_{ov2}} = \underline{\underline{0.133 \text{ mA/V}}}$$

$$r_{o1} = \frac{3.6}{I_{D1}} = \underline{\underline{218 \text{ k}\Omega}} \quad r_{o2} = \frac{3.6}{I_{D2}} = \underline{\underline{180 \text{ k}\Omega}}$$

- [4] (b) Find A_{∞} , L , ϕ , A_{CL} , R_{in} , and R_{out} .

$$A_{\infty} \equiv \frac{v_o}{i_i} \Big|_{L \rightarrow \infty} = \underline{\underline{20k}}$$

$$L = (g_{m1}) \left[\overbrace{\left[(R1 + R2) \parallel r_{o2} \right]}^{99k} \parallel r_{o1} \right] \left(\frac{R1}{R1 + R2} \right)$$

$$L = \underline{\underline{6.8}}$$

$$A_{CL} = A_{\infty} \left(\frac{L}{1+L} \right) = \underline{\underline{17.4k}}$$

$$R_{out} = \left[r_{o2} \parallel r_{o1} \parallel (R1 + R2) \right] \left(\frac{1}{1+L} \right) = (60k) \left(\frac{1}{1+L} \right) = \underline{\underline{8.7 \text{ k}\Omega}}$$

$$R_{in} = \left[R1 \parallel (R2 + (r_{o2} \parallel r_{o1})) \right] \left(\frac{L}{1+L} \right) = 74.4 \left(\frac{L}{1+L} \right) = \underline{\underline{9.5 \text{ k}\Omega}}$$

Q6. Consider a feedback amplifier that has a low frequency gain of 10^5 , a dominant pole at 10 rad/s and a pair of non-dominant poles at 10^5 rad/s.

- [4] (a) Assuming the feedback factor, β , is independent of frequency, find the value of β that will result in a 60° phase margin.

$$A(s) = \frac{A_0}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}})^2}$$

$$A_0 = 10^5 \quad \omega_{p1} = 10 \\ \omega_{p2} = 10^5$$

WANT TO FIND ω_{60} WHERE $\angle A(j\omega_{60}) = -120^\circ$
FOR PM = 60°

ASSUME $\omega_{60} \gg \omega_{p1}$ SINCE $A_0 \gg 1$

$$\angle A(j\omega_{60}) = -90^\circ - 2 \tan^{-1}\left(\frac{\omega_{60}}{\omega_{p2}}\right) = -120^\circ$$

$$\Rightarrow \tan^{-1}\left(\frac{\omega_{60}}{\omega_{p2}}\right) = +15^\circ \Rightarrow \omega_{60} = 0.268 \omega_{p2} = 26.8 \text{ kRAD/S}$$

WANT $|A\beta| = 1$ AT $\omega = \omega_{60} = 26.8 \text{ kRAD/S}$

$$\frac{A_0 \beta}{\left(\frac{\omega_{60}}{\omega_{p1}}\right) \left(1 + \left(\frac{\omega_{60}}{\omega_{p2}}\right)^2\right)} = 1 \Rightarrow A_0 \beta = 2872$$

$$\beta = \underline{\underline{0.0287}}$$

- [2] (b) For the β found above and a step voltage applied to the input of the closed-loop amplifier, estimate the time it takes to settle to 90% of the final value.

$$\omega_{3dB}' \approx \omega_{3dB} L_0 = \omega_{3dB} A_0 \beta = (10)(10^5)(0.0287)$$

$$\omega_{3dB}' \approx 287000 \text{ RAD/S} \Rightarrow \tau' = \frac{1}{\omega_{3dB}'} = 34.8 \mu\text{s}$$

TO SETTLE TO 90% OF FINAL VALUE

$$(1 - e^{-\frac{t}{\tau'}}) = 0.9 \Rightarrow e^{-\frac{t}{\tau'}} = 0.1 \Rightarrow \frac{t}{\tau'} = 2.3$$

$$t = 2.3 \times \tau' = \underline{\underline{80.1 \mu\text{s}}}$$

Equation Sheet


Constants: $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \simeq 26\text{mV}$ at 300K; $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$;
 $k_{ox} = 3.9$; $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$; $\omega = 2\pi f$

NMOS: $k_n = \mu_n C_{ox}(W/L)$; $V_{tn} > 0$; $v_{DS} \geq 0$; $V_{ov} = v_{GS} - V_{tn}$
(triode) $v_{DS} \leq V_{ov}$; $v_D < v_G - V_{tn}$; $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$
(active) $v_{DS} \geq V_{ov}$; $i_D = 0.5k_nV_{ov}^2(1 + \lambda v_{DS})$; $g_m = k_nV_{ov} = 2I_D/V_{ov} = \sqrt{2k_nI_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda'I_D|)$

PMOS: $k_p = \mu_p C_{ox}(W/L)$; $V_{tp} < 0$; $v_{SD} \geq 0$; $V_{ov} = v_{SG} - |V_{tp}|$
(triode) $v_{SD} \leq V_{ov}$; $v_D > v_G + |V_{tp}|$; $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$
(active) $v_{SD} \geq V_{ov}$; $i_D = 0.5k_pV_{ov}^2(1 + |\lambda|v_{SD})$; $g_m = k_pV_{ov} = 2I_D/V_{ov} = \sqrt{2k_pI_D}$; $r_s = 1/g_m$;
 $r_o = L/(|\lambda'I_D|)$

BJT: (active) $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$; $g_m = \alpha/r_e = I_C/V_T$; $r_e = V_T/I_E$; $r_\pi = \beta/g_m$; $r_o = |V_A|/I_C$;
 $i_C = \beta i_B$; $i_E = (\beta + 1)i_B$; $\alpha = \beta/(\beta + 1)$; $i_C = \alpha i_E$; $R_b = (\beta + 1)(r_e + R_E)$; $R_e = (R_B + r_\pi)/(\beta + 1)$

Cascode:

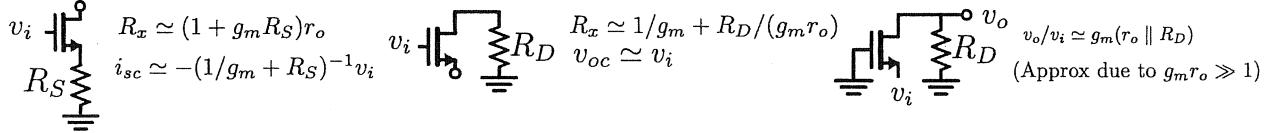

Diff Pair: $A_d = g_m R_D$; $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$; $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$; $V_{OS} = \Delta V_i$; $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$; $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$

1st order: step response $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$; unity gain freq for $T(s) = \frac{A_M}{1 + (s/\omega_{3dB})}$ for $A_M \gg 1 \Rightarrow$
 $\omega_t \simeq |A_M|\omega_{3dB}$

Freq: for real axis poles/zeros $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$
OTC estimate $\omega_H \simeq 1/(\sum \tau_i)$; dominant pole estimate $\omega_H \simeq 1/(\tau_{max})$

Miller: $Z_1 = Z/(1 - K)$; $Z_2 = Z/(1 - 1/K)$

Mos caps: $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$; $C_{gd} = WL_{ov}C_{ox}$; $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$;
 $\omega_t = g_m/(C_{gs} + C_{gd})$; for $C_{gs} \gg C_{gd} \Rightarrow f_t \simeq (3\mu V_{ov})/(4\pi L^2)$

Feedback: $A_f = A/(1 + A\beta)$; $x_i = (1/(1 + A\beta))x_s$; $dA_f/A_f = (1/(1 + A\beta))dA/A$; $\omega_{Hf} = \omega_H(1 + A\beta)$; $\omega_{Lf} = \omega_L/(1 + A\beta)$;

Loop Gain $L \equiv -s_r/s_t$; $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$; $Z_{port} = Z_{po}((1 + L_S)/(1 + L_O))$; $PM = \angle L(j\omega_t) + 180$; $GM = -|L(j\omega_{180})|_{db}$;

Pole splitting $\omega'_{p1} \simeq 1/(g_m R_2 C_f R_1)$; $\omega'_{p2} \simeq (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair: $s^2 + (\omega_o/Q)s + \omega_o^2$; $Q \leq 0.5 \Rightarrow$ real poles; $Q > 1/\sqrt{2} \Rightarrow$ freq resp peaking

Power Amps: Class A : $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$; Class B : $\eta = (\pi/4)(\hat{V}_O/V_{CC})$; $P_{DN,max} = V_{CC}^2/(\pi^2 R_L)$;
Class AB : $i_{n,i_p} = I_Q^2$

2-stage opamp: $\omega_{p1} \simeq (R_1 G_{m2} R_2 C_c)^{-1}$; $\omega_{p2} = G_{m2}/C_2$; $\omega_z = (C_c(1/G_{m2} - R))^{-1}$;
 $SR = I/C_c = \omega_t V_{ov1}$; will not SR limit if $\omega_t \hat{V}_O < SR$

MOS TRANSISTOR: CMOS basic parameters. Channel length = 0.18 μm

	V_t [V]	μC_{ox} [$\mu\text{A}/\text{V}^2$]	λ' [$\mu\text{m V}^{-1}$]	C_{ox} [fF/ μm^2]	t_{ox} [nm]	L_{ov} [μm]	C_{db0}/W [fF μm^{-1}]
NMOS	0.4	240	0.05	8.5	4	0.04	0.3
PMOS	-0.4	60	-0.05	8.5	4	0.04	0.3