

University of Toronto

Final Exam

Date — Dec 20, 2017

Duration — 2.5 hrs

ECE 331 — Analog Electronics

Lecturer — D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

- Equation sheet is on the last page of this test.
- Unless otherwise stated, use transistor parameters on equation sheet and assume  $g_m r_o \gg 1$
- Non-programmable calculator is allowed; No other aids are allowed
- Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.

Last Name: SOLUTIONS

First Name: \_\_\_\_\_


Student #: \_\_\_\_\_

Question	Points	Score
1	6	
2	6	
3	6	
4	6	
5	6	
6	6	
Total:	36	

**Grading Table**  
(do not write in above table)
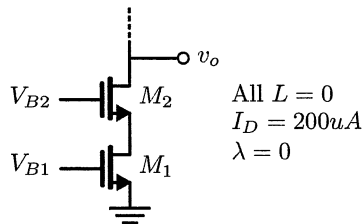
## Q1.

- [3] (a) Consider the wide swing current mirror below where the desired output current is  $200\mu A$ . It is desired that the minimum output voltage,  $v_o$ , be  $0.5V$  while keeping  $M_1/M_2$  active and that  $V_{ov1} = 1.5V_{ov2}$ . Find  $V_{B1}$  and  $V_{B2}$ .



$$V_{ov1} + V_{ov2} = 0.5V$$

$$1.5V_{ov2} + V_{ov2} = 0.5V$$


$$V_{ov2} = 0.2V \quad V_{ov1} = 0.3V$$

$$V_t = 0.4V \Rightarrow V_{B1} = V_{GS1} = V_t + V_{ov1} = \underline{\underline{0.7V}}$$

$$V_{GS2} = V_t + V_{ov2} = 0.6V \quad \text{FOR WIDE SWING } V_{D1} = V_{ov1} = 0.3V$$

$$V_{B2} = V_{ov1} + V_{GS2} = \underline{\underline{0.9V}}$$

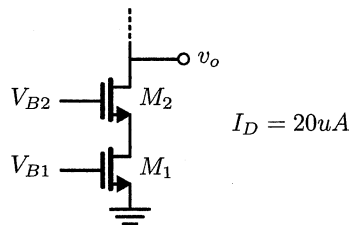- [3] (b) Consider the wide swing current mirror below where the desired output current is  $20\mu A$ ,  $M_1$  and  $M_2$  are identical in size and the minimum output voltage is  $0.4V$ . Find the length of the transistors,  $L$ , such that the current mirror output resistance is  $72M\Omega$ .



$$R_o \cong (1 + g_{m2} r_{o1}) r_{o2} \approx g_{m2} r_o^2 \quad \textcircled{1}$$

$$V_{ov1} + V_{ov2} = 0.4V \Rightarrow V_{ov1} = V_{ov2} = 0.2V$$

$$g_{m1} = \frac{2I_D}{V_{ov}} = \frac{2(20e-6)}{0.2} = 0.2 \text{ mA/V}$$


$$r_o = r_{o1} = r_{o2} = \frac{L}{\lambda' I_D} \quad \lambda' = 0.05 \text{ mm/V}$$

$$I_D = 20e-6 \text{ A}$$

$$\text{FROM } \textcircled{1} \quad 72e6 = (0.2e-3) \frac{L^2}{(\lambda')^2 I_D^2} \Rightarrow L^2 = 0.36$$

$$L = \underline{\underline{0.6 \mu\text{m}}}$$

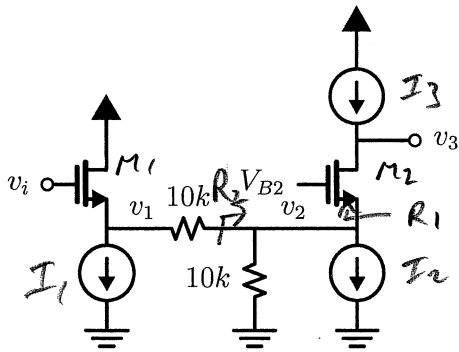Q2. Consider the multistage amplifier shown below. All current sources and transistors have the same output impedance of  $50k\Omega$ . Also, all transistors have  $g_m = 1mA/V$ .



$$r_{s1} = r_{s2} = \frac{1}{g_m} = 1k$$

$$R_1 = \frac{1}{g_{m2}} + \frac{r_{o2} r_{o3}}{g_m} = \frac{2}{g_m} = 2k$$

$$R_2 = 10k \parallel r_{o2} \parallel R_1 \approx 10k \parallel 2k = 1.67k$$

[2] (a) Find small-signal gain  $v_1/v_i$ .

$$R_x \equiv r_{o1} \parallel r_{o2} \parallel (10k + R_2) = 50k \parallel 50k \parallel 11.67k \approx 8k$$

$$\frac{v_1}{v_i} = \frac{R_x}{R_x + r_{s1}} = \frac{8}{8+1} = \underline{\underline{0.889}} \text{ V/V}$$


[2] (b) Find small-signal gain  $v_2/v_1$ .

$$\frac{v_2}{v_1} = \frac{R_2}{R_2 + 10k} = \frac{1.67}{1.67+10} = \underline{\underline{0.143}} \text{ V/V}$$

[2] (c) Find small-signal gain  $v_3/v_2$ .

$$\frac{v_3}{v_2} = g_{m2} (r_{o2} \parallel r_{o3}) = \frac{25k}{1k} = \underline{\underline{25}} \text{ V/V}$$

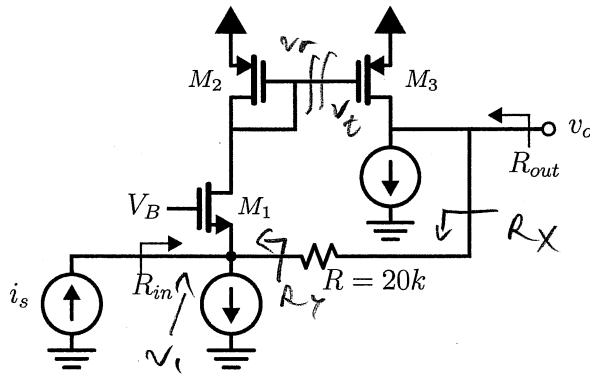Q3. Consider the feedback amp shown below where the input signal,  $i_s$  is a current.



All current sources ideal

$$g_{m1} = g_{m2} = 1 \text{ mA/V}$$

$$g_{m3} = 10 \text{ mA/V}$$

$$r_{o1} = r_{o2} = r_{o3} = 40 \text{ k}$$

$$R_Y = \frac{1}{g_{m1}} + \frac{1}{g_{m2}} \approx \frac{1}{g_{m1}} = 1 \text{ k}$$

$$R_X = R_Y + R = 2 \text{ k}$$

[3] (a) Using loop-gain analysis, find  $L$ ,  $A_{\infty}$ ,  $d$  and  $v_o/i_s$ .

$$\frac{v_o}{v_t} = -g_{m3}(r_{o3} \parallel R_X) = (10 \text{ e-3})(40 \text{ k} \parallel 2 \text{ k}) = -138 \text{ V/V}$$

$$\frac{v_i}{v_o} = \frac{R_Y}{R_Y + R} = \frac{1}{1+2} = 0.0476$$

$$\frac{v_r}{v_i} = g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{o1} \right) \approx 1 \Rightarrow L \equiv -\frac{v_r}{v_t} = \underline{\underline{6.57 \text{ V/V}}}$$

$$A_{\infty} = \frac{v_o}{v_s} \Big|_{L \rightarrow \infty} = \underline{\underline{-20 \text{ k}}} \quad d \equiv \frac{v_o}{v_s} \Big|_{L=0} \Rightarrow \frac{v_i}{v_s} = \frac{1}{g_{m1}} \parallel (R + r_{o3})$$

$$\approx \frac{1}{g_{m1}} = 1 \text{ k}$$

$$\frac{v_o}{v_i} = \frac{r_{o3}}{r_{o3} + R} = \frac{2}{3}$$

$$d = \underline{\underline{0.667 \text{ k}}}$$

$$\frac{v_o}{v_s} = A_{\infty} \left( \frac{L}{1+L} \right) + d \left( \frac{1}{1+L} \right)$$

$$= 20 \text{ k} \left( \frac{6.57}{7.57} \right) + 0.667 \text{ k} \left( \frac{1}{7.57} \right)$$

$$\frac{v_o}{v_s} = \underline{\underline{-17.4 \text{ k}\Omega}}$$

[3] (b) Find  $R_{in}$  and  $R_{out}$ .

$$R_{i0}^{\circ} = \frac{1}{g_{m1}} \parallel (R + r_{o3}) \approx \frac{1}{g_{m1}} = 1 \text{ k}$$

$$R_{in} = R_{i0}^{\circ} \left( \frac{1+L}{1+L_0} \right) = \underline{\underline{132 \Omega}}$$

$$R_o^{\circ} = R_X \parallel r_{o3} = (2 \text{ k} \parallel 40 \text{ k}) = 13.8 \text{ k}$$

$$R_{out} = R_o^{\circ} \left( \frac{1+L}{1+L_0} \right) = \underline{\underline{1.82 \text{ k}}}$$



$$L_S = 0 \quad L_0 = L = 6.57$$

Q4. Assume an opamp is ideal but has the following open-loop gain.


$$A(s) = \frac{0.5 \times 10^5}{(1+s/\omega_{p1})(1+s/\omega_{p2})(1+s/\omega_{p3})} \text{ where } \omega_{p1} = 10^1, \omega_{p2} = 10^6 \text{ and } \omega_{p3} = 10^9$$

[3] (a) Draw the Bode plot for the above open loop gain (Label all plot axis).

$$A_0|_{dB} = 94dB$$

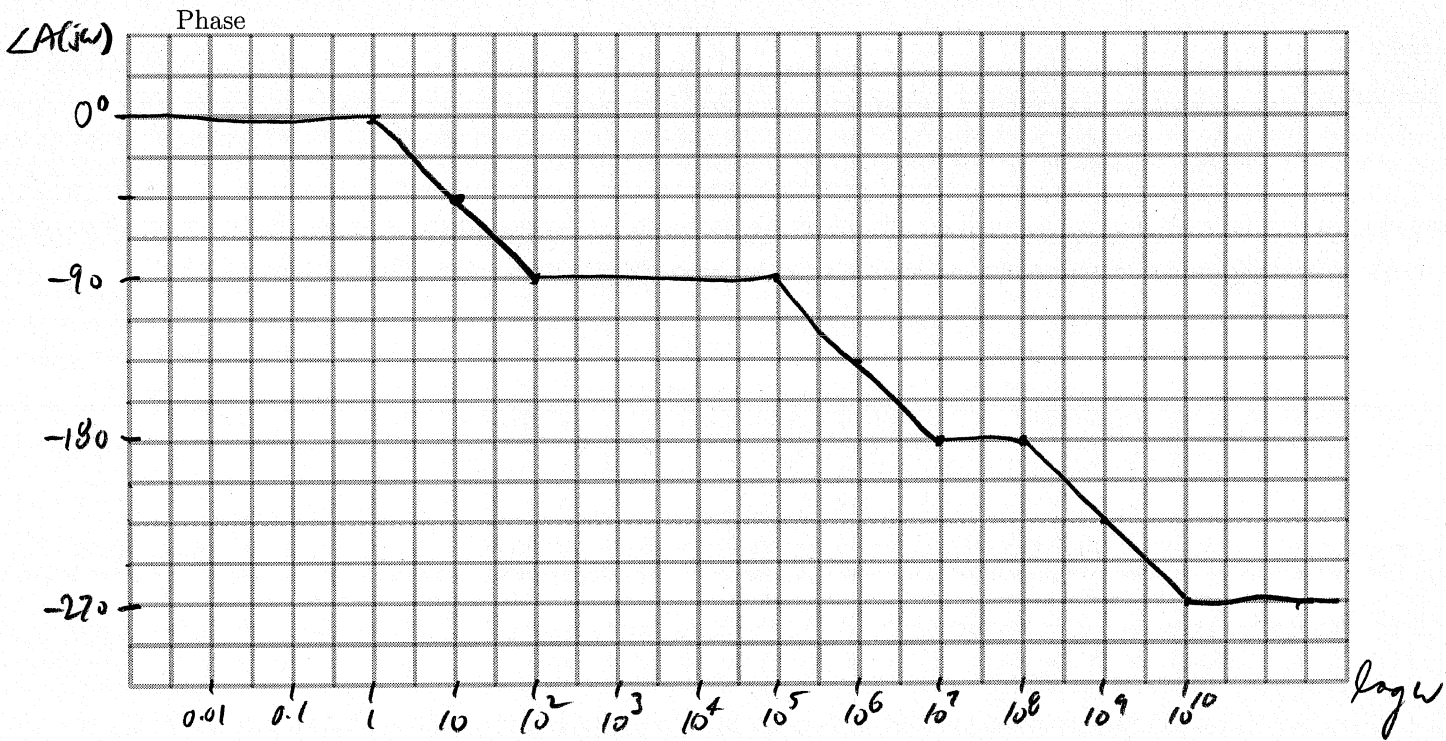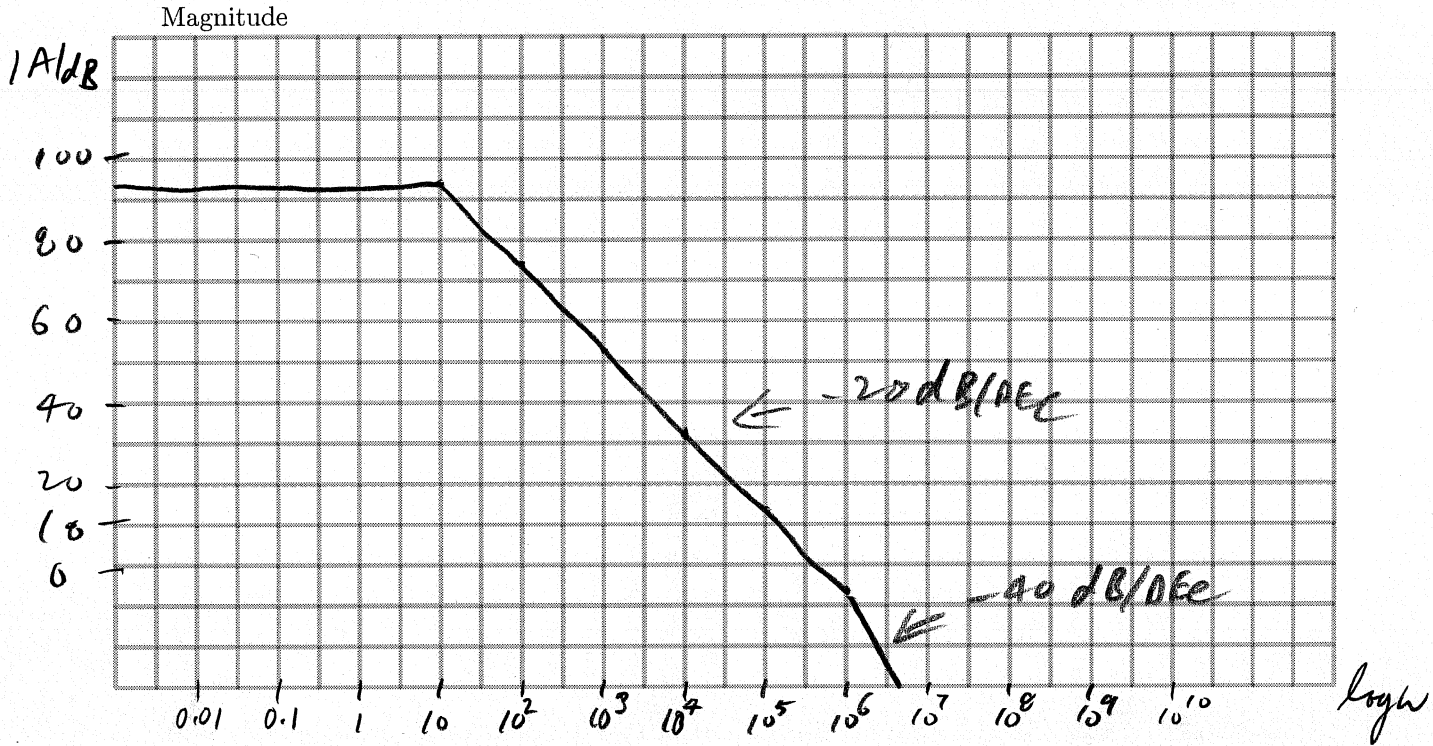

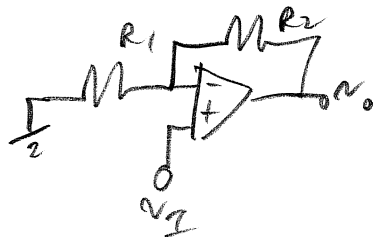- [3] (b) Estimate the phase-margin (PM) if the above opamp is used to create a gain of +2 using 2 resistors (a non-inverting configuration) (Hint: Note that the unity-gain frequency is much greater than  $\omega_{p1}$  and much less than  $\omega_{p3}$ .)



$$\frac{v_o}{v_I} = \left(1 + \frac{R_2}{R_1}\right) = 2 \Rightarrow R_2 = R_1 \Rightarrow \beta = 0.5$$

$$L(s) = \beta A(s) = \frac{0.25e5}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^6}\right)\left(1 + \frac{s}{10^9}\right)}$$

$$|L(j\omega_t)| = 1 \quad \downarrow \quad 10 \ll \omega_t \ll 10^9 \quad \text{given}$$

$$|L(j\omega_t)| \approx \frac{(0.25e5)}{\left|\frac{j\omega_t}{10}\right| \left|1 + \frac{j\omega_t}{10^6}\right|} = 1$$

$$\frac{(0.25e5)^2}{\left(\frac{\omega_t}{10}\right)^2 \left(1 + \left(\frac{\omega_t}{10^6}\right)^2\right)} = 1 \Rightarrow \frac{(10^2)(10^{12})(0.25e5)^2}{\omega_t^2 (10^{12} + \omega_t^2)} = 1$$


$$(\omega_t^2)^2 + 10^{12} \omega_t^2 - 6.25e22 = 0 \Rightarrow \omega_t^2 = 5.9e10$$

$$\omega_t = 2.4e5$$

$$\angle L(j\omega_t) \approx -90^\circ - \tan^{-1}\left(\frac{2.5e5}{1e6}\right) = -90^\circ - 13.7^\circ = -103.7^\circ$$

$$PM = \angle L(j\omega_t) - (-180^\circ) = \underline{\underline{76^\circ}}$$

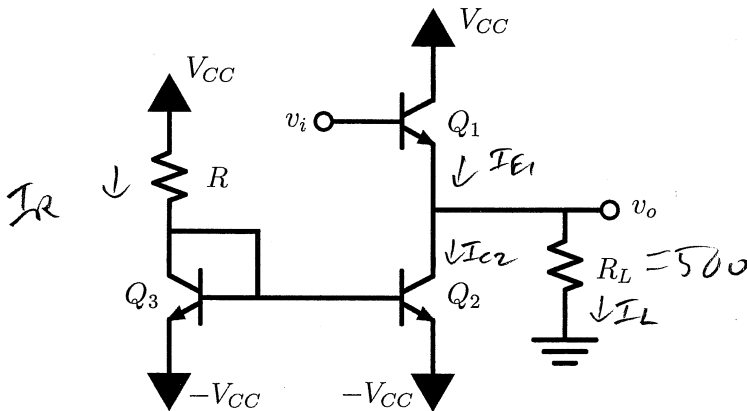Q5. Consider the class A BJT power amp shown below where  $V_{CC} = 10V$ , all transistors are matched and have large  $\beta$  (such that base currents can be ignored) and  $V_{cesat} = 0.2V$  for all transistors. The load resistance is  $500\Omega$ .



- [2] (a) Assuming the desired output swing is  $\pm 8V$ , find  $R$  for the minimum power consumption.

$$\text{FOR } v_o = -8V \Rightarrow I_{E1} = 0 \text{ \& } I_{C2} = -I_L = \frac{8}{500} = 16 \text{ mA} = I_R$$

$$I_R = \frac{2V_{CC} - 0.7}{R} \Rightarrow R = \frac{2V_{CC} - 0.7}{I_R} = \frac{19.3}{16 \text{ mA}} = \underline{\underline{1.21 \text{ k}\Omega}}$$

- [2] (b) What is the efficiency of the above design when driving an  $8V$  sinusoidal waveform?

$$P_L = \frac{(8/\sqrt{2})^2}{R_L} = 64 \text{ mW} \quad P_{CC} = (I_{C3} + I_{C2}) 2V_{CC}$$

LOAD Power

$$V_{CC} \text{ Power} = (32 \text{ mA})(20) = 640 \text{ mW}$$

$$\eta = \frac{P_L}{P_{CC}} \times 100 = \underline{\underline{10\%}}$$

- [2] (c) Assuming a large input signal,  $v_i$ , for the above design, what value of  $R_L$  would cause  $Q_2$  to saturate?

$$Q_2 \text{ SATURATES WHEN } v_o = -10V + 0.2 = -9.8V$$

$$\text{\& } I_{E1} = 0$$

$$\text{\& } v_o = -9.8V \text{ OCCURS FOR}$$


$$v_o = i_L R_L = -I_{C2} R_L = -9.8V$$

$$R_L = \frac{9.8}{16 \text{ mA}} = \underline{\underline{612.5 \Omega}}$$

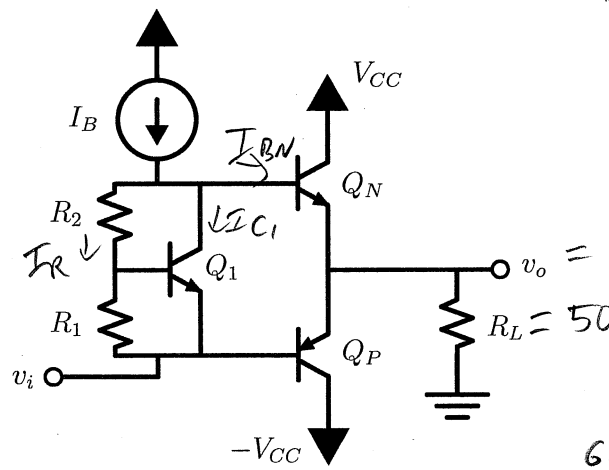Q6.

Consider a class AB BJT output stage with a  $V_{be}$  multiplier used for biasing as shown below. The load resistor is  $50\Omega$  and  $V_{CC} = 12V$ . Assume the output is sinusoidal with a maximum amplitude of  $10V$  and the power transistors  $Q_N/Q_P$  are matched with  $I_S = 10^{-13}A$  and  $\beta = 40$ . The bias transistor has  $I_S = 10^{-14}A$  and  $\beta = 200$ . Design the bias circuit for a quiescent current of  $10mA$  and a minimum current of  $1mA$  through the  $V_{be}$  multiplier circuit (Find  $I_B$ ,  $R_1$  and  $R_2$ ).

$\beta_N = 40$   
 $\alpha_N = \frac{40}{41}$   
 $= 0.975$



$V_T = 25 mV$   
 $I_{BN-MAX} = \left( \frac{\hat{V}_o}{R_L} \times \frac{\alpha_N}{\beta} \right) = \frac{10 \times 0.975}{50 \times 40} \approx 5 mA$

$v_o = \pm 10V \text{ SINUSOID}$  GIVEN  
 $I_B = 5 mA + 1 mA = \underline{\underline{6 mA}}$

AT QUIESCENT  $\Rightarrow I_N = I_P = I_Q = 10 mA \Rightarrow I_{BN} = \frac{10}{40} = 0.25 mA$  GIVEN

$Q_N \text{ \& } Q_P \text{ MATCHED} \Rightarrow V_{BEN} = V_{EBP} = \frac{V_{BB}}{2}$   
 $I_Q = \left( \frac{I_{SN}}{\alpha_N} \right) e^{\frac{V_{BB}}{2V_T}} \Rightarrow V_{BB} = 2V_T \ln \left( \frac{I_Q \alpha_N}{I_{SN}} \right) = (50e-3) \ln \left( \frac{10e-3 \times 0.975}{1e-13} \right)$

$V_{BB} = 1.265 V$

CHOOSE  $I_R = 0.5 mA \Rightarrow I_{C1} = 6 - 0.5 - 0.25 = 5.25 mA$  AT QUIESCENT

$V_{BE1} = V_T \ln \left( \frac{I_{C1}}{I_{S1}} \right) = 25e-3 \ln \left( \frac{5.25e-3}{1e-14} \right) = 0.6747 V$

$I_R = \frac{V_{BE1}}{R_1} \Rightarrow R_1 = \frac{0.6747}{0.5 mA} = \underline{\underline{1.35 k\Omega}}$  ASSUMING  $I_B \approx 0$  SINCE  $\beta = 200$

$V_{BB} \approx V_{BE1} \left( 1 + \frac{R_2}{R_1} \right) \Rightarrow R_2 = \left( \frac{V_{BB}}{V_{BE1}} - 1 \right) R_1 = \underline{\underline{1.18 k\Omega}}$



## Equation Sheet

**Constants:**  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26 \text{ mV}$  at 300K;  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ ;

$$k_{ox} = 3.9; C_{ox} = (k_{ox}\epsilon_0)/t_{ox}; \omega = 2\pi f$$

**NMOS:**  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{tn} > 0$ ;  $v_{DS} \geq 0$ ;  $V_{ov} = V_{GS} - V_{tn}$

$$\text{(triode)} \quad v_{DS} \leq V_{ov}; \quad v_D < v_G - V_{tn}; \quad i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$$

$$\text{(active)} \quad v_{DS} \geq V_{ov}; \quad i_D = 0.5k_nV_{ov}^2(1 + \lambda v_{DS}); \quad g_m = k_nV_{ov} = 2I_D/V_{ov} = \sqrt{2k_nI_D}; \quad r_s = 1/g_m;$$

$$r_o = L/(|\lambda'|I_D)$$

**PMOS:**  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{tp} < 0$ ;  $v_{SD} \geq 0$ ;  $V_{ov} = V_{SG} - |V_{tp}|$


$$\text{(triode)} \quad v_{SD} \leq V_{ov}; \quad v_D > v_G + |V_{tp}|; \quad i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$$

$$\text{(active)} \quad v_{SD} \geq V_{ov}; \quad i_D = 0.5k_pV_{ov}^2(1 + |\lambda|v_{SD}); \quad g_m = k_pV_{ov} = 2I_D/V_{ov} = \sqrt{2k_pI_D}; \quad r_s = 1/g_m;$$


$$r_o = L/(|\lambda'|I_D)$$

**BJT:** (active)  $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$ ;  $g_m = \alpha/r_e = I_C/V_T$ ;  $r_e = V_T/I_E$ ;  $r_\pi = \beta/g_m$ ;  $r_o = |V_A|/I_C$ ;

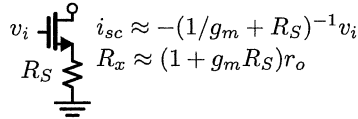
$$i_C = \beta i_B; \quad i_E = (\beta + 1)i_B; \quad \alpha = \beta/(\beta + 1); \quad i_C = \alpha i_E; \quad R_b = (\beta + 1)(r_e + R_E); \quad R_e = (R_B + r_\pi)/(\beta + 1)$$



(Approx due to  $g_m r_o \gg 1$ )

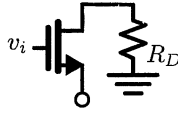

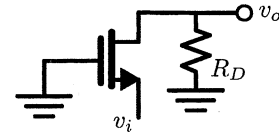$v_{oc} \approx v_i$   
 $R_x \approx 1/g_m + R_D/(g_m r_o)$



$v_o/v_i \approx g_m(r_o || R_D)$

**Diff Pair:**  $A_d = g_m R_D$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$ ;  $V_{OS} = \Delta V_t$ ;  $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$ ;  $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$

**1st order:** step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ ; unity gain freq for  $T(s) = \frac{A_M}{1 + (s/\omega_{3dB})}$  for  $A_M \gg 1 \Rightarrow$

$$\omega_t \approx |A_M|\omega_{3dB}$$

**Freq:** for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$

OTC estimate  $\omega_H \approx 1/(\sum \tau_i)$ ; dominant pole estimate  $\omega_H \approx 1/(\tau_{max})$

**Miller:**  $Z_1 = Z/(1 - K)$ ;  $Z_2 = Z/(1 - 1/K)$

**Mos caps:**  $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$ ;  $C_{gd} = WL_{ov}C_{ox}$ ;  $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$ ;

$$\omega_t = g_m/(C_{gs} + C_{gd}); \quad \text{for } C_{gs} \gg C_{gd} \Rightarrow f_t \approx (3\mu V_{ov})/(4\pi L^2)$$

**Feedback:**  $A_f = A/(1 + A\beta)$ ;  $x_i = (1/(1 + A\beta))x_s$ ;  $dA_f/A_f = (1/(1 + A\beta))dA/A$ ;  $\omega_{Hf} = \omega_H(1 + A\beta)$ ;  $\omega_{Lf} = \omega_L/(1 + A\beta)$ ;

Loop Gain  $L \equiv -s_r/s_t$ ;  $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$ ;  $Z_{port} = Z_{p^o}((1 + L_S)/(1 + L_O))$ ;  $PM = \angle L(j\omega_t) + 180$ ;  $GM = -|L(j\omega_{180})|_{db}$ ;

Pole splitting  $\omega'_{p1} \approx 1/(g_m R_2 C_f R_1)$ ;  $\omega'_{p2} \approx (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

**Pole Pair:**  $s^2 + (\omega_o/Q)s + \omega_o^2$ ;  $Q \leq 0.5 \Rightarrow$  real poles;  $Q > 1/\sqrt{2} \Rightarrow$  freq resp peaking

**Power Amps:** Class A:  $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$ ; Class B:  $\eta = (\pi/4)(\hat{V}_O/V_{CC})$ ;  $P_{DN-max} = V_{CC}^2/(\pi^2 R_L)$ ;

$$\text{Class AB: } i_n i_p = I_Q^2$$

**2-stage opamp:**  $\omega_{p1} \approx (R_1 G_{m2} R_2 C_c)^{-1}$ ;  $\omega_{p2} = G_{m2}/C_2$ ;  $\omega_z = (C_c(1/G_{m2} - R))^{-1}$ ;

$$SR = I/C_c = \omega_t \hat{V}_O; \quad \text{will not SR limit if } \omega_t \hat{V}_O < SR$$

**MOS TRANSISTOR:** CMOS basic parameters. Minimum channel length =  $0.18 \mu\text{m}$

	$V_t$ [V]	$\mu C_{ox}$ [ $\mu\text{A/V}^2$ ]	$\lambda'$ [ $\mu\text{m V}^{-1}$ ]	$C_{ox}$ [fF/ $\mu\text{m}^2$ ]	$t_{ox}$ [nm]	$L_{ov}$ [ $\mu\text{m}$ ]	$C_{db0}/W$ [fF $\mu\text{m}^{-1}$ ]
NMOS	0.4	240	0.05	8.5	4	0.04	0.3
PMOS	-0.4	60	-0.05	8.5	4	0.04	0.3