

University of Toronto

Final Exam

Date — Dec 19, 2019: 2pm

Duration — 2.5 hrs

ECE 331 — Analog Electronics

Lecturer — D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

- Equation sheet is on the last page of this test.
  - Unless otherwise stated, assume  $g_m r_o \gg 1$
  - Notation: 1.5e+04 is equivalent to  $1.5 \times 10^4$
  - Non-programmable calculator is allowed; No other aids are allowed
  - Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.
- 

Last Name: \_\_\_\_\_


First Name: \_\_\_\_\_

Student #: \_\_\_\_\_

Question	Points	Score
1	6	
2	6	
3	6	
4	6	
5	6	
6	6	
Total:	36	

**Grading Table**  
(do not write in above table)

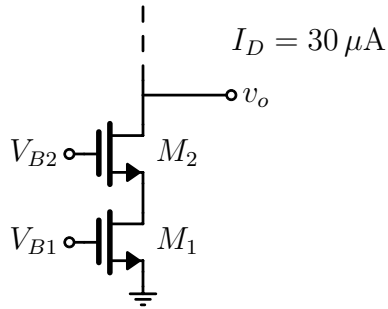- [6] **Q1.** Consider the wide-swing current mirror shown below where the desired output current is  $30 \mu\text{A}$ . Given that  $M_1$  and  $M_2$  are identical in size and the minimum output voltage is  $0.5 \text{ V}$ , find the length of the transistors such that the current mirror output resistance is  $60 \text{ M}\Omega$



$V_{tn}$	$0.3 \text{ V}$
$u_n C_{ox}$	$160 \mu\text{A}/\text{V}^2$
$\lambda'_n$	$0.04 \mu\text{m}/\text{V}$

**Solution**

$$V_o(\min) = 0.5 \text{ mV} = 2V_{ov} \Rightarrow V_{ov} = 0.25 \text{ V}$$


$$g_m = \frac{2I_D}{V_{ov}} = \frac{2(30e-6)}{0.25} = 240.0 \mu\text{A}/\text{V}$$

$$R_{out} \approx g_m r_o^2 \Rightarrow r_o = \sqrt{\frac{R_{out}}{g_m}} = \sqrt{\frac{60e6}{240.0e-6}} = 0.5 \text{ M}\Omega$$

$$r_o = \frac{L}{|\lambda'_n| I_D} \Rightarrow L = r_o |\lambda'_n| I_D = (0.5e6)(0.04e-6)(30e-6) = 0.6 \mu\text{m}$$

$$L = 0.6 \mu\text{m}$$

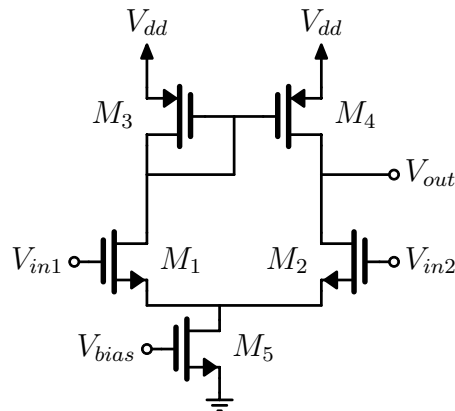**Q2.** Consider the differential to single ended amplifier shown below. All transistor lengths are  $0.2 \mu\text{m}$  and have  $V_{ov} = 0.15 \text{ V}$ . Also,  $I_{D5} = 80 \mu\text{A}$  and  $V_{dd} = 1.8 \text{ V}$ .



$V_{tn}$	0.25 V
$u_n C_{ox}$	$200 \mu\text{A}/\text{V}^2$
$\lambda'_n$	$0.05 \mu\text{m}/\text{V}$
$V_{tp}$	-0.3 V
$u_p C_{ox}$	$60 \mu\text{A}/\text{V}^2$
$\lambda'_p$	$-0.04 \mu\text{m}/\text{V}$

- [3] (a) Find the small-signal gain  $V_{out}/v_{id}$  where  $v_{id} \equiv V_{in2} - V_{in1}$

**Solution**

Since  $I_{D5} = 80 \mu\text{A}$ ,  $I_{D1}$  to  $I_{D4}$  all equal  $40.0 \mu\text{A}$

$$r_{o2} = \frac{L_2}{|\lambda'_n| I_{D2}} = 100.0 \text{ k}\Omega$$

$$r_{o4} = \frac{L_4}{|\lambda'_p| I_{D4}} = 125.0 \text{ k}\Omega$$

$$R_{out} = r_{o2} || r_{o4} = 55.556 \text{ k}\Omega$$

$$g_{m2} = \frac{2I_{D2}}{V_{ov2}} = 533.333 \mu\text{A}/\text{V}$$

$$V_{out}/v_{id} = -g_{m2} R_{out}$$

$$V_{out}/v_{id} = -29.63 \text{ V}/\text{V}$$

- [3] (b) Find the maximum ( $V_{cm(max)}$ ) and minimum ( $V_{cm(min)}$ ) common-mode input voltages that keep all transistors in the active region.

**Solution**

$$V_{cm(min)} = V_{ov5} + V_{tn} + V_{ov2} = 0.15 + 0.25 + 0.15 = 0.55 \text{ V}$$

$$V_{cm(min)} = 0.55 \text{ V}$$

For  $V_{cm(max)}$ , first find the bias voltage for  $V_{D1}$


$$V_{D1} = V_{dd} - |V_{tp}| - V_{ov3} = 1.8 - 0.3 - 0.15 = 1.35 \text{ V}$$

$V_{in1}$  can go up to  $V_{tn}$  above  $V_{D1}$  so

$$V_{cm(max)} = V_{D1} + V_{tn} = 1.6 \text{ V}$$



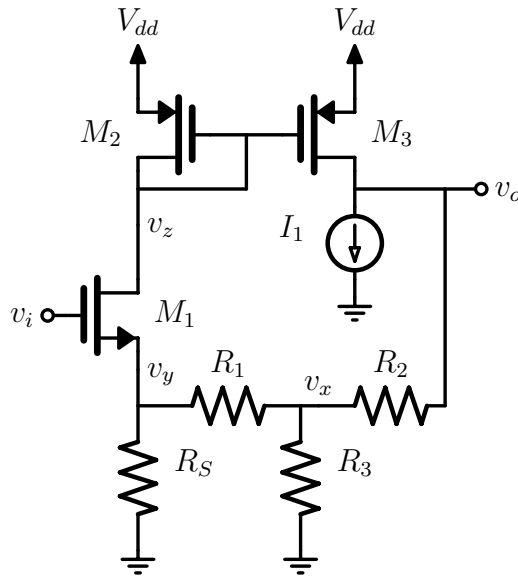- [6] Q4. Consider the feedback amp shown below with the input signal,  $v_i$ . All current sources are ideal (i.e. infinite output resistance)



$$\begin{aligned}
 g_{m1} &= g_{m2} = 0.1 \text{ mA/V} \\
 g_{m3} &= 5 \text{ mA/V} \\
 r_{o1} &= r_{o2} = r_{o3} \rightarrow \infty \\
 R_1 &= 10 \text{ k}\Omega & R_2 &= 10 \text{ k}\Omega \\
 R_3 &= 10 \text{ k}\Omega & R_S &= 10 \text{ k}\Omega
 \end{aligned}$$

Using loop-gain analysis, find  $L$ ,  $A_\infty$  and  $v_o/v_i$ . (assume  $d = 0$ ).

### Solution

Define  $R_y$  to be the impedance looking into the source of  $M_1$

Define  $R_x$  to be the impedance looking into  $R_1$  from  $v_x$  side

Define  $R_o$  to be the impedance looking into  $R_2$  from  $v_o$  side

$$R_y \equiv (1/g_{m1}) = 10.0 \text{ k}\Omega$$

$$R_x \equiv (R_y || R_S + R_1) = 15.0 \text{ k}\Omega$$

$$R_o \equiv ((R_x || R_3) + R_2) = 16.0 \text{ k}\Omega$$

Breaking the loop at the  $M_3$  gate, we have

$$v_o/v_{g3} = -g_{m3}R_o = -80.0 \quad v_x/v_o = \frac{R_x || R_3}{(R_x || R_3) + R_2} = 0.375$$

$$v_y/v_x = \frac{R_y || R_S}{(R_y || R_S) + R_1} = 0.333 \quad v_z/v_y = \frac{g_{m1}}{g_{m2}} = 1.0$$

$$L = -v_o/v_{g3} \times v_x/v_o \times v_y/v_x \times v_z/v_y \Rightarrow L = 10.0$$

For  $A_\infty$ ,  $L \rightarrow \infty$  which results in  $v_z \rightarrow 0$ . Since  $v_z = 0$ ,  $i_{D1} = 0$  resulting in  $v_y = v_i$  and no current flows into the source of  $M_1$


$$\text{As a result, } v_x/v_i = 1 + R_1/R_S = 2.0 \quad \text{and } v_o/v_x = 1 + R_2/(R_3 || (R_1 + R_S)) = 2.5$$

$$\text{Resulting in } A_\infty = v_o/v_x \times v_x/v_i \Rightarrow A_\infty = 5.0$$

$$v_o/v_i = A_\infty \frac{L}{1+L} = 5.0 \frac{10.0}{1+10.0}$$



$$v_o/v_i = 4.545$$

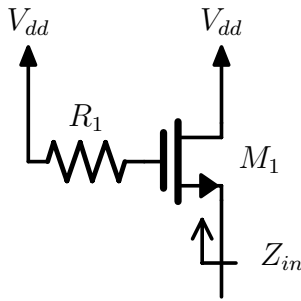**Q5.** Consider the input impedance looking into the source of the circuit below. Let  $r_o \rightarrow \infty$  and only consider capacitance  $C_{gs}$ .



[3] (a) Draw the small signal model and find the loop gain.

**Solution**

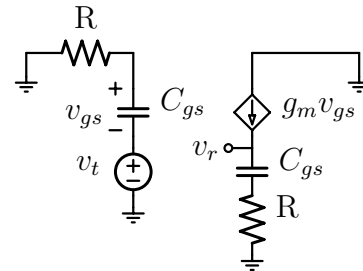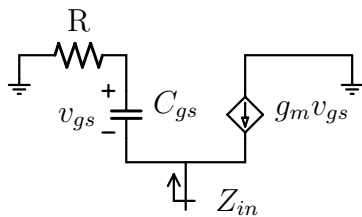

$$L_O \equiv -v_r/v_t = -\left(\frac{-1/sC_{gs}}{1/sC_{gs}+R}\right)g_m\left(\frac{1+sC_{gs}R}{sC_{gs}}\right) = \frac{g_m}{sC_{gs}}$$

$$L_O = \frac{g_m}{sC_{gs}}$$

$$L_S = 0$$

[3] (b) Using the loop gain found above, find  $Z_{in}$ .

**Solution**

$$Z_{P0} = R + \frac{1}{sC_{gs}} = \frac{1+sC_{gs}R}{sC_{gs}}$$


$$Z_{in} = Z_{P0} \left[ \frac{1+L_S}{1+L_O} \right] = \left( \frac{1+sC_{gs}R}{sC_{gs}} \right) \left( \frac{1}{1+\frac{g_m}{sC_{gs}}} \right)$$

$$Z_{in} = \left( \frac{1}{g_m} \right) \left( \frac{1+sC_{gs}R}{1+sC_{gs}/g_m} \right)$$

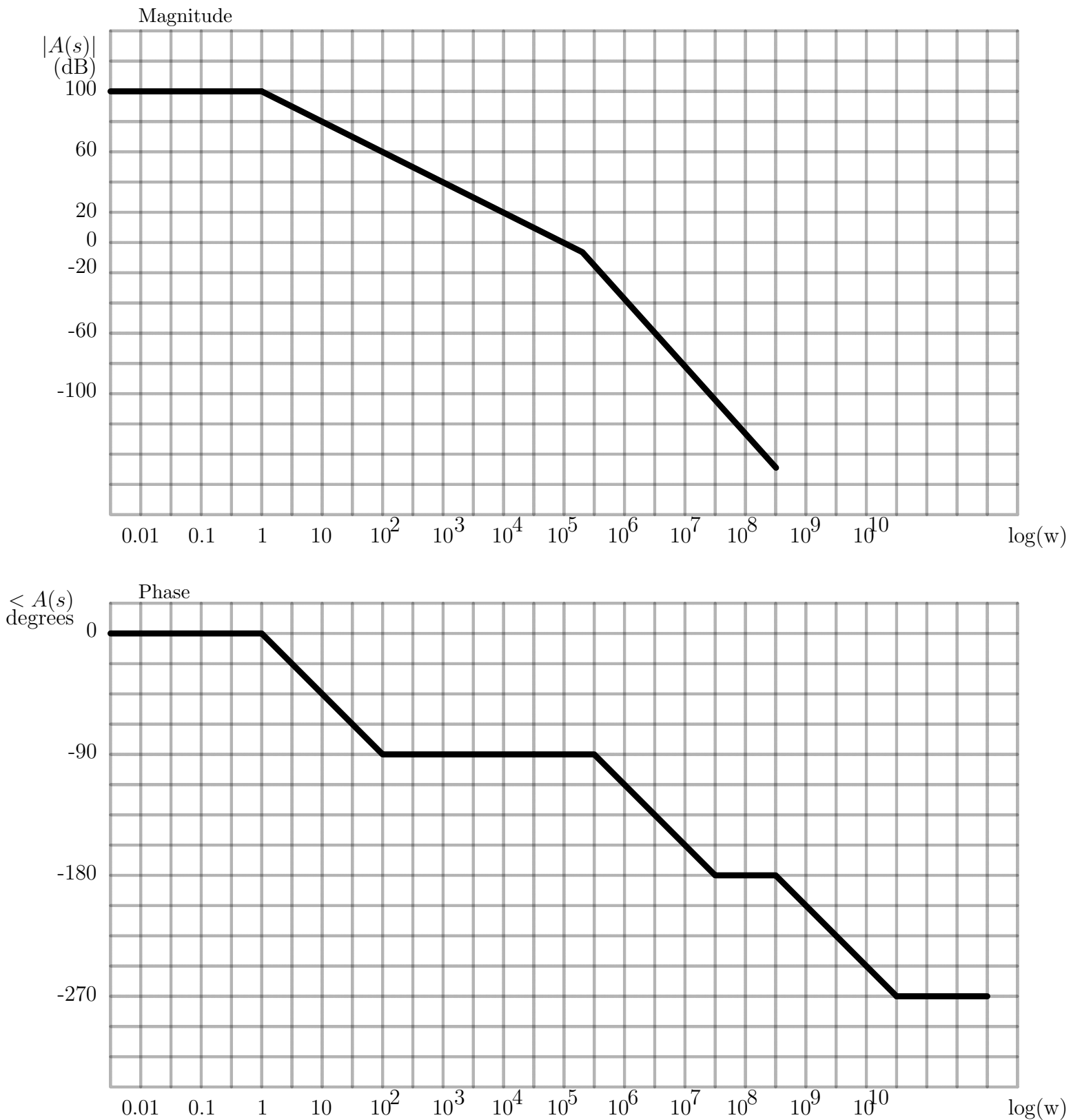**Q6.** Assume an opamp is ideal but has the following open-loop gain.

$$A(s) = \frac{1.0e+05}{(1+s/\omega_{p1})(1+s/\omega_{p2})(1+s/\omega_{p3})} \text{ where } \omega_{p1} = 1.0e+01, \omega_{p2} = 2.0e+06 \text{ and } \omega_{p3} = 2.0e+09$$

[3] (a) Draw the Bode plot for the above open loop gain (Label all plot axis).



- [3] (b) Estimate the phase-margin (PM) if the above opamp is used to create a gain of +3 using 2 resistors (a non-inverting configuration) (Hint: Note that the unity-gain frequency is much greater than  $\omega_{p1}$  and much less than  $\omega_{p3}$ .)

**Solution**

For a non-inverting opamp gain of +3,  $\beta = 1/3 = 0.333$  resulting in the loop gain equal to

$$L(s) = \beta A(s) = \frac{L_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})(1+s/\omega_{p3})} \text{ where } L_0 = 3.33e + 04 \text{ and } \omega_{p1}, \omega_{p2}, \omega_{p3} \text{ given above.}$$

For frequencies near  $\omega_t$  where  $\omega_{p1} \ll \omega_t \ll \omega_{p3}$ , we can approximate  $L(s)$  as

$$L(s) \approx \frac{L_0}{(s/\omega_{p1})(1+s/\omega_{p2})} \quad \text{and making use of } |L(j\omega_t)| = 1, \text{ we have}$$

$$\frac{L_0^2}{(\omega_t/\omega_{p1})^2(1+(\omega_t/\omega_{p2})^2)} = 1 \Rightarrow \frac{\omega_{p1}^2 \omega_{p2}^2 L_0^2}{\omega_t^2 (\omega_t^2 + \omega_{p2}^2)} = 1 \Rightarrow (\omega_t^2)^2 + \omega_{p2}^2 (\omega_t^2) - \omega_{p1}^2 \omega_{p2}^2 L_0^2 = 0$$

$$(\omega_t^2)^2 + 4.000e + 12(\omega_t^2) - 4.444e + 23 = 0 \text{ Solving for } \omega_t^2, \text{ we have } \omega_t^2 = 1.082e + 11 \text{ rad/s}$$

resulting in  $\omega_t = 3.289e + 05 \text{ rad/s}$

So now, we can find the phase of  $L(j\omega_t)$  as ( $-90^\circ$  is due to the  $\omega_{p1}$ )

$$\angle L(j\omega_t) \approx -90^\circ - \tan^{-1}\left(\frac{\omega_t}{\omega_{p2}}\right) = -90^\circ - 9.339^\circ = -99.339^\circ$$

Finally, the phase-margin can be found as

$$PM \equiv \angle L(j\omega_t) - (-180^\circ) = 80.661^\circ$$




## Equation Sheet

**Constants:**  $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26\text{mV}$  at 300K;  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ ;  
 $k_{ox} = 3.9$ ;  $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$ ;  $\omega = 2\pi f$


**NMOS:**  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{tn} > 0$ ;  $v_{DS} \geq 0$ ;  $V_{ov} = V_{GS} - V_{tn}$   
(triode)  $v_{DS} \leq V_{ov}$ ;  $v_D < v_G - V_{tn}$ ;  $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$   
(active)  $v_{DS} \geq V_{ov}$ ;  $i_D = 0.5k_nV_{ov}^2(1 + \lambda v_{DS})$ ;  $g_m = k_nV_{ov} = 2I_D/V_{ov} = \sqrt{2k_nI_D}$ ;  $r_s = 1/g_m$ ;  
 $r_o = L/(|\lambda'I_D)$

**PMOS:**  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{tp} < 0$ ;  $v_{SD} \geq 0$ ;  $V_{ov} = V_{SG} - |V_{tp}|$   
(triode)  $v_{SD} \leq V_{ov}$ ;  $v_D > v_G + |V_{tp}|$ ;  $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$   
(active)  $v_{SD} \geq V_{ov}$ ;  $i_D = 0.5k_pV_{ov}^2(1 + |\lambda|v_{SD})$ ;  $g_m = k_pV_{ov} = 2I_D/V_{ov} = \sqrt{2k_pI_D}$ ;  $r_s = 1/g_m$ ;  
 $r_o = L/(|\lambda'I_D)$


**BJT:** (active)  $i_C = I_S e^{(v_{BE}/V_T)}(1 + (v_{CE}/V_A))$ ;  $g_m = \alpha/r_e = I_C/V_T$ ;  $r_e = V_T/I_E$ ;  $r_\pi = \beta/g_m$ ;  $r_o = |V_A|/I_C$ ;  
 $i_C = \beta i_B$ ;  $i_E = (\beta + 1)i_B$ ;  $\alpha = \beta/(\beta + 1)$ ;  $i_C = \alpha i_E$ ;  $R_b = (\beta + 1)(r_e + R_E)$ ;  $R_e = (R_B + r_\pi)/(\beta + 1)$

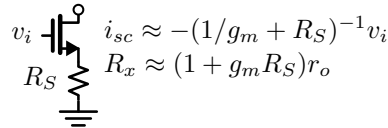

(Approx due to  $g_m r_o \gg 1$ )

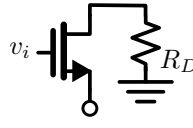

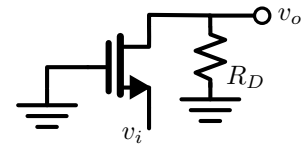$v_{oc} \approx v_i$   
 $R_x \approx 1/g_m + R_D/(g_m r_o)$



$v_o/v_i \approx g_m(r_o || R_D)$

**Diff Pair:**  $A_d = g_m R_D$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$ ;  $V_{OS} = \Delta V_t$ ;  $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$ ;  $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$

**1st order:** step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ ; unity gain freq for  $T(s) = \frac{A_M}{1 + (s/\omega_{3dB})}$  for  $A_M \gg 1 \Rightarrow$   
 $\omega_t \approx |A_M|\omega_{3dB}$

**Freq:** for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$   
OTC estimate  $\omega_H \approx 1/(\sum \tau_i)$ ; dominant pole estimate  $\omega_H \approx 1/(\tau_{max})$

**Miller:**  $Z_1 = Z/(1 - K)$ ;  $Z_2 = Z/(1 - 1/K)$

**Mos caps:**  $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$ ;  $C_{gd} = WL_{ov}C_{ox}$ ;  $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$ ;  
 $\omega_t = g_m/(C_{gs} + C_{gd})$ ; for  $C_{gs} \gg C_{gd} \Rightarrow f_t \approx (3\mu V_{ov})/(4\pi L^2)$

**Feedback:**  $A_f = A/(1 + A\beta)$ ;  $x_i = (1/(1 + A\beta))x_s$ ;  $dA_f/A_f = (1/(1 + A\beta))dA/A$ ;  $\omega_{Hf} = \omega_H(1 + A\beta)$ ;  $\omega_{Lf} = \omega_L/(1 + A\beta)$ ;

Loop Gain  $L \equiv -s_r/s_t$ ;  $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$ ;  $Z_{port} = Z_{p^\circ}((1 + L_S)/(1 + L_O))$ ;  $PM = \angle L(j\omega_t) + 180$ ;  $GM = -|L(j\omega_{180})|_{db}$ ;

Pole splitting  $\omega'_{p1} \approx 1/(g_m R_2 C_f R_1)$ ;  $\omega'_{p2} \approx (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

**Pole Pair:**  $s^2 + (\omega_o/Q)s + \omega_o^2$ ;  $Q \leq 0.5 \Rightarrow$  real poles;  $Q > 1/\sqrt{2} \Rightarrow$  freq resp peaking

**Power Amps:** Class A:  $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$ ; Class B:  $\eta = (\pi/4)(\hat{V}_O/V_{CC})$ ;  $P_{DN\_max} = V_{CC}^2/(\pi^2 R_L)$ ;  
Class AB:  $i_n i_p = I_Q^2$ ;  $I_Q = (I_S/\alpha)e^{V_{BB}/(2V_T)}$ ;  $i_n^2 - i_L i_n - I_Q^2 = 0$

**2-stage opamp:**  $\omega_{p1} \approx (R_1 G_{m2} R_2 C_c)^{-1}$ ;  $\omega_{p2} = G_{m2}/C_2$ ;  $\omega_z = (C_c(1/G_{m2} - R))^{-1}$ ;  
 $SR = I/C_c = \omega_t \hat{V}_O$ ; will not SR limit if  $\omega_t \hat{V}_O < SR$