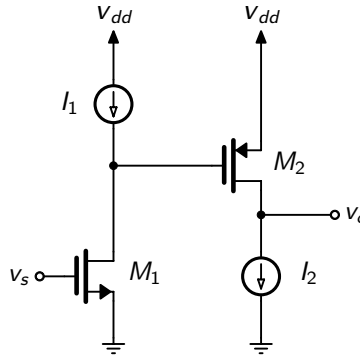


Problem Set 3 - Cascode

Question 1

Given a two-stage common-source amplifier where the biasing current sources I_1 and I_2 have output resistances equal to those of M_1 and M_2 respectively, determine an expression for the voltage gain, v_o/v_s , in terms of g_{m1} , g_{m2} , r_{o1} and r_{o2} .



Solution

Looking at the first stage, and defining v_1 to be the small signal voltage at the drain of M_1 , we have an output impedance at v_1 given by

$$r_{out1} = r_{o1} || r_{I1} = r_{o1}/2$$

since it was given that the output impedance of I_1 is equal to r_{o1} .

As a result, we get a voltage transfer function of:

$$v_1/v_s = -g_{m1}r_{out1} = -g_{m1}r_{o1}/2$$

Looking at the second stage, we get a voltage transfer function of:

$$v_o/v_1 = -g_{m2}r_{out2} = -g_{m2}r_{o2}/2$$

As such, the total transfer function is:

$$v_o/v_s = (v_1/v_s)(v_o/v_1) = (g_{m1}g_{m2}r_{o1}r_{o2})/4$$


$$v_o/v_s = (g_{m1}g_{m2}r_{o1}r_{o2})/4$$

Question 2

Given transistor M_1 which has $\mu_n C_{ox} = 240 \mu\text{A}/\text{V}^2$, $\lambda'_n = 50 \text{nm}/\text{V}$, $V_t = 0.5 \text{V}$, $W = 1 \mu\text{m}$, and $L = 200 \text{nm}$:

a) Ignoring any DC current in R_2 and assuming $r_o \rightarrow \infty$, determine V_{GS} .

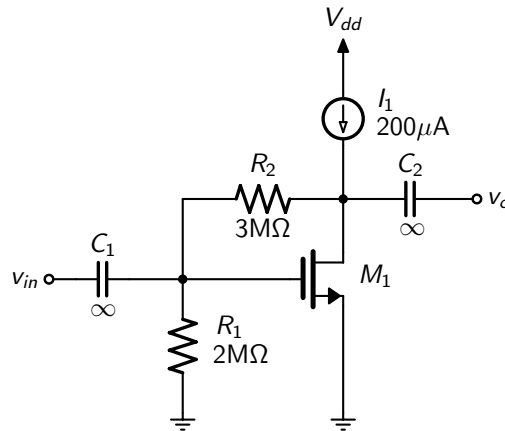- b) Determine the DC current in R_2 , determine V_{DS} , and justify your neglect of the DC current when calculating V_{GS} in part a).
- c) Determine the small-signal voltage gain v_o/v_{in} . (Assume an ideal current source)
- d) Assuming the negative swing of the output limits the overall output swing, what is the min output voltage, max output voltage and output peak-to-peak swing?
- e) What is the corresponding input amplitude, max and min voltages at the gate?



Solution

- a) Assuming all the current goes through the channel and none goes into R_2 since it is so large:

$$I_D = 0.5\mu_n C_{ox}(W/L)V_{ov}^2$$

$$V_{ov} = \sqrt{2 * I_D / (\mu_n C_{ox} * (W/L))} = \sqrt{2 * (200e-6) / ((240e-6) * ((1e-6) / (200e-9)))} = 0.5774V$$

$$V_{GS} = V_{ov} + V_t = (0.5774) + (0.5) = 1.077V$$

- b) Rearranging the voltage division rule: $V_{GS} = V_{DS} * R_1 / (R_1 + R_2)$

$$V_{DS} = V_{GS} + R_2 * V_{GS} / R_1 = (1.077) + (3e6) * (1.077) / (2e6) = 2.693V$$

$$V_{DS} = 2.693V$$

As such, the current in R_2 is:


$$I_{FB} = V_{DS} / (R_1 + R_2) = (2.693) / ((2e6) + (3e6)) = 538.7nA$$

This is quite small compared to I_{D1} so ignoring this current in part (a) is justified.

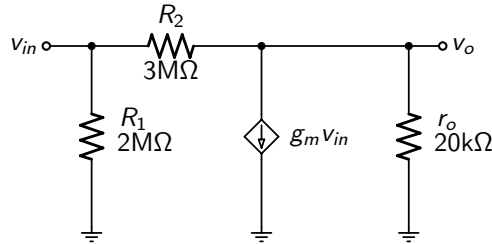c) First, g_m and r_o are calculated:

$$g_m = 2 * I_D / (V_{GS} - V_t) = 2 * (200e - 6) / ((1.077) - (0.5)) = 692.8 \mu\text{A/V}$$

$$r_o = L / (\lambda'_n * I_D) = (200e - 9) / ((50e - 9) * (200e - 6)) = 20\text{k}\Omega$$



Second, using KCL:

$$((v_o - v_{in})/R_2) + (g_m v_{in}) + (v_o/r_o) = 0$$

$$v_o/v_{in} = (1/R_2 - g_m)/(1/R_2 + 1/r_o) = (1/(3e6) - (692.8e - 6))/(1/(3e6) + 1/(20e3)) = -13.76\text{V/V}$$

$$v_o/v_{in} = -13.76\text{V/V}$$

d) For M_1 to remain in the active region, we require that $V_{DS} \geq V_{ov}$. We can also write this condition as

$$V_D - V_S \geq V_G - V_S - V_t$$

or equivalently

$$V_D \geq V_G - V_t$$

In other words, the drain voltage must stay higher than the gate voltage minus the threshold voltage for the device to remain in the active region.

Now let us write V_{G1} as $V_G + \Delta V_G$ and V_{D1} as $V_D + \Delta V_D$

where V_G and V_D are the bias voltages for the gate and drain respectively

So we have the requirement

$$V_D + \Delta V_D \geq V_G + \Delta V_G - V_t$$

Now, define $A_v \equiv v_o/v_{in}$ and from small-signal analysis, $A_v \equiv \Delta V_D/\Delta V_G$ or $\Delta V_G = \Delta V_D/A_v$.

Putting this into the above equation, we have

$$V_D + \Delta V_D \geq V_G + (\Delta V_D/A_v) - V_t$$

and setting it to equality to find the max ΔV_D (which is the min V_{D1}), we have

$$\Delta V_D(1 - 1/A_v) = V_G - V_t - V_D$$

From this, we can solve for ΔV_D

$$\Delta V_D = (V_G - V_t - V_D)/(1 - (1/A_v)) = ((1.077) - (0.5) - (2.693))/(1 - (1/(-13.76))) = -1.973$$

This gives the max output peak-to-peak output swing of

$$V_{o,pp} = 2 * |\Delta V_D| = 2 * |(-1.973)| = 3.945V$$

$$V_{o,min} = V_D + \Delta V_D = (2.693) + (-1.973) = 0.7207V$$

$$V_{o,max} = V_D - \Delta V_D = (2.693) - (-1.973) = 4.666V$$

e) The maximum input swing at the gate is related by:

$$V_{G,pp} = V_{o,pp}/|A_v| = (3.945)/|(-13.76)| = 0.2868V$$

Since the input voltage, V_G is set to a dc bias of $V_{GS} = 1.077V$, the min/max values at the gate are

$$V_{G,min} = V_{GS} - V_{G,pp}/2 = (1.077) - (0.2868)/2 = 0.934V$$

$$V_{G,max} = V_{GS} + V_{G,pp}/2 = (1.077) + (0.2868)/2 = 1.221V$$

Question 3

In a MOS cascode amplifier, the cascode transistor is required to raise the output resistance by a factor of 40 over that of a non-cascode amplifier. If the transistor is operated at $V_{ov} = 0.2V$, what must its λ_n be? If the process technology specifies λ'_n as $50nm/V$, what channel length must the transistor have?

Solution

Let $K \equiv 40$

A cascode current source increases the output resistance by a factor of $g_{m2}r_{o2}$ compared to a non-cascode current source. And since $g_m = 2I_D/V_{ov}$ and $r_o = L/(\lambda'_n I_D)$ we have

$$K = g_{m2}r_{o2} = \frac{2L}{\lambda'_n V_{ov}}$$

so

$$\lambda_n = \lambda'_n/L = 2/(KV_{ov})$$


$$\lambda_n = 2/(K * V_{ov}) = 2/((40) * (0.2)) = 0.25V^{-1}$$

and if $\lambda'_n = 50nm/V$, then

$$L = \lambda'_n/\lambda_n = (50nm/V)/(0.25V^{-1}) = 200nm$$

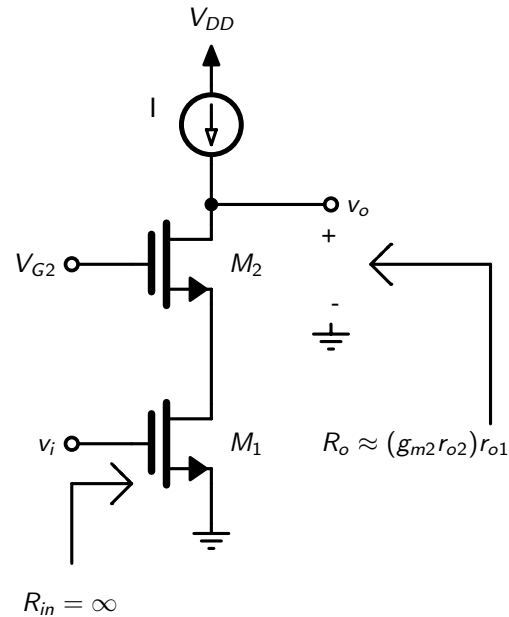Question 4

Design the cascode amplifier shown below to obtain $g_{m1} = 1mA/V$ and $R_o = 400k\Omega$. Use a $0.18 - \mu m$ technology for which $V_{tn} = 0.5V$, $\lambda'_n = 200nm/V$ and $\mu_n C_{ox} = 400\mu A/V^2$. Determine L , W/L , V_{G1} , V_{G2} , and I . Use identical transistors operated at $V_{ov} = 0.2V$, and design for the maximum possible negative signal swing at the output. What is the value of the minimum permitted output voltage?



Solution

$g_{m1} = \frac{2I_D}{V_{ov}}$, so,

$$I = I_D = g_{m1} * V_{ov}/2 = (1e-3) * (0.2)/2 = 100\mu A$$

$$R_o = (g_{m2}r_{o2})r_{o1}$$

However, if we make $g_{m2} = g_{m1} = g_m$ and $r_{o1} = r_{o2} = r_o$, we can say that:

$$r_o = \text{sqrt}(R_o/g_{m1}) = \text{sqrt}((400e3)/(1e-3)) = 20k\Omega$$

Since $r_o = \frac{L}{\lambda'_n I_D}$, we have

$$L = \lambda'_n * I_D * r_o = (200e-9) * (100e-6) * (20e3) = 400\text{nm}$$

$g_m = \sqrt{2\mu_n C_{ox}(W/L)I_D}$ so that

$$W/L = g_m^2 / (2 * \mu_n C_{ox} * I_D) = (1e-3)^2 / (2 * (400e-6) * (100e-6)) = 12.5$$

$$W/L = 12.5$$

Since $V_{ov} = 0.2\text{V}$ for both transistors, we have

$$V_{G1} = V_{ov} + V_{tn} = (0.2) + (0.5) = 0.7\text{V}$$

For V_{G2} , we want to bias it such that the drain of M_1 is high enough such that M_1 remains in the active region which is a value of $V_{ov} = 0.2\text{V}$. As a result, we set V_{G2} to


$$V_{G2} = V_{ov} + V_{tn} + V_{ov} = (0.2) + (0.5) + (0.2) = 0.9\text{V}$$

As a result, the minimum output voltage will be

$$V_{o,min} = 2 * V_{ov} = 2 * (0.2) = 0.4V$$

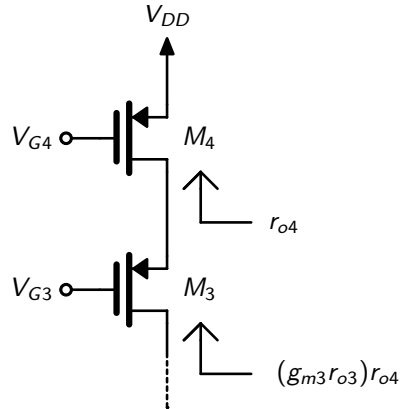Question 5

Design the circuit shown below to provide an output of $I_D = 100\mu A$. Use $V_{DD} = 3.3V$, and assume the PMOS transistors to have $\mu_p C_{ox} = 60\mu A/V^2$, $V_{tp} = -0.8V$, $L = 250nm$, and $\lambda'_p = -50nm/V$. The current source is to have the widest possible signal swing at its output. Design for $V_{ov} = 0.2V$, and specify the width, W , of the transistors and of V_{G3} and V_{G4} . What is the highest allowable voltage at the output? What is the value of output impedance, R_o ?



Solution

$$I_{D3} = I_{D4} = I_D = 0.5\mu_p C_{ox}(W/L)V_{ov}^2$$

$$W = (2 * I_D * L) / (\mu_p C_{ox} * V_{ov}^2) = (2 * (100e - 6) * (250e - 9)) / ((60e - 6) * (0.2)^2) = 20.83\mu m$$

For V_{G4} , we can write

$$V_{SG4} = V_{ov} + |V_{tp}| = (0.2) + |(-0.8)| = 1V$$

$$V_{G4} = V_{DD} - V_{SG4} = (3.3) - (1) = 2.3V$$

For V_{G3} and maximum swing, we want to set the bias voltage of the drain of M_4 to be at the edge of the active region, so

$$V_{SD4} = V_{ov} = (0.2) = 0.2V$$

$$V_{D4} = V_{DD} - V_{SD4} = (3.3) - (0.2) = 3.1V$$

$$V_{SG3} = V_{ov} + |V_{tp}| = (0.2) + |(-0.8)| = 1V$$

$$V_{G3} = V_{D4} - V_{SG3} = (3.1) - (1) = 2.1V$$

The highest allowable maximum voltage to keep M_3 in the active region is

$$V_{o,max} = V_{DD} - 2 * V_{ov} = (3.3) - 2 * (0.2) = 2.9V$$

To find R_o , we have

$$r_{o3} = L / (|\lambda'_p| * I_D) = (250e - 9) / (|-50e - 9| * (100e - 6)) = 50k\Omega$$

$$r_{o4} = L/(|\lambda'_p| * I_D) = (250e-9)/((-50e-9) * (100e-6)) = 50k\Omega$$


$$g_{m3} = (2 * I_D)/V_{ov} = (2 * (100e-6))/(0.2) = 1e-3$$

$$R_o = g_{m3} * r_{o3} * r_{o4} = (1e-3) * (50e3) * (50e3) = 2.5M\Omega$$

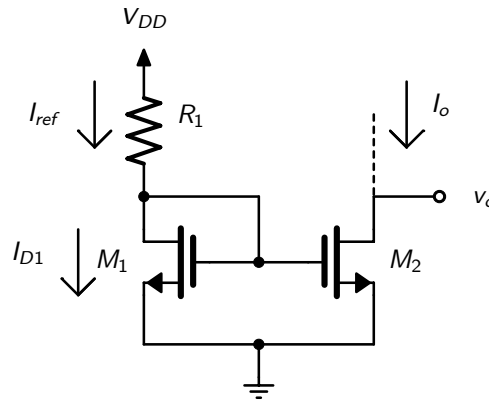Question 6

For $V_{DD} = 1.8V$ and using $I_{ref} = 100\mu A$, it is required to design the circuit below to obtain an output current whose nominal value is $I_{ref} = 100\mu A$.

- Find R if M_1 and M_2 are matched with channel lengths of $L = 500nm$, channel widths of $W = 4\mu m$, $V_{tn} = 0.5V$, and $\mu_n C_{ox} = 400\mu A/V^2$.
- What is the lowest possible value for V_o ?
- Assuming that for this process technology $\lambda'_n = 50nm/V$, find the output resistance of the current source.
- Find the current change in output current resulting from a $+0.5V$ change in V_o .



Solution

a)

$$I_o = I_{D1} = I_{ref}$$

$$I_{D1} = 0.5\mu_n C_{ox} (W/L) V_{ov}^2$$

$$V_{ov} = \sqrt{(2 * I_{D1}) / (\mu_n C_{ox} * (W/L))} = 0.25V$$

$$V_{DS1} = V_{GS1} = V_{ov} + V_{tn} = (0.25) + (0.5) = 0.75V$$

$$R = (V_{DD} - V_{GS1}) / I_{ref} = ((1.8) - (0.75)) / (100e-6) = 10.5k\Omega$$

b) The lowest V_o will be when

$$V_{o,min} = V_{ov} = 0.25V$$

c) The output resistance is r_{o3}

$$r_{o3} = L / (\lambda'_n * I_o) = (500e-9) / ((50e-9) * (100e-6)) = 100k\Omega$$

d)

$$\Delta I_D = \Delta V_o / r_{o3} = (0.5) / (100e3) = 5\mu A$$
