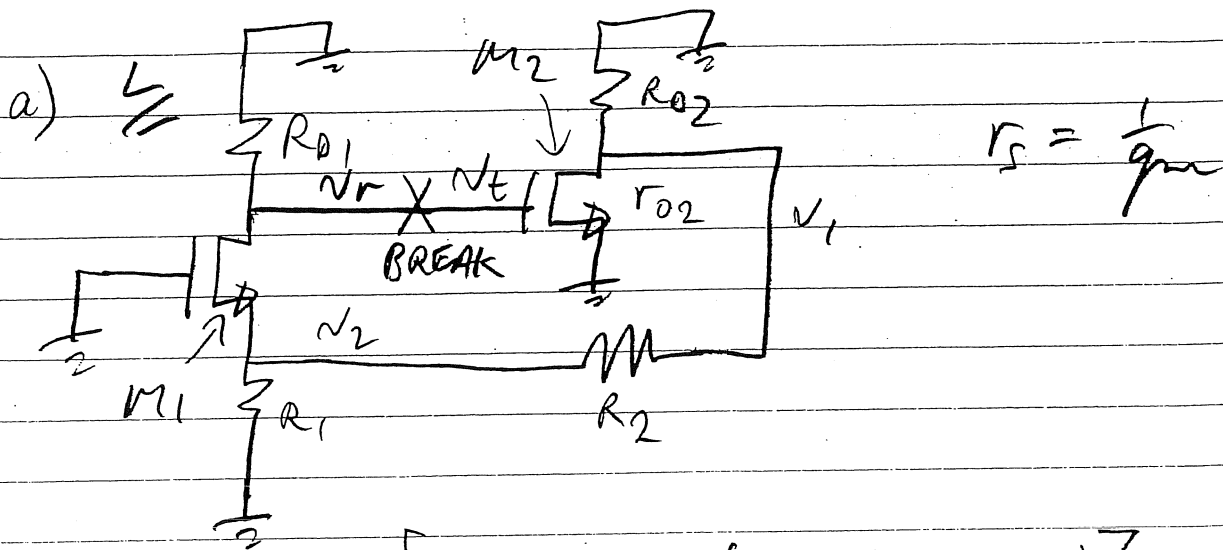


SOLUTIONS - PROBLEMS 8




$$\frac{V_1}{N_t} = - \frac{[R_{02} \parallel r_{02} \parallel (R_2 + (R_1 \parallel r_{s1}))]}{r_{s2}}$$

$$\frac{V_2}{N_t} = \frac{R_1 \parallel r_{s1}}{R_1 \parallel r_{s1} + R_2}$$

$$\frac{V_r}{N_2} = \frac{R_{01}}{r_{s1}}$$

$$L = \frac{V_r}{N_t} = \frac{[R_{02} \parallel r_{02} \parallel (R_2 + (R_1 \parallel r_{s1}))] R_{01} (R_1 \parallel r_{s1})}{r_{s1} r_{s2} [(R_1 \parallel r_{s1}) + R_2]}$$

a) CONTINUED

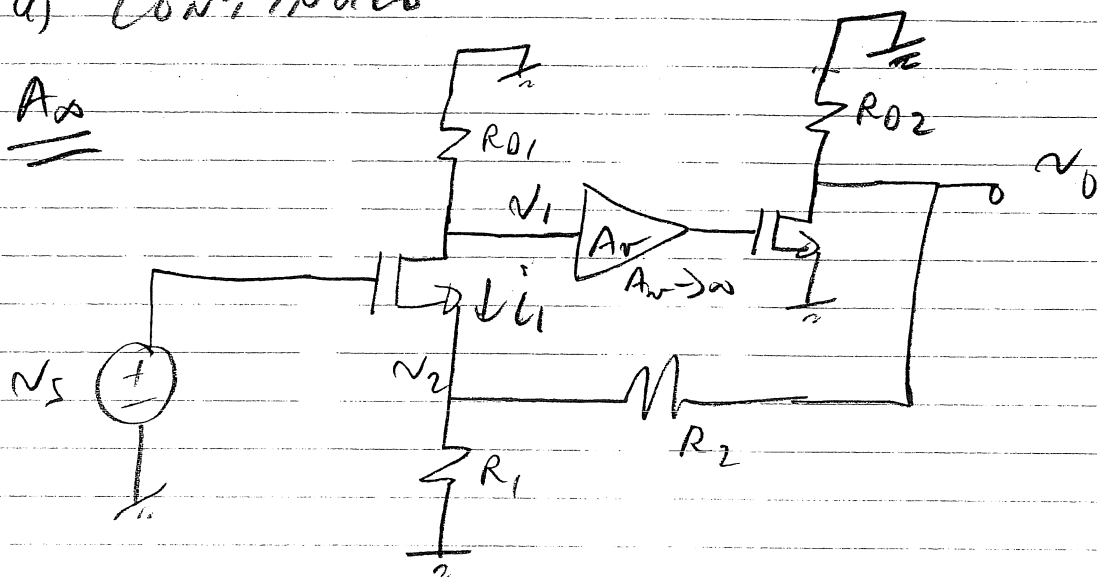


$$A_v \rightarrow \infty \Rightarrow v_1 \rightarrow 0, i_1 \rightarrow 0$$

$$v_2 = v_s$$

$$v_2 = \frac{R_1}{R_1 + R_2} v_o \Rightarrow \underline{\underline{A_{\infty} \equiv \frac{v_o}{v_s} \Big|_{A_v \rightarrow \infty} = \frac{R_1 + R_2}{R_2}}}$$

d

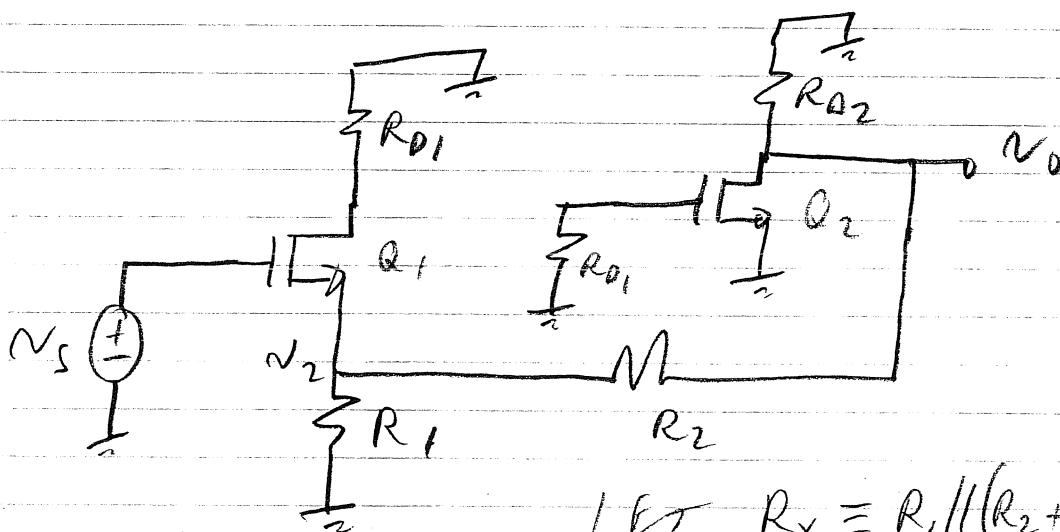

$$\text{LET } R_x \equiv R_1 \parallel (R_2 + (R_{o2} \parallel r_{o2}))$$


$$\underline{\underline{\frac{v_2}{v_s} = \frac{R_x}{R_x + r_{i1}}}}$$

3

$$\frac{v_o}{v_2} = \frac{R_{o2} \parallel r_{o2}}{(R_{o2} \parallel r_{o2}) + R_2}$$

$$\underline{\underline{d}} = \frac{v_o}{v_2} \times \frac{v_2}{v_s} = \frac{(R_{o2} \parallel r_{o2}) \cdot (R_x)}{(R_{o2} \parallel r_{o2} + R_2) (R_x + r_{s1})}$$

b) $\underline{\underline{L}}$

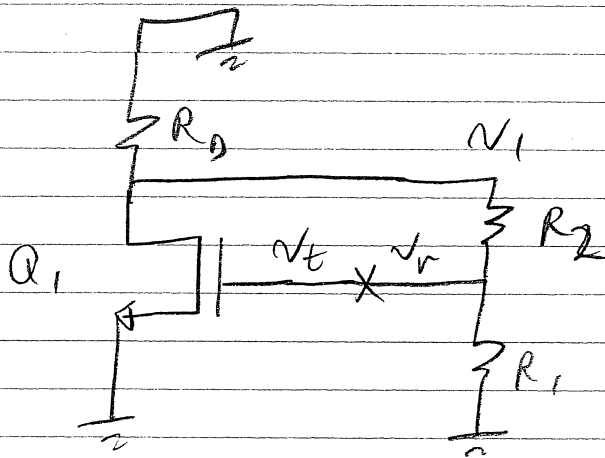


$$r_{s1} = \frac{1}{g_{m1}}$$

$$\frac{v_1}{v_t} = - \frac{R_D \parallel (R_1 + R_2)}{r_{s1}} = \frac{-(R_1 + R_2) R_D}{(R_1 + R_2 + R_D) r_{s1}}$$

$$\frac{v_r}{v_1} = \frac{R_1}{R_1 + R_2}$$

$$\underline{\underline{L}} = - \frac{v_r}{v_t} = \frac{g_{m1} R_1 R_D}{R_1 + R_2 + R_D}$$

b) CONT
 A_{∞}

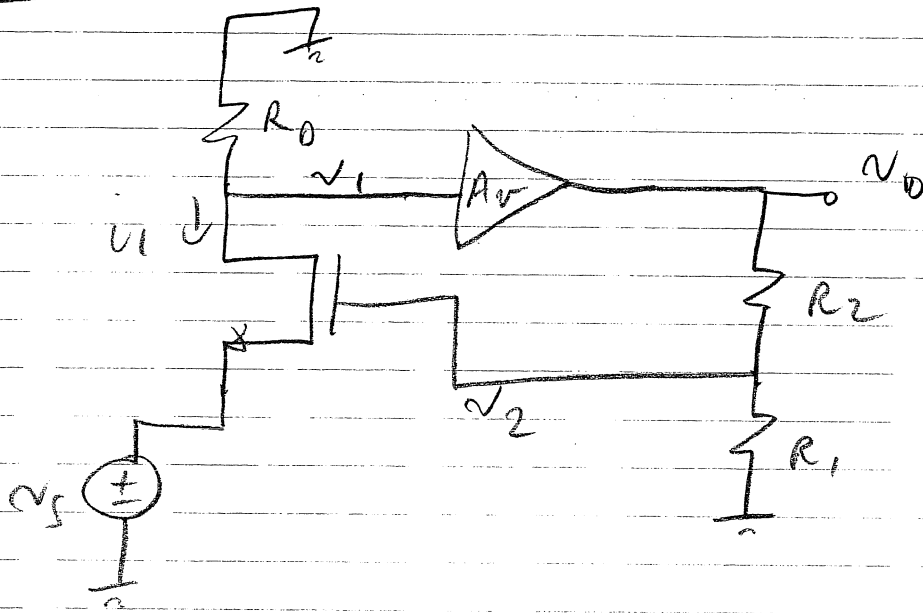


$$A_v \rightarrow \infty \Rightarrow v_1 \rightarrow 0, i_1 \rightarrow 0$$


$$\Rightarrow v_2 = v_s$$

$$v_s = \frac{R_1}{R_1 + R_2} v_o \Rightarrow A_{\infty} \equiv \frac{v_o}{v_s} \Big|_{L \rightarrow \infty} = \frac{R_1 + R_2}{R_1}$$

d

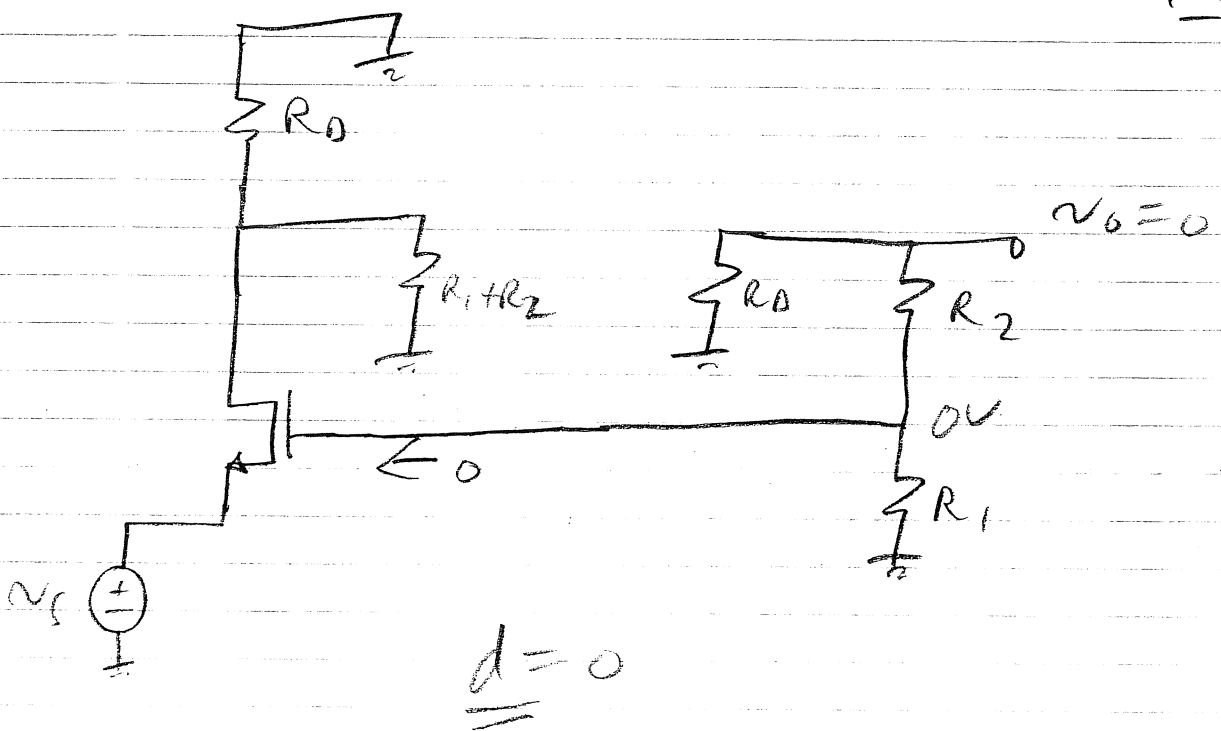

$$\underline{d = 0}$$

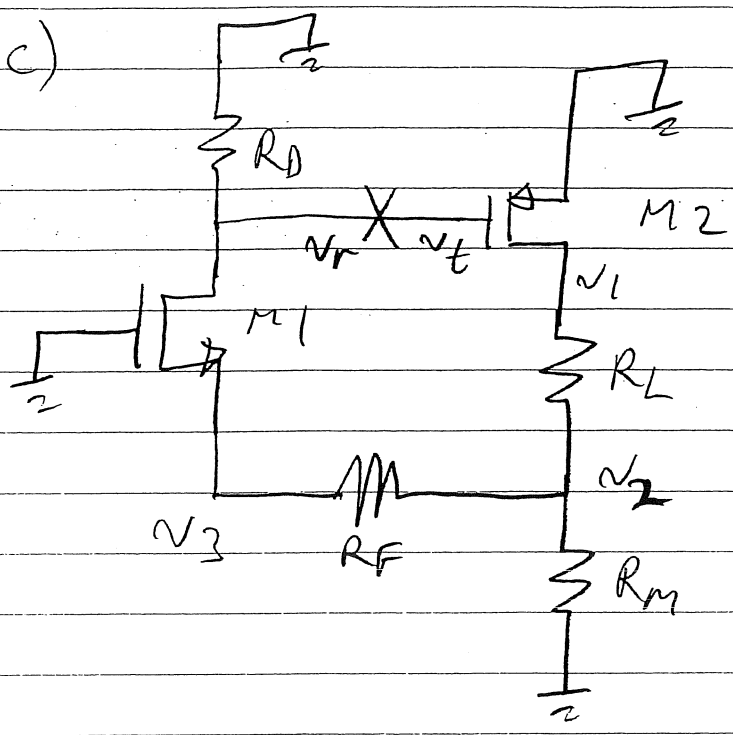

$$\frac{v_1}{v_E} = \frac{R_L + (R_M \parallel (R_F + r_{S1}))}{r_{S2}}$$

$$\frac{v_2}{v_1} = \frac{R_M \parallel (R_F + r_{S1})}{[R_M \parallel (R_F + r_{S1})] + R_L}$$



$$\frac{v_3}{v_2} = \frac{r_{S1}}{r_{S1} + R_F}$$

$$\frac{v_F}{v_3} = \frac{R_D}{r_{S1}}$$

$$L \equiv \frac{-v_F}{v_E} = \frac{[R_M \parallel (R_F + r_{S1})] R_D}{r_{S2} (r_{S1} + R_F)}$$

C) CONT.


6

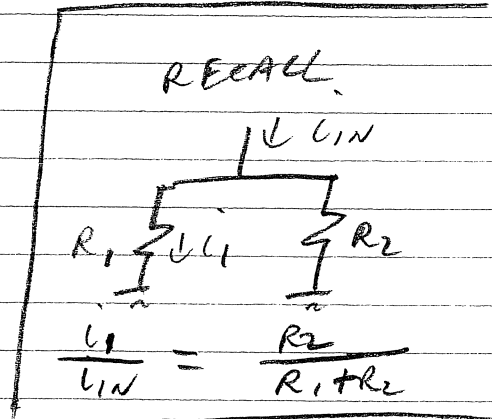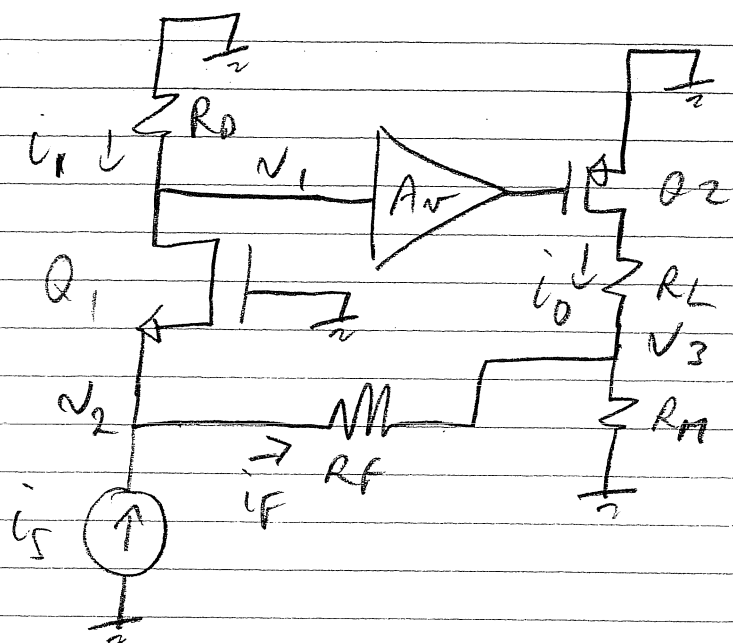

$A_v \rightarrow \infty \Rightarrow v_1 \rightarrow 0, i_1 \rightarrow 0 \Rightarrow i_F = i_S, v_2 = 0$

$-i_S = -i_F = i_0 \left(\frac{R_m}{R_m + R_F} \right)$ CURRENT DIVIDER

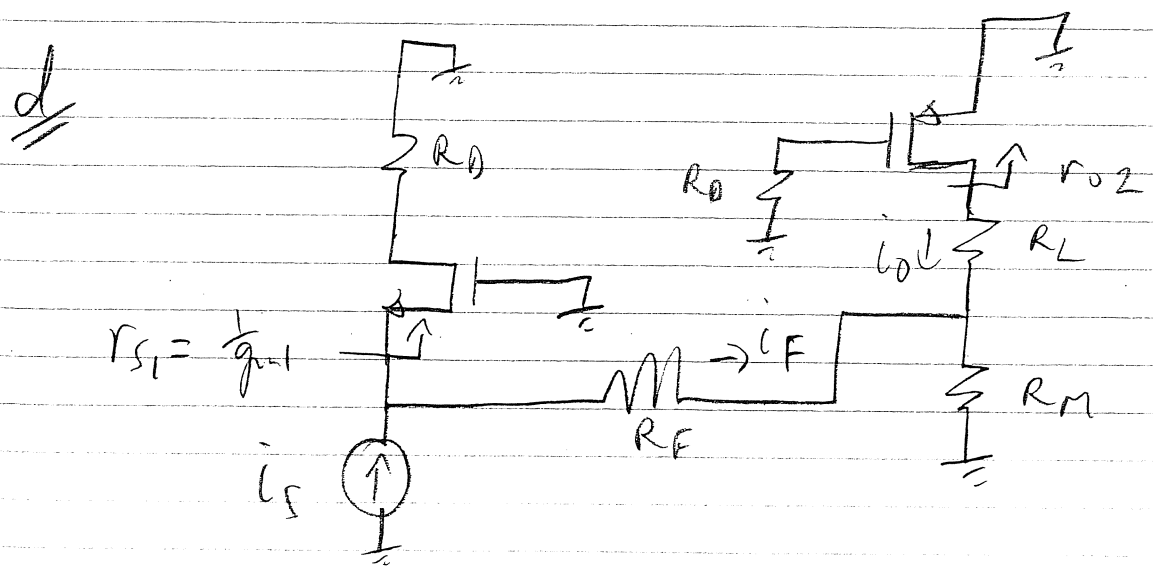$A_{v0} \equiv \frac{i_0}{i_S} = -\frac{(R_m + R_F)}{R_m}$



c) cont


(7)

$$\frac{i_F}{i_S} = \frac{r_{S1}}{r_{S1} + R_F + [R_M \parallel (R_L + r_{O2})]}$$

$$\frac{i_O}{i_F} = \frac{-R_M}{R_M + (R_L + r_{O2})}$$

$$d = \left. \frac{i_O}{i_S} \right|_{\rightarrow 0} = \frac{-R_M \cdot r_{S1}}{(R_M + R_L + r_{O2}) [r_{S1} + R_F + (R_M \parallel (R_L + r_{O2}))]}$$

d)

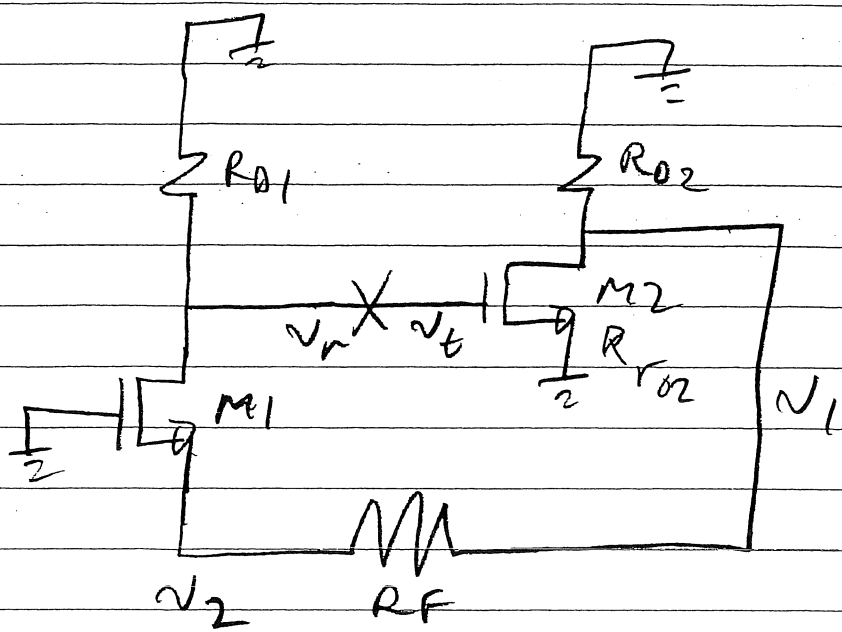

$$\frac{v_1}{v_t} = - \frac{R_{02} \parallel (R_F + r_{S1}) \parallel r_{02}}{r_{S2}}$$


$$\frac{v_2}{v_1} = \frac{r_{S1}}{r_{S1} + R_F}$$

$$\frac{v_R}{v_2} = \frac{R_{01}}{r_{S1}}$$

$$L = - \frac{v_R}{v_t} = \frac{[R_{02} \parallel (R_F + r_{S1}) \parallel r_{02}] R_{01}}{r_{S2} (r_{S1} + R_F)}$$

d) CONT

9

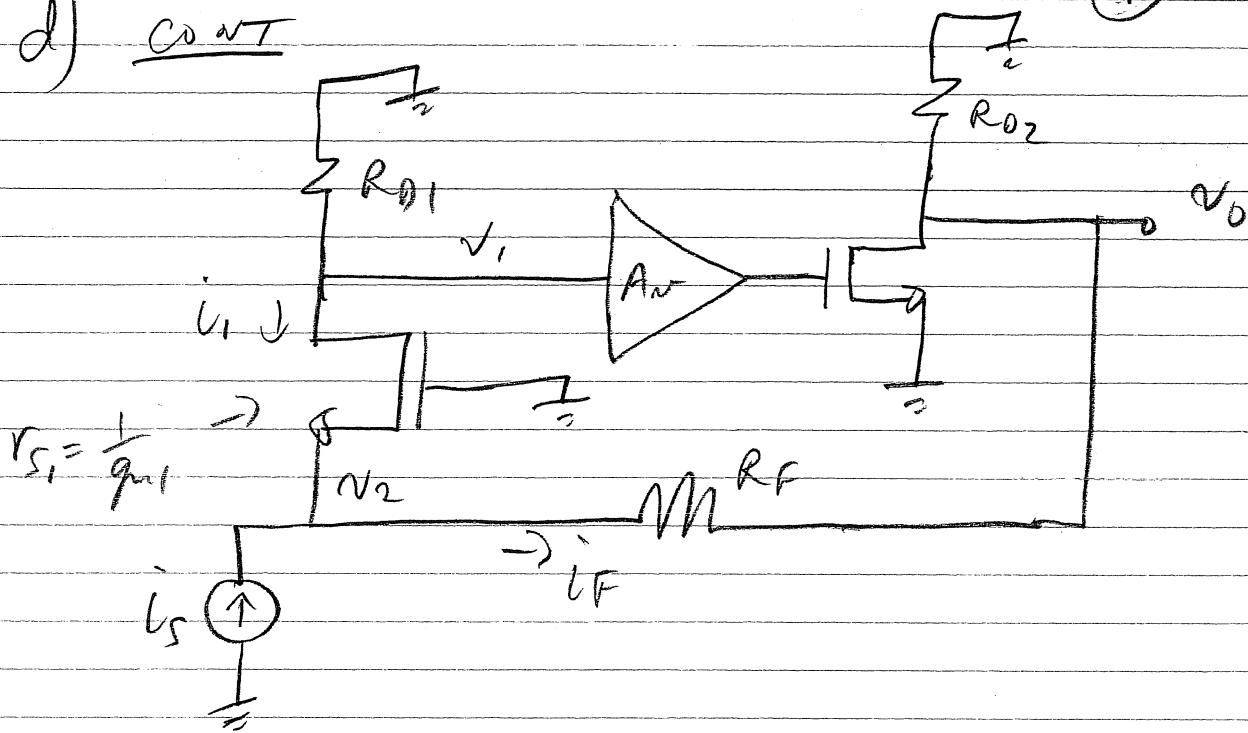

$$A_{ov} \rightarrow \infty \Rightarrow v_1 \rightarrow 0, \dot{I}_i \rightarrow 0 \Rightarrow v_2 = 0$$

$$\dot{I}_F = \dot{I}_S$$

$$v_o = -\dot{I}_F R_F = -\dot{I}_S R_F$$


$$\underline{\underline{A_{\infty} \equiv \frac{v_o}{v_S} = -R_F}}}$$

$$\underline{\underline{d}} \quad \frac{\dot{I}_F}{\dot{I}_S} = \frac{r_{S1}}{r_{S1} + R_F + (R_{02} \parallel r_{o2})}$$

$$v_o = \dot{I}_F (R_{02} \parallel r_{o2})$$

$$d = \frac{v_o}{\dot{I}_S} = \frac{r_{S1} (R_{02} \parallel r_{o2})}{r_{S1} + R_F + (R_{02} \parallel r_{o2})}$$

e)

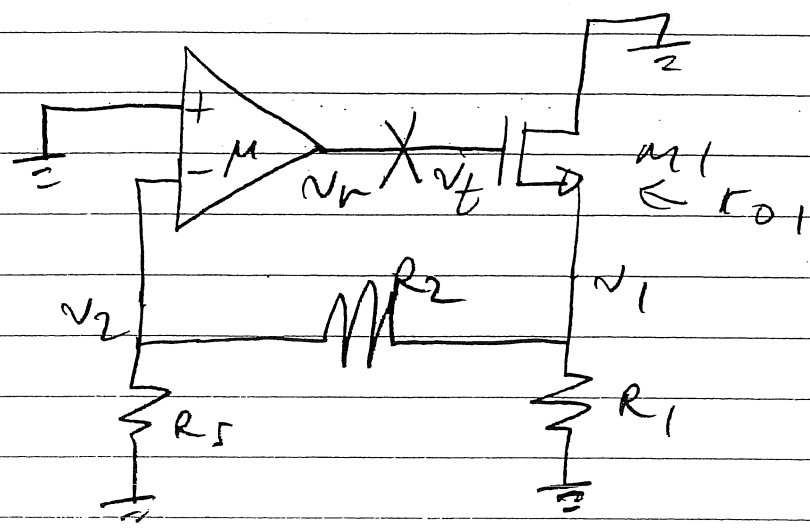

$$\frac{v_1}{v_t} = \frac{R_1 \parallel (R_2 + R_5) \parallel r_{o1}}{(R_1 \parallel (R_2 + R_5) \parallel r_{o1}) + r_{s1}}$$

$$\frac{v_2}{v_1} = \frac{R_5}{R_5 + R_2}$$


$$\frac{v_n}{v_2} = -\mu$$

$$L \equiv -\frac{v_n}{v_t} = \frac{R_1 \parallel (R_2 + R_5) \parallel r_{o1}}{(R_1 \parallel (R_2 + R_5) \parallel r_{o1}) + r_{s1}} \times \frac{\mu R_5}{R_5 + R_2}$$

e) CONT

(11)

A_{∞}

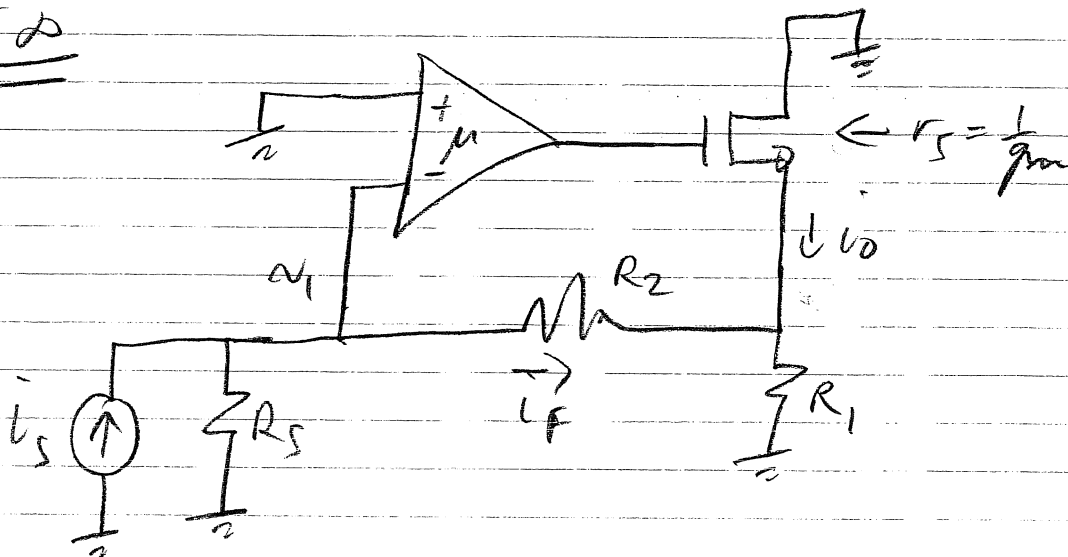

$$\mu \rightarrow \infty \Rightarrow v_1 \rightarrow 0 \Rightarrow i_F = i_S$$

$$-i_S = -i_F = -\frac{R_1}{R_1 + R_2} i_o$$


$$\underline{\underline{A_{\infty}}} \equiv \left. \frac{i_o}{i_S} \right|_{L \rightarrow \infty} = -\frac{(R_1 + R_2)}{R_1}$$

$$\underline{\underline{d}} \quad \frac{i_F}{i_S} = \frac{R_5}{R_5 + R_2 + (R_1 \parallel r_s \parallel r_o)}$$

$$\frac{i_o}{i_F} = \frac{R_1}{R_1 + (r_s \parallel r_o)}$$

$$d \equiv \left. \frac{i_o}{i_S} \right|_{L \rightarrow \infty} = \frac{R_1 R_5}{[R_1 + (r_s \parallel r_o)] [R_5 + R_2 + (R_1 \parallel r_s \parallel r_o)]}$$

f)

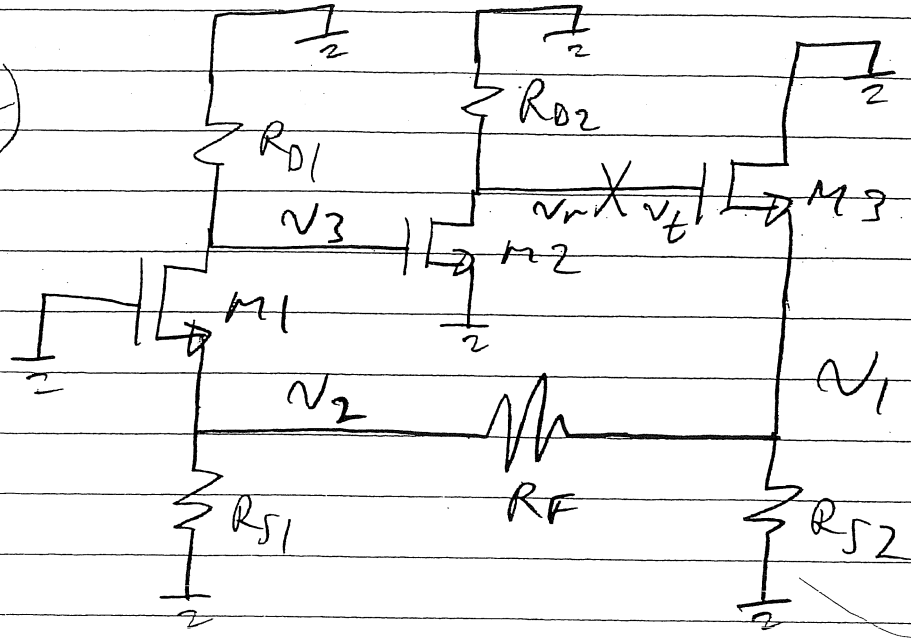

R_x'

$$\frac{v_1}{v_t} = \frac{R_{S2} \parallel [R_F + (R_{S1} \parallel r_{S1})] \parallel r_{O3}}{R_{S2} \parallel [R_F + (R_{S1} \parallel r_{S1})] \parallel r_{O3} + r_{S3}}$$

$$\frac{v_2}{v_1} = \frac{R_{S1} \parallel r_{S1}}{(R_{S1} \parallel r_{S1}) + R_F}$$

$$\frac{v_3}{v_2} = \frac{R_{O1}}{r_{S1}}$$

$$\frac{v_r}{v_3} = \frac{R_{O2} \parallel r_{O2}}{r_{S2}}$$

$$L \equiv \frac{v_r}{v_t} = \frac{R_x'}{R_x' + r_{S3}} \times \frac{R_{S1} \parallel r_{S1}}{R_{S1} \parallel r_{S1} + R_F} \times \frac{R_{O1}}{r_{S1}} \times \frac{R_{O2} \parallel r_{O2}}{r_{S2}}$$

A) CONT

(13)

$$\underline{\underline{A_{\infty}}} \quad v_2 = v_5$$

$$v_5 = v_2 = \frac{R_{S1}}{R_{S1} + R_F} v_0$$

$$\underline{\underline{A_{\infty}}} \equiv \frac{v_0}{v_5} \Big|_{L \rightarrow \infty} = \underline{\underline{\frac{R_{S1} + R_F}{R_{S1}}}}$$

$$\underline{\underline{d}} \quad \text{LET } R_Y \equiv R_{S1} \parallel (R_F + (R_{S2} \parallel r_{03}))$$

$$\frac{v_2}{v_5} = \frac{R_Y}{R_Y + r_{S1}}$$

$$\frac{v_0}{v_2} = \frac{(R_{S2} \parallel r_{03})}{(R_{S2} \parallel r_{03}) + R_F}$$

$$\underline{\underline{d}} \equiv \frac{v_0}{v_5} \Big|_{L \rightarrow \infty} = \frac{R_Y (R_{S2} \parallel r_{03})}{(R_Y + r_{S1}) [(R_{S2} \parallel r_{03}) + R_F]}$$