

Chapter 3 - Problems

3.1) Nominal $I_{out} = \frac{25\mu\text{m}}{100\mu\text{m}} \times 80\mu\text{A} = \underline{20\mu\text{A}}$

$$\begin{aligned}\therefore R_{out} &= r_{DS2} = 8000 \times \frac{1.6\mu\text{m}}{0.02\text{mA}} \\ &= \underline{640\text{ k}\Omega}\end{aligned}$$

Minimum output voltage = V_{eff}

$$\begin{aligned}&= \sqrt{\frac{2I_D}{\mu_n C_{ox} W/L}} \\ &= \sqrt{\frac{2 \times 20 \times 10^{-6}}{92 \times 10^{-6} \times 25/1.6}} \\ &= \underline{170\text{ mV}}\end{aligned}$$

3.2) DC gain, $A_v = -g_{m1} (r_{DS1} // r_{DS2})$

where $r_{DS1} = \frac{8000L}{I_{bias}}$, $r_{DS2} = \frac{12000L}{I_{bias}}$

$$\begin{aligned}\therefore r_{DS1} // r_{DS2} &= \frac{96000L^2}{20000L I_{bias}} \\ &= \underline{\frac{4800L}{I_{bias}}}\end{aligned}$$

Also,

$$g_{m1} = \sqrt{2\mu_n C_{ox} (W/L) I_{bias}}$$


$$\therefore A_v = -4800 \sqrt{\frac{2\mu_n C_{ox} WL}{I_{bias}}}$$

This result suggests that higher gains are obtained by using smaller bias currents, and/or larger transistor sizes in both width and length.

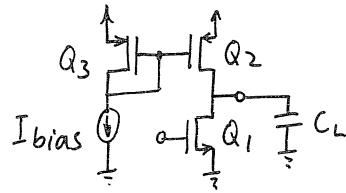3.3)

∴ C_L dominates the frequency response,

$$\omega_{3dB} \approx \frac{1}{R_{out} C_L}$$



for

$$R_{out} = r_{os1} // r_{os2}$$

$$= \frac{4800L}{I_{bias}} \text{ from Problem 3.2}$$

$$\therefore \omega_{3dB} = \frac{I_{bias}}{4800L \times C_L}$$

Increasing the bias current speeds up the circuit.

3.4)

$$V_i (G_{in} + sC_{gs1} + sC_{gd1}) - V_{in} G_{in} - V_{out} sC_{gd1} = 0 \quad (3.101)$$

$$\text{Isolating } V_i \text{ gives } V_i = \frac{V_{in} G_{in} + V_{out} sC_{gd1}}{G_{in} + sC_{gs1} + sC_{gd1}} \quad \textcircled{A}$$

$$\text{sub } \textcircled{A} \rightarrow (3.102)$$

$$V_{out} (G_2 + sC_{gd1} + sC_2) - (sC_{gd1} - g_{m1}) \times \frac{V_{in} G_{in} + V_{out} sC_{gd1}}{G_{in} + sC_{gs1} + sC_{gd1}} = 0$$

$$\text{or } \gamma(s) V_{out} = G_{in} (sC_{gd1} - g_{m1}) V_{in}$$

$$\text{where } \gamma(s) = (G_2 + s(C_{gd1} + C_2))(G_{in} + s(C_{gs1} + C_{gd1})) - sC_{gd1} (sC_{gd1} - g_{m1})$$

$$= G_2 G_{in} + s(G_2 C_{gs1} + G_2 C_{gd1} + G_{in} C_{gd1} + G_{in} C_2 + g_{m1} C_{gd1}) + s^2(C_{gd1} + C_{gs1} + C_{gd1}^2 + C_2 C_{gs1} + C_2 C_{gd1} - C_{gd1}^2)$$

$$= G_2 G_{in} [1 + s(R_{in}(C_{gs1} + C_{gd1}(1 + g_{m1} R_2)) + R_2(C_{gd1} + C_2)) + s^2 R_{in} R_2 (C_{gd1} C_{gs1} + C_{gs1} C_2 + C_{gd1} C_2)]$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{G_{in} (sC_{gd1} - g_{m1})}{\gamma(s)} = \frac{sC_{gd1} - g_{m1}}{G_2 (1 + sa + s^2 b)} = \frac{-g_{m1} R_2 (1 - s \frac{C_{gd1}}{g_{m1}})}{1 + sa + s^2 b}$$

where

$$a = R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} R_2)] + R_2 (C_{gd1} + C_2)$$


$$b = R_{in} R_2 (C_{gd1} C_{gs1} + C_{gs1} C_2 + C_{gd1} C_2)$$

Q.E.D.

3.5)

* Assume minimum feature size, $\lambda = 0.8 \mu\text{m}$ *

A sample layout of a transistor:

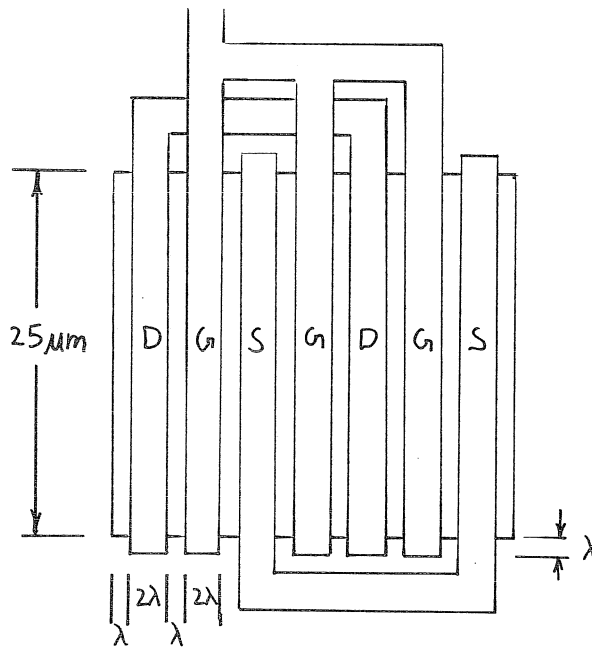

Estimating parasitic capacitances found in the layout above:

$$\begin{aligned} C_{gs1} &= \frac{2}{3} W L C_{ox} + C_{gs-ov} W \\ &= \frac{2}{3} \times 75 \times 1.6 \times 1.9 \times 10^{-15} + 0.2 \times 10^{-15} \times 75 \\ &= \underline{167 \text{ fF}} \end{aligned}$$

$$\begin{aligned} C_{gd1} &= W C_{gd-ov} = 75 \times 0.2 \times 10^{-15} \\ &= \underline{15 \text{ fF}} \end{aligned}$$

For C_{db1} & C_{db2} , we need to first calculate C_{jd} and C_{jsw} .

(assume $V_{SB} = V_{DB} = 5V - 2.5V = 2.5V$)

$$C_{jd1} = \frac{C_{jdo}}{\sqrt{1 + V_{DB}/\Phi_0}} = \frac{2.4 \times 10^{-4}}{\sqrt{1 + 2.5/0.9}} = 1.23 \times 10^{-4} \text{ PF}/\mu\text{m}^2$$

$$C_{jsw1} = \frac{C_{jsw0}}{\sqrt{1 + V_{SB}/\Phi_{sw}}} = \frac{2.0 \times 10^{-4}}{\sqrt{1 + 2.5/0.9}} = 1.03 \times 10^{-4} \text{ PF}/\mu\text{m}$$


(cont.)

3.5) (cont.) Similarly, $C_{jd2} = 2.3 \times 10^{-4} \text{ pf}/\mu\text{m}^2$ and $C_{jsw2} = 1.29 \times 10^{-4} \frac{\text{pf}}{\mu\text{m}}$

$$\begin{aligned} C_{db1} &= A_{d1} C_{jd1} + P_{d1} C_{jsw1} \\ &= 2 \times 25 \times 4 \times 0.8 \times 1.23 \times 10^{-4} + (25 + 4 \times 4 \times 0.8) \times 1.03 \times 10^{-4} \\ &= \underline{24 \text{ fF}} \end{aligned}$$

$$\begin{aligned} C_{db2} &= A_{d2} C_{jd2} + P_{d2} C_{jsw2} \\ &= 2 \times 25 \times 4 \times 0.8 \times 2.3 \times 10^{-4} + (25 + 4 \times 4 \times 0.8) \times 1.29 \times 10^{-4} \\ &= \underline{42 \text{ fF}} \end{aligned}$$

Small-signal model :

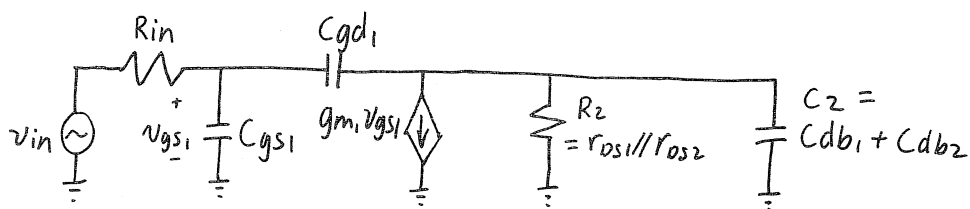

$$\omega_{3dB} \cong \frac{1}{R_{in} [C_{gs1} + C_{gd1} (1 + g_{m1} R_2)] + R_2 (C_{gd1} + C_2)}$$

where


$$\begin{aligned} R_2 &= r_{ods1} // r_{ods2} = \frac{4800 L}{I_{bias}} \text{ from Problem 3.2} \\ &= \frac{4800 \times 1.6}{75 \mu\text{A}} \\ &= \underline{102 \text{ k}\Omega} \end{aligned}$$

$$\begin{aligned} g_{m1} &= \sqrt{2 \mu_n C_{ox} W/L I_{bias}} = \sqrt{2 \times 92 \times 10^{-6} \times 75 / 1.6 \times 75 \times 10^{-6}} \\ &= 0.804 \text{ mA/V} \end{aligned}$$

If we assume $R_{in} \approx R_2 = 102 \text{ k}\Omega$,

$$\begin{aligned} \omega_{3dB} &\cong \frac{1}{102 \times 10^3 [167 + 15 (1 + 0.804 \times 10^3 \times 102 \times 10^3)] \times 10^{-15} + 102 \times 10^3 \times 10^{-15} \times (15 + 24 + 42)} \\ &= 6.57 \times 10^6 \text{ rads/sec} = \underline{2\pi \times 1.05 \text{ MHz}} \end{aligned}$$

3.6)

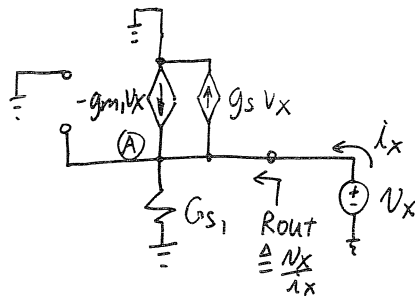

Summing currents at node (A) :

$$i_x - g_{m1}V_x - g_s V_x - N_x C_{s1} = 0$$

$$\therefore C_{out} = 1/R_{out} = i_x/N_x \\ = g_{m1} + g_s + C_{s1}$$

where $C_{s1} = g_{Ds1} + g_{Ds2}$


$$\text{or } R_{out} = [g_{m1} + g_s + \overbrace{g_{Ds1} + g_{Ds2}}^{C_{s1}}]^{-1} \cong \frac{1}{g_{m1} + g_s}$$

3.7)

Following the same analysis as in Problem 3.6, this time ignoring R_{s1} (i.e., C_{s1}), the impedance looking into the source is

$$R_{out} = [g_{m1} + g_s]^{-1}$$

3.8)

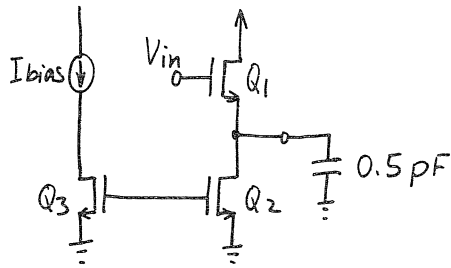

Find ω_0 , Q and zero frequency.

$$a) \quad g_{m1} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_{bias}} = \sqrt{2 \times 92 \times 10^{-6} \times \frac{100}{1.6} \times 100 \times 10^{-6}} = 1.06 \frac{mA}{V}$$

$$r_{ds1} = r_{ds2} = \frac{8000 L}{I_{bias}} = \frac{8000 (1.6 \times 10^{-6})}{100 \times 10^{-6}} k\Omega = 128 k\Omega$$

$$g_{s1} = \frac{\gamma g_m}{2\sqrt{V_{SB} + 12\Phi_F}} \approx \frac{0.5 g_m}{2\sqrt{2 + 0.7}} = 0.16 mA/V$$

$$C_{in} = [180 \times 10^3]^{-1} = 5.56 \times 10^{-6} F$$

$$G_{s1} = g_{s1} + g_{ds1} + g_{ds2} = 0.176 mA/V$$

$$C_s = C_L + C_{sb1} = 0.5 + 0.04 pF = 0.54 pF$$

$$C_{in}' = C_{in} + C_{gd1} = 45 pF$$

$$\therefore \omega_0 = \sqrt{\frac{C_{in} (g_{m1} + G_{s1})}{C_{gs1} C_s + C_{in}' (C_{gs1} + C_s)}} \quad \text{where } C_{gs1} = 0.2 pF$$

$$= 2.21 \times 10^9 \text{ rads/sec} = \underline{2\pi \times 35 \text{ MHz}}$$

$$Q = \frac{\sqrt{C_{in} (g_{m1} + G_{s1}) [C_{gs1} C_s + C_{in}' (C_{gs1} + C_s)]}}{C_{in} C_s + C_{in}' (g_{m1} + G_{s1}) + C_{gs1} C_s}$$

$$= \frac{3.1149 \times 10^{-17}}{9.382 \times 10^{-17}} = \underline{0.332}$$

$$\omega_z = -\frac{g_{m1}}{C_{gs1}} = 5.3 \times 10^9 \text{ rads/sec} = \underline{2\pi \times 844 \text{ MHz}}$$

(cont.)

3.8)(cont.)

b) Source is connected to the substrate.

Assume C_{gs} , C_{gd1} , and C_{sb1} remain unchanged, and that the only difference is the elimination of transconductance, g_{s1} .

∴ All parameters unchanged except

$$G_{s1} = g_{ds1} + g_{ds2} = 15.6 \mu A/V$$

$$\omega_0 = \sqrt{\frac{5.976 \times 10^{-9}}{1.413 \times 10^{-25}}} = 2.06 \times 10^8 \frac{\text{rads}}{\text{sec}} = \underline{2\pi \times 33 \text{ MHz}}$$

$$Q = \frac{2.906 \times 10^{-17}}{5.140 \times 10^{-17}} = \underline{0.57}$$

$$\omega_z = \underline{2\pi \times 844 \text{ MHz}} \quad (\text{unchanged from part a})$$

As expected, the elimination of the body effect increases Q .

$$\begin{aligned} 3.9) \quad a) \quad C_1 &= \frac{g_{m1} C_{gs1} C_s}{(g_{m1} + G_{s1})(C_{gs1} + C_s)} = \frac{(1.06 \times 10^{-3})(0.2 \times 10^{-12})(0.54 \times 10^{-12})}{(1.06 \times 10^{-3} + 0.176 \times 10^{-3})(0.2 + 0.54) \times 10^{-12}} \\ &= \frac{1.145 \times 10^{-28}}{9.146 \times 10^{-16}} = \underline{0.125 \text{ pF}} \end{aligned}$$

$$\begin{aligned} R_1 &= \frac{(C_{gs1} + C_s)^2}{C_{gs1} C_s g_{m1}} = \frac{(0.74 \times 10^{-12})^2}{0.2 \times 0.54 \times 10^{-24} \times 1.06 \times 10^{-3}} \\ &= \frac{5.476 \times 10^{-25}}{1.145 \times 10^{-28}} = \underline{4780 \Omega} \end{aligned}$$

$$P_1 \cong \frac{C_{in}}{C_{gs1} + C_{in}} = \underline{2\pi \times 3.61 \text{ MHz}} \quad (\text{unchanged from Ex. 3.10})$$

$$P_2 = \frac{g_{m1} + G_{s1}}{C_{gs} + C_L} = \frac{1.236 \times 10^{-3}}{0.7 \times 10^{-12}} = \underline{2\pi \times 281 \text{ MHz}}$$

(cont.)

3.9) b) Now $g_{s1} = g_{ds1} + g_{bs2} = 15.6 \mu A/V$

With all other values unchanged,


$$C_1 = \frac{1.145 \times 10^{-28}}{1.075 \times 10^{-3} \times 0.74 \times 10^{-12}} = \underline{\underline{0.144 \text{ pF}}}$$

$$R_1 = \underline{\underline{4780 \Omega}} \quad (\text{unchanged from part a})$$

$$p_1 = \underline{\underline{2\pi \times 3.61 \text{ MHz}}} \quad (\text{same as in part a})$$


$$p_2 = \frac{1.075 \times 10^{-3}}{0.7 \times 10^{-12}} = \underline{\underline{244 \text{ MHz} \times 2\pi}}$$

3.10)

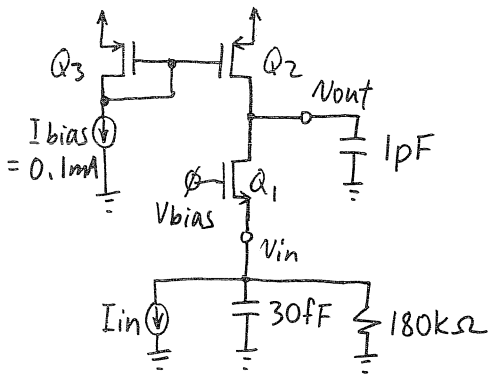

Find the -3dB frequency.

Small-signal model:

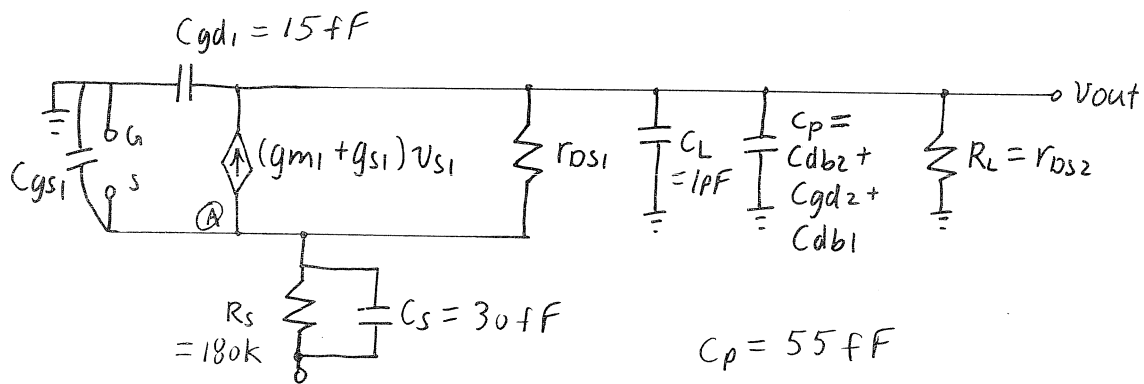

$$r_{ds1} = \frac{8000 \times 1.6}{0.1} = 128 \text{ k}\Omega$$

$$r_{ds2} = \frac{12,000 \times 1.6}{0.1} = 192 \text{ k}\Omega$$

(cont.)

3.10) (cont.)



using the open-circuit time-constant approach,
the output node dominates.

$$\omega_{3dB} \cong \frac{1}{[r_{ds2} \parallel (r_{ds1} + R_S)] [C_L + C_P + C_{gd1}]}$$

$$= \frac{1}{(118.3 \text{ k}\Omega)(1.07 \text{ pF})} = 2\pi \times 1.26 \text{ MHz}$$

Roughly $f_{3dB} = \underline{1.3 \text{ MHz}}$

3.11)

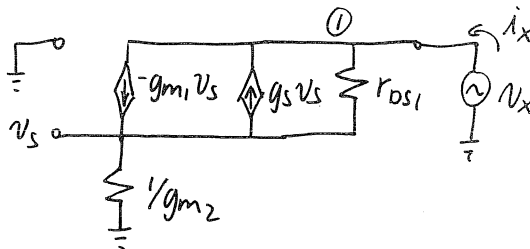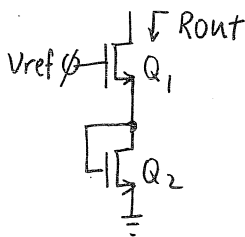

Use test voltage, v_x , to find R_{out} .

K.C.L. at node ① :

$$-g_{m1} v_s - g_s v_s - i_x + v_x g_{os1} - v_s g_{os1} = 0$$

$$-v_s (g_{m1} + g_s + g_{os1}) - i_x + v_x g_{os1} = 0 \quad \text{(A)}$$

K.C.L. at v_s :

$$v_s g_{m2} + (g_{s1} + g_{m1}) v_s + (v_s - v_x) g_{os1} = 0$$

$$v_s (g_{m1} + g_{m2} + g_{s1} + g_{os1}) - v_x g_{os1} = 0$$

$$\therefore v_s = \frac{g_{os1}}{g_{m1} + g_{m2} + g_{s1} + g_{os1}} v_x \quad \text{(B)}$$

(cont.)

3.11 (cont.)


sub (B) \rightarrow (A)

$$\left[-\frac{g_{ds1}(g_{m1} + g_{s1} + g_{ds1})}{(g_{m1} + g_{s1} + g_{ds1} + g_{m2})} + g_{ds1} \right] v_x = i_x$$

$$\begin{aligned} \therefore R_{out} &\triangleq \frac{v_x}{i_x} = \frac{g_{m1} + g_{s1} + g_{ds1} + g_{m2}}{g_{ds1} g_{m2}} \\ &= r_{ds1} + \frac{g_{m1} + g_{s1}}{g_{m2}} \times r_{ds2} + \frac{1}{g_{m2}} \end{aligned}$$

\therefore $R_{out} \approx 2 r_{ds1}$ which is consistent with the value obtained using the source degeneration formula.

3.12)

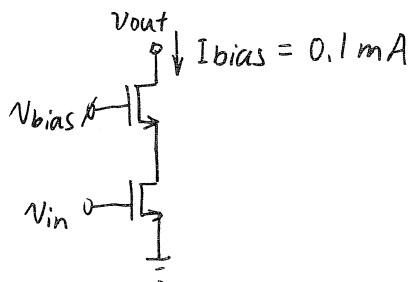


From (3.40),

$$v_{out} > v_{ds2} + v_{eff} = 2 v_{eff} + v_{tn1}$$

$$\text{where } v_{eff1} = \sqrt{\frac{2 I_{bias}}{\mu_n C_{ox} \frac{w}{L}}} = 0.264 \text{ V}$$

$$\therefore v_{out} \geq 2 \times 0.264 + 0.8 \text{ V} = \underline{1.33 \text{ V}}$$

3.13)

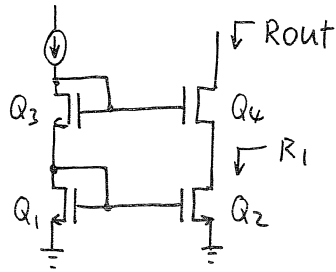


Find R_{out} ,

From section 3.1,

$$R_1 = r_{DS2}$$

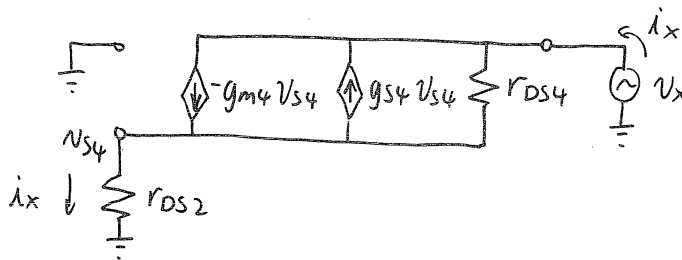Giving us the resulting small signal model:



KCL at output:

$$-(g_{m4} + g_{s4})v_{s4} + g_{DS4}v_x - g_{DS4}v_{s4} - i_x = 0$$

$$\therefore (g_{m4} + g_{s4} + g_{DS4})v_{s4} + i_x = g_{DS4}v_x$$

$$\text{But } v_{s4} = i_x / g_{DS2}$$


$$\therefore i_x \left[(g_{m4} + g_{s4} + g_{DS4}) / g_{DS2} + 1 \right] = g_{DS4}v_x$$

$$\therefore R_{out} \triangleq \frac{v_x}{i_x} = \frac{1}{g_{DS4}} \left[1 + \frac{1}{g_{DS2}} (g_{m4} + g_{s4} + g_{DS4}) \right]$$

$$\underline{R_{out} = r_{DS4} \left[1 + r_{DS2} (g_{m4} + g_{s4} + g_{DS4}) \right]}$$


This result is consistent with that obtained using source degeneration equation (3.29).

3.14)

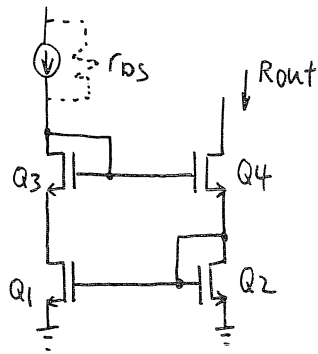

Find R_{out}

Method 1: Nodal Analysis

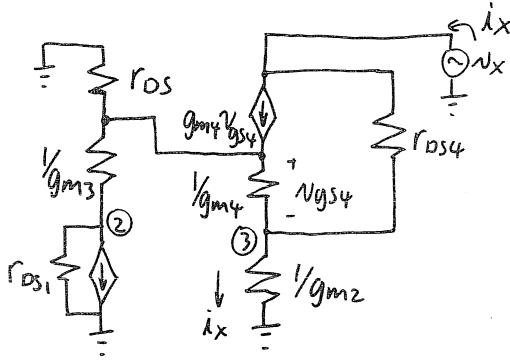

$$v_{gs4} = v_{g4} - v_{s4} = v_{(2)} \times \frac{r_{DS}}{1/g_{m3} + r_{DS}} - v_{(3)}$$

But $r_{DS} \gg 1/g_{m3}$

$\therefore \frac{r_{DS}}{1/g_{m3} + r_{DS}} \approx 1$ and

$$v_{gs4} \approx v_{(2)} - v_{(3)}$$

KCL at output:

$$-i_x + g_{m4} v_{gs4} + g_{DS4} (v_x - v_{(3)}) = 0$$

$$-i_x + g_{m4} (v_{(2)} - v_{(3)}) + g_{DS4} (v_x - v_{(3)}) = 0$$

$$\therefore -i_x - v_{(3)} (g_{m4} + g_{DS4}) + g_{m4} v_{(2)} + g_{DS4} v_x = 0 \quad (A)$$

But $v_{(3)} = i_x / g_{m2}$ and

$$v_{(2)} = -g_{m1} v_{(3)} \times [r_{DS1} \parallel (1/g_{m3} + r_{DS})]$$

$$\approx -\frac{g_{m1} r_{DS1}}{2 g_{m2}} \times i_x \quad (B)$$

(cont.)

3.14 (cont.)

sub (B) \rightarrow (A)

$$-i_x - \frac{1}{g_{m2}} (g_{m4} + g_{D54}) i_x - \frac{g_{m1} g_{m4} r_{D51}}{2 g_{m2}} i_x + g_{D54} v_x = 0$$

$$g_{D54} v_x = i_x \left(1 + \frac{g_{m4} + g_{D54}}{g_{m2}} + \frac{g_{m1} g_{m4}}{2 g_{m2}} r_{D51} \right)$$

$$\therefore R_{out} \triangleq \frac{v_x}{i_x} \approx r_{D54} \times \left(2 + \frac{g_{m1}}{2} r_{D51} \right)$$


$$\because \frac{g_{m1} r_{D51}}{2} \gg 2$$

$$\therefore \underline{R_{out} \approx r_{D54} \left(\frac{g_{m1} r_{D51}}{2} \right)} \quad \text{Q.E.D.}$$

Method 2: Feedback Analysis

$$R_{out} = (1 - A\beta) R_{out} \text{ (open loop)}$$

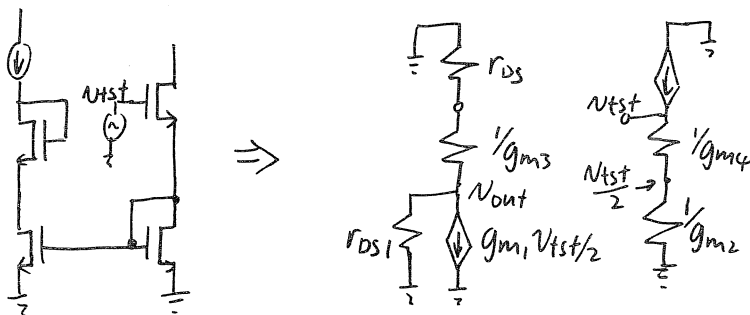where $A\beta$ is the loop gain. To determine $A\beta$, break the feedback loop and apply a test voltage as follows:




$$v_{out} = -g_{m1} \times \frac{v_{tst}}{2} \times (r_{D51} \parallel r_{DS})$$

$$\therefore \text{Loop gain} = A\beta = -\frac{g_{m1} r_{D51}}{4}$$

$$\therefore R_{out} = \left(1 + \frac{g_{m1} r_{D51}}{4} \right) \times 2 r_{D54}$$

$$\therefore \underline{R_{out} \approx \left(\frac{g_{m1} r_{D51}}{2} \right) \times r_{D54}} \quad \text{Q.E.D.}$$

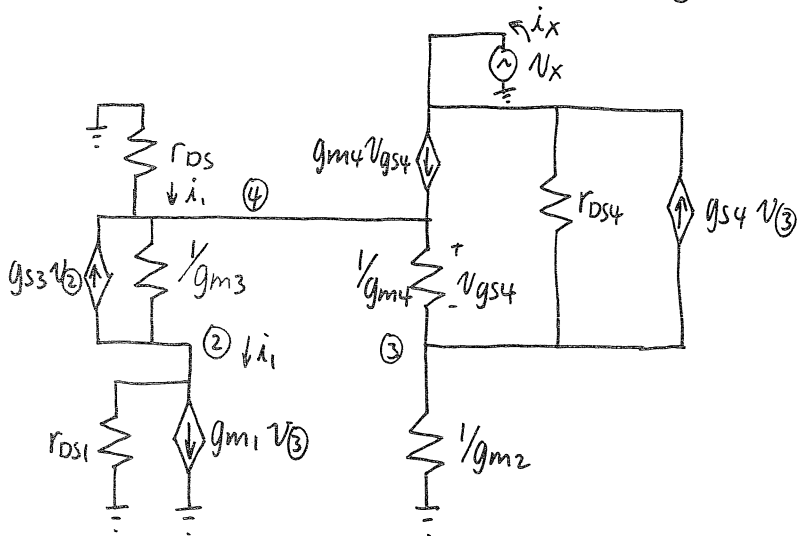3.15) Small signal model incorporating the body effect :



$$V_{gs4} = V_{(4)} - V_{(3)}$$

$$V_{(4)} = V_{(2)} + (i_1 + g_{s3} V_{(2)}) / g_{m3} \quad \text{[A]}$$

$$i_1 = -g_{os} V_{(4)} \quad \text{[B]}$$

[B] \rightarrow [A]

$$\therefore V_{(4)} \left(1 + \frac{g_{os}}{g_{m3}} \right) = \left(1 + \frac{g_{s3}}{g_{m3}} \right) V_{(2)}$$

$$V_{(4)} = \frac{g_{m3} + g_{s3}}{g_{m3} + g_{os}} V_{(2)}$$

$$V_{(4)} \approx \left(1 + \frac{g_{s3}}{g_{m3}} \right) V_{(2)}$$

$$\therefore V_{gs4} \approx \left(1 + \frac{g_{s3}}{g_{m3}} \right) V_{(2)} - V_{(3)}$$

$\left(1 + \frac{g_{s3}}{g_{m3}} \right)$ new term due to body effect.

KCL at output :

$$-i_x + g_{m4} V_{gs4} + g_{os4} (V_x - V_{(3)}) - g_{s4} V_{(3)} = 0$$

$$-i_x + g_{m4} \left(\left(1 + \frac{g_{s3}}{g_{m3}} \right) V_{(2)} - V_{(3)} \right) + g_{os4} V_x - V_{(3)} (g_{os4} + g_{s4}) \approx 0$$

$$-i_x - V_{(3)} (g_{m4} + g_{os4} + g_{s4}) + g_{m4} \left(1 + \frac{g_{s3}}{g_{m3}} \right) V_{(2)} + g_{os} V_x \approx 0 \quad \text{[C]}$$

$\left(1 + \frac{g_{s3}}{g_{m3}} \right)$ new terms

(cont.)

3.15 (cont.)

But $V_{(3)} = i_x / g_{m2}$ □

$$\begin{aligned} V_{(2)} &= (i_1 - g_{m1} V_{(3)}) r_{DS1} \\ &= -(N_{(4)} g_{DS} + g_{m1} V_{(3)}) r_{DS1} \\ &= -\left[\left(1 + g_{S3}/g_{m3}\right) g_{DS} V_{(2)} + g_{m1} V_{(3)} \right] r_{DS1} \end{aligned}$$

$$\therefore V_{(2)} = \frac{-g_{m1} r_{DS1}}{2 + g_{S3}/g_{m3}} V_{(3)} \quad \square$$

□, □ → □


$$-i_x - \frac{i_x}{g_{m2}} \left(g_{m4} \left(1 + \left(1 + \frac{g_{S3}}{g_{m3}} \right) \frac{g_{m1} r_{DS1}}{2 + g_{S3}/g_{m3}} \right) + g_{DS4} + g_{S4} \right) + g_{DS4} V_x \approx 0$$

$$\begin{aligned} \therefore R_{out} \triangleq \frac{V_x}{i_x} &\approx r_{DS4} \left[1 + \frac{g_{m4}}{g_{m2}} \left(1 + \left(1 + \frac{g_{S3}}{g_{m3}} \right) \frac{g_{m1} r_{DS1}}{2 + g_{S3}/g_{m3}} + \frac{g_{S4}}{g_{m2}} + \frac{g_{DS4}}{g_{m2}} \right) \right] \\ &\approx r_{DS4} \left[2 + \left(1 + \frac{g_{S3}}{g_{m3}} \right) \frac{g_{m1} r_{DS1}}{2 + g_{S3}/g_{m3}} + \frac{g_{S4}}{g_{m2}} \right] \end{aligned}$$

$$R_{out} \approx r_{DS4} \left(1 + \frac{g_{S3}}{g_{m3}} \right) \times \frac{g_{m1} r_{DS1}}{2 + g_{S3}/g_{m3}} \rightarrow r_{DS4} \left(\frac{g_{m1} r_{DS1}}{2} \right) \text{ as } g_{S3} \rightarrow 0$$

Q.E.D.

3.16)

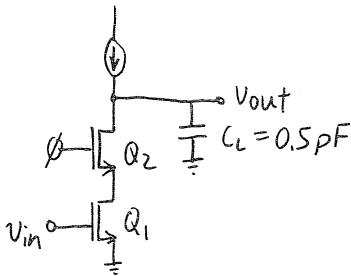

$$C_{S2} = 0.26 \text{ pF}$$

$$C_{d2} = C_{gd2} + C_{db2} + C_L + C_{bias}$$

$$= 15 + 20 + 500 + 20 \text{ fF}$$

$$= 555 \text{ fF}$$

$$\left. \begin{aligned} \therefore \tau_{Cgs1} &= 36 \text{ nsec} \\ \tau_{Cgd1} &= 75 \text{ nsec} \\ \tau_{CS2} &= 13 \text{ nsec} \end{aligned} \right\} \text{ unchanged}$$

$$\tau_{Cd2} = C_{d2} \frac{g_{m2} r_{DS2}}{2} = 555 \times 10^{-15} \times \frac{10^{-3} \times 10^{10}}{2} = 2.8 \mu\text{sec}$$

$$\therefore \tau_{Cd2} \gg \tau_{Cgd1}, \tau_{Cgs1}, \text{ and } \tau_{CS2}$$

$$\therefore \omega_{-3dB} \approx \frac{1}{\tau_{Cd2}} = \underline{2\pi \times 57 \text{ kHz}}$$

3.17) Derive ω_{odB}

From (3.161)

$$|A(s)| \approx \frac{g_{m1}}{sC_L} \quad \text{for } s=j\omega, \omega \gg \omega_{-3\text{dB}}$$

for the unity gain frequency

$$|A(s)| \Big|_{s=j\omega_{\text{odB}}} \approx \frac{g_{m1}}{\omega_{\text{odB}} C_L} \equiv 1$$

$$\therefore \omega_{\text{odB}} = \frac{g_{m1}}{C_L}$$

Assuming $C_L = 2 \text{ pF}$,

$$\omega_{\text{odB}} = \frac{1 \text{ mA/V}}{2 \text{ pF}} = 5 \times 10^8 \text{ rads/sec} = \underline{2\pi \times 80 \text{ MHz}}$$


In order to use (3.161), we need to verify that

$\omega_{\text{odB}} \ll \omega_{p2}$. From (3.165),

$$\omega_{p2} \approx \frac{g_{m2}}{C_{S2}} = \frac{1 \text{ mA/V}}{0.26 \text{ pF}} = \underline{2\pi \times 610 \text{ MHz}} \gg \omega_{\text{odB}} \checkmark$$

\therefore assumption is valid.

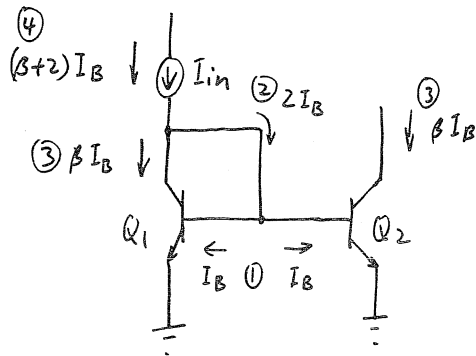3.18) Derive current gain. For $\beta \gg 1$, show $\frac{I_{out}}{I_{in}} \approx 1 - \frac{2}{\beta}$



* Numbers indicate process of reasoning or analysis *

① Because $V_{be1} = V_{be2}$
 $\therefore I_{B1} = I_{B2} \triangleq I_B$

From above analysis,


$$I_{out} = \beta I_B$$

$$I_{in} = (\beta + 2) I_B$$

$$\therefore \frac{I_{out}}{I_{in}} = \frac{\beta I_B}{(\beta + 2) I_B} = \frac{\beta + 2}{\beta + 2} - \frac{2}{\beta + 2}$$

$$\therefore \frac{I_{out}}{I_{in}} \approx 1 - \frac{2}{\beta} \quad \text{if } \beta \gg 1 \quad \text{Q.E.D.}$$

3.19)

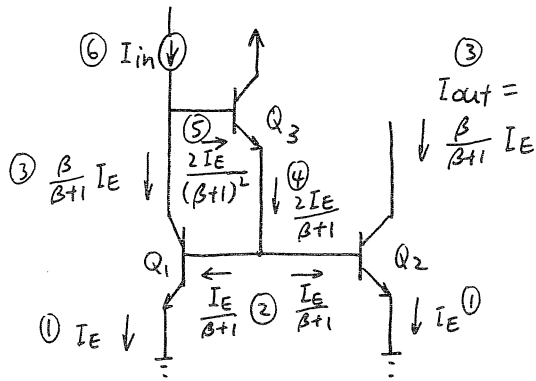Show $\frac{I_{out}}{I_{in}} \approx 1 - \frac{2}{\beta^2}$ for $\beta \gg 1$ 

* Numbers indicate process of analysis *

$$\begin{aligned} \textcircled{1} \quad \because V_{be1} &= V_{be2} \\ \therefore I_{E1} &= I_{E2} \triangleq I_E \end{aligned}$$

$$\textcircled{3} \quad I_{out} = \frac{\beta}{\beta+1} I_E$$

$$\textcircled{6} \quad I_{in} = \frac{\beta}{\beta+1} I_E + \frac{2}{(\beta+1)^2} I_E$$


$$\therefore \frac{I_{out}}{I_{in}} = \frac{\beta/\beta+1}{\frac{\beta}{\beta+1} + \frac{2}{(\beta+1)^2}} = \frac{\beta(\beta+1)}{\beta(\beta+1) + 2}$$

$$= \frac{\beta(\beta+1) + 2}{\beta(\beta+1) + 2} - \frac{2}{\beta(\beta+1) + 2} = 1 - \frac{2}{\beta^2 + \beta + 2}$$

$$\therefore \frac{I_{out}}{I_{in}} \approx 1 - \frac{2}{\beta^2} \quad \text{for } \beta \gg 1$$

Q.E.D.

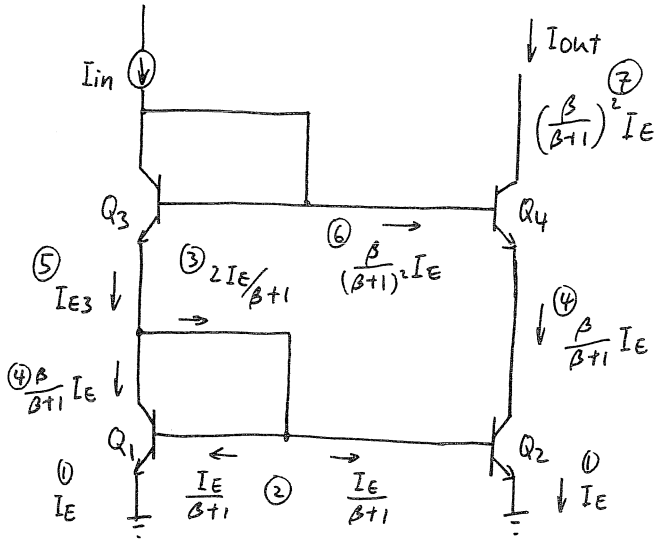3.20) Show $\frac{I_{out}}{I_{in}} \approx 1 - \frac{4}{\beta}$ for $\beta \gg 1$



$$\textcircled{1} \because V_{be1} = V_{be2},$$

$$\therefore I_{E1} = I_{E2} \triangleq I_E$$

$$\textcircled{7} I_{out} = \left(\frac{\beta}{\beta+1}\right)^2 I_E$$

$$\textcircled{5} I_{E3} = \frac{\beta}{\beta+1} I_E + \frac{2}{\beta+1} I_E = \left(\frac{\beta+2}{\beta+1}\right) I_E$$

$$\therefore I_{B3} = \frac{\beta+2}{(\beta+1)^2} I_E, \quad I_{C3} = \frac{\beta(\beta+2)}{(\beta+1)^2} I_E$$

$$I_{in} = I_{C3} + I_{B3} + I_{B4}$$


$$= \left[\frac{(\beta+2)\beta}{(\beta+1)^2} + \frac{\beta+2}{(\beta+1)^2} + \frac{\beta}{(\beta+1)^2} \right] I_E$$

$$= \frac{1}{(\beta+1)^2} [\beta^2 + 4\beta + 2] I_E$$

$$\therefore \frac{I_{out}}{I_{in}} = \frac{\beta^2}{\beta^2 + 4\beta + 2} = \frac{\beta^2 + 4\beta + 2}{\beta^2 + 4\beta + 2} - \frac{4\beta + 2}{\beta^2 + 4\beta + 2}$$

$$\therefore \frac{I_{out}}{I_{in}} \approx 1 - \frac{4\beta}{\beta^2} = 1 - \frac{4}{\beta} \quad \text{Q.E.D.}$$

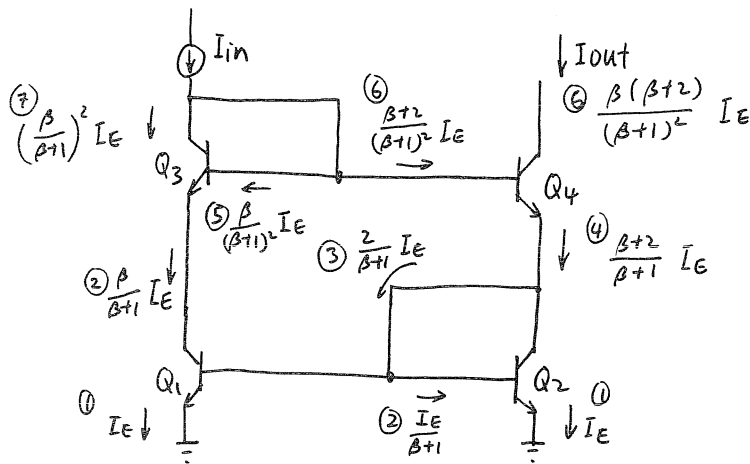3.21) Show $\frac{I_{out}}{I_{in}} = 1 - \frac{2}{\beta^2 + 2\beta + 2}$



(1) $\therefore V_{be1} = V_{be2}$
 $\therefore I_{E1} = I_{E2} = I_E$

From the above schematic analysis,

$$I_{in} = I_{C3} + I_{B3} + I_{B4} = \left[\left(\frac{\beta}{\beta+1}\right)^2 + \frac{\beta}{(\beta+1)^2} + \frac{\beta+2}{(\beta+1)^2} \right] I_E$$



$$I_{out} = \frac{\beta(\beta+2)}{(\beta+1)^2} I_E$$

$$\therefore \frac{I_{out}}{I_{in}} = \frac{\beta(\beta+2)}{\beta^2 + \beta + \beta + 2} = \frac{\beta^2 + 2\beta}{\beta^2 + 2\beta + 2}$$

$$\therefore \frac{I_{out}}{I_{in}} = \frac{\beta^2 + 2\beta + 2}{\beta^2 + 2\beta + 2} - \frac{2}{\beta^2 + 2\beta + 2} = 1 - \frac{2}{\beta^2 + 2\beta + 2}$$

Q.E.D.

3.22)

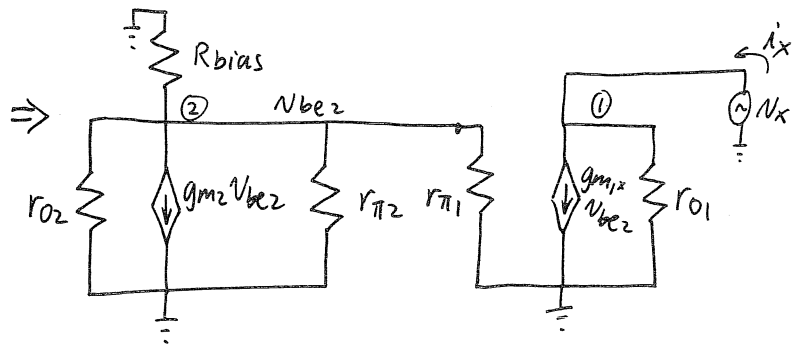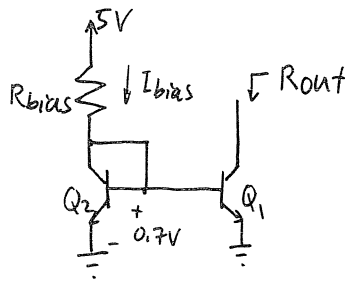

KCL at ①:

$$-i_x + g_{m1} V_{be2} + N_x / r_{o1} = 0 \quad \text{[A]}$$

KCL at ②: Let $R_T \triangleq R_{bias} // r_{o2} // r_{\pi2} // r_{\pi1}$

$$\frac{V_{be2}}{R_T} + g_{m2} V_{be2} = 0 \quad \text{which implies}$$

$$R_T = -1/g_{m2} \quad \text{or} \quad \underline{\underline{V_{be2} = 0}} \quad \checkmark$$

X (impossible as $R_T \geq 0 \Omega$)

$$\therefore \text{[A]} \quad -i_x + N_x / r_{o1} = 0$$

$$\Rightarrow \underline{\underline{R_{out} \triangleq \frac{N_x}{i_x} = r_{o1}}}$$


For $I_{bias} = 0.2 \text{ mA}$, assuming $V_{be2} \approx 0.7 \text{ V}$

$$R_{bias} = \frac{5 - 0.7 \text{ V}}{0.2 \text{ mA}} = \underline{\underline{21.5 \text{ k}\Omega}}$$

And

$$R_o = r_{o1} = \frac{V_A}{I_C} = \frac{80 \text{ V}}{0.2 \text{ mA}} = \underline{\underline{400 \text{ k}\Omega}}$$

3.23)

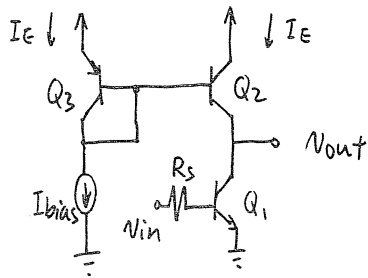Find A_v

$$I_{bias} = \frac{\beta+2}{\beta+1} I_E \Rightarrow I_E = \frac{\beta+1}{\beta+2} I_{bias}$$

$$I_{C1} = \frac{\beta}{\beta+1} I_E = \frac{\beta}{\beta+2} I_{bias}$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \frac{\beta}{\beta+2} \frac{I_{bias}}{V_T}$$

$$A_v \triangleq \frac{V_{out}}{V_{in}} = -g_{m1} (r_{o1} \parallel r_{o2}) \times \frac{r_{\pi 1}}{r_{\pi 1} + R_S}$$

$$\text{where } r_{\pi 1} = \beta / g_{m1} \\ = (\beta+2) V_T / I_{bias}$$

$$r_{o1} \approx r_{o2} = \frac{V_A}{I_{C2}} = \frac{V_A}{\left(\frac{\beta}{\beta+2}\right) I_{bias}} = \frac{\beta+2}{\beta} \frac{V_A}{I_{bias}}$$

$$\therefore r_{o1} \parallel r_{o2} = \frac{\beta+2}{2\beta} \frac{V_A}{I_{bias}}$$


$$\therefore A_v = -g_{m1} (r_{o1} \parallel r_{o2}) \frac{r_{\pi 1}}{r_{\pi 1} + R_S} \\ = -\frac{\beta}{\beta+2} \times \frac{I_{bias}}{V_T} \times \frac{\beta+2}{2\beta} \times \frac{V_A}{I_{bias}} \times \frac{(\beta+2) V_T / I_{bias}}{R_S + (\beta+2) V_T / I_{bias}}$$

$$A_v = -\frac{V_A}{2V_T} \times \frac{1}{1 + \frac{I_{bias}}{(\beta+2)V_T} \times R_S}$$


$$\text{IF } R_S \rightarrow 0 \text{ then } A_v = -\frac{V_A}{2V_T}$$

AND is independent of I_{bias} .

3.24)

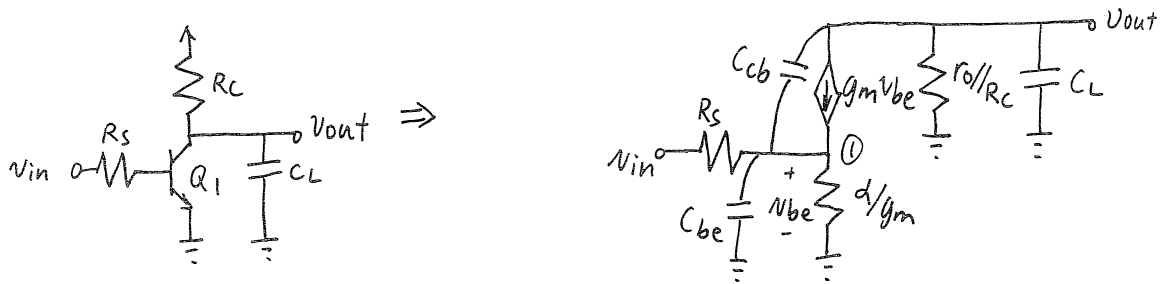


↙ Using Miller's Theorem

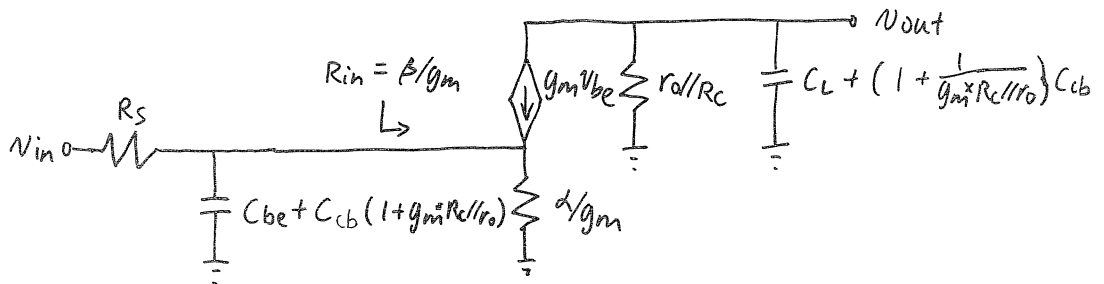

Using the method of adding time constants,

$$\left\{ \begin{array}{l} \omega_{-3dB} \approx \frac{1}{\tau_0} + \frac{1}{\tau_{out}} \quad \text{where} \\ \tau_0 = [R_s \parallel \beta/g_m] [C_{be} + C_{cb} (1 + g_m \times (R_c \parallel r_o))] \\ \tau_{out} = [r_o \parallel R_c] [C_L + (1 + \frac{1}{g_m \times (R_c \parallel r_o)}) C_{cb}] \\ \approx [r_o \parallel R_c] C_L \end{array} \right.$$

3.25)

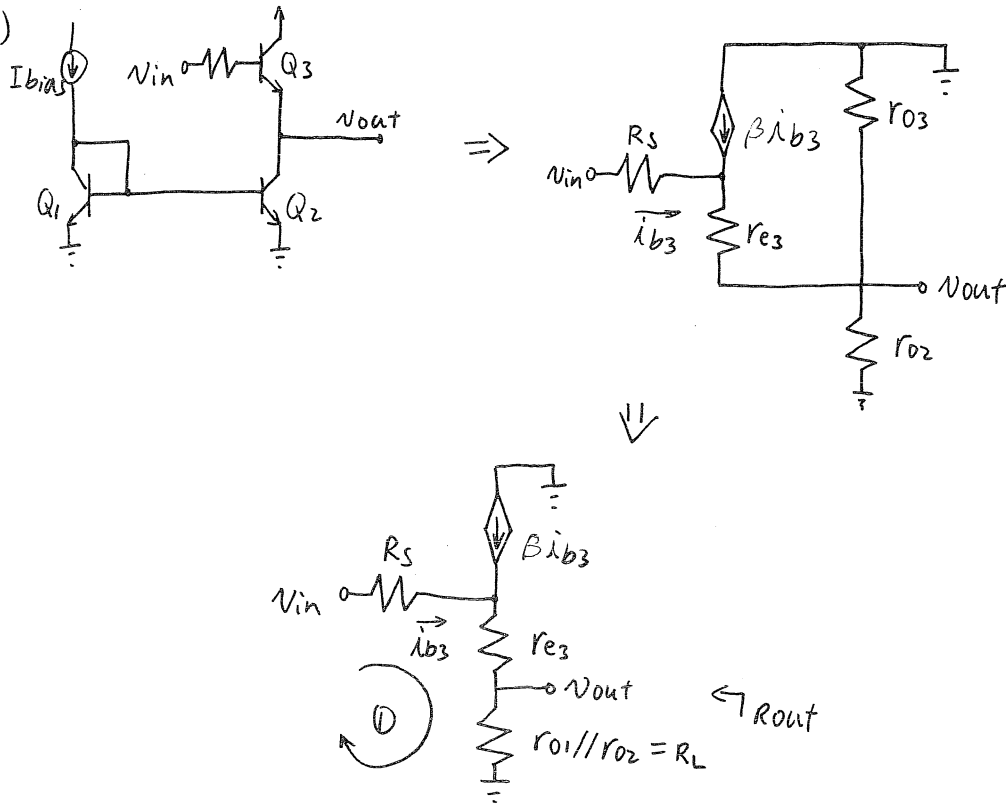


DC gain:

KVL ①: $V_{in} = R_s i_{b3} + (\beta + 1) i_{b3} (r_{e3} + R_L)$


and $V_{out} = (\beta + 1) i_{b3} R_L$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{(\beta + 1) R_L}{(\beta + 1)(r_{e3} + R_L) + R_s} = \frac{R_L}{r_{e3} + R_L + \frac{R_s}{\beta + 1}}$$

Calculating R_{out} :

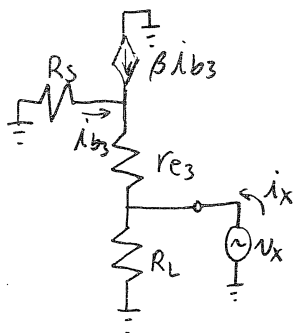

By source absorption

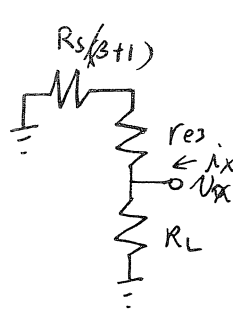

$$R_{out} \triangleq \frac{v_x}{i_x}$$

$$R_{out} = R_L \parallel \left(r_{e3} + \frac{R_s}{\beta + 1} \right)$$

(cont.)

3.25 (cont.)

When $I_{bias} = 0.5 \text{ mA}$, and assuming $\frac{R_s}{\beta+1} \ll r_{e3}$,

$$I_{c3} \approx I_{c2} = \frac{\beta}{\beta+2} I_{bias} = \frac{100}{102} \times 0.5 \text{ mA} = 0.49 \text{ mA}$$

and $r_{o3} \approx r_{o2} = \frac{V_A}{I_{c2}} = \frac{80 \text{ V}}{0.49 \text{ mA}} = 163 \text{ k}\Omega$

$$\therefore R_L = r_{o1} \parallel r_{o2} = 81 \text{ k}\Omega, \quad r_{e3} = \frac{\beta}{(\beta+1)g_{m3}} = \frac{\beta}{(\beta+1)} \frac{I_{c3}}{V_T}$$

and $\frac{N_{out}}{N_{in}} \approx \frac{81 \text{ k}\Omega}{81 \text{ k}\Omega + 53 \Omega} = \frac{100}{101 \times \frac{0.49 \text{ mA}}{26 \text{ mV}}} = 53 \Omega$

$$= 0.9993$$


$$R_{out} = R_L \parallel (r_{e3} + \frac{R_s}{\beta+1})$$

$$\approx R_L \parallel r_{e3}$$

$$= 81 \text{ k}\Omega \parallel 53 \Omega$$

$$= 52 \Omega$$

3.26)

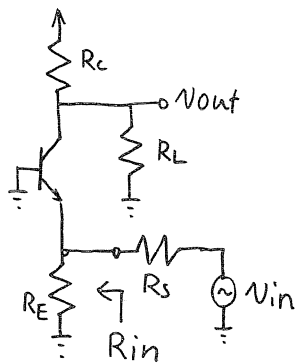

Find $\frac{V_{out}}{V_{in}}$ and R_{in}

From the small signal diagram it is clear that $R_{in} = r_e \parallel R_E$.

Also, $V_e = \frac{r_e \parallel R_E}{R_s + r_e \parallel R_E} V_{in}$ (voltage divider)


$$V_{out} = +g_m V_e \times R_c \parallel R_L \quad \text{where}$$

$$g_m = d/r_e = \frac{\beta}{(\beta+1)r_e}$$


$$\therefore V_{out} = +\frac{\beta}{(\beta+1)r_e} \times \frac{r_e \parallel R_E}{R_s + r_e \parallel R_E} \times R_c \parallel R_L V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\beta}{(\beta+1)R_E} \times \frac{R_E R_E}{r_e + R_E} \times \frac{1}{R_s + \frac{R_E R_E}{r_e + R_E}} \times R_c \parallel R_L$$

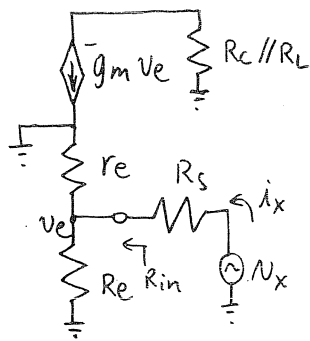
$$\frac{V_{out}}{V_{in}} = \frac{\beta}{\beta+1} \times \frac{R_E}{r_e R_s + R_E R_s + r_e R_E} \times R_c \parallel R_L$$



3.27)

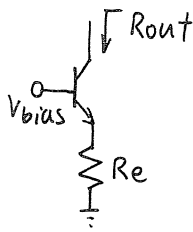

⇒

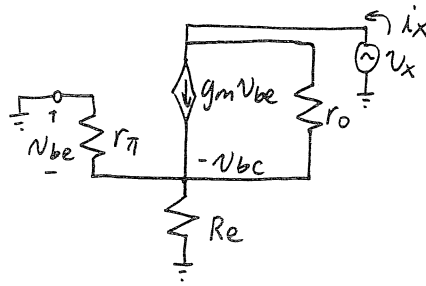

KCL at the output :

$$-i_x + g_m V_{be} + \frac{V_x + V_{be}}{r_o} = 0 \quad \text{[1]}$$

$$\text{But } i_x = -\frac{V_{be}}{r_{\pi} // R_e} \Rightarrow V_{be} = -i_x \times (r_{\pi} // R_e) \quad \text{[2]}$$

[2] → [1]

$$+i_x + g_m i_x \times r_{\pi} // R_e + \frac{i_x}{r_o} (r_{\pi} // R_e) = V_x / r_o$$



$$\therefore R_{out} \stackrel{\Delta}{=} \frac{V_x}{i_x} = r_o \left(1 + \left(g_m + \frac{1}{r_o} \right) r_{\pi} // R_e \right)$$

$$\because g_m \gg 1/r_o$$

$$\therefore \underline{R_{out} \approx r_o (1 + g_m \times (R_e // r_{\pi}))} \quad \text{Q.E.D.}$$

3.28) * Refer to problems 3.20 and 3.21. *

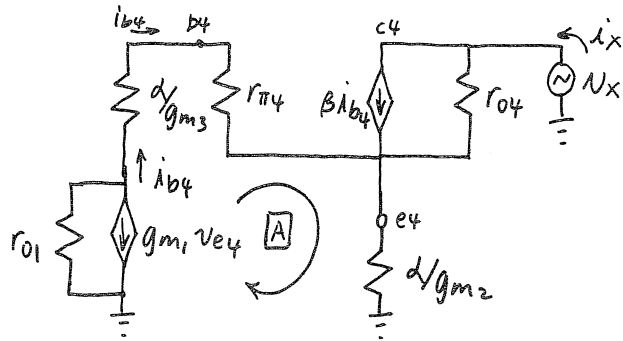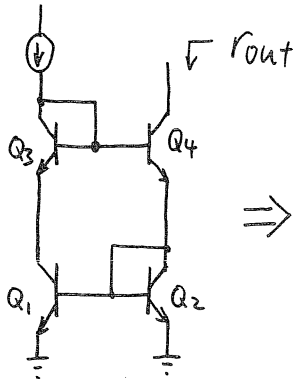3.29) Show $r_{out} \approx \frac{\beta r_o}{2}$



KCL at output: $i_x - \beta i_{b4} - (V_x - V_{e4})/r_{o4} = 0$ [1]

KCL at e_4 : $i_x + i_{b4} - V_{e4}g_{m2}/\alpha = 0$ [2]

Now express i_{b4} and V_{e4} in terms of i_x and V_x .

[1] $\times r_{o4}$ $(i_x - \beta i_{b4})r_{o4} - V_x + V_{e4} = 0$
 $V_{e4} = V_x + (\beta i_{b4} - i_x)r_{o4}$ [3]

[3] \rightarrow [2] $i_x + i_{b4} - [V_x + (\beta i_{b4} - i_x)r_{o4}]g_{m2}/\alpha = 0$
 $i_x + i_{b4} + (i_x - \beta i_{b4})r_{o4} \cdot g_{m2}/\alpha = \frac{g_{m2}}{\alpha} V_x$
 $i_x \underbrace{\left(1 + \frac{r_{o4}g_{m2}}{\alpha}\right)}_{\gg 1} + i_{b4} \underbrace{\left(1 - (\beta+1)r_{o4}g_{m2}\right)}_{\gg 1} = \frac{g_{m2}}{\alpha} V_x$

$\therefore r_{o4}g_{m2}i_x - i_{b4}(\beta+1)r_{o4}g_{m2} \approx g_{m2}V_x$

$\Rightarrow i_{b4} \approx \frac{1}{(\beta+1)r_{o4}g_{m2}} [r_{o4}g_{m2}i_x - g_{m2}V_x]$

$i_{b4} \approx \frac{i_x}{\beta+1} - \frac{V_x}{(\beta+1)r_{o4}}$ [4]

[4] \rightarrow [2] $i_x + \frac{i_x}{\beta+1} - \frac{V_x}{(\beta+1)r_{o4}} - V_{e4} \frac{g_{m2}}{\alpha} = 0$

$i_x \underbrace{\left(1 + \frac{1}{\beta+1}\right)}_{\ll 1} - \frac{V_x}{(\beta+1)r_{o4}} = V_{e4} \frac{g_{m2}}{\alpha}$

$V_{e4} \approx \frac{\alpha}{g_{m2}} \left[i_x - \frac{V_x}{(\beta+1)r_{o4}} \right]$

[5]

(cont.)

3.29 (cont.)

KVL around bias network loop [A] :

$$(g_m v_{e4} + i_{b4}) r_{o1} + (\alpha/g_{m3} + r_{\pi4}) i_{b4} + v_{e4} = 0$$

$$\boxed{4} \quad v_{e4} (\underbrace{g_{m1} r_{o1} + 1}_{\gg 1}) + i_{b4} (\underbrace{r_{o1} + r_{\pi4} + \alpha/g_{m3}}_{\ll r_{o1}}) = 0 \quad \boxed{6}$$

$\boxed{5} \rightarrow \boxed{6}$

$$\frac{\alpha}{g_{m2}} \left[i_x - \frac{N_x}{(\beta+1)r_{o4}} \right] g_{m1} r_{o1} + \left(\frac{i_x}{\beta+1} - \frac{N_x}{(\beta+1)r_{o4}} \right) r_{o1} \approx 0$$

$$r_{o1} \left[i_x - \frac{N_x}{(\beta+1)r_{o4}} \right] + \frac{i_x r_{o1}}{\beta+1} - \frac{N_x}{\beta+1} \approx 0$$


$$i_x r_{o1} \left(1 + \frac{1}{\beta+1} \right) - N_x \times \frac{2}{\beta+1} \approx 0$$

$\ll 1$

$$\therefore r_{out} \triangleq \frac{v_x}{i_x} \approx \frac{\beta+1}{2} r_{o1} \approx \frac{\beta}{2} r_{o1}$$

$$\therefore \underline{r_{out} \approx \frac{\beta}{2} r_{o1}} \quad \text{Q.E.D.}$$

3.30) Show $r_{out} \approx \beta r_o/2$

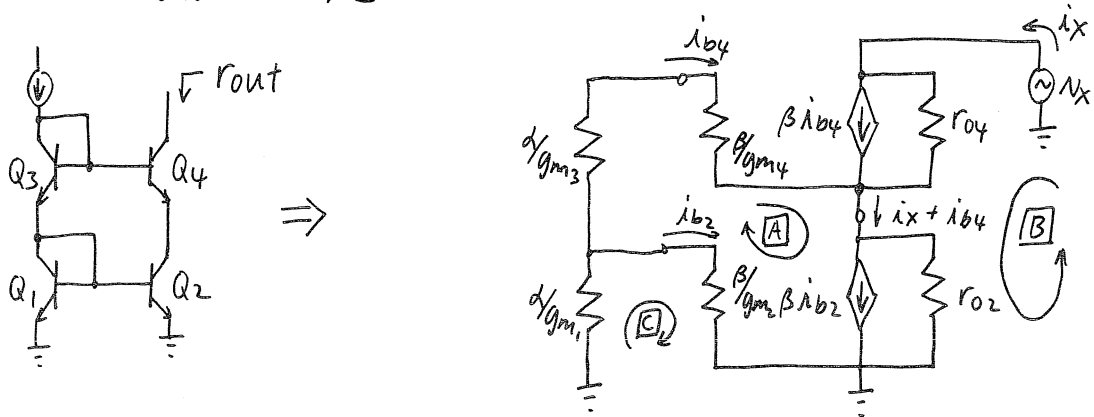

KVL about loop **B**:

$$-N_x + (\dot{i}_x - \beta \dot{i}_{b4}) r_o + (\dot{i}_x + \dot{i}_{b4} - \beta \dot{i}_{b2}) r_o = 0$$

$$2 r_o \dot{i}_x + (1 - \beta) r_o \dot{i}_{b4} - \beta r_o \dot{i}_{b2} = N_x \quad [1]$$

KVL about loop **A**:

$$(\alpha/g_{m3} + \beta/g_{m4}) \dot{i}_{b4} + (\dot{i}_x + \dot{i}_{b4} - \beta \dot{i}_{b2}) r_o - \dot{i}_{b2} \beta/g_{m2} = 0$$

$$(\alpha/g_{m3} + \beta/g_{m4} + r_o) \dot{i}_{b4} + r_o \dot{i}_x - (\beta r_o + \beta/g_{m2}) \dot{i}_{b2} = 0 \quad [2]$$

KVL about loop **C**:

$$(\dot{i}_{b4} + \dot{i}_{b2}) \alpha/g_{m1} + \dot{i}_{b2} \beta/g_{m2} = 0$$

$$\alpha/g_{m1} \dot{i}_{b4} + (\beta/g_{m2} + \alpha/g_{m1}) \dot{i}_{b2} = 0$$

$$\dot{i}_{b4} = -\frac{g_{m1}}{\alpha} \left(\frac{\beta}{g_{m2}} + \frac{\alpha}{g_{m1}} \right) \dot{i}_{b2}$$

$$= -\left((\beta+1) \frac{g_{m1}}{g_{m2}} + 1 \right) \dot{i}_{b2}$$

$$\dot{i}_{b4} \approx -(\beta+2) \dot{i}_{b2} \quad [3]$$

[3] \rightarrow [1]

$$2 r_o \dot{i}_x + (\beta-1)(\beta+2) r_o \dot{i}_{b2} - \beta r_o \dot{i}_{b2} = N_x$$

$$\therefore \dot{i}_{b2} = \frac{2 r_o \dot{i}_x - N_x}{r_o (-\beta^2 - 2\beta + 2)} \quad [4]$$

[3], [4] \rightarrow [2]

$$\underbrace{(\alpha/g_{m3} + \beta/g_{m4} + r_o)}_{\approx \beta/g_{m4} + r_o} \dot{i}_{b4} - \underbrace{(\beta+2)}_{\approx \beta} \frac{2 r_o \dot{i}_x - N_x}{r_o (-\beta^2 - 2\beta + 2)} + \dot{i}_x r_o - \underbrace{(\beta r_o + \beta/g_{m2})}_{\approx \beta r_o} \frac{2 r_o \dot{i}_x - N_x}{r_o (-\beta^2 - 2\beta + 2)} = 0$$

(cont.)

3.30 (cont.)

$$\frac{2r_o i_x - N_x}{r_o(-\beta^2 - \beta + 2)} \left[\left(\frac{\beta}{g_{m4}} + r_o \right) (-\beta) - \beta r_o \right] + i_x r_o \approx 0$$

$$\frac{2r_o i_x - N_x}{r_o(+\beta^2)} \left[2\beta r_o + \beta^2 / g_{m4} \right] + i_x r_o \approx 0$$

$$i_x \left(\underbrace{\frac{4r_o}{\beta} + \frac{2}{g_{m4}} + r_o}_{\approx r_o} \right) - N_x \left[\underbrace{\frac{2}{\beta} + \frac{1}{r_o g_m}}_{2/\beta} \right] \approx 0$$

$$\therefore r_{out} \triangleq \frac{N_x}{i_x} \approx \frac{\beta}{2} r_o \quad \text{Q.E.D.}$$

3.31) Find DC gain and ω -3dB


$$\text{DC gain} \triangleq \frac{V_{out}}{V_{in}} = g_{m1} \times r_{DS2} // r_{DS4}$$

$$g_{m1} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} \cdot I_{bias}/2} = \sqrt{2 \times 92 \times 10^{-6} \times \frac{100}{1.6} \times 0.05 \times 10^{-3}}$$

$$= \underline{0.758 \text{ mA/V}}$$

$$\left. \begin{aligned} r_{DS2} &= \frac{8000L}{I_o} = \frac{8000 \times 1.6}{0.05 \text{ mA}} = 256 \text{ k}\Omega \\ r_{DS4} &= \frac{12000L}{I_o} = \frac{12000 \times 1.6}{0.05 \text{ mA}} = 384 \text{ k}\Omega \end{aligned} \right\} r_{DS2} // r_{DS4} = 154 \text{ k}\Omega$$
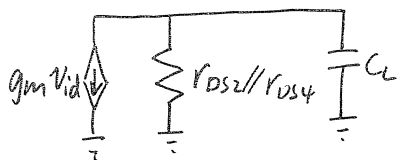
$$\therefore \text{DC gain} = 0.758 \times 10^{-3} \times 154 \times 10^3 = \underline{116}$$



$$\omega\text{-3dB} = \frac{1}{r_{DS2} // r_{DS4} \times C_L}$$

$$= \frac{1}{154 \times 10^3 \times 100 \times 10^{-12}}$$

$$= \underline{2\pi \times 10 \text{ kHz}}$$