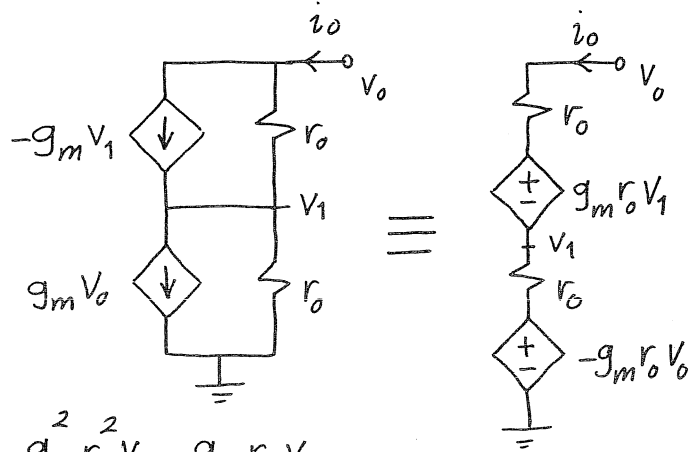


Chapter 6 - Problems

6.1) KVL:

$$\begin{cases} V_o = r_o i_o + g_m r_o V_1 + i_o r_o + (-g_m r_o V_o) \\ V_1 = r_o i_o - g_m r_o V_o \end{cases}$$



$$\therefore V_o = 2r_o i_o + g_m r_o^2 i_o - g_m^2 r_o^2 V_o - g_m r_o V_o$$

$$\Rightarrow r_{out} = \frac{V_o}{i_o} = \frac{r_o (2 + g_m r_o)}{g_m^2 r_o^2 + g_m r_o + 1}$$

Assuming $g_m r_o \gg 1 \Rightarrow g_m^2 r_o^2 \gg g_m r_o$

$$\Rightarrow r_{out} \approx \frac{r_o (g_m r_o)}{g_m^2 r_o^2} \approx \frac{1}{g_m}$$

6.2) For transistors Q_1 to Q_4 :

$$50 \mu A = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_i (0.2)^2 \quad \text{for } i=1 \text{ to } 4$$

$$\Rightarrow \left(\frac{W}{L}\right)_i = 27.2 \quad \text{for } i=1 \text{ to } 4$$

Also, $V_{GS5} = V_{GS4} + V_{DS3} = V_{eff4} + V_{tn} + V_{eff3} + 0.15 = 1.35 \text{ V}$

$$\Rightarrow V_{eff5} = V_{GS5} - V_{tn} = 0.55 \text{ V}$$

Using $I_{BIAS} = 50 \mu A \Rightarrow$

$$50 \mu A = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_5 (0.55)^2 \Rightarrow \left(\frac{W}{L}\right)_5 = 3.6$$

6.3) Reducing L by 1.6 will decrease V_{eff} by a factor of $\sqrt{1.6}$. Therefore,

$$\begin{aligned} V_{DS3} &= V_{GS5} - V_{GS4} = 1.35 - (V_{tn} + V_{eff}) \\ &= 1.35 - (0.8 + 0.16) = \underline{0.39 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_{DS4} &= V_{D4} - V_{DS3} = V_{GS3} - V_{DS3} = (V_{tn} + V_{eff}) - 0.39 \\ &= (0.8 + 0.16) - 0.39 = \underline{0.57 \text{ V}} \end{aligned}$$

$$6.4) I_{D3} = I_{D2} \Rightarrow \left(\frac{W}{L}\right)_2 V_{eff2}^2 = \left(\frac{W}{L}\right)_3 V_{eff3}^2 \Rightarrow \underline{V_{eff3} = 2 V_{eff2}}$$

$$\text{Also, } V_{GS3} = V_{GS2} + R_B I$$

$$\Rightarrow V_{eff3} = \frac{V_{eff3}}{2} + R_B \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_3 V_{eff3}^2$$

$$\Rightarrow \underline{10 \mu_n C_{ox} R_B V_{eff3} = 1}$$

$$\text{Using } V_{eff3} = 0.2 \Rightarrow \underline{R_B = 5.43 \text{ K}\Omega}$$

6.5) Using the result of Problem 6.4, we have:

$$10 \mu_n C_{ox} R_B V_{eff3} = 1$$

$$\text{Also, } \frac{\mu_n(100^\circ\text{C})}{\mu_n(20^\circ\text{C})} = \left(\frac{373}{293}\right)^{-1.5} = \underline{0.7}$$

Therefore, V_{eff3} will be increased by $\frac{1}{0.7}$.

$$\text{Equivalently, } V_{eff3} = \frac{1}{0.7} \times 0.2 = \underline{0.29 \text{ V}}$$


$$6.6) R_B(100^\circ\text{C}) = (1 + 80 \times \frac{0.3}{100}) R_B(20^\circ\text{C}) = \underline{6.73 \text{ K}\Omega}$$

Using the result of Problem 6.5, $\mu_n R_B$ is decreased at 100°C by a factor of $0.7 \times 1.24 = 0.868$.

Therefore, $V_{\text{eff}3}$ will increase by $\frac{1}{0.868}$.

$$\therefore V_{\text{eff}3} = \frac{1}{0.868} \times 0.2 = \underline{0.23 \text{ V}}$$

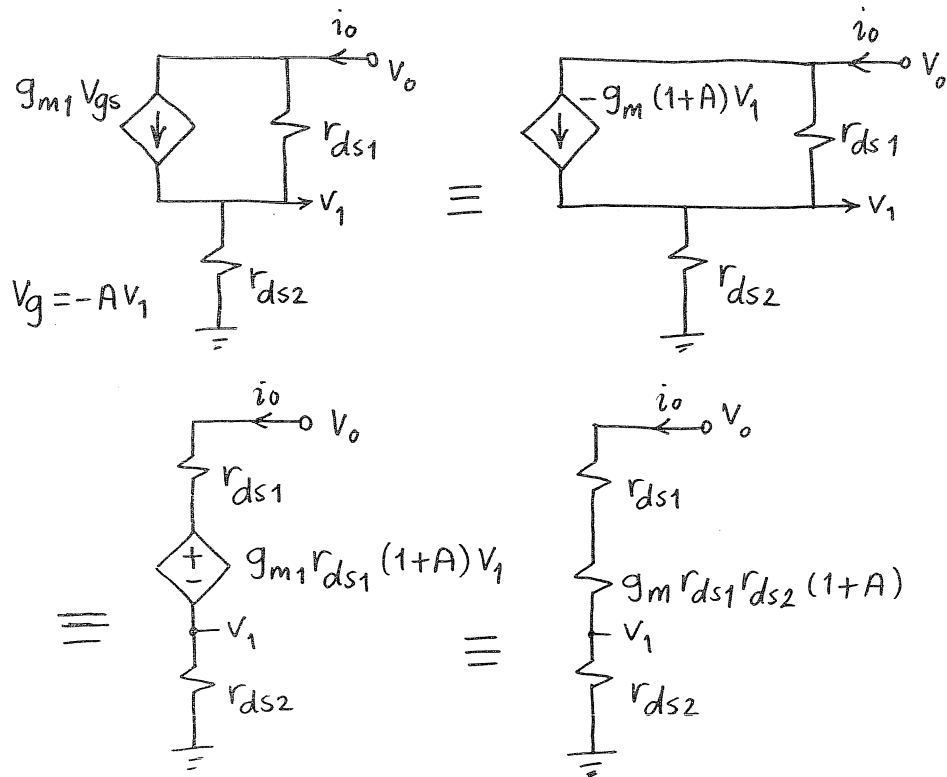6.7) The equivalent circuit of Fig. 6.3 can be simplified:




$$\Rightarrow r_o = \frac{V_o}{i_o} = r_{ds1} + r_{ds2} + (1+A)g_{m1}r_{ds1}r_{ds2}$$

ignoring the first two terms:


$$\underline{r_o \approx (1+A)g_{m1}r_{ds1}r_{ds2}}$$

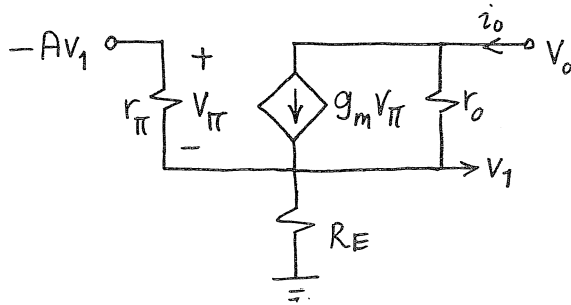6.8) The equivalent circuit of Fig. P6.8 can be simplified as:



Noting that $-AV_1 = V_{\pi} + V_1 \Rightarrow V_{\pi} = -(1+A)V_1$

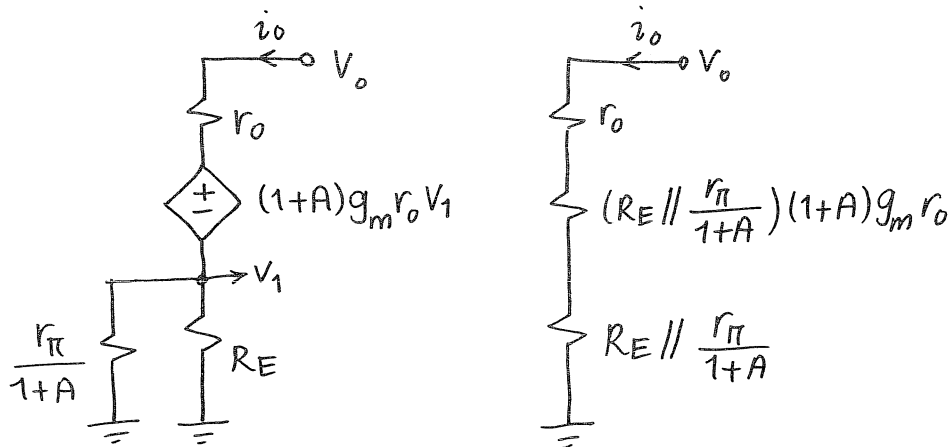The circuit can be simplified further as :



$$\Rightarrow R_{out} = \frac{V_o}{i_o} = r_o + (R_E \parallel \frac{r_{\pi}}{1+A})(1 + (1+A)g_m r_o)$$

Assuming $R_E \gg r_{\pi} \Rightarrow R_E \parallel \frac{r_{\pi}}{1+A} \approx \frac{r_{\pi}}{1+A}$

$$\Rightarrow R_{out} \approx r_o + \frac{r_{\pi}}{1+A}(1+A)g_m r_o = r_o(1 + r_{\pi}g_m) = r_o(1 + \beta)$$

This result is independent of A !

6.9) Using (6.10): $R_{out} = g_{m1} r_{ds1} r_{ds2} (1+A)$

where $A = g_{m3} r_{ds3}$ for the circuit of Fig. 6.6.

∴ $R_{out} = g_{m1} r_{ds1} r_{ds2} (1 + g_{m3} r_{ds3})$

$I_{BIAS} = 50 \mu A \Rightarrow I_{D1} = I_{D2} = 350 \mu A$ & $I_{D3} = 200 \mu A$

$\Rightarrow r_{ds1} = r_{ds2} = \frac{8K \times 1.6}{0.35} = \underline{36.57 \text{ k}\Omega}$

$r_{ds3} = \frac{8K \times 1.6}{0.2} = \underline{64 \text{ k}\Omega}$

$g_{m1} = \sqrt{2 I_{D1} \mu_n C_{ox} \frac{70}{1.6}} = 1.68 \text{ mA/V}$

$g_{m3} = \sqrt{2 I_{D3} \mu_n C_{ox} \frac{10}{1.6}} = 0.48 \text{ mA/V}$

$\Rightarrow R_{out} = 2.27 \text{ M}\Omega (1 + 30.72) = \underline{7.13 \times 10^7 \Omega}$
enhanced output

the impedance is 32 times larger than that of

a wide-swing cascode current mirror given by

$R'_{out} = g_{m1} r_{ds1} r_{ds2} = \underline{2.25 \text{ M}\Omega}$

6.10) $2 I_{D3} = \frac{1 \text{ mW}}{4 \text{ V}} = 250 \mu A \Rightarrow I_{D3} = I_{D4} = 125 \mu A$.

Also, $5 I_{D5} = 125 \mu A \Rightarrow I_{D5} = I_{D6} = 25 \mu A$

& $I_{D1} = I_{D2} = 100 \mu A$

$g_{m1} = \sqrt{2 I_{D1} \mu_n C_{ox} (W/L)_1} = 1.9 \text{ mA/V}$

$\omega_t = g_{m1} / C_L = \frac{1.9 \text{ mA/V}}{10 \text{ pF}} = 1.9 \times 10^8 \text{ rad/s} \Rightarrow \underline{f_t = 30.2 \text{ MHz}}$
(cont.)

6.10) (cont.) the slew rate without the clamp transistors:

$$SR = \frac{I_{D4}}{C_L} = \underline{12.5 \text{ V}/\mu\text{s}}$$

With the clamp transistors:

$$I_{D11} = \frac{I_{bias2} + \frac{125\mu}{30}}{31} = \frac{200\mu + \frac{125\mu}{30}}{31} = 6.6 \mu\text{A}$$

$$\Rightarrow I_{D3} = 30 I_{D11} = 198 \mu\text{A}$$

$$\Rightarrow SR = \frac{198 \mu\text{A}}{10 \text{ pF}} = \underline{19.8 \text{ V}/\mu\text{s}}$$

6.11) Ignoring the junction capacitances, the total capacitance

at the drain of Q_2 can be calculated as:
(also ignore Q_{13} since it is small)

$$C_{p2} = C_{dq2} + C_{dq4} + C_{sq5} = C_{gd(\text{overlap})} (W_2 + W_4 + W_5) + \frac{2}{3} W_5 L C_{ox}$$
$$= 0.2 \text{ fF}/\mu\text{m} (300 + 300 + 60) + \frac{2}{3} \times 60 \times 1.6 \times 1.9 \text{ fF} = \underline{254 \text{ fF}}$$

the total conductance at this node is dominated by

g_{m5} . Using the result of problem 6.10, we have:

$$g_{m5} = \sqrt{2 I_{D5} \mu_p C_{ox} (W/L)_5} = 0.237 \text{ m}\Omega$$

the second pole (half-circuit concept):

$$\omega_2 = \frac{g_{m5}}{C_{p2}} = 9.33 \times 10^8 \text{ rad/s}$$

$$\Rightarrow f_2 = \frac{\omega_2}{2\pi} = \underline{148.5 \text{ MHz}}$$

(cont.)

6.11) (cont.) Using (5.52), for a 70° phase margin, we must

$$\text{have: } \frac{f'_t}{f_2} = \tan 20^\circ \Rightarrow \underline{f'_t = 54.05 \text{ MHz}}$$

$$\text{Using (6.30): } C'_L = \frac{g_{m1}}{\omega'_t} = \frac{1.9 \text{ m}}{2\pi \times f'_t} = \underline{5.59 \text{ pF}}$$

Finally, using (16.32):

$$SR' = \frac{I_{D4}}{C'_L} = \frac{125 \mu}{5.59 \text{ p}} = \underline{22.3 \text{ V}/\mu\text{s}}$$

$$\text{With the clamp transistors: } SR' = \frac{198 \mu}{5.59 \text{ p}} = \underline{35.4 \text{ V}/\mu\text{s}}$$

6.12) This is equivalent to a 40° phase margin in the original design. Using (5.52), we have:

$$\frac{f'_t}{f_{p2}} = \tan 50^\circ \Rightarrow f'_t = 1.19 f_2 \approx \underline{176.7 \text{ MHz}}$$

$$f_2 = 1.2 f'_t = \underline{212 \text{ MHz}}$$

The final unity-gain frequency: $f'_t = 1.2 f_2 = \underline{212 \text{ MHz}}$

$$\Rightarrow C_L = \frac{g_{m1}}{\omega_t} = \underline{1.43 \text{ pF}}$$

$$\omega_z = \frac{1}{R_c C_L} \Rightarrow R_c = \frac{1}{\omega_z C_L} = \underline{525 \Omega}, \quad SR = \frac{I_{D4}}{C_L} = \underline{87 \text{ V}/\mu\text{s}}$$

$$\text{With the clamp xtors: } SR = \frac{198 \mu}{1.43 \text{ p}} = \underline{138 \text{ V}/\mu\text{s}}$$

$$6.13) \quad I_{D1} = I_{D2} = KI_{D5} = KI_{D6}$$

$$I_{\text{total}} = 2(I_{D1} + I_{D5}) = 2(1+K)I_{D5}$$

$$\Rightarrow I_{D5} = \frac{I_{\text{total}}}{2(K+1)}, \quad I_{D1} = \frac{K}{K+1} \cdot \frac{I_{\text{total}}}{2}$$

$$g_{m1} = \frac{2I_{D1}}{V_{\text{eff1}}} = \frac{K}{K+1} \frac{I_{\text{total}}}{V_{\text{eff1}}}, \quad \omega_t = \frac{K}{K+1} \frac{I_{\text{total}}}{V_{\text{eff1}} \cdot C_L}$$

Assuming a constant I_{total} & V_{eff1} , both g_{m1} & ω_t increase with increasing K .

$$6.14) \quad \text{The dc gain is given by } A_{V0} = g_{m1} r_{\text{out}}$$

$$\text{where, approximately: } r_{\text{out}} \approx g_{m8} \frac{r_{ds8}^2}{2}$$

$$\text{and } g_{m8} = \frac{2I_{D8}}{V_{\text{eff8}}}, \quad r_{ds8} = \frac{\alpha L}{I_{D8}}, \quad \alpha \text{ is constant!}$$

$$\Rightarrow r_{\text{out}} \approx \frac{\alpha^2 L^2}{V_{\text{eff8}} I_{D8}}$$

$$\Rightarrow A_{V0} = \frac{2I_{D1}}{V_{\text{eff1}}} \frac{\alpha^2 L^2}{V_{\text{eff8}} I_{D8}} = \left(\frac{I_{D1}}{I_{D8}} \right) \left(\frac{2 \alpha^2 L^2}{V_{\text{eff1}} V_{\text{eff8}}} \right)$$

Noting $I_{D8} = I_{D5}$ and $I_{D1} = KI_{D5}$ results in:

$$A_{V0} = K \left(\frac{2 \alpha^2 L^2}{V_{\text{eff1}} V_{\text{eff8}}} \right)$$

A_{V0} increases with K !

6.15) For the folded-cascode amplifier of Fig. 6.9, we have:

$$\omega_t = \frac{g_{m1}}{C_L} = \frac{\sqrt{2I_{D1}\mu_n C_{ox}(W/L)_1}}{C_L}$$

Also, $2I_{D1} + \frac{2}{K} I_{D1} = I_{total} \Rightarrow I_{D1} = \frac{K}{2(K+1)} I_{total}$

$$\Rightarrow \omega_t (\text{folded-cascode}) = \frac{1}{C_L} \sqrt{\frac{\mu_n C_{ox} I_{total} (W/L)_1 K}{K+1}}$$

For the current-mirror opamp, ω_t is given by (6.48).

Therefore,

$$\frac{\omega_t (\text{folded-cas.})}{\omega_t (\text{current-mir.})} = \sqrt{\frac{K+3}{2K(K+1)}}$$

K	1	2	4
ω_t Ratio	1	0.645	0.418

6.16) From example 6.4 : $C_p = 0.46$ pF

$$C_L = 5 + 5 + \frac{5(1+0.46)}{1+0.46+5} = 11.13 \text{ pF}$$

$$\omega_t = \frac{K g_{m1}}{C_L} = \frac{2 \times 1.7 \text{ mA/V}}{11.13 \text{ pF}} = 3.05 \times 10^8 \text{ rad/s} \text{ or } f_t = 48.6 \text{ MHz}$$

$$\beta = \frac{C_2}{C_1 + C_p + C_2} = \frac{5}{1 + 0.46 + 5} = 0.77$$

$$\Rightarrow \tau = \frac{1}{\beta \omega_t} = 4.24 \text{ nsec}$$

For a 1% accuracy, we need 4.6τ or 19.5 nsec.

6.17) Using (6.53) & (6.68): $SR = 25.4 \text{ V}/\mu\text{s}$.

Assuming a high-gain opamp:


$$A_V = \frac{\Delta V_o}{\Delta V_{in}} = \frac{-C_1}{C_2} = \frac{-5 \text{ pF}}{5 \text{ pF}} = -1 \Rightarrow \Delta V_o = -1 \text{ V}.$$

\Rightarrow the output voltage rate of change would be

$$\left. \frac{dV_o}{dt} \right|_{\max} = \frac{\Delta V_o}{\tau} = \frac{1}{7.8 \text{ ns}} = 128 \text{ V}/\mu\text{s} > 25.4 \text{ V}/\mu\text{s}$$

Therefore, the output will be limited by the slew rate!

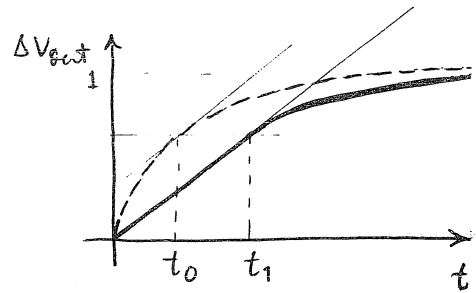The output voltage will ramp up with $25.4 \text{ V}/\mu\text{s}$ until the exponential-curve derivative is equal to the slew rate:



At time t_0 , we have: $\frac{1}{\tau} e^{-t_0/\tau} = 25.4 \text{ V}/\mu\text{s}$

$$\Rightarrow \underline{t_0 = 12.63 \text{ ns}} \quad \& \quad (1 - e^{-t_0/\tau}) = 0.8 \text{ V}$$

\Rightarrow at time $t = t_1$, the output has reached to 80%

of its final value. ($t_1 = 31.5 \text{ ns}$)

$$\text{For } t \geq t_1 : \Delta V_o(t) = 0.8 + 0.2(-e^{-(t-t_1)/\tau} + 1)$$

$$\text{For } \Delta V_o(t) = 0.99 \Rightarrow \underline{t - t_1 = 23.37 \text{ ns}}$$

This is the time required after t_1 for the output to settle to 1% of its final value.

6.18) Fully dif. folded-cas. :

$$\text{positive SR} = \frac{I_3 - I_q}{C_L} = \frac{(K+1)I_q - I_q}{C_L} = \frac{K I_q}{C_L}$$

$$\text{negative SR} = \frac{I_q}{C_L}$$

∴ for $K=2$ and $I_q = 40 \mu A$:

$$\text{positive SR} = 8 \text{ V}/\mu\text{s} \quad \text{negative SR} = 4 \text{ V}/\mu\text{s}$$

Fully dif. current-mir. :

$$\text{positive SR} = \text{negative SR} = \frac{K I_{BIAS}}{2 C_L}$$

∴ for $K=2$ & $I_{BIAS} = 160 \mu A$, we have :

$$\text{positive SR} = \text{negative SR} = 16 \text{ V}/\mu\text{s}$$

$$6.19) \left. \frac{dV_{out+}}{dt} \right|_{\max} = \left. \frac{dV_{out-}}{dt} \right|_{\max} = \frac{K I_{BIAS}}{C_L}$$

Note that both maximums occur simultaneously.

$$6.20) \omega_t = \frac{K g_{m4}}{C_L} \quad \text{where} \quad g_{m4} = \sqrt{2 I_{D4} \mu_n C_{ox} (W/L)_4}$$

$$\text{Also, } I_{\text{total}} = (2+K) I_{D4} \Rightarrow I_{D4} = \frac{I_{\text{total}}}{2+K}$$

$$\therefore \omega_t = \frac{K}{C_L} \sqrt{\frac{2}{2+K} I_{\text{total}} \mu_n C_{ox} (W/L)_4}$$

6.21) The maximum value of V_{eff} without the I_B -transistor going into the triode region is $2 - |V_{TP}| = 1.1V$. At this voltage, all the bias current will flow through either Q_1 or Q_2 .

Therefore, $I = K(1.1)^2$

For the bias condition ($V_{out+} = 0$), we have:

$$I/2 = K V_{eff}^2 \Rightarrow \underline{V_{eff} = \frac{1.1}{\sqrt{2}} = 0.78V}$$

Transistor Q_1 will shut off when $V_{S_{G1}} = |V_{TP}| = 0.9V$. At this point, $V_{S1} = 2V$ and I_B flows through Q_2 .

$$\therefore \underline{V_{out+}|_{max} = 2 - 0.9 = 1.1V}$$

When V_{out+} goes below zero, V_{S1} starts to fall off from its bias value (i.e. $1.68V$) until it reaches $0.9V$. At this point, Q_2 shuts off and I_B will pass through Q_1 .

$$\therefore \underline{V_{out+}|_{min} = 0.9 - 2 = -1.1V}$$

Note that a V_{eff} (bias) that is higher than the optimum value (i.e. $0.78V$) will cause I_B -transistor to enter the triode region at a lower V_{out+} voltage. Also, a V_{eff} (bias) that is lower than the optimum will shut off Q_1 at a lower V_{out+} voltage. In both cases, the voltage range of V_{out+} for linear operation is reduced.

$$6.22) |V_{tp}| = |V_{tp0}| + \gamma (\sqrt{|V_{SB}| + |2\phi_F|} - \sqrt{|2\phi_F|})$$

$$\text{For } V_S = 2 \text{ V \& } V_B = 2.5 \text{ V, } |2\phi_F| \approx 0.7 \text{ V}$$

$$\Rightarrow |V_{tp}| = 1.1 \text{ V} \Rightarrow I = K(2 - 1.1)^2$$

For the bias condition ($V_{out+} = 0$), we have


$$I/2 = K (V_{eff})^2 \Rightarrow V_{eff} = \frac{0.9}{\sqrt{2}} = \underline{0.63 \text{ V}}$$

$$V_{out+}|_{\max} = 2 - 1.1 = \underline{0.9 \text{ V}}$$

$$V_{out+}|_{\min} = |V_{tp}| - V_{SG1} = |V_{tp}| - (|V_{tp}| + 0.9) = \underline{-0.9 \text{ V}}$$

$$6.23) V_{in} = V_o \frac{R_1 \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}}}{R_2 + R_1 \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{m2}}}$$
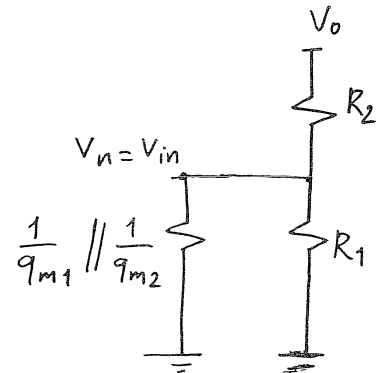
$$\Rightarrow \frac{V_o}{V_{in}} = \frac{R_1 + R_2}{R_1} + \underline{R_2 (g_{m1} + g_{m2})}$$



The first term can be recognized as the

voltage gain when $g_{m1} = g_{m2} = 0$

6.24) Using Eq. (6.62), (6.64), (6.65), and (6.66):

$$\tau = \frac{1}{\omega_{3dB}} = \frac{1}{\beta \omega_t} \quad \text{where} \quad \beta = \frac{C_1/M}{C_1/M + C_1 + C_p} \quad \& \quad \omega_t = \frac{K g_m}{C_0 + \frac{C_1/M(C_1 + C_p)}{C_1/M + C_1 + C_p}}$$

$$\Rightarrow \tau = \frac{1}{K g_m} \left[(M+1)C_0 + C_p + \frac{M C_0 C_p}{C_1} + C_1 \right]$$

$$\frac{\partial \tau}{\partial C_1} = 0 \Rightarrow -\frac{C_0 C_p}{C_1^2} + \frac{1}{M} = 0 \Rightarrow \underline{C_{1,opt} = \sqrt{M C_0 C_p}}$$

6.25) $\tau = \frac{1}{K g_m} \left[2C_0 + C_p + \frac{C_0 C_p}{C_1} + C_1 \right] = \frac{1}{K g_m} \left[2.05 + \frac{0.05}{C_1} + C_1 \right] \text{ ps}$

where C_1 must be expressed in pF unit.

$$C_{1,opt} = \sqrt{C_0 C_p} = \underline{0.22 \text{ pF}}$$

$$\Rightarrow K g_m \tau \Big|_{\min} = \underline{2.5 \text{ ps}}$$

The following table shows $K g_m \tau$ for some other values of C_1

C_1 (pF)	0.1	0.3	0.5	0.7	0.9	1
$K g_m \tau$ [ps]	2.65	2.52	2.65	2.82	3	3.1

