

# A Quadrature Bandpass $\Delta\Sigma$ ADC for a Multi-Standard TV Tuner


R. Schreier

High-Speed Converters Group  
Analog Devices, Wilmington, MA

University of Toronto  
Cider Seminar  
Oct. 19 2006

1

# TV Tuner System

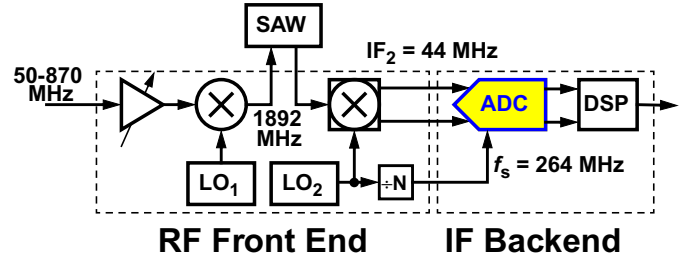


- Dual-conversion super-heterodyne receiver with an ADC at second IF
- ADC input is current-mode I&Q at 44 MHz  
BW = 8.5 MHz

2

# A Quadrature $\Delta\Sigma$ ADC Is:

[Jantzi 1997]

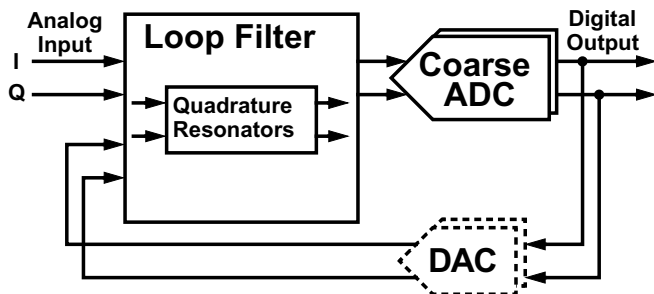

- A  $\Delta\Sigma$  ADC with quadrature everything  
NTF and STF are complex

3


# Worry List

- 1 DAC linearity and noise at high  $f_s$   
⇒ Current-mode DAC, mismatch-shaping
- 2 Resonator Accuracy:  $f_0$  and Q  
⇒ Coming soon!
- 3 Path Matching  
⇒ Large devices, symmetric/merged layout

4


# Ideal NTF– Poles and Zeros

4<sup>th</sup>-order NTF:

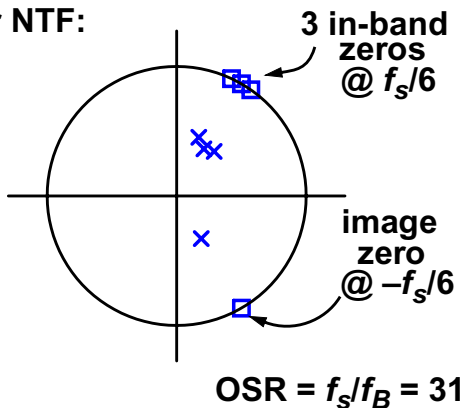


5

# NTF Magnitude

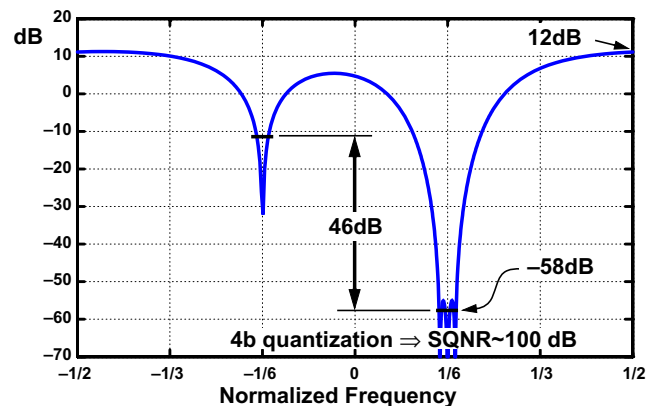


6

## ADC Architecture

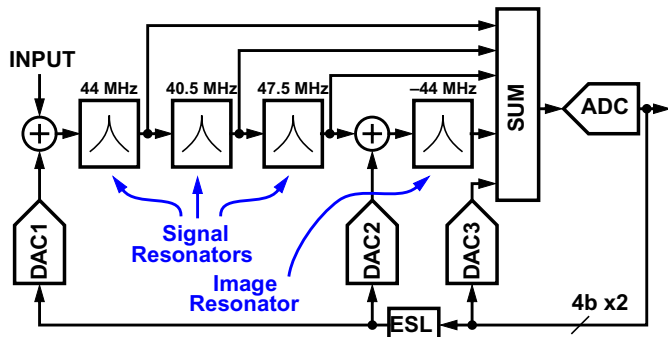

7


## Loop Filter Schematic

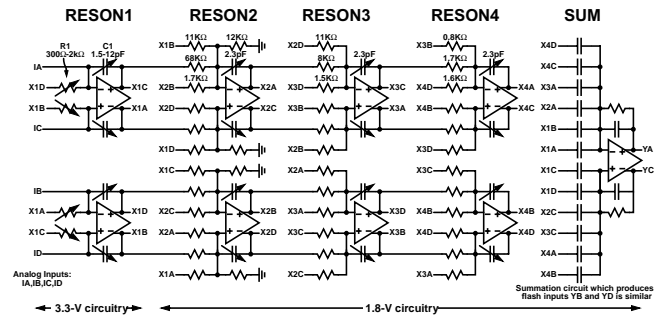

8

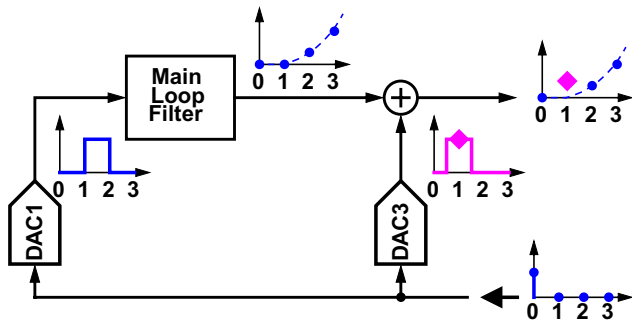
## Why DAC3?

- DAC3 allows any LF/NTF to be realized Even though DAC1 has 1 clock cycle of delay DAC3 supplies the missing point



9


## Why DAC2?

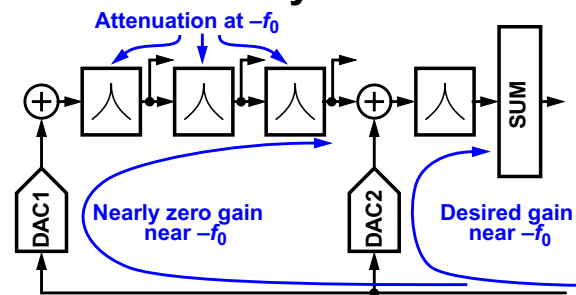

- DAC2 provides a low-attenuation feedback path for signals in the vicinity of  $-f_0$  Thereby resolving a near singularity in the coefficient calculation procedure

10

## Resonator Structure

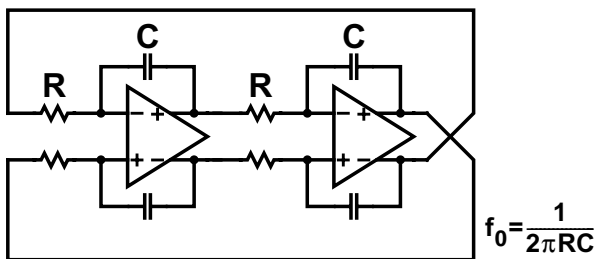


- Tuned by adding positive feedback to make an oscillator and adjusting C until the desired resonance is achieved
- Amplifier drives both R and C  $\Rightarrow$  trouble?

11

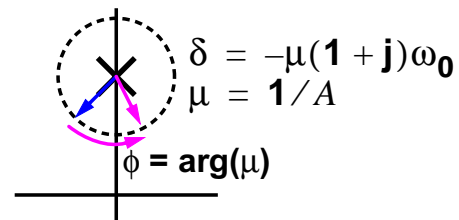
## Amplifier Gain and Phase

- Finite gain degrades Q
- Phase lag enhances Q
- Analysis shows  $\phi = 45^\circ$  yields high Q, regardless of amplifier gain




12
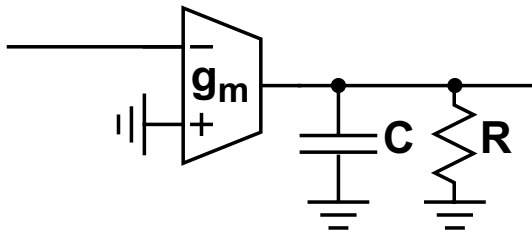
## An Amplifier with $\phi = 45^\circ @ f_0$ :



13

## Resulting High-Q Resonator

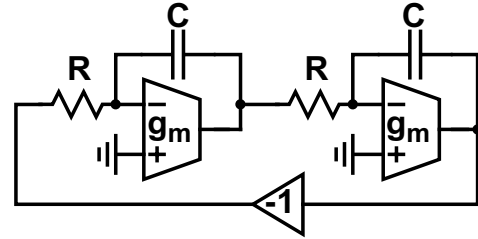


- Amplifier load yields  $\phi = 45^\circ @ f_0$
- Finite  $g_m$  shifts the pole frequency, but does not degrade Q!

14
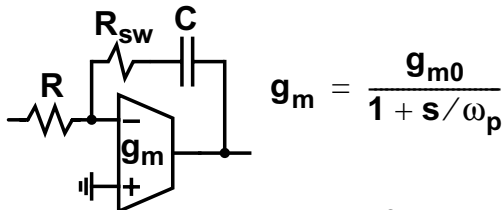
## Finite $g_m$ Bandwidth & Non-Zero Switch Resistance

- Switch resistance degrades Q
- Finite  $g_m$  bandwidth enhances Q




$$g_m = \frac{g_{m0}}{1 + s/\omega_p}$$

- Cancellation occurs if  $R_{sw} = \frac{2\omega_0}{g_{m0}\omega_p}$

15

## 1<sup>st</sup> Resonator's Amplifier

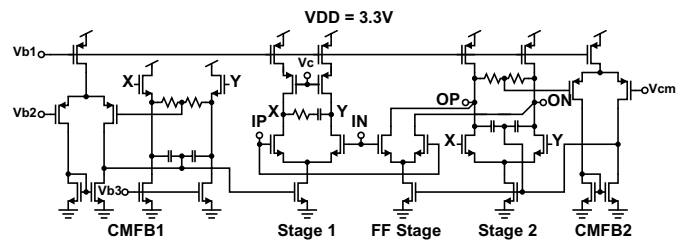

- 2-stage amplifier with feedforward stage and all-NMOS signal path


16

## Gain-Scaling

- 12-dB gain range implemented by scaling DAC1's LSB over a 4:1 range
- At the minimum LSB setting, DAC1's noise is 6 dB lower than at the maximum LSB setting
- Changes in DAC gain are counteracted by inverse change in Reson1 gain  
Keeps gain of DAC1-Reson1 independent of LSB setting
- The gain-scaling burden is on the front end  
No other circuits need to be adjusted

17


## Gain-Scaling Arrangement

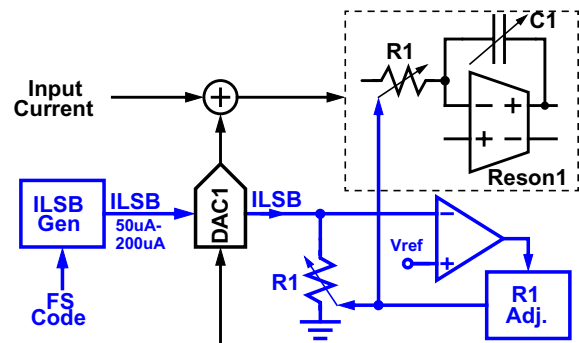

- Gain of DAC1+Reson1 kept constant


18

## ADC Front-End

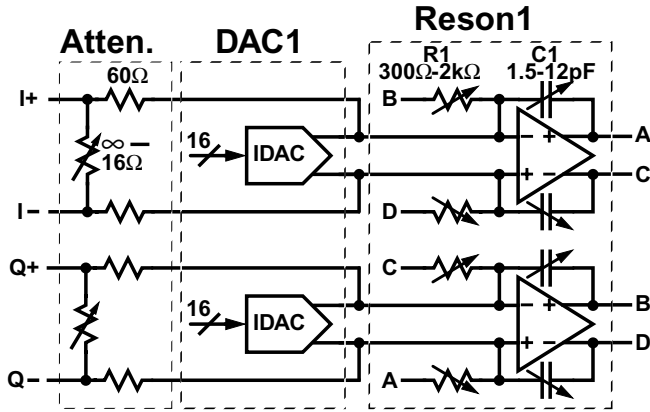


19

## Results: STF & NTF

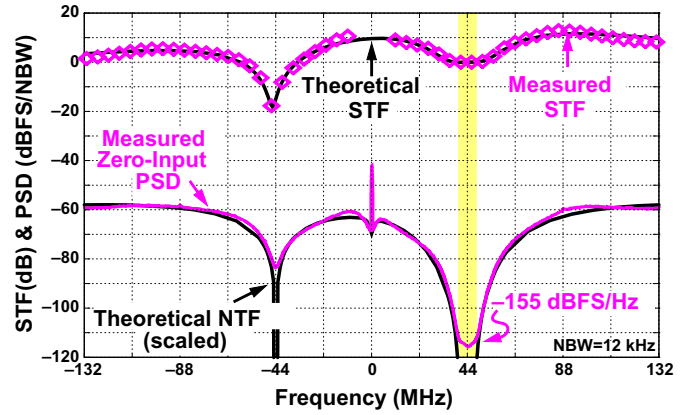


20

## Wideband STF

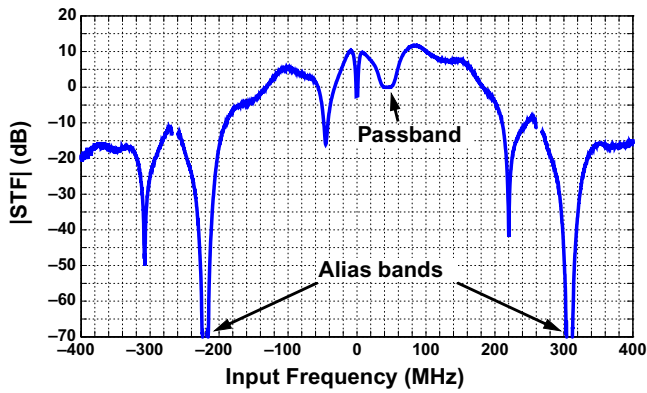


21

## STF in +1 Alias Band

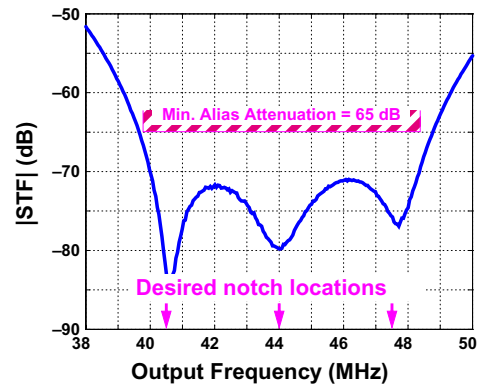


22

## Noise vs. Full-Scale Setting

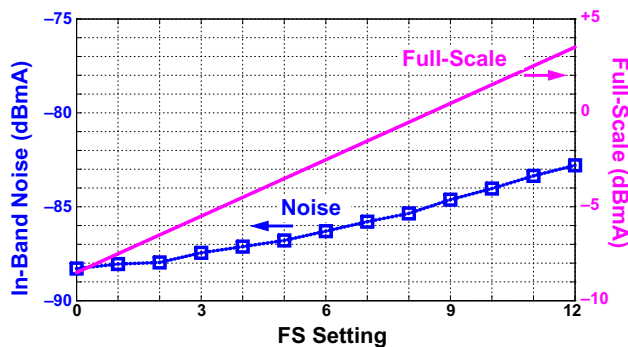


23

## SNR vs. Input Level

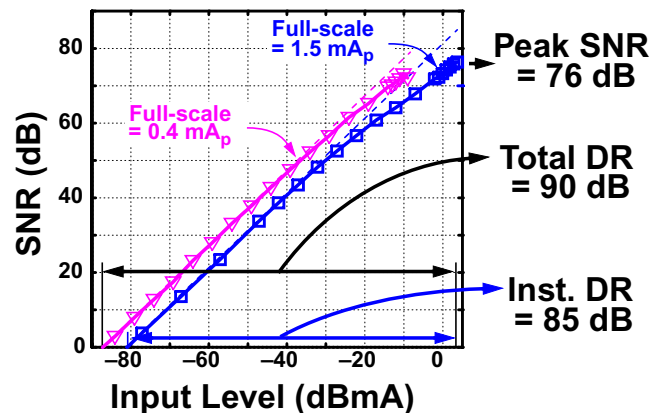

24

## Two-Tone Spectrum

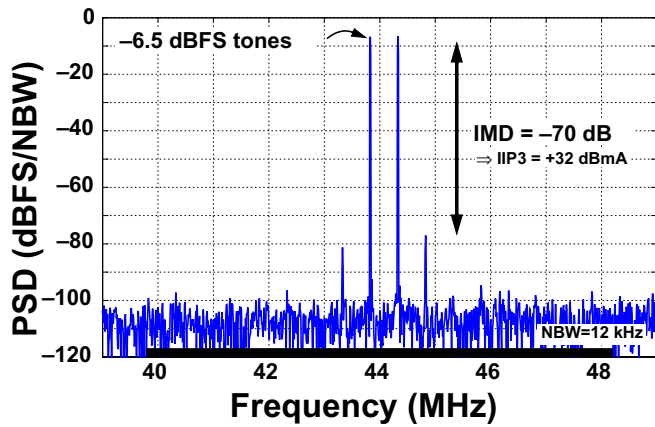


25

## Performance Summary

Bandwidth	8.5	MHz
Center Frequency	44	MHz
Clock Frequency	264	MHz
Inst. Dynamic Range	85	dB
Full-Scale Range	12	dB
Total Dynamic Range	90	dB
Area in 0.18um CMOS	2.5	mm <sup>2</sup>
Power Consumption	375	mW

26

## Performance Comparison

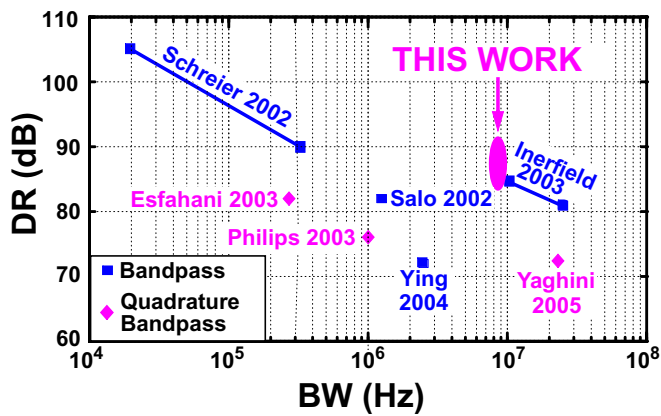


27

## Conclusions

- 💡 A feedforward implementation of a Quadrature Bandpass  $\Delta\Sigma$  ADC needs an extra DAC  
An input attenuator is a good idea too.
- 💡 High Q resonance can be achieved by
  1. Using a simple  $g_m$  instead of a true op amp
  2. Balancing finite  $g_m$  bandwidth and non-zero switch resistance
 Measured Q > 40
- 💡 Gain-scaling extends DR

28

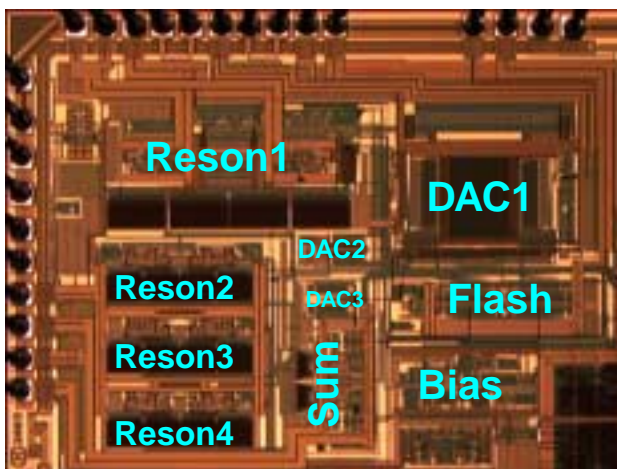

29