

University of Toronto  
 Department of Electrical and Computer Engineering  
 Faculty of Applied Science and Engineering  
 Final Examination - December 10, 1997  
 Second Year - Programs 7 and 9  
**ECE241** - Digital Systems  
 Examiners: S.D. Brown and J.S. Rose

EXAM Type: D

Last Name: \_\_\_\_\_  
 First Name: \_\_\_\_\_  
 Student Number: \_\_\_\_\_

Duration: **2.5 Hours**

**You should answer ALL questions except question**

**5b, which is a bonus question.**

**All answers should be on these sheets.**

**No aids permitted.**

**See Instructions on page 2.**

**EXAMINER'S REPORT**

1	_____	/16
2	_____	/22
3	_____	/22
4	_____	/18
5	_____	/22

TOTAL: \_\_\_\_\_ /100

**Instructions**

- READ ALL QUESTIONS CAREFULLY BEFORE ANSWERING.
- Attempt all questions.
- If you need to make any assumptions, state them clearly with your answers.
- Write your answers neatly. Messy work is very hard to read and may cause you to lose marks.
- For questions that specify minterms using the notation in the example below


$$f(x_1, x_2, x_3) = \sum m(1, 3, 5)$$

the minterms are to be interpreted as used in class. Specifically, minterm  $m_1$  represents  $x_1x_2x_3 = 001$ , minterm  $m_3$  represents  $x_1x_2x_3 = 011$ , and so on. Answers that fail to interpret the minterms in this way will be considered incorrect.


**Question 1** — Short Answers [16 marks]

a. Use algebraic manipulation to derive the minimum-cost expressions in sum-of-products form for the following expressions. Be sure to show all of your steps.

i.  $f = x \oplus y \oplus xy$

 


ii.  $g = BC\bar{D} + \bar{B} + \bar{C}$

 


- b. Use **one** 4-to-1 multiplexer and NOT gates to implement the following function:

$$f(x_1, x_2, x_3) = \sum m(3, 5, 6)$$

 

- c. The function  $f(A, B, C) = \sum m(3, 4, 6)$  can be implemented using **one** 2-input multiplexer, **one** 2-input AND gate, and **one** NOT gate. Design the circuit using exactly these gates.

 

**Question 2** — Short answers II [22 marks]

- a. In class you learned about carry-lookahead adders. For an 8-bit carry-lookahead adder with inputs called  $x_7, \dots, x_0$  and  $y_7, \dots, y_0$ , you are to derive the equation for the carry-lookahead carry-out from the second stage of the adder,  $c_2$ . Assume that the carry-in to the adder is called  $c_0$ . Draw a block diagram of the first two stages of the adder and label all of the signals, including generate and propagate. Derive the expression for  $c_2$  in terms of  $x_i, y_i, x_0, y_0$  and  $c_0$ . Show the steps in your derivation.

Draw the block diagram with signal labels in this space

Derive the expression for  $c_2$  in this space

b. Represent the following numbers in 2's complement notation. Use the least number of bits possible for each number:

i. 37

ii. -52

iii. -128

c. Show how the following function can be implemented using 3-input lookup tables (LUTs).

$$f(x_1, x_2, x_3, x_4) = \sum m(1, 2, 4, 7, 8, 11, 13, 14)$$

Use the least number of lookup tables that you can. Draw the circuit containing the LUTs, and indicate the function of each LUT by showing the logic expression that it implements. For example, if a LUT implements the function  $g = A\bar{B}C + ABC$ , then you would draw this LUT in your circuit as shown below:



Show your answer in this space. Use the space on the next page for rough work.

Space for rough work for Question 2c. A truth table is provided for your convenience only.

$x_1, x_2, x_3, x_4$	f
0000	
0001	
0010	
0011	
0100	
0101	
0110	
0111	
1000	
1001	
1010	
1011	
1100	
1101	
1110	
1111	

d. You are to design a circuit with three inputs and two outputs. The inputs are called  $x_2, x_1, x_0$  and represent a 3-bit positive integer. The output is called  $y_1, y_0$ , and represents the number of bits in  $x_2, x_1, x_0$  that are equal to 1. What basic circuit that you have seen in class can implement this function?

Answer:

**Question 3** — Word problem [22 marks]

a. You are to design a circuit that has four inputs called  $a_1, a_0, b_1, b_0$ , and produces four outputs called  $P = p_3, p_2, p_1, p_0$ . Each pair of input represents a 2-bit positive integer (i.e.  $A = a_1a_0$  and  $B = b_1b_0$ ) and the outputs represent the 4-bit arithmetic product (i.e.,  $P = A \times B$ ) of those integers.

i. Fill in the truth table below that shows the four outputs.

$a_1 a_0 b_1 b_0$	$p_3$	$p_2$	$p_1$	$p_0$
0000				
0001				
0010				
0011				
0100				
0101				
0110				
0111				
1000				
1001				
1010				
1011				
1100				
1101				
1110				
1111				

ii. Derive a minimal sum-of-products expression for each of  $p_3, p_2, p_1$  and  $p_0$ , using the K-maps given below.

K-map for  $p_3$ :

 

Minimum-cost expression for  $p_3$ :

K-map for  $p_2$ :


Minimum-cost expression for  $p_2$ :


- b. For this part you are to design another combinational circuit. The inputs to the circuit are  $p_3, p_2, p_1$  and  $p_0$  directly from the outputs of the circuit of part a. The circuit has one output, called  $f$ . The function  $f$  should be logic 1 only if  $p_3p_2p_1p_0$  have the value 0001, 0100, or 1001. Design a circuit for  $f$  using the minimum number of NOR gates. You can use only NOR gates, but they can be of any size. Use the K-map given below. Use the space on the following page for any rough work.

K-map for  $p_1$ :




Minimum-cost expression for  $p_1$ :

K-map for  $p_0$ :

 

Minimum-cost expression for  $p_0$ :

K-map for  $f$

 


Show the circuit for  $f$  in the space below:



Space for rough work for Question 3b.

**Question 4** — Sequential Circuits [18 marks]

 - a. A logic circuit has two inputs, *clock* and *start*, and two outputs, *f* and *g*. The behavior of the circuit is described by the timing diagram below. When a pulse is received on the start input, the circuit produces pulses on the *f* and *g* outputs as shown in the timing diagram. Design a suitable circuit using only the following components: 3-bit resettable positive-edge triggered synchronous counter, and basic logic gates. Assume that the delays through all logic gates and the counter are negligible.



Show your answer in this space. Use the space on the next page for rough work.

Space for rough work for Question 4a.

b. Consider the VHDL architecture body shown below.


```
ARCHITECTURE Structure OF example IS
SIGNAL x: STD_LOGIC;
BEGIN
  tff_0: tff PORT MAP (
    t=>e, clk=>clock, clrn=>Resetn, prm=>Presetn, q=>q0);
  tff_1: tff PORT MAP (
    t=>q0, clk=>clock, clrn=>Resetn, prm=>Presetn, q=>q1);
  tff_2: tff PORT MAP (
    t=>x, clk=>clock, clrn=>Resetn, prm=>Presetn, q=>q2);
  x <= NOT(NOT q0 OR NOT q1);
END Structure;
```

Note that the corresponding ENTITY declaration is not shown, but it would define signals *e*, *clock*, *Resetn*, and *Presetn* as inputs, and signals *q0*, *q1*, and *q2* as outputs. The tff module is a positive-edge-triggered T flip-flop. The meaning of the statement

```
tff_0: tff PORT MAP (
  t=>e, clk=>clock, clrn=>Resetn, prm=>Presetn, q=>q0);
```

is to create a T flip-flop with the following connections to signals: the *t* input is connected to the *e* signal, *clk* is connected to the *clock* signal, *clrn* to *Resetn*, *prm* to *Presetn*, and *q* to *q0*.

 i. In the space below, draw the circuit represented by the VHDL code.




**ii.** What is the purpose of this circuit (i.e., what does the circuit do)?

Answer:



**iii.** Assume the following timing parameters: propagation delay through a logic gate is 2 ns, time from clock edge to change of flip-flop output is 1 ns, and flip-flop setup time is 2 ns. What is the maximum clock frequency for which the circuit will work properly?


Answer:

 

**Question 5** — Finite State Machine [20 marks]

**a.** Consider a Moore-type finite-state machine with one input,  $x$ , and one output,  $z$ . The machine should produce the output  $z = 1$  if the values of  $x$  on successive clock cycles have the following pattern: 10101. Otherwise,  $z$  should be 0.

Draw a state diagram for the machine. Use the least possible number of states.




b. The state table given below represents a Moore-type finite-state machine.

Present State	Next State		Output $z$
	$x = 0$	$x = 1$	
A	A	B	0
B	C	B	0
C	A	D	0
D	C	E	0
E	C	B	1


i. Using a sequential state assignment, fill in the state-assigned table below. By sequential state assignment, we mean that state A is encoded as 000, state B as 001, state C as 010, and so on. Note that the state flip-flop outputs are called  $y_1, y_2$  and  $y_3$ .

Present State		Next State				Output $z$
		$x = 0$		$x = 1$		
Label	Code $y_1 y_2 y_3$	Label	Code $Y_1 Y_2 Y_3$	Label	Code $Y_1 Y_2 Y_3$	

 ii. Use the K-maps given below to derive minimal expressions (sum-of-products) for the state flip-flops and output to implement the machine. Make use of don't-cares if they exist.




Minimum-cost expression for  $Y_1$ :

 

Minimum-cost expression for  $Y_2$ :


Answer to Question 5b, part ii continued

K-map for  $Y_3$ :

 


Minimum-cost expression for  $Y_3$ :

K-map for  $z$ :

 

Minimum-cost expression for  $z$ :

 iii. Draw the complete circuit for the finite-state machine.



- c. **BONUS QUESTION. You do not have to do this question, but extra marks will be given for it if you do.** The state table below defines a finite-state machine that has one input,  $x$ , and one output,  $z$ . Using the formal procedure described in class, determine if the number of states in the machine can be reduced. Show your steps to derive the minimum possible number of states.

Present State	Next State		Output	
	$x = 0$	$x = 1$	$z$	$z$
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	E	1	0
E	A	F	0	0
F	D	F	0	0

Answer (use the back of this page for rough work if extra space is needed):

**EXTRA SPACE — USE ONLY IF NEEDED**

**EXTRA SPACE — USE ONLY IF NEEDED**