

University of Toronto
Department of Electrical and Computer Engineering

ECE241 - Digital Systems

Midterm Examination
October 1998

Last Name: _____
First Name: _____
Student Number: _____
Signature: _____

Duration: **1 Hour**

Answer ALL questions on this test paper. There is extra space at the end if you need it.


EXAMINER'S REPORT

1	_____	/15
2	_____	/10
3	_____	/12
4	_____	/13

TOTAL: _____ /50

Question 1 — [15 marks]

 - a. The circuit shown below has the output f and the inputs x , and y . You are to derive the logic expressions for the intermediate nodes a , b , c and the output f , and then on the next page, minimize the expression for f .




Use **algebraic manipulation** to find the minimal sum-of-products expression for the function f derived above. You must show all of the steps.

b. **Circle all the legal VHDL statements below which correctly represent the function**
 $f = \bar{x}y + x\bar{y}$. A legal statement has the correct syntax and semantics.


- $f <= (x \text{ AND } \text{NOT } y) \text{ OR } (\text{NOT } x \text{ AND } y)$;
- $f <= (\text{NOT } x \text{ AND } \text{NOT } y) \text{ OR } x$;
- $f <= \text{NOT } x \text{ AND } y \text{ OR } x \text{ AND } \text{NOT } y$;
- $f <= (\text{NOT } x \text{ OR } y) \text{ AND } \text{NOT } y$;
- $f <= (\text{NOT } x \text{ AND } y) \text{ OR } (x \text{ AND } \text{NOT } y)$;

c. Draw the **output waveform** for the function $f = \bar{a}b + a\bar{b}$ on the timing diagram below.

 


Question 2 — [10 marks]

 a. The CMOS circuit below contains an error in the pull-up network (the “P-part”). Draw the corrected PUN (P-part) in the space given below (you do not have to draw the PDN (N-part)).




ANSWER:

 

- b. Draw a CMOS complex gate that implements the function below. Use as few transistors as you can in your solution (Hint: consider f).

$$f = xy + xz$$

ANSWER:

 

Question 3 — [12 marks]

- a. Consider a truth table in which there are a total of k entries that are marked as d , for don't care. The other entries are set as either 1 or 0. How many different logic functions are represented by this truth table?

ANSWER: _____

- b. Consider the logic function

$$f = \sum m(0, 2, 3, 4, 6, 7, 8, 10, 11, 12)$$

What are the prime implicants of this function (there is extra space for rough work at the end of this test paper)?

ANSWER: _____

What are the essential prime implicants:


ANSWER: _____

Give a minimal cover in sum-of-products form:

ANSWER: _____

- c. The circuit below shows a 3-input logic function, f . Can any of the AND gates in this circuit be removed from the circuit without changing the logic function? If so, which gate(s) is it (1, 2, or 3)?

ANSWER: _____

 

EXTRA SPACE — USE ONLY IF NEEDED

Question 4 — [13 marks]

The K-maps for two 4-variable logic functions, f and g , are shown below. Indicate on the K-maps how the two functions should be implemented such that the resulting 2-output circuit has minimal cost. Use a sum-of-products realization for both functions. Show your expressions for f and g in the spaces provided below and give the cost of the 2-output circuit. In your cost calculation, you should count the NOT gates needed to invert the inputs.

K-map for f :

$x_1^1 x_2^2$	$x_3^3 x_4^4$	0	0	0	0
		1	1	1	0
		1	1	d	0
		0	1	0	0

K-map for g :

$x_1^1 x_2^2$	$x_3^3 x_4^4$	0	d	0	0
		1	0	1	1
		1	0	1	1
		0	1	d	0

Expression for f : _____

Expression for g : _____

Total cost: _____

EXTRA SPACE — USE ONLY IF NEEDED

EXTRA SPACE — USE ONLY IF NEEDED