 


MULTI STAGE CONVERTERS

①


RECALL




QUANTIZATION ERROR

$$V_{IN} = V_{REF} D_{OUT} - EQ$$
 
$$-\frac{1}{2} V_{LSB} \leq EQ \leq \frac{1}{2} V_{LSB} = \frac{1}{2} \frac{V_{REF}}{2^N}$$



$$V_{OUT} = V_{REF} D_{IN}$$

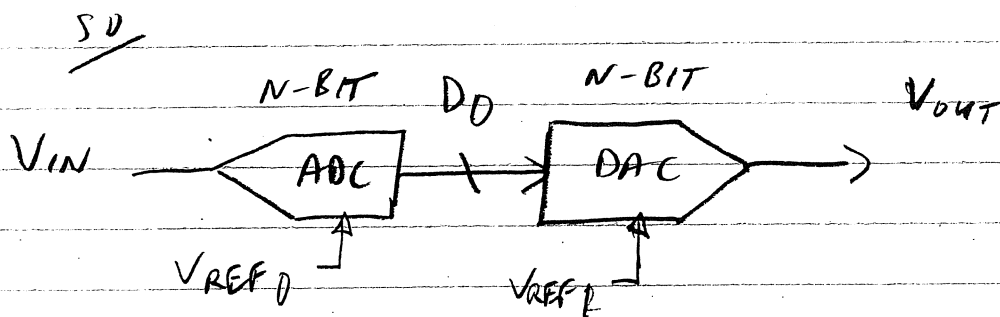

2

$$V_{IN} = V_{REF0} D_0 - E_Q$$

$$D_0 = \frac{V_{IN}}{V_{REF0}} + \frac{E_Q}{V_{REF0}}$$


$$V_{OUT} = V_{REF1} D_0$$

$$V_{OUT} = V_{IN} \left(\frac{V_{REF1}}{V_{REF0}} \right) + E_Q \left(\frac{V_{REF1}}{V_{REF0}} \right)$$

IF $V_{REF1} = V_{REF0} \equiv V_{REF}$

FROM NOW ON
ALL ADCS &
DACs USE
"VREF"


$$V_{OUT} = V_{IN} + E_Q$$

 

$$D_0 = \frac{V_{IN} + E_Q}{V_{REF}}$$

MULTI-STAGE CONVERTER (2 STAGE)

3

 

$$D_0 = \frac{V_{IN} + EQ_0}{V_{REF}}$$

$$D_1 = \frac{-G_1 EQ_0 + EQ_1}{V_{REF}}$$

$$D_{OUT} = D_0 + \frac{1}{G_1} D_1$$

$$= \left(\frac{1}{V_{REF}} \right) V_{IN} + \frac{1}{G_1} \frac{EQ_1}{V_{REF}} \quad (1)$$

FINAL QUANTIZATION ERROR IS $\frac{EQ_1}{G_1 V_{REF}}$

SO " G_1 " TIMES SMALLER THAN $\frac{EQ_1}{V_{REF}}$

$N_{TOTAL} = N_1 + \log_2(G_1)$ OVERALL CONVERTER BITS.

(3A)

TO ALLOW FOR MORE TOLERANCE
ON ADC CONVERTERS USE
OVERLAP CORRECTION

IF NO ADC IDEAL THEN

$G_1 = 2^{N_0}$ SO THAT FULL SCALE

VALUE AT V_1 IS $\pm \frac{V_{REF}}{2}$

HOWEVER, ANY ERRORS IN ADC 0

WILL CAUSE $|E_Q| > \frac{1}{2} V_{LSB}$ AND

WILL OVERLOAD ADC, SINCE $V_1 > \pm \frac{V_{REF}}{2}$

REDUCE G_1

LET $G_1 = 2^{N_0-1}$

EX IF $N_0 = 3$ LET $G_1 = 2^2 = 4$



AS A RESULT OVERALL ADC WILL HAVE
LARGER QUANTIZATION ERROR (SEE ①)

AND OVERALL BIT ACCURACY OF
 N_{TOTAL}

IN GENERAL

LET

SHOWN AS

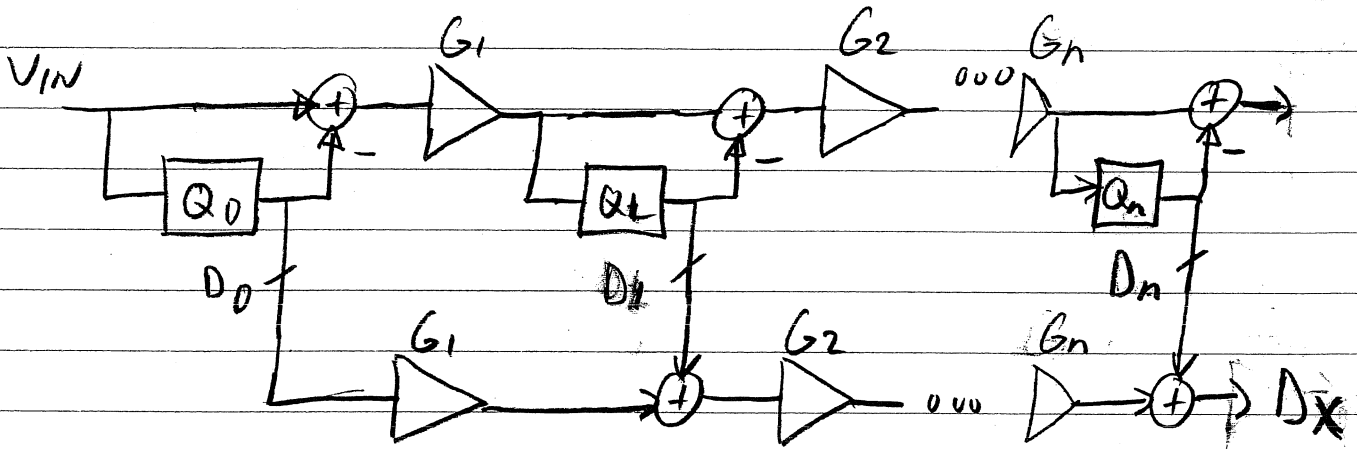 

$$D_{OUT} = \left(\prod_{i=1}^n G_i \right)^{-1} D_X$$

$$= \left(\frac{1}{V_{REF}} \right) V_{IN} + \left(\prod_{i=1}^n G_i \right)^{-1} \frac{EQ_n}{V_{REF}}$$


EXAMPLE

COMMON APPROACH IS 1.5 BITS/STAGE

AND $G_i = 2$ FOR EACH STAGE

ASSUME FULL SCALE INPUT IS $\pm \frac{V_R}{2}$

ONE STAGE
(EVEN STAGE)

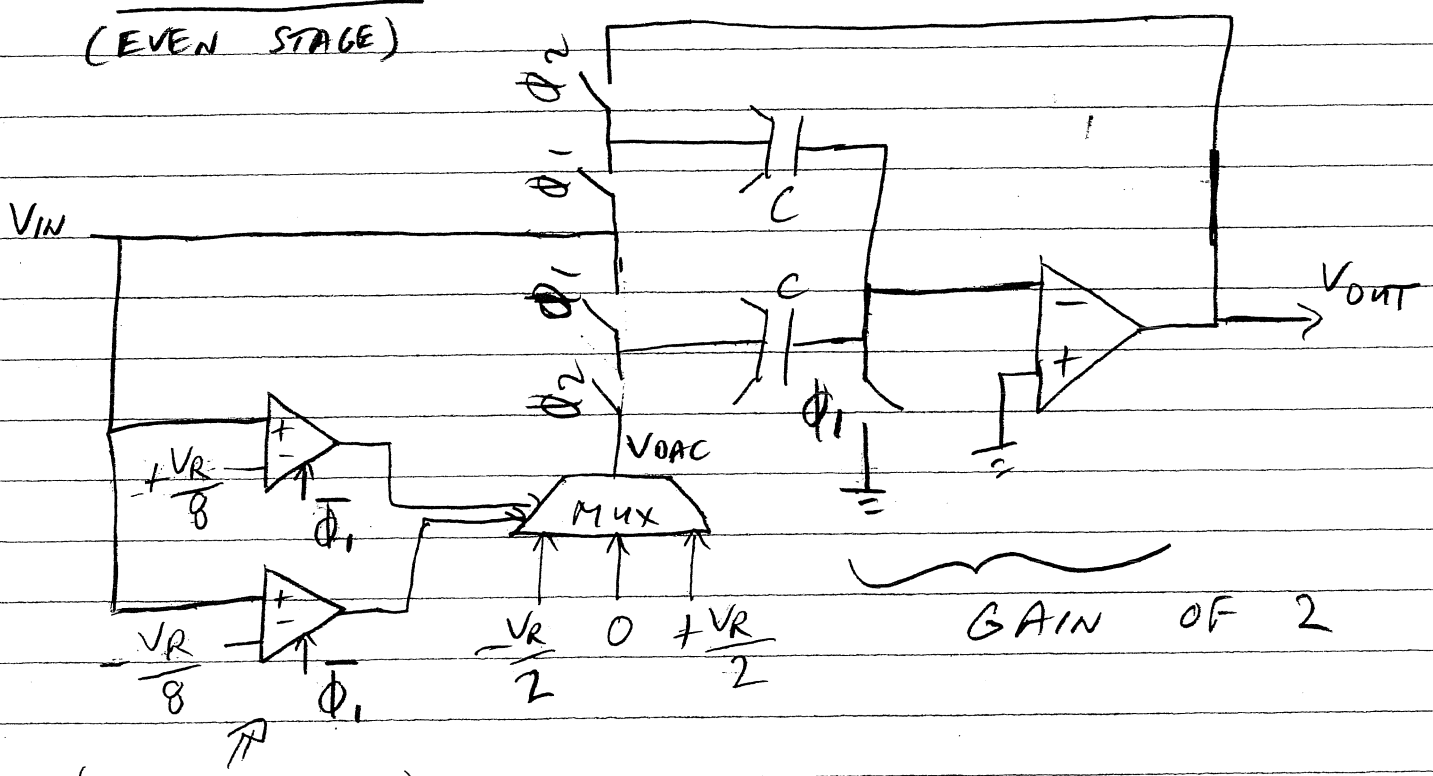

GAIN OF 2

(TRIGGER ON RISING EDGE)


ODD STAGES ARE SAME BUT SAMPLED ON OPPOSITE PHASES

6


SO DELAY IN 10 BIT PIPELINED ADC WITH 1.5 BITS/STAGES IS ONLY 5 CLOCK CYCLES.

ALSO OPAMP CAN BE POWERED DOWN DURING ϕ_1 TO SAVE POWER

ϕ_1

 


ϕ_2

 

$$V_{DAC} = \begin{cases} +\frac{V_R}{2} \\ 0 \\ -\frac{V_R}{2} \end{cases}$$

$$= 2V_{IN} - V_{DAC}$$

V_{IN} vs V_{OUT}

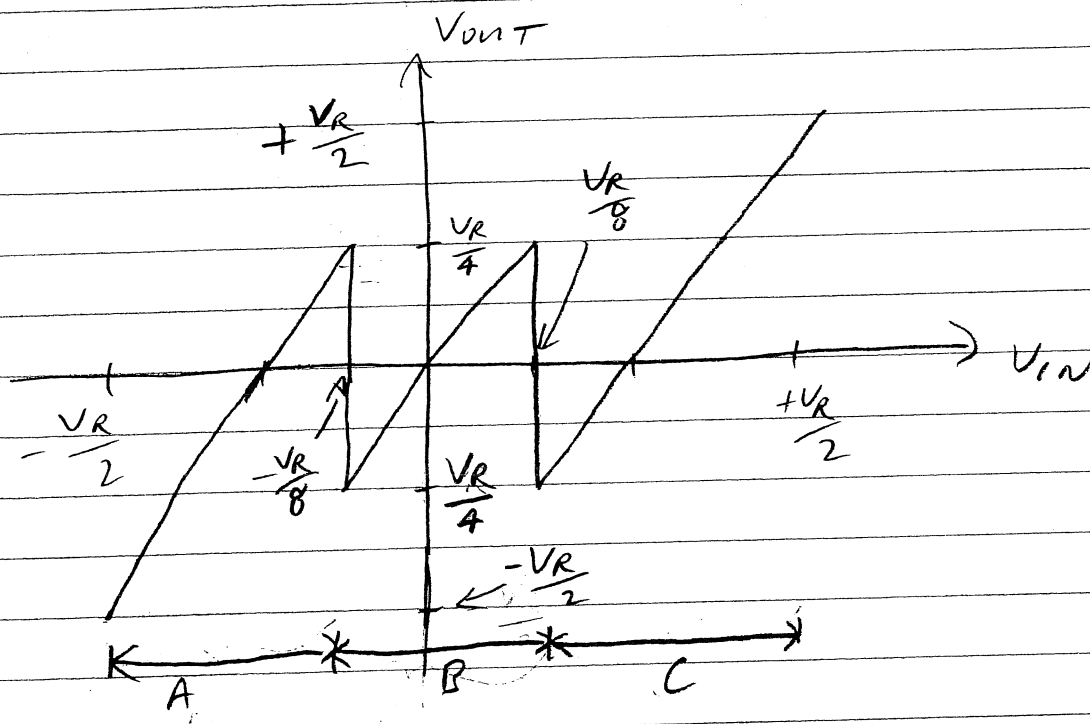

A \Rightarrow $V_{OUT} = 2V_{IN} + \frac{V_R}{2}$

B \Rightarrow $V_{OUT} = 2V_{IN}$

C \Rightarrow $V_{OUT} = 2V_{IN} - \frac{V_R}{2}$