Single Transistor Gain Circuit

David Johns

University of Toronto

david.johns@utoronto.ca

# Single Transistor Gain Circuit

- In general, a gain circuit consists of
  - Drive stage
  - Load stage
- Drive stage
  - Single transistor
- Load stage is one of
  - Resistor
  - Current source (made with a transistor)
- "Single transistor" gain circuit refers to the drive stage consisting of a single transistor



- $V_{tn} = 0.3$ V;  $\mu_n C_{ox} = 240 \mu A/V^2$
- (W/L) = 100
- Let  $\lambda_n = 0$ 
  - results in  $r_o \rightarrow \infty$
- Want to plot v<sub>O</sub> vs v<sub>I</sub>
  - as  $v_l$  goes from 0 to  $V_{DD}$

### Gain Circuit with Resistor Load



# Gain Circuit with Resistor Load

- $M_1$  is cutoff in region (1)
  - $-v_l$  is less than  $V_{tn}$
- $M_1$  is active in region (2)
  - As soon as  $v_l > V_{tn}$ ,  $M_1$  on and active
  - remains active until  $v_O < v_I V_{tn}$

when drain voltage is less than gate voltage by a threshold voltage

 $v_O = V_{DD} - i_D * R_D$ 

 $i_D = 0.5 \mu_n C_{ox} (W/L) (v_l - V_{tn})^2$ 

- In this case, end of active is  $v_l = 0.67V$ ,  $v_O = 0.37V$ 

•  $M_1$  is triode in region (3)  $v_O = V_{DD} - i_D * R_D$  $i_D = \mu_n C_{ox} (W/L) (v_I - V_{tn} - 0.5 v_O) v_O$ 

- Largest small signal gain
  - where the slope of  $v_O/v_I$  is largest in magnitude
  - Then a small change in  $v_l$  can cause a large change in  $v_O$
- For above example, occurs at  $v_l = 0.67$ V
  - But this bias point would give very little headroom as  $M_1$  would go into triode as  $v_0$  decreases and gain would drop
  - A better bias point might be around  $v_0 = 1$ V

# Small Signal Gain Analysis

- Good method to find small signal voltage gain
  - Model circuit as Norton equivalent
  - Find output impedance, *R*<sub>o</sub>, at output node
  - Find short circuit current,  $i_{sc}$  at output node as function of  $v_i$

 $- v_o = i_{sc}R_o$ 



# Small Signal - Gain Circuit/Resistor Load

Active region



•  $R_o = R_D$ ;  $i_{sc} = -g_m v_i$ 

• 
$$v_o = -g_m R_D v_i$$

- $v_o/v_i = -g_m R_D$
- To increase gain... increase  $g_m$  or  $R_D$
- Recall

$$g_m = \mu_n C_{ox}(W/L) V_{ov}$$
  

$$g_m = 2I_D/V_{ov}$$
  

$$g_m = \sqrt{2\mu_n C_{ox}(W/L) I_D}$$

- μ<sub>n</sub>C<sub>ox</sub> set by fabrication and not controlled by designer
- If output bias voltage fixed at say 1V, then I<sub>D</sub> is fixed if R<sub>D</sub> is fixed.

# Small Signal - Gain Circuit/Resistor Load

- Can increase  $g_m$  by decreasing  $V_{ov}$  but...
  - $-g_m$  does not increase for  $V_{ov}$  below about 50mV
  - a practical effect seen with better modelling
- What about increasing R<sub>D</sub>?
  - If  $R_D$  increased,  $I_D$  must decrease to keep  $v_O$  around 1V
- In summary, it is difficult to get a large gain from a gain circuit with a resistor load
- Would like a large load resistance that does not need to have a large of dc bias voltage across it

#### - Replace $R_D$ with a current source

## Practical Ideal Current Source

- Ideal current source would give constant current no matter what voltage, V<sub>x</sub>, across it
- "Practical ideal" current source

 $V_x > 0$  then  $I_x = I_B$  $V_x = 0$  then  $0 < I_x < I_B$  $V_x < 0$  then  $I_x = 0$ 

•  $I_B$  is desired current;  $I_x$  is actual current



# Practical Ideal Current Source

• For  $V_{DD} = 2V$ ;  $R_D = 1k\Omega$  $I_R = 1mA$ ;  $V_R = 1V$ 

 $I_{R} \downarrow \bigvee_{I_{B}} V_{DD}$ 

Practical Ideal

- For  $V_{DD} = 3V$ ;  $R_D = 1k\Omega$  $I_R = 1mA$ ;  $V_R = 1V$
- For  $V_{DD} = 0.5$ V;  $R_D = 1$ k $\Omega$  $I_R = 0.5$ mA;  $V_R = 0.5$ V
- For  $V_{DD} = 2V$ ;  $R_D = 4k\Omega$  $I_R = 0.5mA$ ;  $V_R = 2V$
- For  $V_{DD} = -1$ V;  $R_D = 1$ k $\Omega$  $I_R = 0$ mA;  $V_R = 0$ V

## Current Source/Current Source Circuit

Practical Ideal

• For 
$$I_1 = 1 \text{mA}$$
;  $I_2 = 0.5 \text{mA}$   
 $V_x = V_{DD} = 2 \text{V}$ 



For 
$$I_1 > I_2$$
  
 $V_x = V_{DD} = 2V$ 

• For  $I_1 < I_2$  $V_x = 0$ V

• For  $I_1 = I_2$  $0 < V_x < V_{DD}$ 

 $V_x$  can be anywhere between 0 and  $V_{DD}$ 

# Gain Circuit with Current Source Load: $\lambda = 0$

 $V_{DD} = 2V$   $I_B$  I.64mA  $V_O$   $V_I \circ I$ 

- Ideal current source (always assume practical)
- $V_{tn} = 0.3$ V;  $\mu_n C_{ox} = 240 \mu A/V^2$
- (*W*/*L*) = 100
- Let  $\lambda_n = 0$ 
  - − results in  $r_0 \rightarrow \infty$
- Want to plot vo vs vi
  - as  $v_{\rm I}$  goes from 0 to  $V_{\rm DD}$

## Gain Circuit with Current Source Load: $\lambda = 0$



# Gain Circuit with Current Source Load: $\lambda = 0$

- $M_1$  is cutoff in region (1)
- $M_1$  is active in region (2)
  - $-I_{D1} < I_B = 1.64 \text{mA}$
  - Results in  $v_O = V_{DD}$
  - Current pulled from  $V_{DD}$  is  $I_{D1}$
- $M_1$  is active in region (3)
  - $I_{D1} = I_B = 1.64 \text{mA}$
  - $v_O$  somewhere between  $V_{DD}$  and where  $M_1$  goes into triode

- In region (3)- Gain is  $\infty$  since slope is  $\infty$
- $M_1$  is triode in region (4)
  - Edge of triode at ...
  - drain of  $M_1$  is  $V_{G1} V_{tn}$
  - and  $V_{G1} = V_1$
  - $-I_{D1} = I_B = 1.64$ mA in this region

- $V_1$  found from  $I_{D1} = 0.5 \mu_n C_{ox} (W/L) (V_1 V_{tn})^2 = I_B$
- $V_1 = 0.67 V$

# Gain Circuit with Current Source Load: $\lambda$ finite

- Now let  $\lambda > 0$
- Same as before except that region (3) has a finite slope

## Gain Circuit with Current Source Load: $\lambda$ finite



# Small Signal - Gain Circuit/Ideal Current Source Load

- In region (2), *I<sub>B</sub>* acts as a short circuit
   Small signal gain = 0
- In region (3), we have the following



# Small Signal - Gain Circuit/Ideal Current Source Load

Active region



•  $R_o = r_o; i_{sc} = -g_m v_i$ 

• 
$$v_o = -g_m r_o v_i$$

• 
$$v_o/v_i = -g_m r_o$$

• 
$$g_m = 2I_D/V_{ov}$$

• 
$$r_o = L/(\lambda' I_D)$$

• 
$$v_o/v_i = \frac{-2L}{\lambda' V_{ov}}$$

- Intrinsic gain of single transistor with  $L = 0.2 \mu m$
- Typical values
  - V<sub>ov</sub> = 0.2V;  $\lambda'$  = 0.1 $\mu$ m/V
  - Intrinsic gain:  $v_o/v_i = 20V/V$

 Use a single PMOS transistor to build current source load for NMOS drive transistor



- $V_B$  is a constant dc voltage
  - When  $M_2$  active,  $M_2$  acts like a current source
  - $-M_2$  will be triode when  $v_O$  close to  $V_{DD}$



21/26

- Region 1

  M1 cutoff; M2 triode

  Region 2

  M1 active; M2 triode

  Region 3
  - $M_1$  active;  $M_2$  active
- Region 4
  - $-M_1$  triode;  $M_2$  active
- As a gain circuit, want the circuit to be in region (3)
  - Small signal model for  $M_2$  is just a resistor of value  $r_{o2}$



• Since  $v_{gs} = 0$ ,  $g_m v_{gs} = 0$  so ... Looking into the drain of  $M_2$  is  $r_{o2}$ 

# Small Signal - Gain Circuit/PMOS Load

Active region



- $R_o = r_{o1} || r_{o2}; \ i_{sc} = -g_m v_i$
- $v_o/v_i = -g_{m1}(r_{o1}||r_{o2})$
- If  $r_o \equiv r_{o1} = r_{o2}$  $v_o/v_i = -\frac{g_{m1}r_o}{2}$
- The typical gain is one half of the intrinsic transistor gain

# Small Signal - Gain Circuit/PMOS Load

- $g_m = 2I_D/V_{ov}$ ;  $r_o = L/(\lambda'I_D)$
- $v_o/v_i = -\frac{g_{m1}r_o}{2} = L/(\lambda' V_{ov})$
- How can we increase gain?
- Decrease V<sub>ov</sub>
  - Stops increasing  $g_m$  when  $V_{ov} < 50 \text{mV}$
- Increase L
  - Need to also increase W to maintain same  $V_{ov}$
  - Increases input capacitance so slower circuit
- Is there another way?.. Yes!
  - Cascade amp
  - Cascode amp

- Single transistor gain circuit
- Small-signal gain analysis
- Replace load R<sub>D</sub> with current source
- Gain circuit with PMOS load