

Single Time-Constant Circuits

David Johns


University of Toronto

david.johns@utoronto.ca

Single-Time Constant (STC) Circuits

- Here we will only concern ourselves with RC circuits
- STC circuits are circuits that when the independent sources are set to zero, the circuit can be reduced to a single capacitor and single resistor
- STC circuits have a first-order $H(s)$
- 2 main types of STC circuits
 - Lowpass
 - Highpass
- The important parameter is τ
 - τ determines the speed of settling
 - $\tau = RC$ where R and C are the single capacitor/resistor that occur when independent sources are set to zero and the circuit is reduced.
 - In the freq domain, $\omega_o = 1/\tau$
 - ω_o is the pole frequency (3 dB freq)

Lowpass STC Circuit (Freq Response)

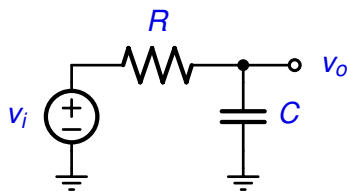

$$H(s) \equiv \frac{V_o(s)}{V_i(s)} = \frac{1/sC}{(1/sC) + R} = \frac{1}{1 + sRC} \quad (1)$$

- Defining $\tau \equiv RC$ and $\omega_o \equiv 1/\tau = 1/(RC)$

$$H(s) = \frac{1}{1 + s\tau} = \frac{1}{1 + (s/\omega_o)} \quad (2)$$

Lowpass STC Circuit (Freq Response)

- In general, a lowpass STC transfer-function is ...

$$H(s) = \frac{K_{dc}}{1 + (s/\omega_o)} \quad (3)$$

— where $\omega_o = 1/\tau$

- Magnitude response

$$|H(j\omega)| = \left| \frac{K_{dc}}{1 + (j\omega/\omega_o)} \right| = \left| \frac{K_{dc}}{\sqrt{1 + (\omega/\omega_o)^2}} \right| \quad (4)$$

— For ...

$$\omega \ll \omega_o \quad \Rightarrow \quad |H(j\omega)| \approx |K_{dc}|$$

$$\omega = \omega_o \quad \Rightarrow \quad |H(j\omega)| = \frac{|K_{dc}|}{\sqrt{2}} \quad (3\text{dB freq})$$

$$\omega \gg \omega_o \quad \Rightarrow \quad |H(j\omega)| = \frac{|K_{dc}|\omega_o}{\omega}$$

Lowpass STC Circuit (Freq Response)

- Phase response (assume $K_{dc} > 0$)

$$\angle H(j\omega) = \angle(K_{dc}) - \angle(1 + (j\omega/\omega_o)) = -\tan^{-1}(\omega/\omega_o) \quad (5)$$


- For ...

$$\omega \ll \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx 0^\circ$$



$$\omega = \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx -45^\circ$$

$$\omega \gg \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx -90^\circ$$

Lowpass STC Circuit (Freq Response)

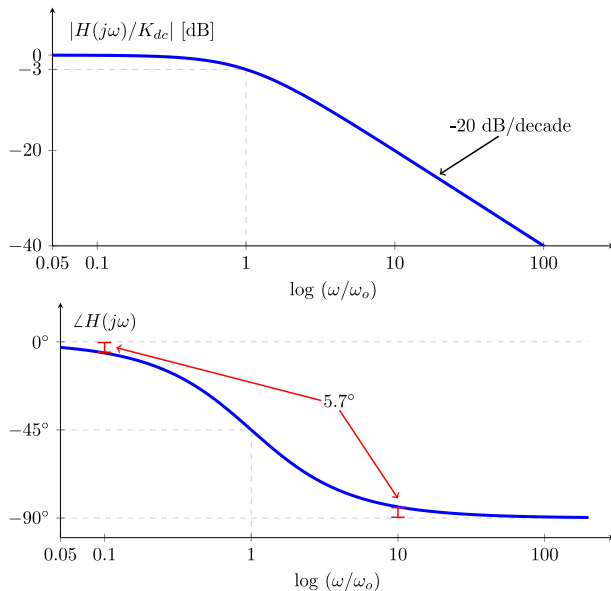

STC Circuit - Time (Step Response)

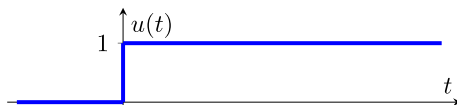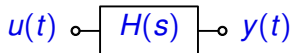

- Step response

- For **both lowpass and highpass** STC circuits, the step response settles in an exponential behavior


$$y(t) = Y_{\infty} - (Y_{\infty} - Y_{0+})e^{-t/\tau} \quad (6)$$

- Y_{∞} is the final value
- Y_{0+} is the initial value
- τ is the time-constant

Lowpass STC Circuit - Time (Step Response)


$$H(s) = \frac{K_{dc}}{1 + (s/\omega_o)} \quad \omega_o = 1/\tau \quad (7)$$

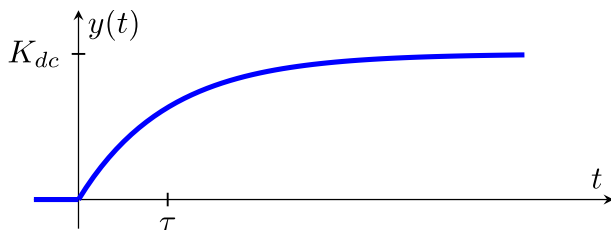- $Y_\infty = K_{dc}; \quad Y_{0+} = 0$
 $y(t) = K_{dc}(1 - e^{-t/\tau}) \quad (8)$




- Initial slope at $t = 0$ is K_{dc}/τ

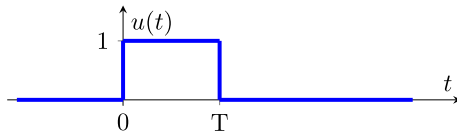
Lowpass STC Circuit - Time (Pulse Response)




$$\tau \ll T$$

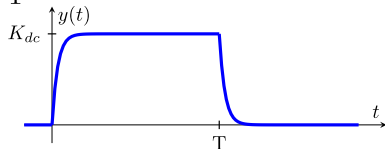


$$\tau = T/3$$

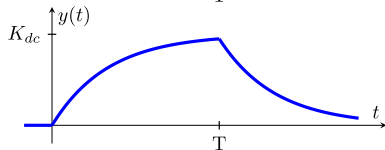

$$\tau \gg T$$

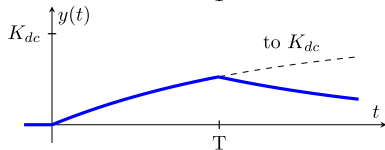

Highpass STC Circuit (Freq Response)

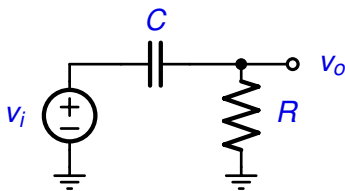

$$H(s) \equiv \frac{V_o(s)}{V_i(s)} = \frac{R}{(1/sC) + R} = \frac{sCR}{sCR + 1} = \frac{s}{s + (1/RC)} \quad (9)$$

- Defining $\tau \equiv RC$ and $\omega_o \equiv 1/\tau = 1/(RC)$

$$H(s) = \frac{s}{s + (1/\tau)} = \frac{s}{s + \omega_o} \quad (10)$$

Highpass STC Circuit (Freq Response)

- In general, a highpass STC transfer-function is ...

$$H(s) = \frac{K_{\infty}s}{s + \omega_o} \quad (11)$$

– where $\omega_o = 1/\tau$

- Magnitude response

$$|H(j\omega)| = \left| \frac{K_{\infty}\omega}{j\omega + \omega_o} \right| = \left| \frac{K_{\infty}}{\sqrt{1 + (\omega_o/\omega)^2}} \right| \quad (12)$$

– For ...

$$\omega \ll \omega_o \quad \Rightarrow \quad |H(j\omega)| \approx \frac{|K_{\infty}|\omega}{\omega_o}$$

$$\omega = \omega_o \quad \Rightarrow \quad |H(j\omega)| = \frac{|K_{\infty}|}{\sqrt{2}} \quad (\text{3dB freq})$$

$$\omega \gg \omega_o \quad \Rightarrow \quad |H(j\omega)| = |K_{\infty}|$$

Highpass STC Circuit (Freq Response)

- Phase response (assume $K_{\infty} > 0$)

$$\angle H(j\omega) = \angle(jK_{\infty}\omega) - \angle(\omega_o + j\omega) = 90^\circ - \tan^{-1}(\omega/\omega_o) \quad (13)$$


– For ...

$$\omega \ll \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx 90^\circ$$

$$\omega = \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx 45^\circ$$

$$\omega \gg \omega_o \quad \Rightarrow \quad \angle H(j\omega) \approx 0^\circ$$

Highpass STC Circuit (Freq Response)

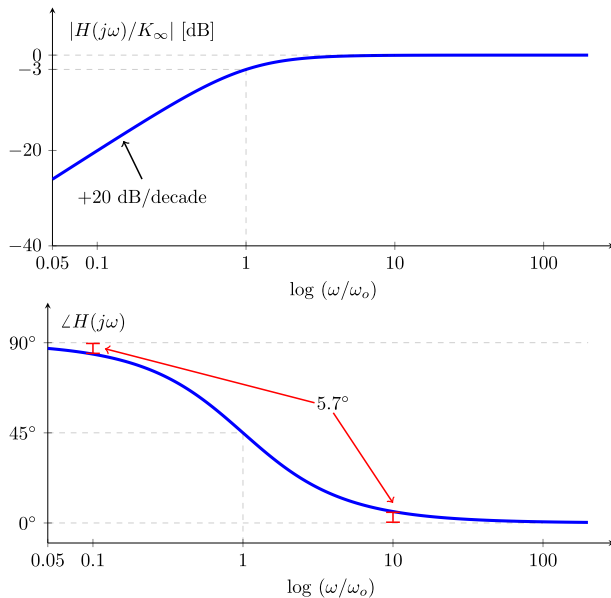


Highpass STC Circuit - Time (Step Response)

$$H(s) = \frac{K_{\infty}s}{s + \omega_o} \quad \omega_o = 1/\tau \quad (14)$$

$$y(t) = Y_{\infty} - (Y_{\infty} - Y_{0+})e^{-t/\tau}$$


- $Y_{\infty} = 0; \quad Y_{0+} = K_{\infty}$
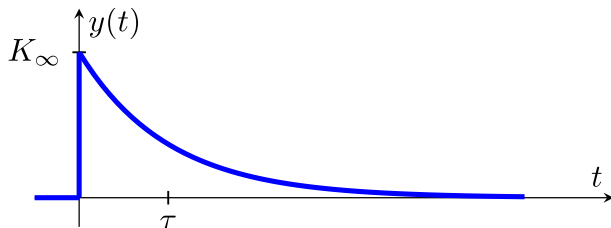
$$y(t) = K_{\infty}e^{-t/\tau} \quad (15)$$



- Initial slope at $t = 0$ is $-K_{\infty}/\tau$

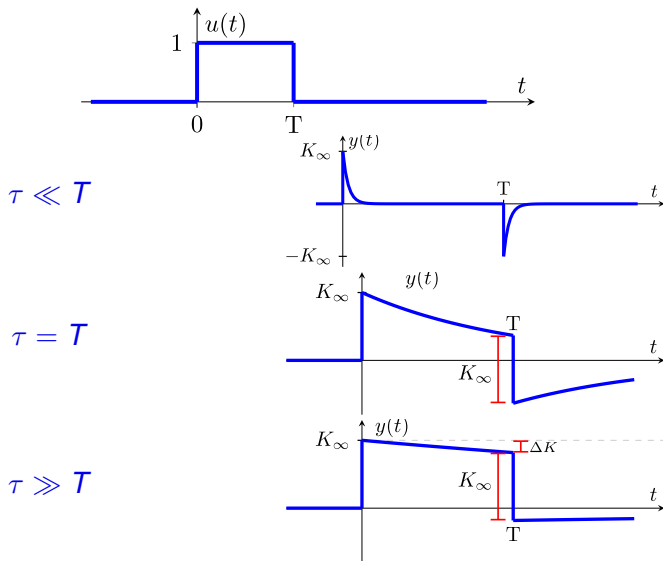Highpass STC Circuit - Time (Pulse Response)



Highpass STC Circuit - Time (Pulse Response)

- For the case $\tau \gg T$
 - ΔK can be found using the exponential equation
 - However, it can also be approximately found since the decay is mostly in the linear region at the beginning
 - Slope is $-K_{\infty}/\tau$ resulting in

$$\Delta K \approx \frac{K_{\infty}}{\tau} \times T \quad (16)$$

- So the percentage "sag", **SAG**, is given by

$$\text{SAG} = \frac{\Delta K}{K_{\infty}} \times 100 = \frac{T}{\tau} \times 100 \quad (17)$$


- So the **SAG** decreases as τ is increased

Finding τ from STC Circuits


- STC circuits are circuits that when the independent sources are set to zero, the circuit can be reduced to a single capacitor and single resistor.
- The following are STC circuits
 - Any circuit with a single capacitor and multiple resistors
 - Any circuit with a single resistor and multiple capacitors
- To find τ
 - Set all independent sources to zero
 - If a single capacitor... find the equivalent resistance, R_{eq} that is across the capacitor... $\tau = R_{eq}C$
 - If a single resistor... find the equivalent capacitance, C_{eq} that is across the resistor... $\tau = RC_{eq}$

Finding τ from STC Circuits

• Examples

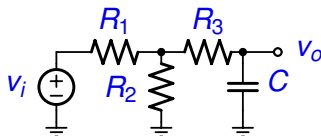


- When $v_i = 0$, the source becomes a short circuit
- $R_{eq} = (R_1 || R_2) + R_3$
- $\tau = R_{eq}C$

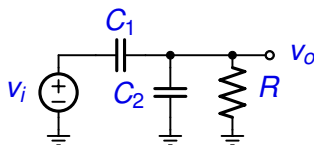


- When $v_i = 0$, the source becomes a short circuit
- $C_{eq} = C_1 + C_2$
- $\tau = RC_{eq}$

Finding τ from STC Circuits

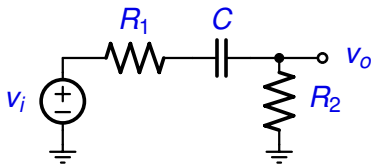


- $\tau = C(R_1 + R_2)$ $\omega_o = \frac{1}{C(R_1 + R_2)}$
- $K_\infty = \left| \frac{v_o}{v_i}(j\infty) \right| = \frac{R_2}{R_1 + R_2}$ since the cap is a short circuit at high freq

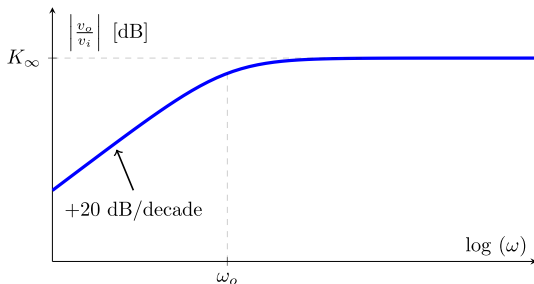

Unity-Gain Freq of Lowpass STC

- Consider a lowpass STC circuit with a LARGE dc gain

$$H(s) = \frac{A_M}{1 + (s/\omega_{3dB})} \quad |A_M| \gg 1 \quad (18)$$

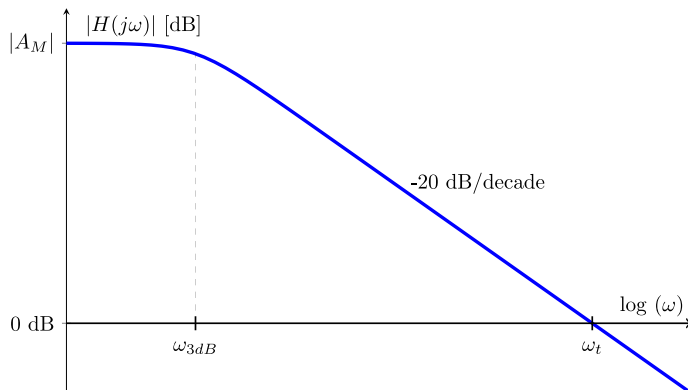

Unity-Gain Freq of Lowpass STC

- ω_t occurs when $|H(j\omega_t)| = 1$

$$\left| \frac{A_M}{1 + (j\omega_t/\omega_{3dB})} \right| = 1 \quad (19)$$

- since $|A_M| \gg 1$, we know $\omega_t \gg \omega_{3dB}$

$$\left| \frac{A_M}{j\omega_t/\omega_{3dB}} \right| \approx 1 \quad (20)$$

$$\omega_t \approx |A_M| \omega_{3dB} \quad (21)$$

and in Hz

$$f_t \approx |A_M| f_{3dB} \quad (22)$$

Topics Covered

- Lowpass STC freq and time responses
- Highpass STC freq and time responses
- Finding τ from STC circuits
- Unity gain freq of STC when large dc gain