

DELAY FROM V_{IN} TO V_5 IS GIVEN BY

$$t_{I(1 \rightarrow 5)} = (5)(15ps)(f + 1) \text{ WHERE } f = 4$$

$$= 300 ps$$

DELAY FROM V_5 TO V_{OUT} IS

$$t_{I6} = (15ps) \left(\frac{20pF}{3.07pF} \right) = 97.7 ps$$

$$TOTAL DELAY = 300 + 97.7 \approx 397.7 ps$$

↑
400

2/

SOLUTIONS

tive to variations in parasitics from one process to another.

- 4.23 The adder delay is 6.6 FO4 inverter delays, or about 133 ps in the 70 nm process.
- 4.24 $F = (10 \text{ pF} / 20 \text{ fF}) = 500$. $N = \log_4 F = 4.5$. Use a chain of four inverters with a stage (5 would also work, but would produce the opposite polarity). $D = 4F^{1/4} + 4 = 22.9 \tau = 4.58 \text{ FO4 delays}$.
- 4.25 If the first upper inverter has size x and the lower $100-x$ and the second upper inverter has the same stage effort as the first (to achieve least delay), the least delays are: $D = 2(300/x)^{1/2} + 2 = 300/(100-x) + 1$. Hence $x = 49.4$, $D = 6.9 \tau$, and the sizes are 49.4 and 121.7 for the upper inverters and 50.6 for the lower inverter. Such circuits are called *forks* and are discussed in depth in [Sutherland99].
- 4.26 The clock buffer from Exercise 4.25 is an example of a 1-2 fork. In general, if a 1-2 fork has a maximum input capacitance of C_1 and each of the two legs drives a load of C_2 , what should the capacitance of each inverter be and how fast will the circuit operate? Express your answer in terms of p_{inv} .

Let the sizes be x and y in the 2-stage path and $C_1 - x$ in the 1-stage path.

$$D = 2\sqrt{\frac{C_2}{x}} + 2p_{\text{inv}} = \frac{C_2}{C_1 - x} + p_{\text{inv}}$$

*** doesn't seem to have any closed-form solution

- 4.27 $P = \alpha CV^2 f = 0.1 * (150 \text{e}^{-12} * 70) * (0.9)^2 * 450 \text{e}^6 = 0.38 \text{ W}$.
- 4.28 Dynamic power consumption will go down because it is quadratically dependent on V_{DD} . Static power will go up because subthreshold leakage is exponentially dependent on V_p .
- 4.29 Simplify using $V_{DD} \gg v_T$:

(a)

$$\begin{aligned} I_1 &= I_{ds0} e^{\frac{-V_i}{V_T}} \left[1 - e^{\frac{-V_{DD}}{V_T}} \right] \approx I_{ds0} e^{\frac{-V_i}{V_T}} \\ I_2 &= I_{ds0} e^{\frac{-V_i}{V_T}} \left[1 - e^{\frac{-1}{V_T}} \right] = I_{ds0} e^{\frac{-V_i - 1}{V_T}} \left[1 - e^{\frac{-V_{DD} + 1}{V_T}} \right] \\ I_2 &\approx I_1 \left[1 - e^{\frac{-1}{V_T}} \right] = I_1 e^{\frac{-1}{V_T}} \\ 1 - e^{\frac{-1}{V_T}} &= e^{\frac{-1}{V_T}} \Rightarrow e^{\frac{-1}{V_T}} = \frac{1}{2} \Rightarrow I_2 / I_1 = 1/2 \end{aligned}$$

(b) Increasing η increases I_1 because the threshold is effectively reduced. The

PROBLEMS 4 SOLUTIONS

3
Q1)

STATIC

OUTPUT
HIGH

$$P_{OH} = (2V) \left(\frac{1.8V}{20k} \right) = 180 \mu W$$

OUTPUT
LOW

$$P_{OL} = (2V)(0) = 0 W$$

$$\begin{aligned} P_{static} &= P_{(V_o=1)} P_{OH} + P_{(V_o=0)} P_{OL} \\ &= (0.3)(180 \mu W) = \underline{\underline{54 \mu W}} \end{aligned}$$

2.) DYNAMIC

$$P_{dyn} \approx P_{1 \rightarrow 0} f C_L (V_{OH} - V_{OL})^2$$


$$P_{1 \rightarrow 0} = P_{V_o=1} P_{V_o=0} = (0.3)(0.7) = 0.21$$

$$f = 1/10ns = 100e6$$

$$\begin{aligned} P_{dyn} &= (0.21)(100e6)(100e-15)(1.8-0)^2 \\ &= \underline{\underline{6.8 \mu W}} \end{aligned}$$

PROBLEMS & SOLUTIONS

Q2)

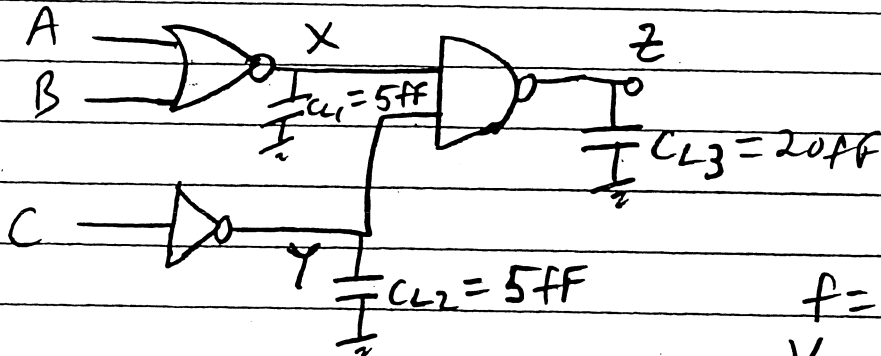

$$f = 1e9$$

$$V_{DD} = 2V$$

$$P_{Y(1 \rightarrow 0)} = (0.5)(0.5) = 0.25$$

$$P_{X=1} = P_{A=0} P_{B=0} = (0.6)(0.8) = 0.48$$

$$P_{X=0} = 1 - P_{X=1} = 0.52$$

$$P_{X(1 \rightarrow 0)} = P_{X=1} P_{X=0} = (0.48)(0.52) = 0.2496$$

$$P_{Z=0} = P_{X=1} P_{Y=1} = (0.48)(0.5) = 0.24$$

$$P_{Z=1} = 1 - P_{Z=0} = 0.76$$

$$P_{Z(1 \rightarrow 0)} = (0.76)(0.24) = 0.1824$$

$$P_{dyn} = P_{X(1 \rightarrow 0)} f C_{L1} V_{DD}^2 + P_{Y(1 \rightarrow 0)} f C_{L2} V_{DD}^2$$

$$+ P_{Z(1 \rightarrow 0)} f C_{L3} V_{DD}^2$$

$$= (1e9)(2^2) [(0.2496)(5f) + (0.25)(5f) + (0.1824)(20f)]$$

$$= 24.6 \mu W$$