

---

**Lab 1: Common-source Amplifiers TA**

---

**Preparation**

1. The maximum swing is  $V_{DD} - V_{ov}$ . This requires  $I_D R_D = (V_{DD} - V_{ov})/2$  and thus  $R_D = (V_{DD} - V_{ov})/2I_D$ . Since  $g_m = 2I_D/V_{ov}$ ,  $A_v = -g_m R_D = (-2I_D/V_{ov}) \cdot (V_{DD} - V_{ov})/2I_D = -(V_{DD} - V_{ov})/V_{ov}$ .
2.  $V_{ov} = \sqrt{2I_D/\mu C_{ox}W/L}$ .  $g_m = 2I_D/V_{ov}$ . For maximum swing,  $V_o = (V_{DD} - V_{ov})/2$ . For 0.2 V<sub>pp</sub> swing,  $V_o = V_{ov} + 0.2/2$ .  $R_D = (V_{DD} - V_o)/I_D$ .  $A_v = -g_m R_D$ . See Table 1 for numerical values.
3. See Figure 1.
4. See Figure 2.
5. Same as the previous step.
6. See Figure 3.
7. N/A

Table 1: Hand analysis table

$V_{DD}$ (V)	Type	Gain	Swing (V <sub>pp</sub> )	$V_{ov}$ (V)	$I_D$ (A)	$g_m$ (A/V)	$V_o$ (V)	$R_D$ (Ω)	$A_v$ (V/V)
5.0	NMOS	-	max	667 m	1 m	3.00 m	2.83	2.17 k	-6.51
5.0	PMOS	-	max	690 m	0.5 m	1.45 m	2.16	4.37 k	-6.34
1.2	NMOS	max	0.2	471 m	0.5 m	2.12 m	488 m	1.26 k	-2.67

**Lab**

- Emphasize the importance of the 50-Ω termination for correct voltage reading of the signal source.
- Briefly explain how the input bias circuit works.

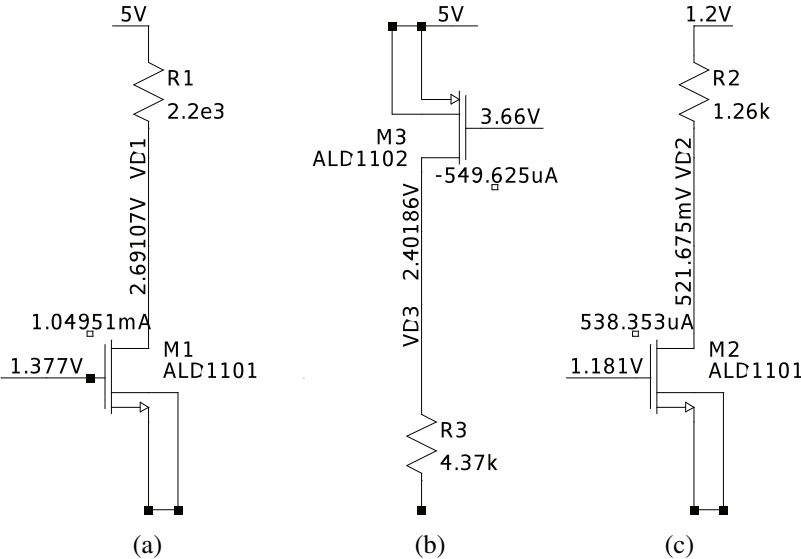


Figure 1: DC operating points of (a) NMOS,  $V_{DD} = 5\text{ V}$  (b) PMOS,  $V_{DD} = 5\text{ V}$ , and (c)  $V_{DD} = 1.2\text{ V}$ .