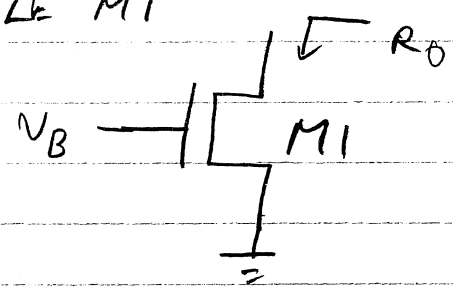


CASCODE AMPLIFIER


TO INCREASE GAIN OF AMPLIFIER  
(AND ALSO INCREASE FREQUENCY RESPONSE)  
(COVERED IN FREQ RESPONSE SECTION)

OUTPUT IMPEDANCE


SINGLE M1




M1 ACTIVE

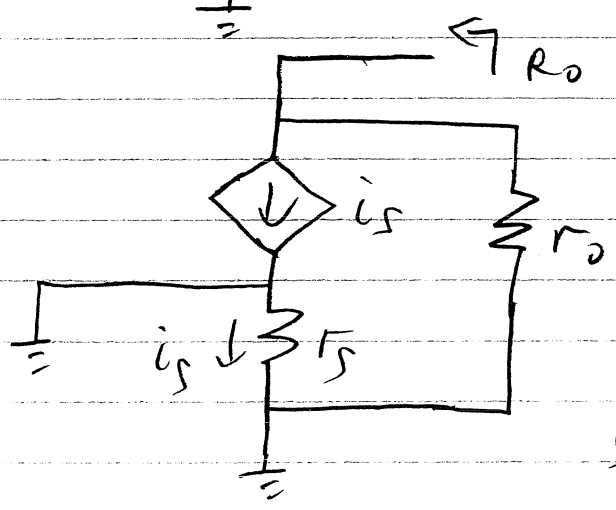


SINCE  $i_s = 0$

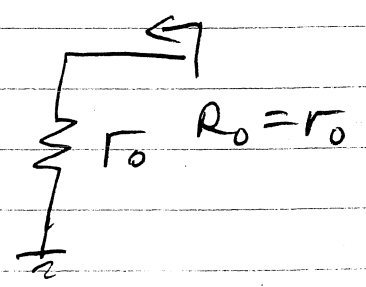

CASCODE TRANSISTOR

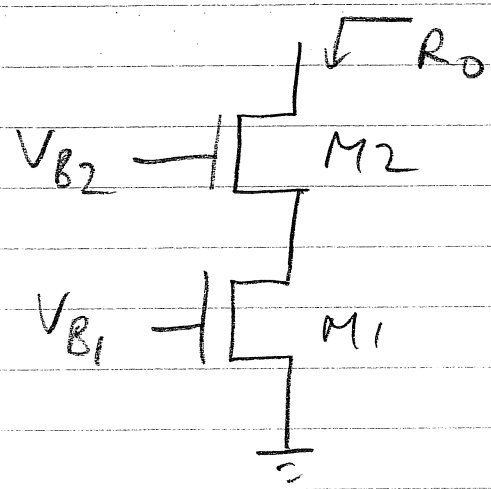

$M_1, M_2$  ACTIVE

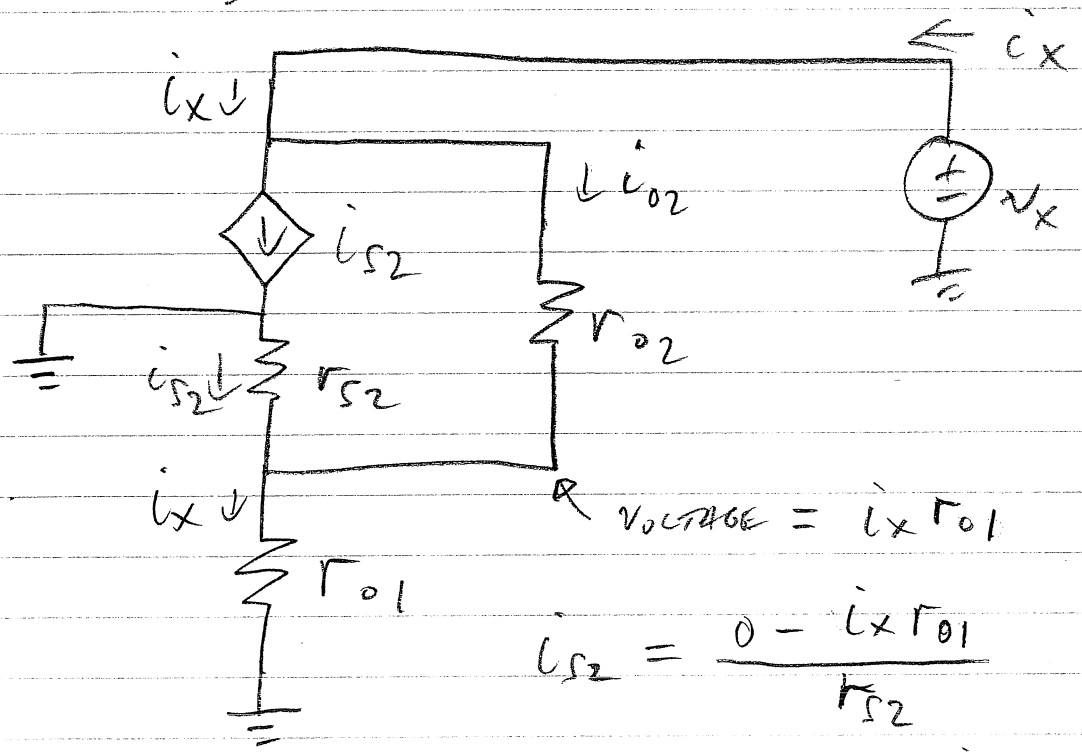

$$i_{S2} = \frac{0 - i_x r_{01}}{r_{S2}}$$

$$i_{02} = \frac{v_x - i_x r_{01}}{r_{02}}$$

$$i_x = i_{02} + i_{S2} = \frac{v_x - i_x r_{01}}{r_{02}} + \frac{-i_x r_{01}}{r_{S2}}$$

(CA3)

$$i_x \left( 1 + \frac{r_{o1}}{r_{o2}} + \frac{r_{o1}}{r_{s2}} \right) = \frac{v_x}{r_{o2}}$$

$$R_o \equiv \frac{v_x}{i_x} = \left( 1 + \frac{r_{o1}}{r_{o2}} + \frac{r_{o1}}{r_{s2}} \right) r_{o2}$$

$$R_o = r_{o1} + r_{o2} + g_{m2} r_{o1} r_{o2} \quad \text{EXACT}$$

SINCE  $r_{s2} = \frac{1}{g_{m2}}$

SINCE  $g_{m2} r_{o2} \gg 1$   
(MORE OR LESS)

APPROX


$$R_o \approx g_{m2} r_{o1} r_{o2}$$

IF  $r_o = r_{o1} = r_{o2}$

and  $g_m = g_{m1} = g_{m2}$

$$R_o \approx g_m r_o^2$$

IN GENERAL

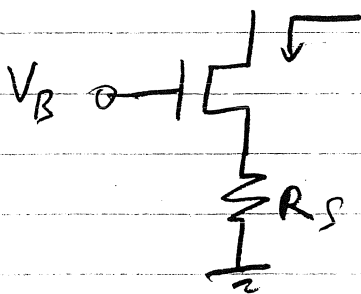


$$R_{out} = R_S + r_o + g_m r_o R_S$$


$$R_{out} \approx (1 + g_m R_S) r_o$$

FOR  $g_m R_o \gg 1$   
(OR  $\frac{R_o}{r_s} \gg 1$ )

A METHOD TO FIND GAIN IN A CIRCUIT

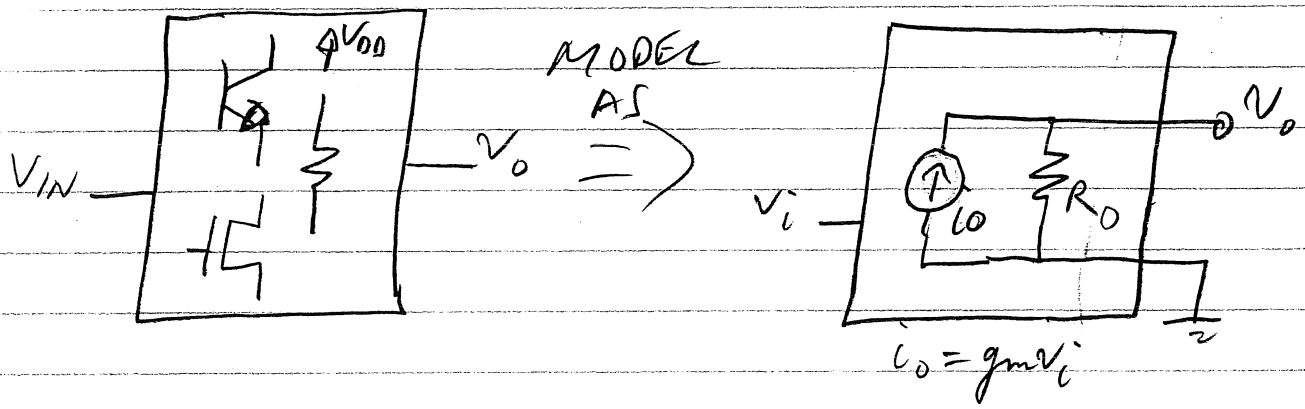

FIND SHORT CIRCUIT CURRENT,  $i_{sc}$

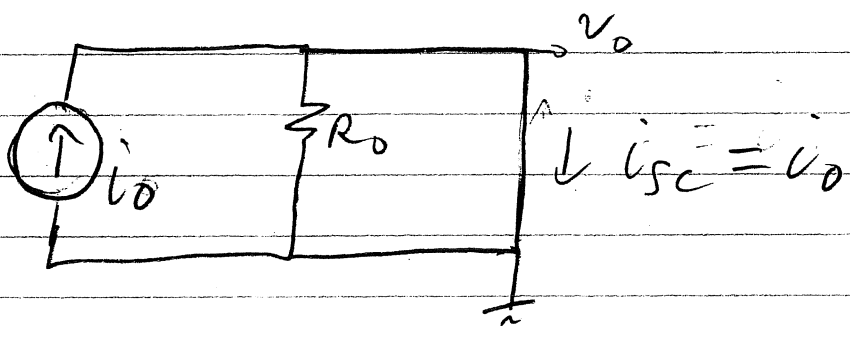


SO OPEN CIRCUIT VOLTAGE  $V_O = i_0 R_O$

WHERE  $R_O$  IS OUTPUT IMPEDANCE OF CIRCUIT.

$\frac{V_o}{V_i}$  GAIN

CA4

CASCODE AMP WITH IDEAL  
CURRENT SOURCE

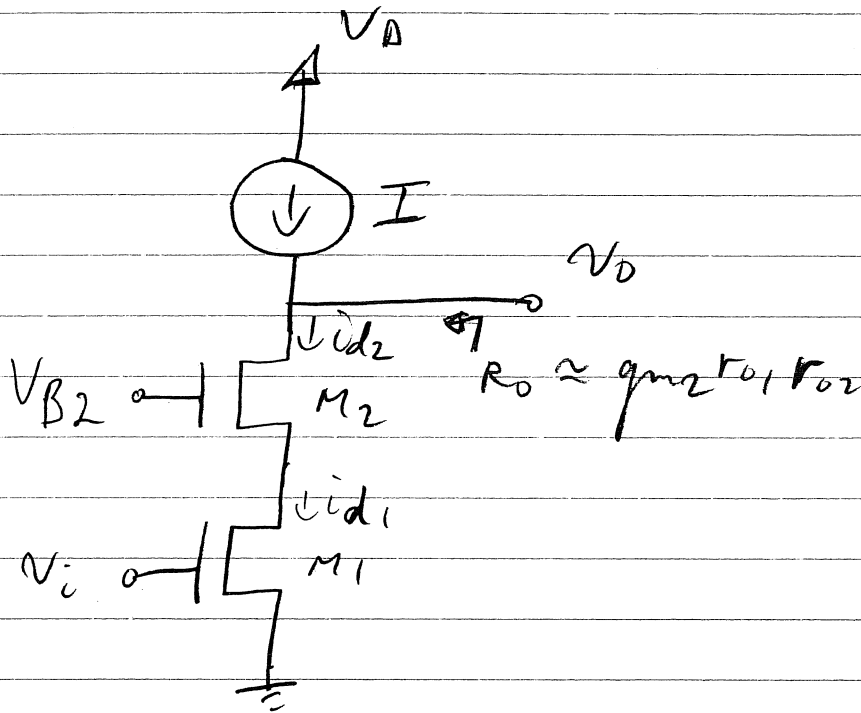


FIRST FIND  $i_{d2}$  IF  $V_o$  GROUNDLED

THEN 
$$\frac{V_o}{V_i} = -i_{d2} R_o$$

CA5

$i_{d2}$

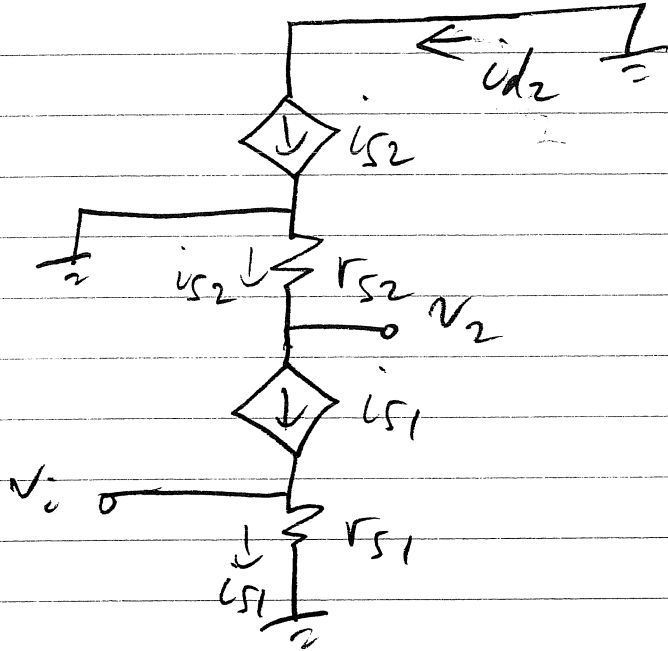ASSUME  $r_{o1} = r_{o2} \rightarrow \infty$



$$i_{d2} = i_{s2} = \frac{0 - v_2}{r_{s2}} = i_{s1} = \frac{v_i}{r_{s1}} = g_{m1} v_i$$

$$i_{d2} = g_{m1} v_i$$


SO

$$\frac{v_o}{v_i} = -g_{m1} R_o$$

CAL

$i_{d2}$

IF  $r_{o1}$  &  $r_{o2}$  FINITE

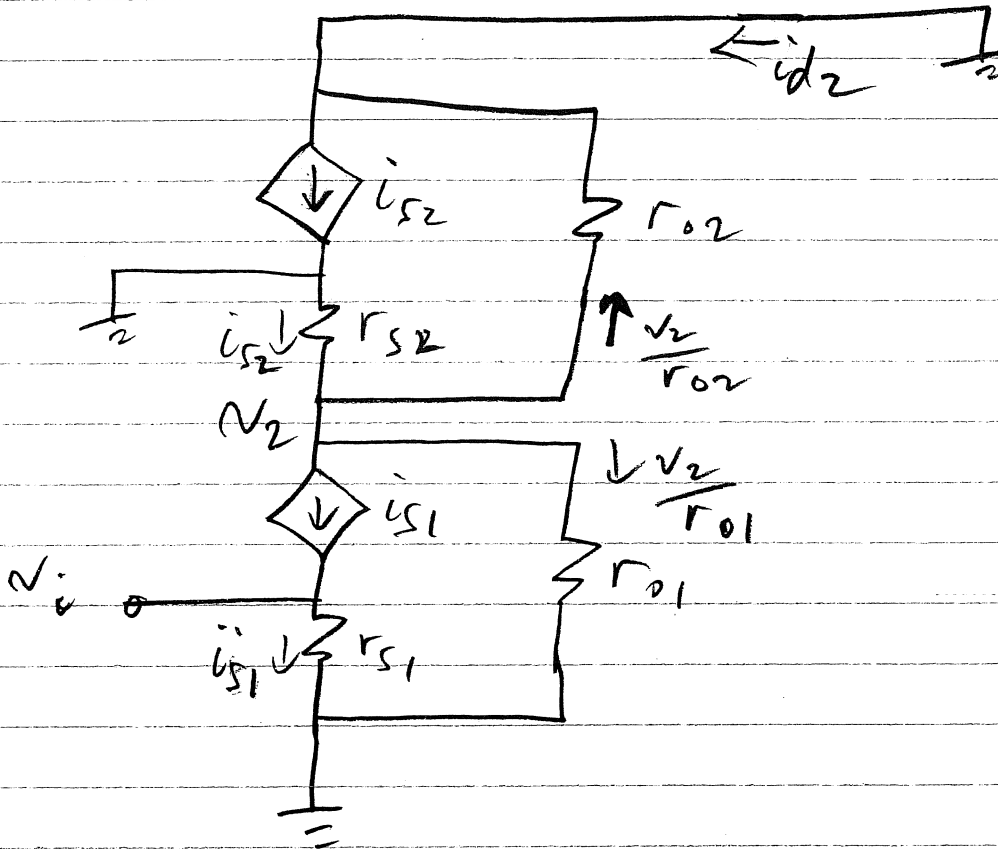

$$\frac{v_i}{r_{s1}} + \frac{v_2}{r_{o1}} + \frac{v_2}{r_{o2}} + \frac{v_2}{r_{s2}} = 0$$

$$v_i \left( \frac{1}{r_{s1}} \right) = -v_2 \left( \frac{1}{r_{o1}} + \frac{1}{r_{o2}} + \frac{1}{r_{s2}} \right)$$

BUT  $r_{s2} \ll r_{o1}$  &  $r_{o2}$  SO

$$v_i \left( \frac{1}{r_{s1}} \right) \approx -v_2 \left( \frac{1}{r_{s2}} \right)$$

$$v_2 \approx - \left( \frac{r_{s2}}{r_{s1}} \right) v_i$$

(CA7)

$$i_{d2} = -\frac{v_2}{r_{o2}} + v_{s2}$$

$$= -\frac{v_2}{r_{o2}} - \frac{v_2}{r_{s2}}$$

$$= v_2 \left( \frac{-1}{r_{o2}} + \frac{-1}{r_{s2}} \right) \quad r_{s2} \ll r_{o2}$$

$$i_{d2} \approx v_2 \left( \frac{-1}{r_{s2}} \right)$$

$$\approx \left( \frac{-r_{s2}}{r_{s1}} \right) \left( \frac{-1}{r_{s2}} \right) v_i$$

$$i_{d2} \approx \left( \frac{1}{r_{s1}} \right) v_i = g_{m1} v_i$$

AS BEFORE

ASSUMING

$$r_{o1}, r_{o2} \gg r_{s1}, r_{s2}$$

$$\text{So } \frac{v_o}{v_i} = -g_{m1} R_o$$



(7A)


IN GENERAL,

LET  $r_o \rightarrow \infty$  WHEN FINDING

$i_{sc}$  BUT MUST INCLUDE

$r_o$  WHEN FINDING  $R_o$

THEN  $V_o = i_o R_o$

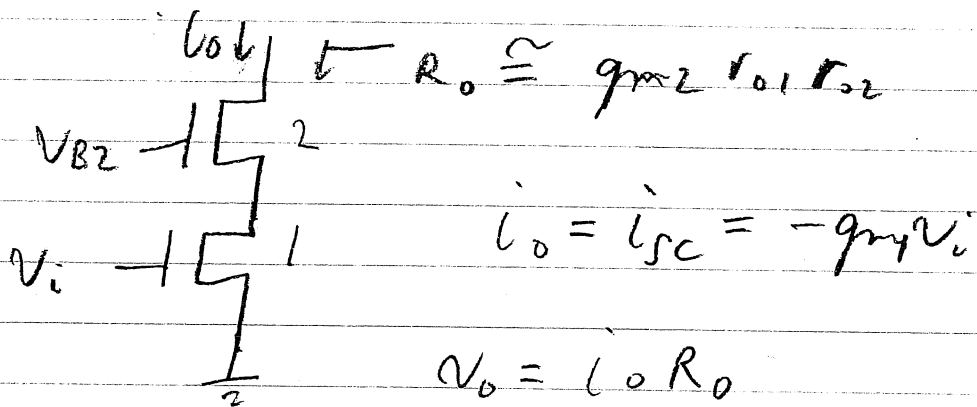

$$\frac{V_o}{V_i} = -g_{m1} g_{m2} r_{o1} r_{o2}$$

CAS

$$\frac{V_o}{V_i} = -g_{m1} R_o$$

$$= -g_{m1} g_{m2} r_{o1} r_{o2}$$

IF  $g_{m1} = g_{m2}$  &  $r_{o1} = r_{o2}$

$$\frac{V_o}{V_i} = -g_m^2 r_o^2 = -(g_m r_o)^2$$


THE GAIN IS <sup>11</sup>  $A^2$  <sup>11</sup> COMPARED  
TO A SINGLE TRANSISTOR!

IF  $A = 40$  FOR SINGLE TRANSISTOR

$$\text{CASCODE GAIN} = 40^2 = 1600$$

CA9

# PRACTICAL CASE

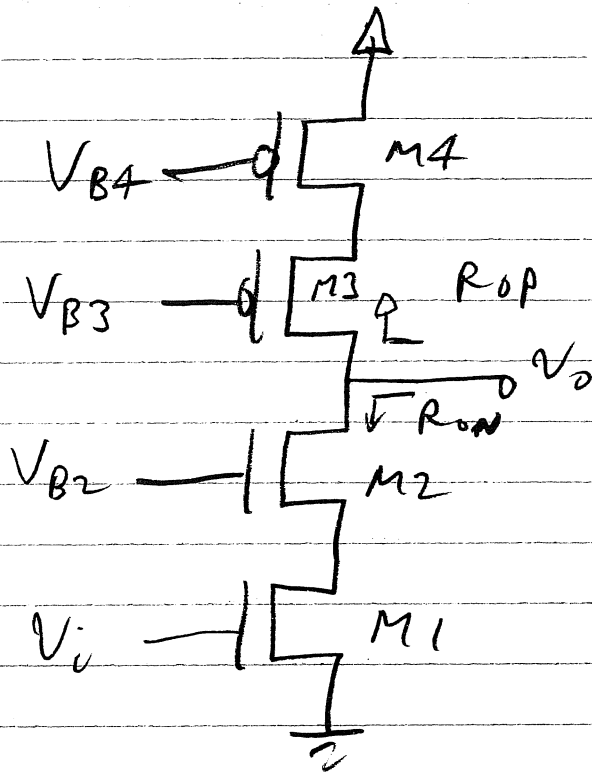


$$R_{on} = g_{m2} r_{o1} r_{o2}$$

$$R_{op} = g_{m3} r_{o3} r_{o4}$$

$$\frac{V_o}{V_i} = -g_{m1} (R_{on} \parallel R_{op})$$

$$\approx -\frac{1}{2} g_{m1} g_{m2} r_{o1} r_{o2}$$

IF  $R_{on} = R_{op}$

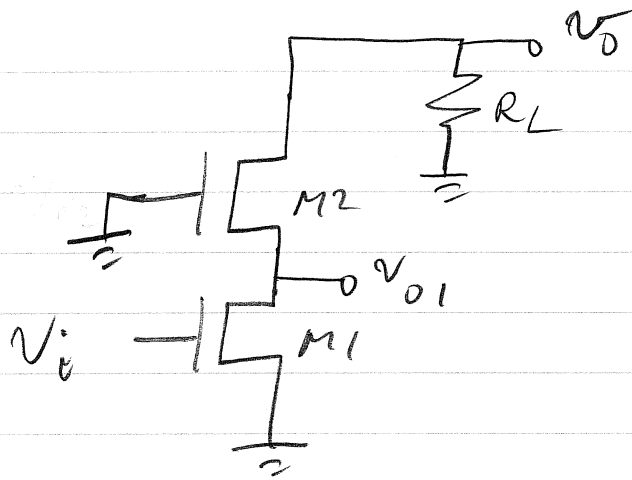


CAS10

SMALL-SIGNAL  
MODEL BUT  
DRAWN WITH  
TRANSISTORS

WHAT IS  $\frac{V_{o1}}{V_i}$  ?

CAN SHOW

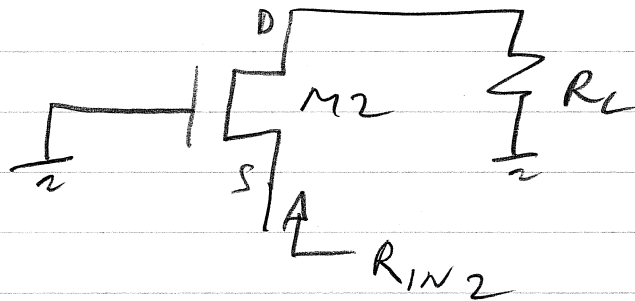

$$R_{in2} = \frac{R_L + r_{o2}}{1 + g_{m2} r_{o2}} \quad \text{EXACT}$$

IF  $g_m r_o \gg 1$

$$R_{in2} \approx \frac{R_L}{g_{m2} r_{o2}} + \frac{1}{g_{m2}}$$

IN THIS CASE  $R_L = R_{OP} = g_{m3} r_{o3} r_{o4}$

SO

$$R_{in2} \approx \frac{g_{m3} r_{o3} r_{o4}}{g_{m2} r_{o2}} + \frac{1}{g_{m2}}$$

CA11

ASSUMING

$$g_{m1} \equiv g_{m2} = g_{m3} = g_{m1}$$

$$r_{o1} \equiv r_{o2} = r_{o3} = r_{o4} = r_{o1}$$

$$R_{in2} \approx r_{o1} + \frac{1}{g_{m1}} \quad \text{+ SINCE } g_{m1} r_{o1} \gg 1$$

$$R_{in2} \approx r_{o1}$$

So


$$\frac{v_{o1}}{v_i} \approx -g_{m1} (R_{in2} \parallel r_{o1})$$

$$\frac{v_{o1}}{v_i} \approx -\frac{1}{2} g_{m1} r_{o1}$$

WHILE


$$\frac{v_{o2}}{v_i} \approx -\frac{1}{2} (g_{m1} r_{o1})^2$$

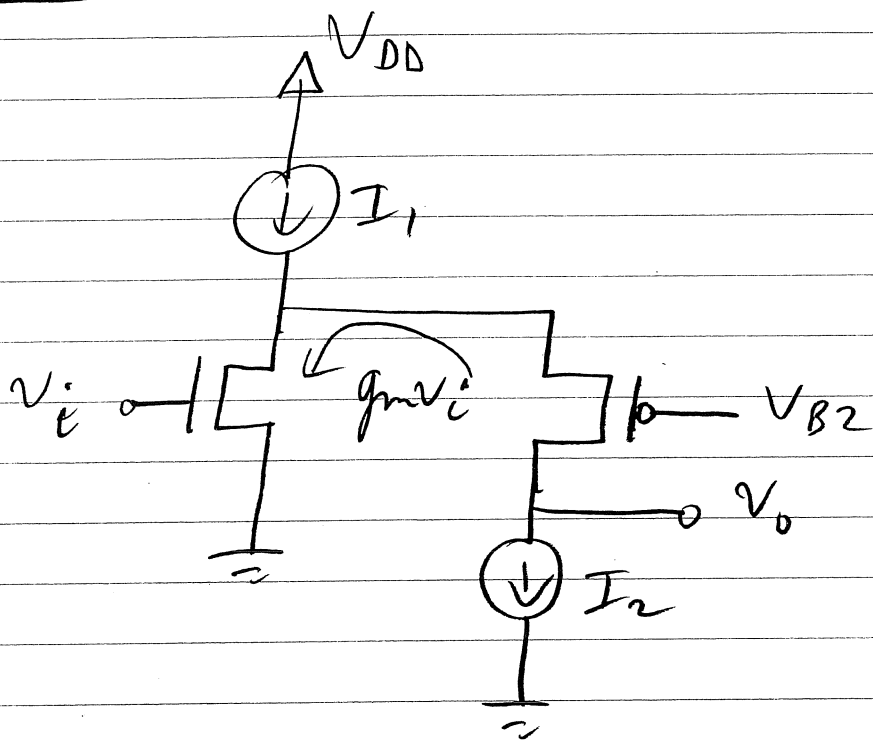SOMETIME POWER SUPPLIES WILL NOT LET CASCODE WORK BUT CAN FOLD IT



FOR INFORMATION ONLY

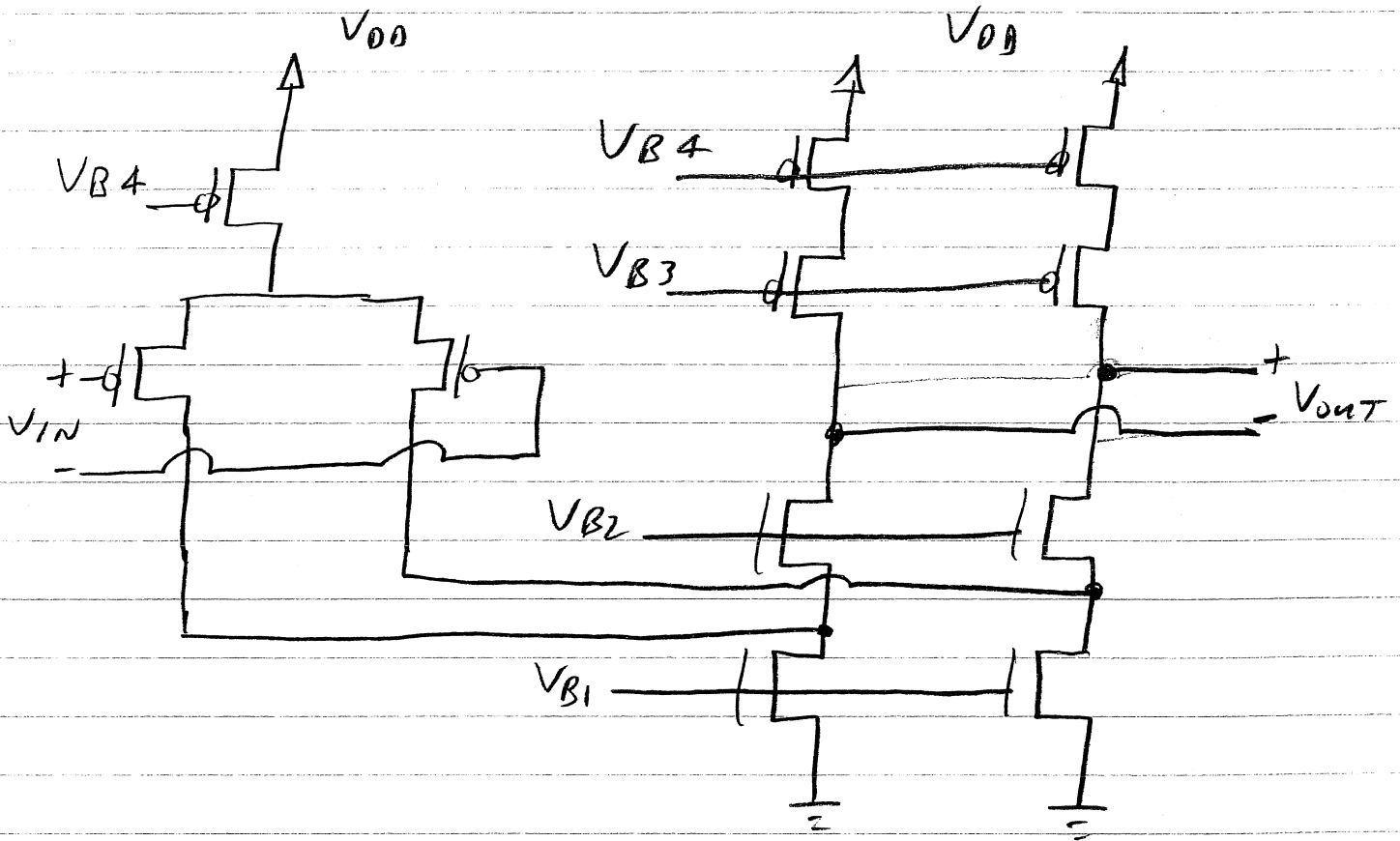A FOLDED-CASCADE OPAMP  
USED IN INTEGRATED CIRCUITS



REQUIRES COMMON-MODE FEEDBACK  
CIRCUIT - NOT SHOWN