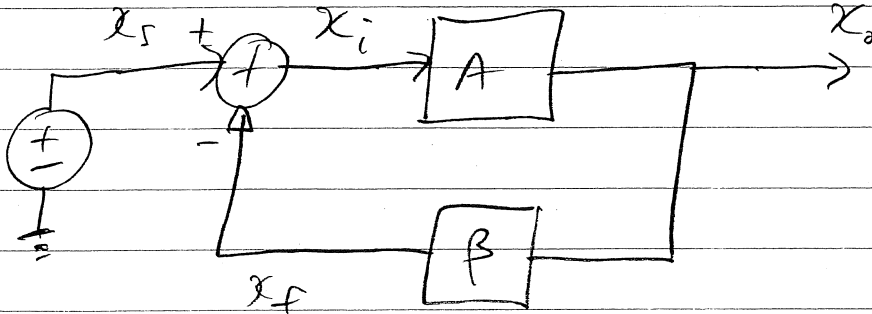


4 BASIC FEEDBACK STRUCTURES



4 BASIC TYPES DEPENDING ON TYPES OF SIGNALS AT x_s, x_f, x_i & x_o

<u>x_s, x_f, x_i</u>	<u>x_o</u>	<u>TYPE</u> (INPUT/OUTPUT)
VOLTAGE	VOLTAGE	SERIES-SHUNT
CURRENT	VOLTAGE	SHUNT-SHUNT
CURRENT	CURRENT	SHUNT-SERIES
VOLTAGE	CURRENT	SERIES-SERIES



SO SERIES-SHUNT MEANS OUTPUT IS A VOLTAGE AND IS SAMPLED WITH A SHUNT NETWORK WHILE INPUT IS ALSO A VOLTAGE AND THE SUBTRACTION IS DONE WITH A SERIES NETWORK.

FFIA

WHY THE TERMINOLOGY => SERIES / SHUNT?



INPUT SUMMATION

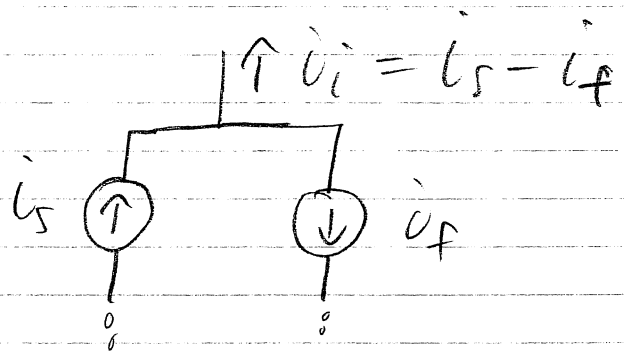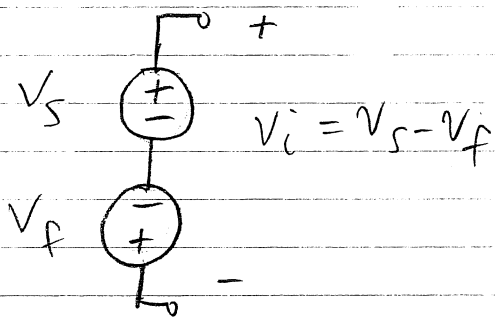VOLTAGES ARE ADDED BY PUTTING THEM IN SERIES WHILE CURRENTS ARE ADDED BY PUTTING THEM IN PARALLEL (SHUNT)




OUTPUT SAMPLING

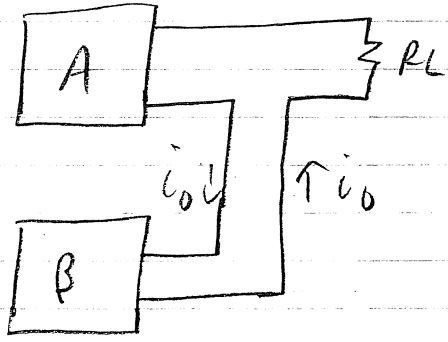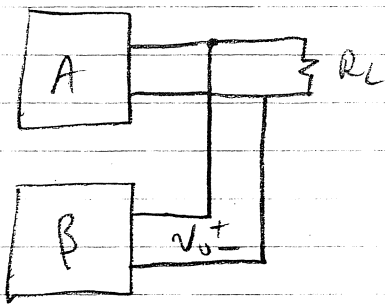VOLTAGES ARE SAMPLED BY A PARALLEL (SHUNT) CONNECTION WHILE CURRENTS ARE SAMPLED BY A SERIES CONNECTION




SERIES-SHUNT EXAMPLES

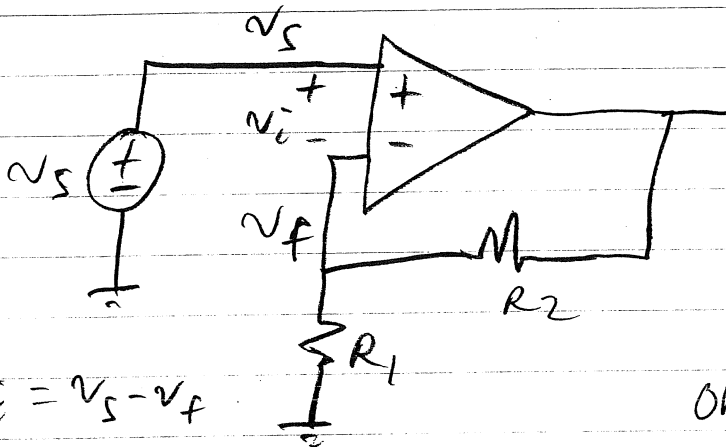

NEG FEEDBACK CHECK

- $v_s \uparrow \Rightarrow v_i \uparrow$
- $v_i \uparrow \Rightarrow v_o \uparrow$
- $v_o \uparrow \Rightarrow v_f \uparrow$
- $v_f \uparrow \Rightarrow v_i \downarrow$ ✓

OPPOSITE OF ORIGINAL v_i CHANGE

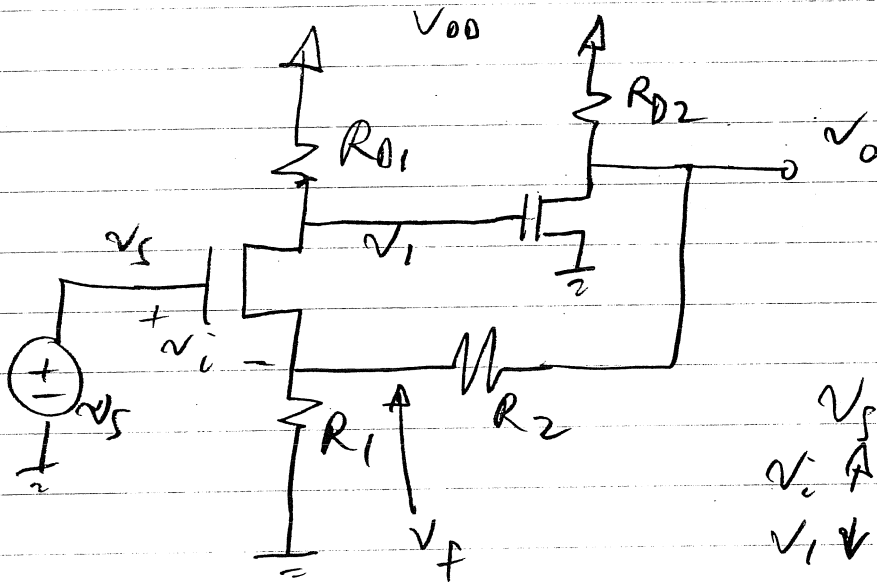


NEG FEEDBACK CHECK

- $v_s \uparrow \Rightarrow v_i \uparrow$
- $v_i \uparrow \Rightarrow v_1 \downarrow$
- $v_1 \downarrow \Rightarrow v_o \uparrow$
- $v_o \uparrow \Rightarrow v_f \uparrow$
- $v_f \uparrow \Rightarrow v_i \downarrow$ ✓

$v_i = v_s - v_f$

FF3

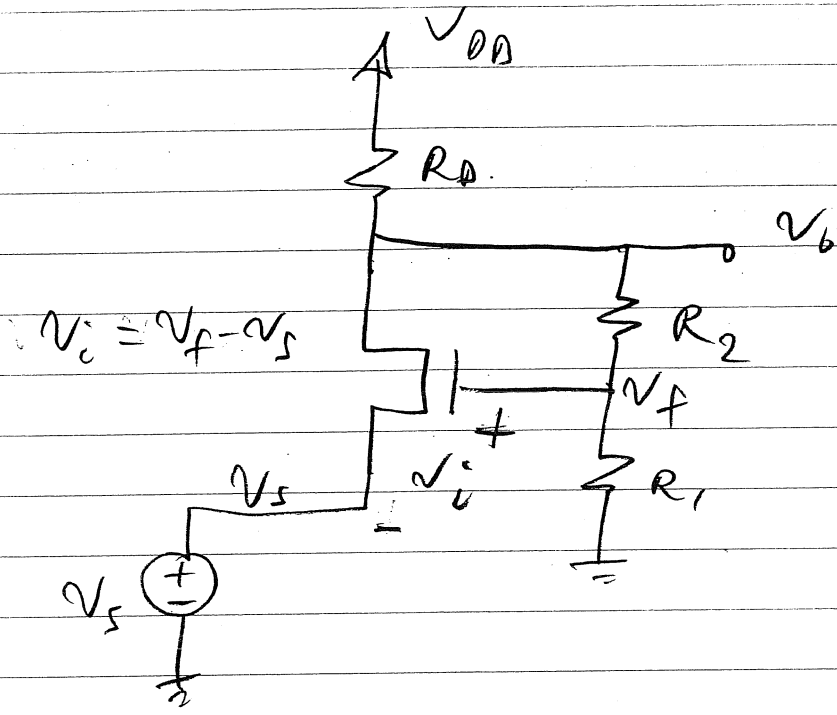


NEG FEEDBACK CHECK

$$v_s \uparrow \Rightarrow v_i \downarrow$$

$$v_i \downarrow \Rightarrow v_o \uparrow$$


$$v_o \uparrow \Rightarrow v_f \uparrow$$
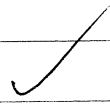
$$v_o \uparrow \Rightarrow \underline{v_i \uparrow}$$




OPPOSITE OF ORIGINAL v_i CHANGE

SHUNT-SHUNT EXAMPLES

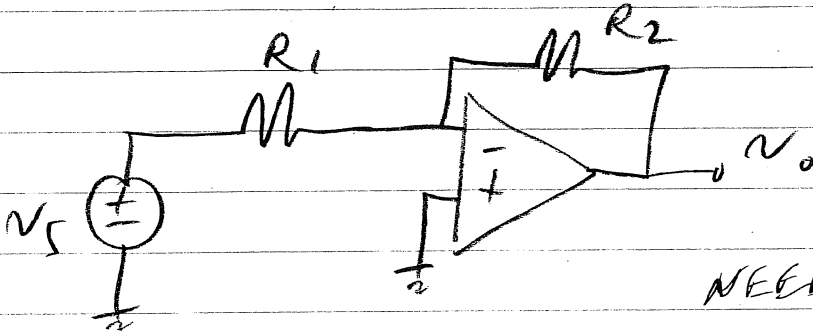

NEEDS MODIFICATION

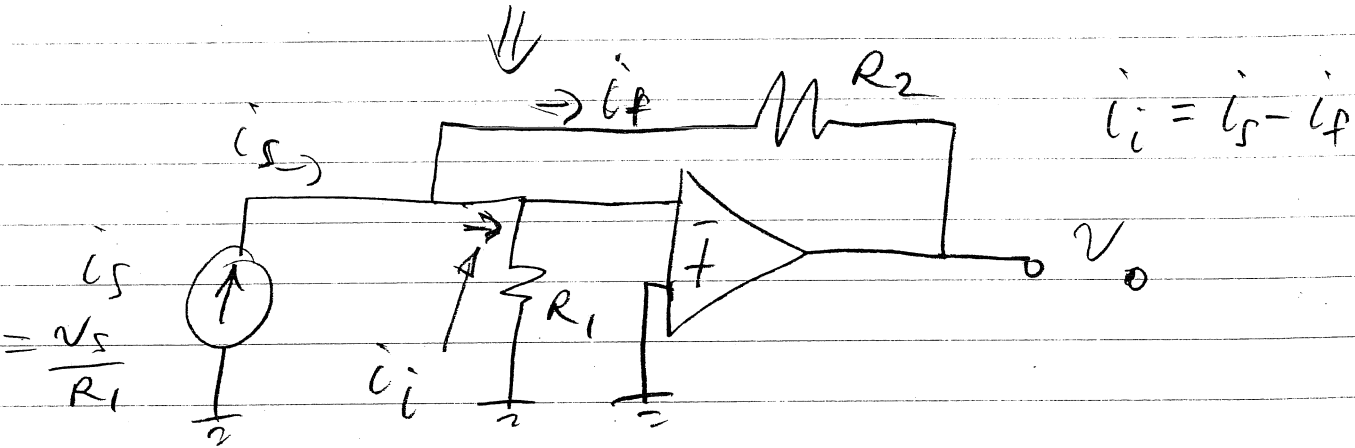

$$i_i = i_s - i_f$$


$$i_s \uparrow \Rightarrow i_i \uparrow$$

$$i_i \uparrow \Rightarrow v_o \downarrow \quad \left(\begin{array}{l} \text{SINCE } v_- \uparrow \text{ DUE TO} \\ i_i \downarrow \quad v_o = A(v_+ - v_-) \end{array} \right)$$

$$v_o \downarrow \Rightarrow i_f \uparrow$$

$$i_f \uparrow \Rightarrow i_i \downarrow \quad \checkmark$$

FF5

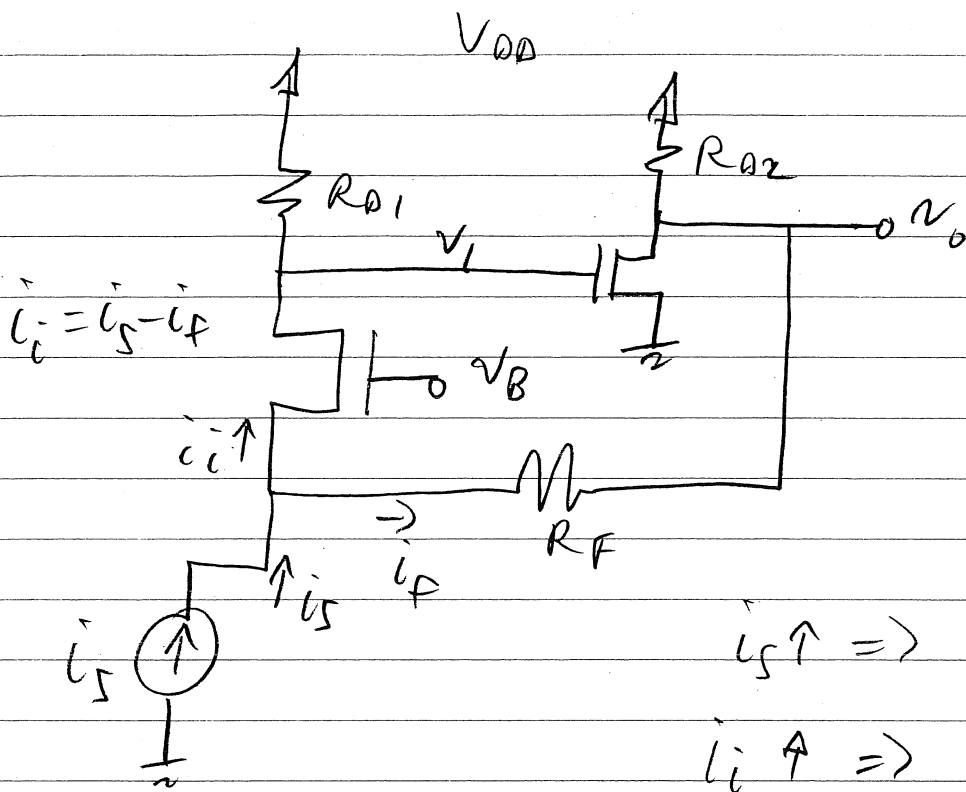

$i_S \uparrow \Rightarrow i_i \uparrow$
 $i_i \uparrow \Rightarrow v_i \uparrow$
 $v_i \uparrow \Rightarrow v_o \downarrow$
 $v_o \downarrow \Rightarrow i_f \uparrow$
 $i_f \uparrow \Rightarrow i_i \downarrow$ ✓

A BIT MORE DIFFICULT TO SEE NEG FEEDBACK HERE. EASIER TO LOOK AROUND LOOP AT v_i WITH $i_S = 0$ (OPEN)


BREAK LOOP AT v_i

INSERT TEST VOLTAGE v_{it} & FIND

RETURN SIGNAL v_{ir}

IF $v_{it} \uparrow$ THEN $v_{ir} \downarrow$

FF-6

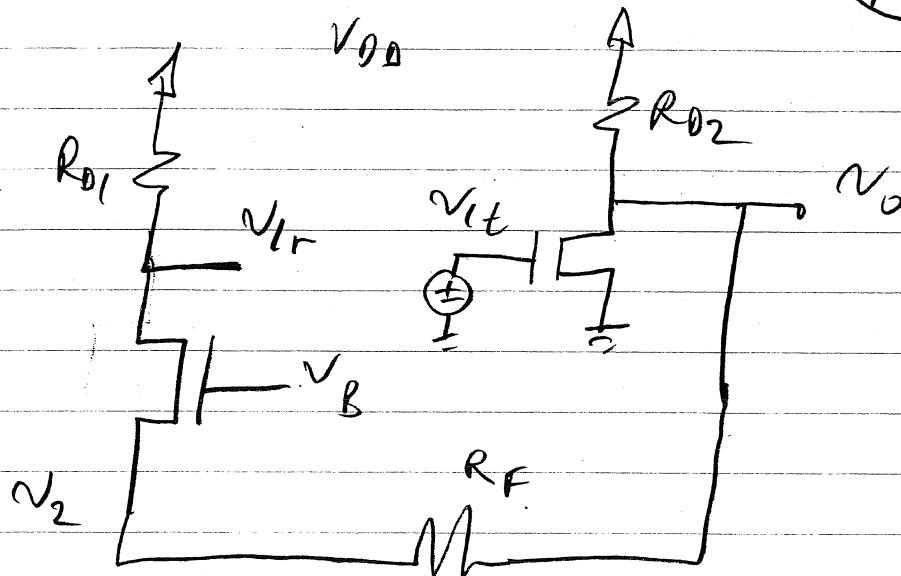

$$V_{IT} \uparrow \Rightarrow V_0 \downarrow$$


$$V_0 \downarrow \Rightarrow V_2 \downarrow$$

$$V_2 \downarrow \Rightarrow V_{IT} \downarrow$$


✓
OPPOSITE OF
 V_{IT}

FF7

SHUNT-SERIES EXAMPLE

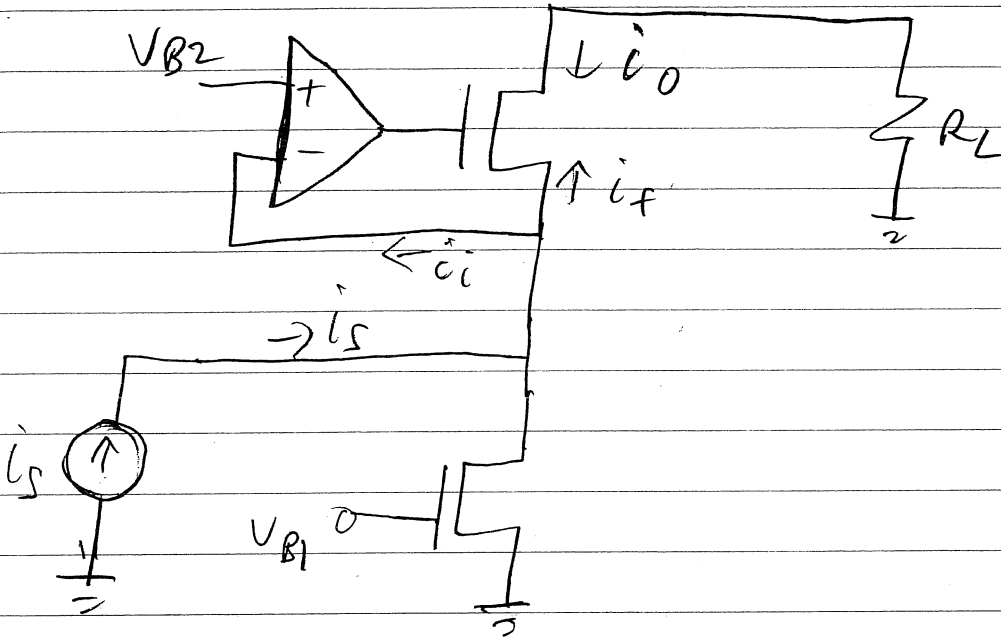

SERIES-SERIES EXAMPLE

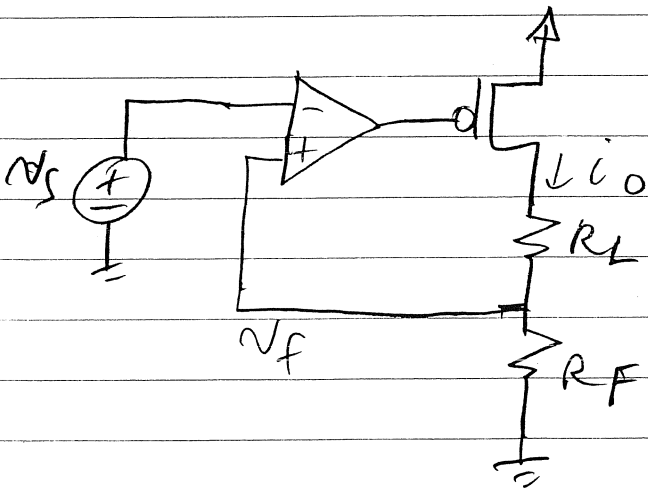

- IN GENERAL, TYPE OF FEEDBACK IS DETERMINED BY WHERE INPUT IS APPLIED AND WHAT IS CONSIDERED TO BE THE OUTPUT.
- THIS MAKES A FEEDBACK APPROACH DIFFICULT TO USE & PRONE TO ERRORS
- WE SHALL DEVIATE FROM TEXTBOOK HERE AND USE THE LOOP GAIN ANALYSIS APPROACH
- IT IS DESCRIBED IN THE 5TH EDITION OF "ANALYSIS AND DESIGN OF ANALOG INTEGRATED CIRCUITS" BY GRAY/HURST/LEWIS/MEYER, 2009
- ANOTHER ISSUE WITH A FEEDBACK APPROACH IS THAT $A\beta$ DEPENDS ON INPUT APPLIED & OUTPUT TAKEN ESPECIALLY WHEN β IS NOT UNIDIRECTIONAL
- THE LOOP GAIN IS UNCHANGED IN THE RETURN-RATIO APPROACH
- LOOP GAIN DETERMINES STABILITY OF A CIRCUIT.