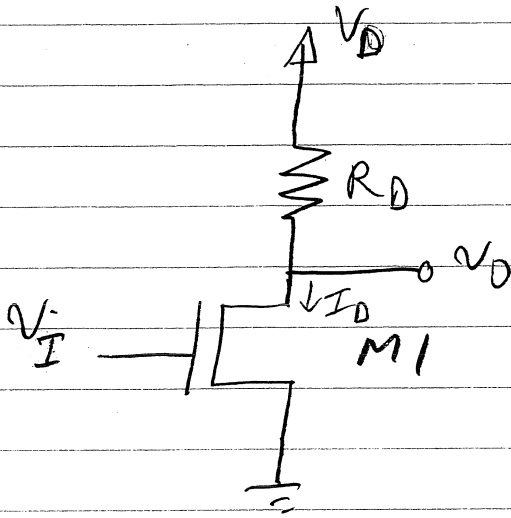



GCI

GAIN CELL



ASSUME $\lambda = 0$
($r_o \rightarrow \infty$)

M1

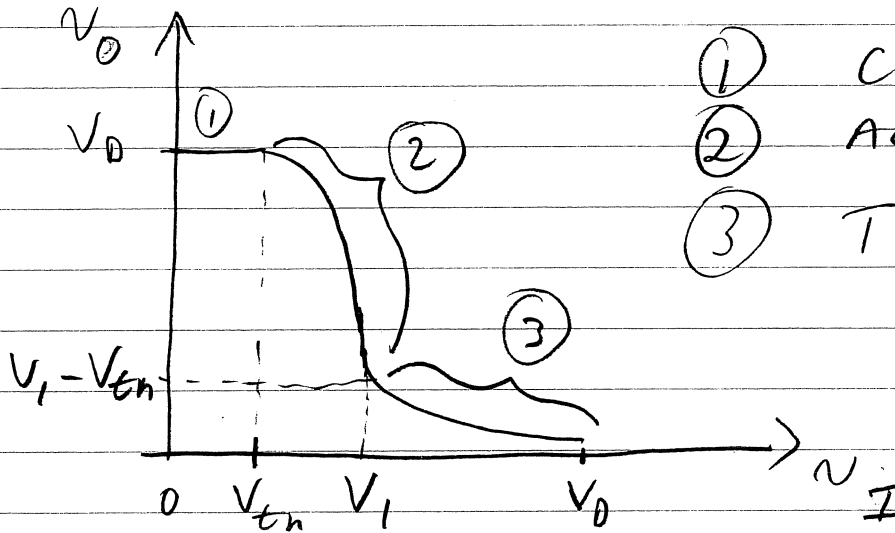

- ① CUTOFF
- ② ACTIVE
- ③ TRIODE

SMALL-SIGNAL

GAIN

$$\frac{v_o}{v_i}$$

IS

$$\frac{dv_o}{dv_i}$$

SO

$$\frac{v_o}{v_i} = 0$$

IN

①

$$\frac{v_o}{v_i}$$

SMALL

IN

③

GC2

IN (2) (ACTIVE)

GAIN DEPENDS ON g_m WHICH
DEPENDS ON I_D

$$\frac{V_o}{V_i} = -g_m R_D \quad g_m = \frac{2I_D}{V_{ov}}$$

$$V_{ov} = V_{GS} - V_{tn}$$

$$V_{ov} = V_I - V_{tn}$$

LARGEST GAIN OCCURS NEAR $V_I = V_t$,

FOR A GIVEN TRANSISTOR & I_D


(HENCE GIVEN g_m) TO INCREASE $\frac{V_o}{V_i}$

NEED TO INCREASE R_D BUT THEN

V_{RD} TOO LARGE.


REPLACE R_D WITH CURRENT SOURCE.

GCS

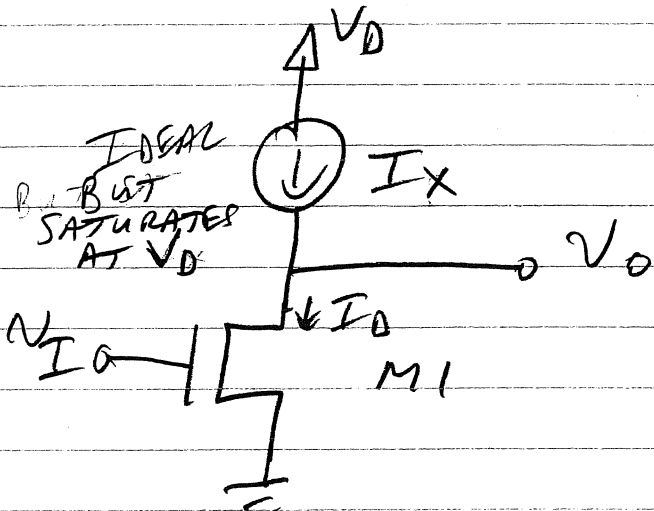

ASSUME $\lambda = 0$
($r_o \rightarrow \infty$)

M1

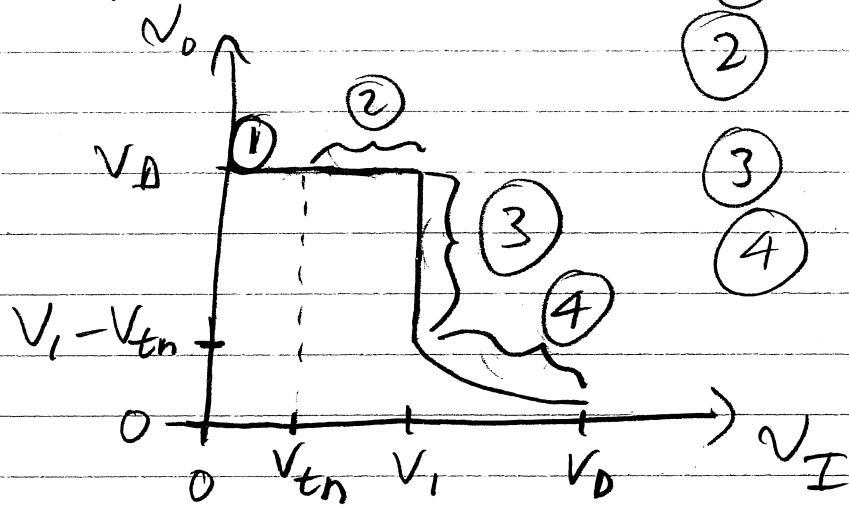

- ① CUTOFF
- ② ACTIVE BUT $I_D < I_X$
- ③ ACTIVE $I_D = I_X$
- ④ TRIODE

V_i OCCURS WHEN


$$I_D = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right) (V_i - V_{th})^2 = I_X$$

GAIN $\frac{V_o}{V_i}$ IN ③ IS ∞ !!

GC3A


IDEAL CURRENT SOURCE

THAT GOES TO $I=0$ IF $V \rightarrow 0$

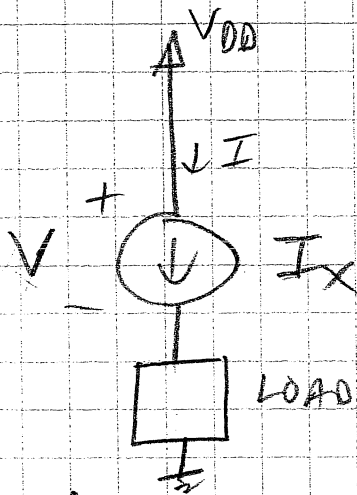


$$I = I_X \quad V > 0$$

$$I = 0 \quad V \leq 0$$

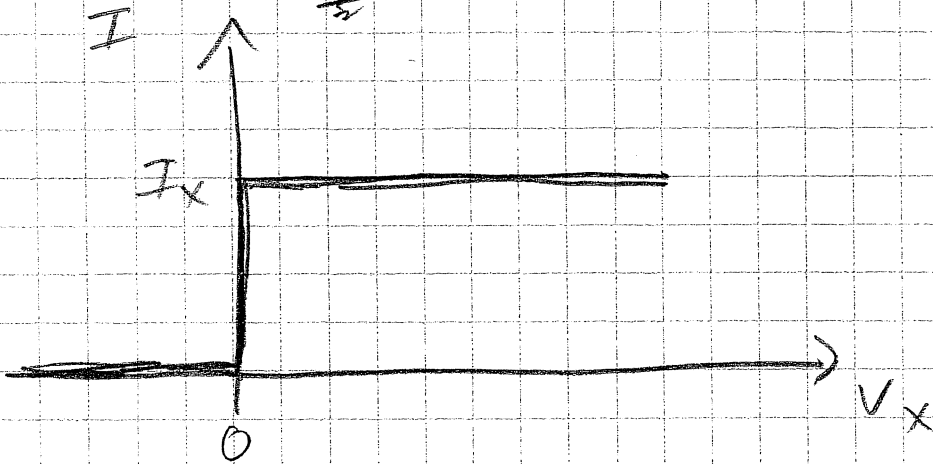

GCA

NOW ASSUME $\lambda \neq 0$ (r_o FINITE)

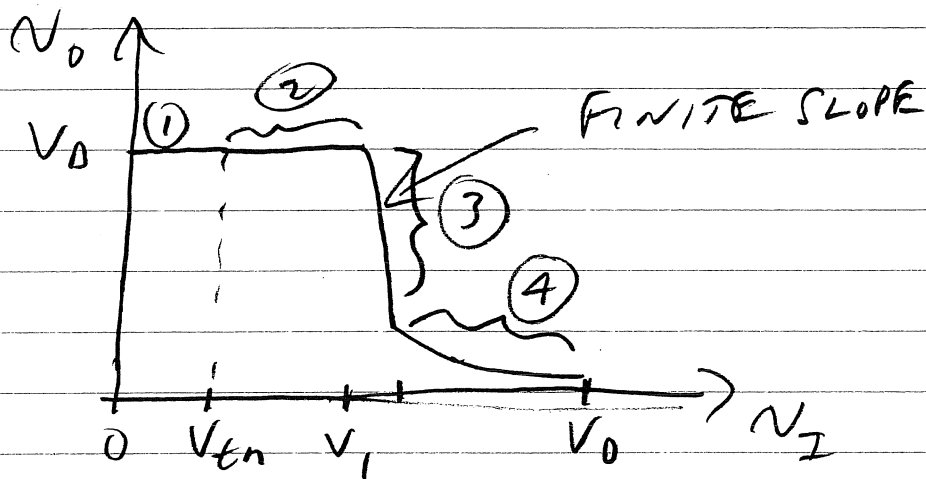

IN (3)

$$g_m = \frac{2I_D}{V_{OV}} \quad r_o = \frac{L}{\lambda I_D} = \frac{V_A' L}{I_D}$$


$$\frac{v_o}{v_i} = -g_m r_o = - \frac{2I_D}{V_{OV}} \frac{V_A' L}{I_D}$$
$$= - \frac{2V_A' L}{V_{OV}}$$

TYPICAL $V_{OV} \approx 0.2 \text{ V}$ } INTRINSIC GAIN
 $V_A' \approx 10 \text{ V}/\mu\text{m}$ } $\approx 20 \text{ V/V}$

$$L = 0.2 \mu\text{m}$$

(6C5)

BJT

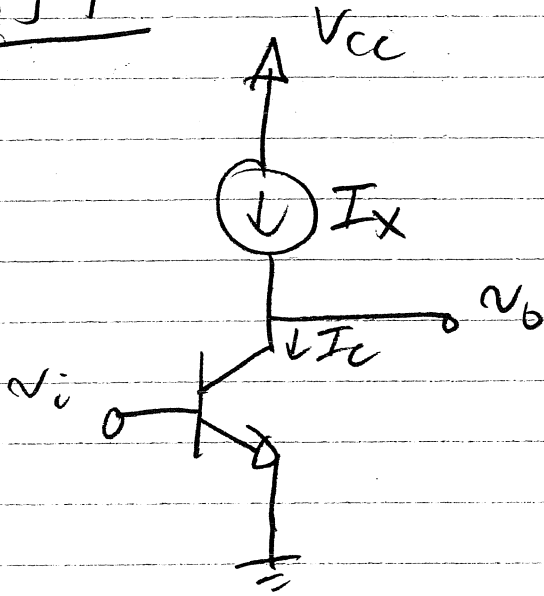

V_A FINITE

ACTIVE WHEN
 $I_C = I_x$

WHEN ACTIVE

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A}{I_C}$$

GAIN $\frac{v_o}{v_i} = -g_m r_o$

$$= - \frac{I_C}{V_T} \frac{V_A}{I_C} = - \frac{V_A}{V_T}$$

TYPICAL

$$V_A \approx 15 \text{ V}$$

$$V_T \approx 25 \text{ mV}$$


INTRINSIC
GAIN

$$\approx 600 \text{ V/V}$$

MUCH HIGHER
THAN MOSFETS

GCB


PRACTICAL CURRENT SOURCE LOAD

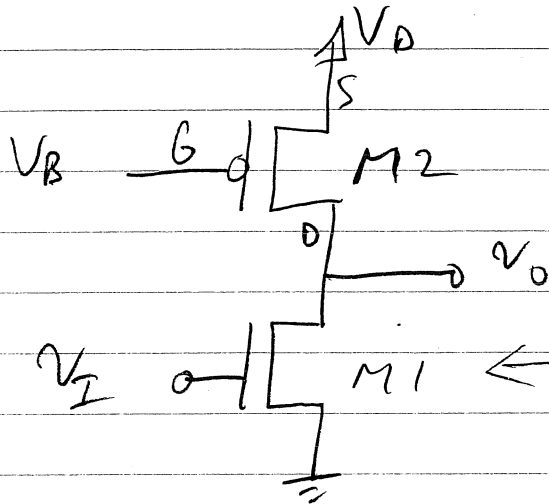

V_B IS CONSTANT DC VOLTAGE TO GENERATE I_x

v_I \rightarrow M1 $\leftarrow g_{m1}, r_{o1}$

SMALL-SIGNAL MODEL FOR M2

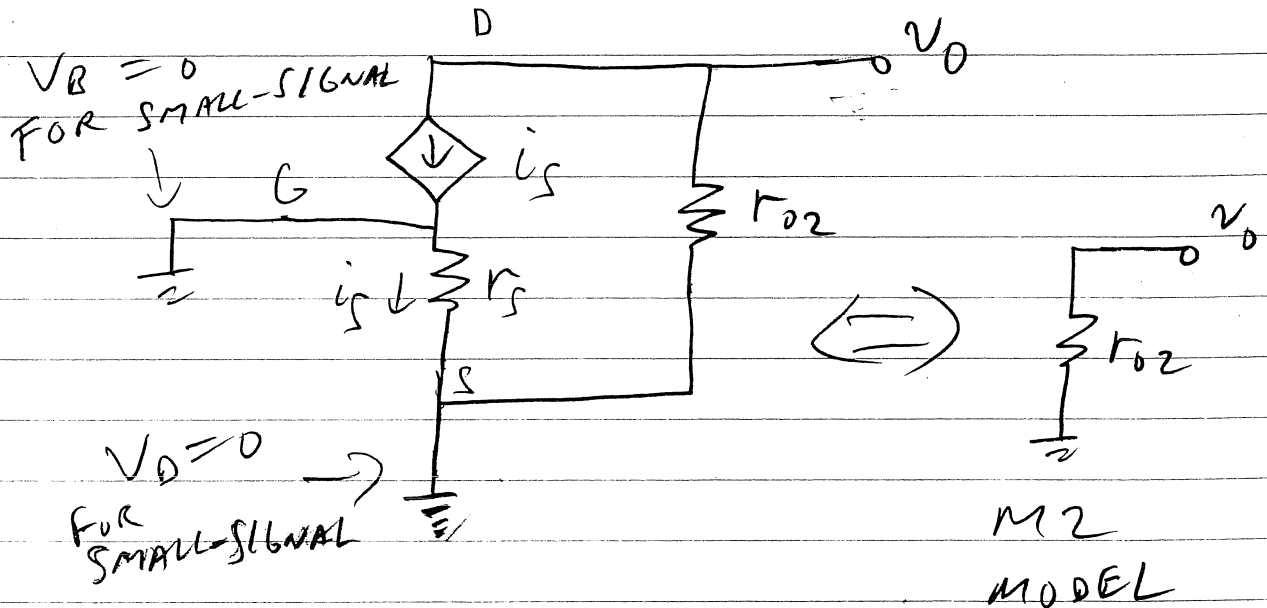

SO INTRINSIC GAIN IS

$$\frac{v_O}{v_I} = -g_{m1} (r_{o1} \parallel r_{o2}) = -\frac{1}{2} g_{m1} r_o$$

IF $r_o = r_{o1} = r_{o2}$