
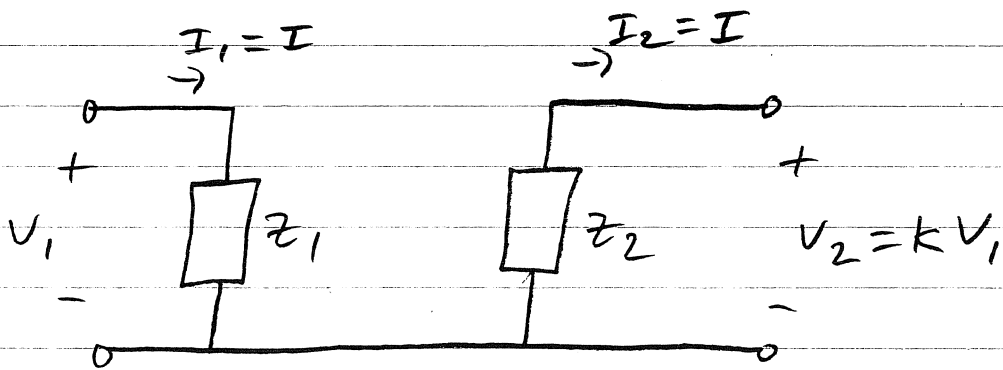
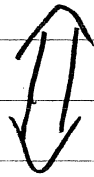


MILLER'S THEOREM

(MT1)

- USED TO BREAKUP A COUPLING
IMPEDANCE BETWEEN 2 NODES

GIVEN $V_2 = kV_1$ k IS GAIN FACTOR

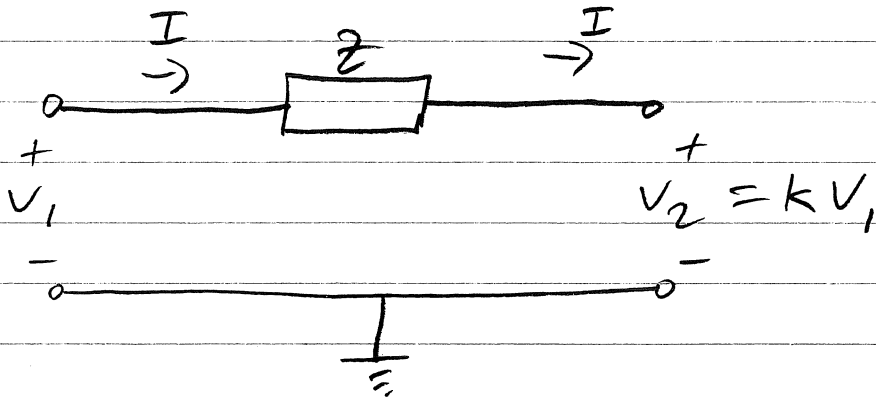

$$z_1 = z / (1 - k)$$

$$z_2 = z / (1 - \frac{1}{k})$$

MT2

PROOF $I_1 = \frac{V_1}{z_1} = I = \frac{V_1 - kV_1}{z} \Rightarrow z_1 = \frac{z}{1-k}$

$$I_2 = \frac{0 - V_2}{z_2} = I = \frac{V_1 - kV_1}{z} \Rightarrow z_2 = \frac{z}{(1 - \frac{1}{k})}$$

NOTE CANNOT USE MILLER'S THEOREM WHEN RATIO OF $\frac{V_2}{V_1}$ CHANGES SUCH AS CHANGING LOCATION OF SIGNAL SOURCE WHEN FINDING OUTPUT IMPEDANCE

IN CASE $z = R$ $\Rightarrow R_1 = \frac{R}{1-k}$



$$R_2 = \frac{R}{(1 - \frac{1}{k})}$$

IN CASE $z = \frac{1}{sC}$ $\Rightarrow C_1 = C(1-k)$

$$C_2 = C(1 - \frac{1}{k})$$

MT3

EX

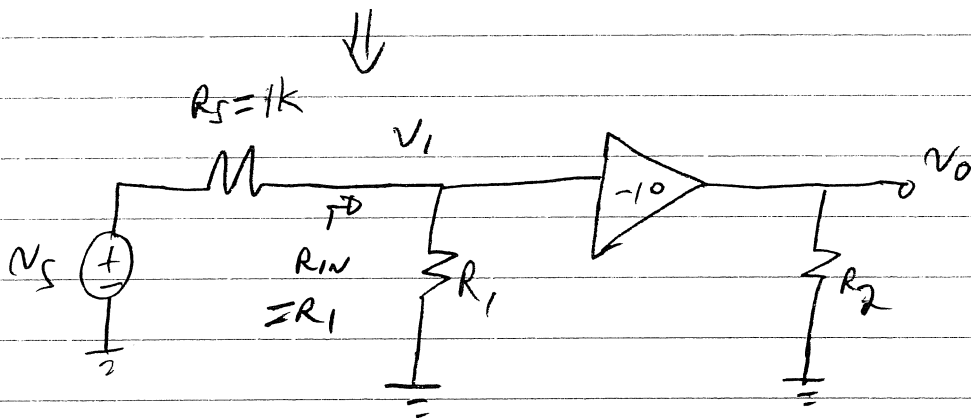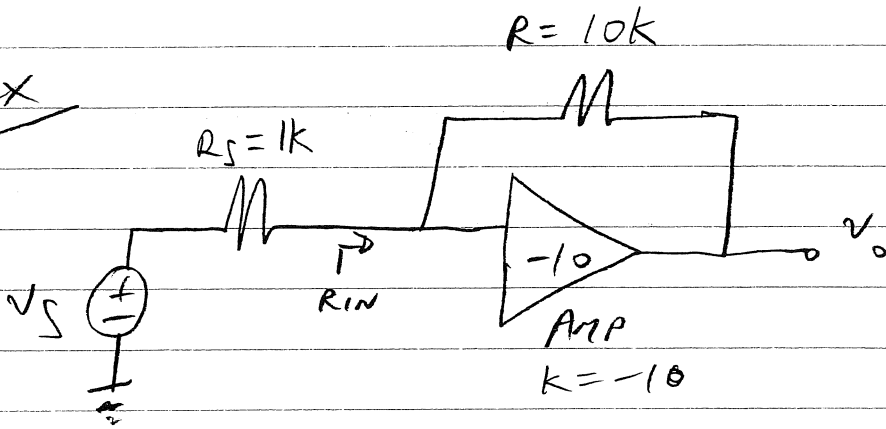

$$R_1 = \frac{R}{1-k} = \frac{10k}{1-(-10)} = \frac{10k}{11} = 909.1 \Omega$$

$$V_1 = \frac{R_1}{R_1 + R_S} V_S = 0.476 V_S$$


$$V_0 = -10 V_1 = -4.76 V_S$$

$$R_2 = \frac{R}{1-\frac{1}{k}} = \frac{10k}{1+(\frac{1}{10})} = 9.1k \approx R$$

NOT
MUCH
CHANGE

MTA


EX

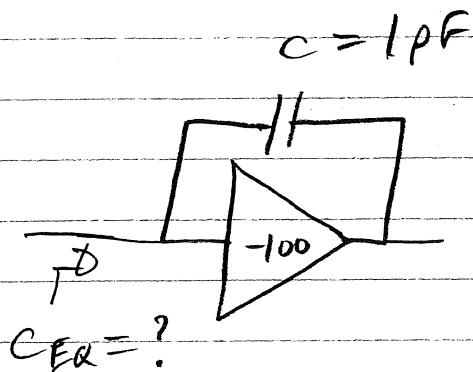

$$C_{EQ} = C(1 + 100) = 101C = 101 \text{ pF}$$

EX

BOOT STRAPPING

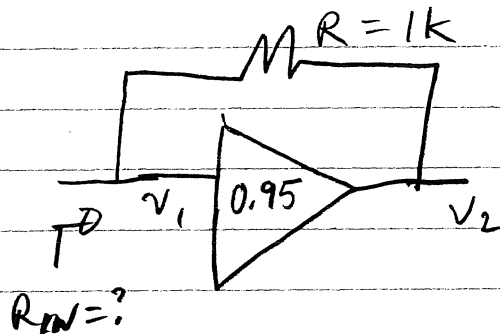

$$R_{IN} = \frac{R}{1 - 0.95} = \frac{R}{0.05} = 20R = 20 \text{ k}\Omega$$

SINCE $v_2 \approx v_1$ LITTLE CURRENT
FLOWS THROUGH R AND IMPEDANCE
INCREASED