



MULTI-STAGE AMPLIFIER HAND ANALYSIS

- THE PURPOSE OF CIRCUIT ANALYSIS IS TO GAIN INSIGHT INTO THE CIRCUIT OPERATION
- IF THE CIRCUIT DOES NOT MEET SPECIFICATIONS (GAIN, FREQ RESPONSE DISTORTION, NOISE, POWER SUPPLY REJECTION, ETC) WHAT CHANGES CAN BE MADE TO IMPROVE CIRCUIT.
- WE ARE GENERALLY FINE WITH UP TO 5% ERRORS (COMPARED TO EXACT ANALYSIS) SINCE HAND ANALYSIS TRANSISTOR MODELS ARE SIMPLIFIED AND IN EXACT (PERHAPS UP TO 15% IN ERROR)
- ONE HELPFUL APPROXIMATION IS TO ASSUME

$$\underline{g_m r_o \gg 1}$$

(OR $r_o \gg \frac{1}{g_m}$) (OR $r_o \gg r_s$)

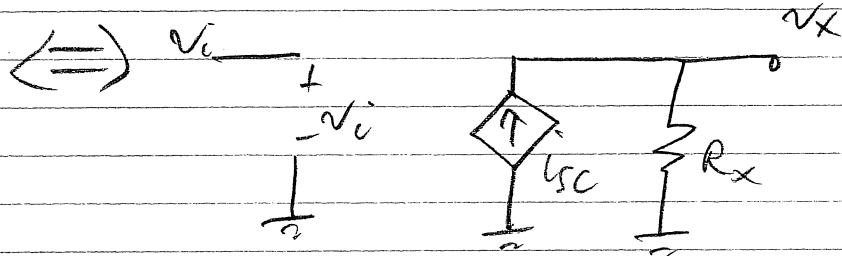
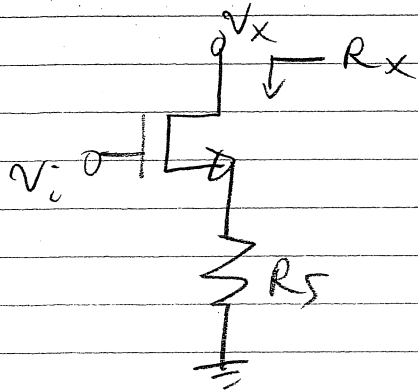
SMALL-SIGNAL MODELS (EXACT) (ALL TRANSISTORS IN ACTIVE REGION)



CS AMP

$$i_{sc} = \frac{-g_m v_o}{r_o + (1 + g_m r_o) R_S} v_i$$


$$R_x = r_o + (1 + g_m r_o) R_S$$

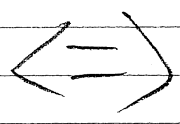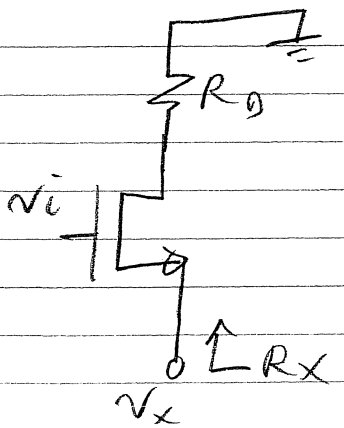

$$v_{oc} = \left(\frac{g_m r_o}{g_m r_o + 1} \right) v_i$$

$$R_x = \frac{r_o + R_D}{1 + g_m r_o}$$

CD AMP

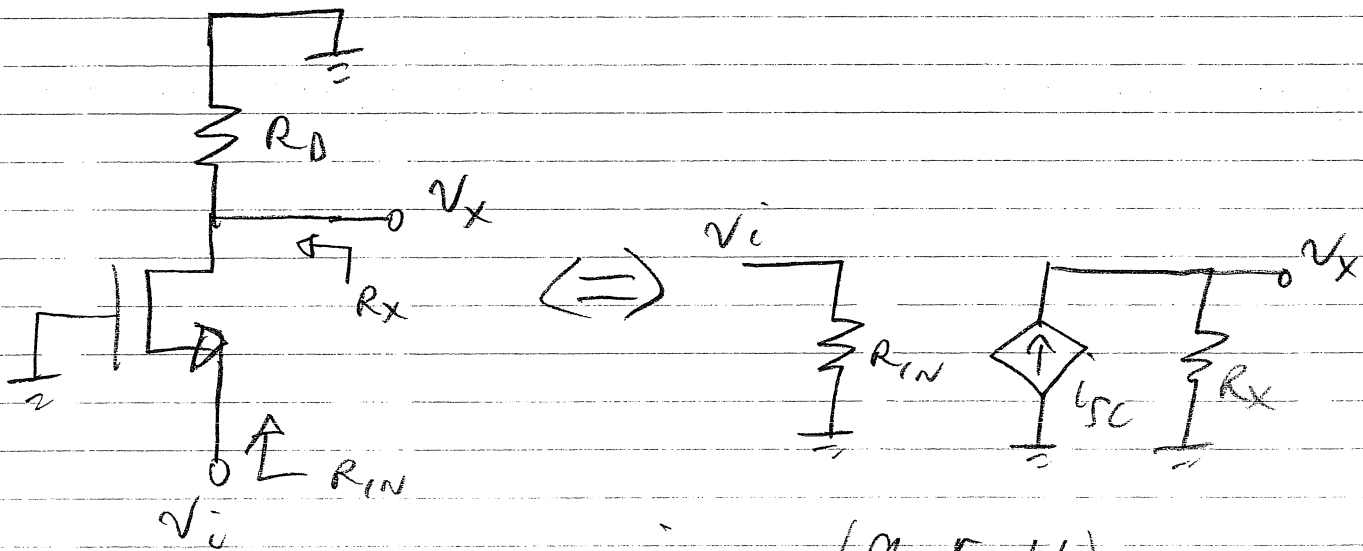

$$i_{SC} = \left(\frac{g_m r_o + 1}{r_o} \right) v_i$$



$$R_x = R_D \parallel r_o$$

$$R_{IN} = \frac{r_o + R_D}{1 + g_m r_o}$$

CG AMP

FOR $g_m r_o \gg 1$

(M53A)

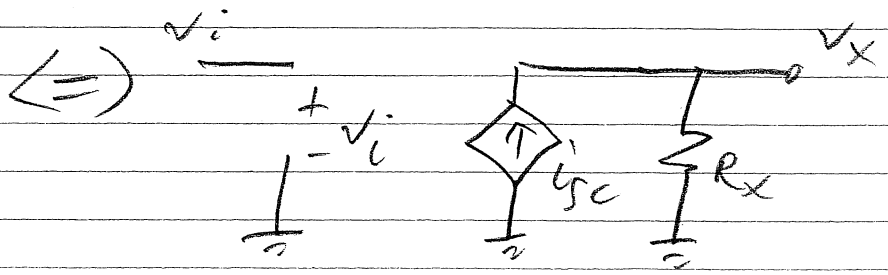
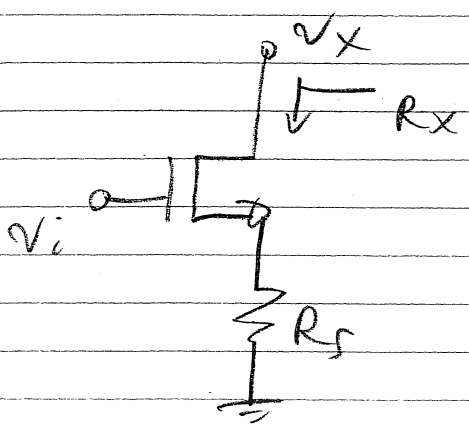


CS AMP

$$i_{sc} \approx \left(\frac{-1}{\frac{1}{g_m} + R_s} \right) v_i$$

$$R_x \approx (1 + g_m R_s) r_o$$

FOR $g_m r_o \gg 1$

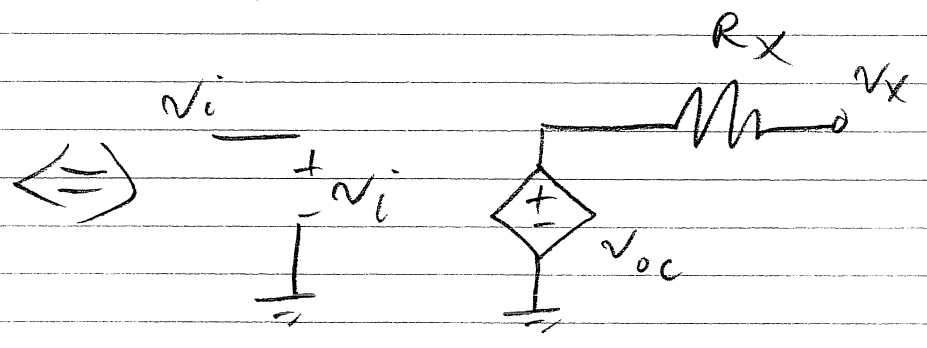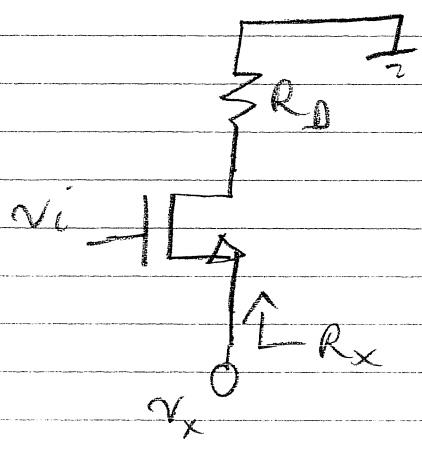


CD AMP

$$v_{oc} \approx v_i$$


$$R_x \approx \frac{1}{g_m} + \frac{R_D}{g_m r_o}$$

FOR $g_m r_o \gg 1$

M53B

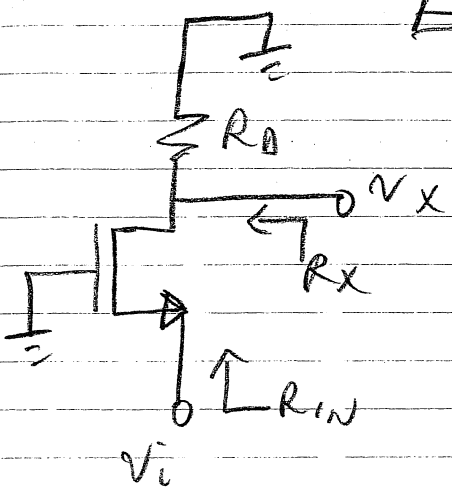

⇔

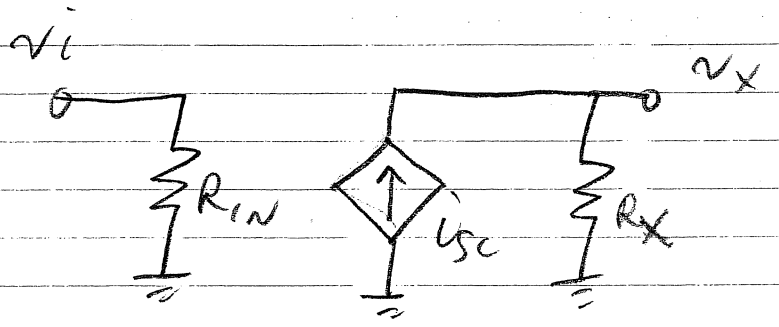

CG AMP

$$i_{sc} \approx g_m v_i$$

$$R_x = R_D \parallel r_o$$


$$R_{in} \approx \frac{1}{g_m} + \frac{R_D}{g_m r_o}$$

(MS4)

EXAMPLE 1

GIVEN $g_m = 1 \text{ mA/V}$ $r_o = 40 \text{ k}\Omega$

(HERE $g_m r_o = 40$)

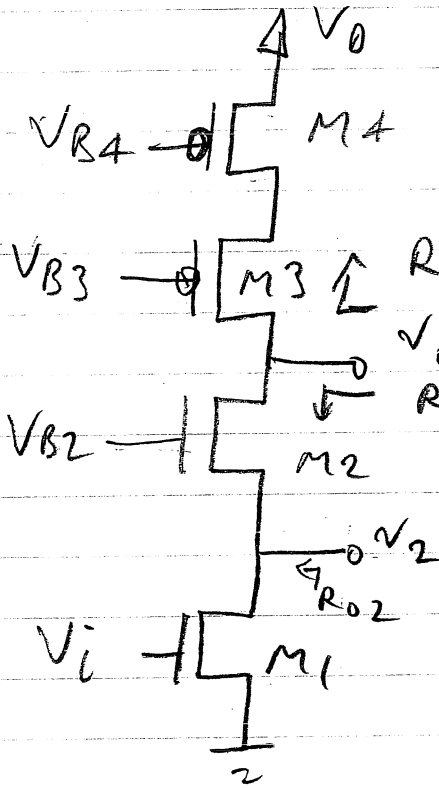

$$R_{OP} = (1 + g_{m3} r_{o4}) r_{o3} \approx g_m r_o^2 = 1.6 \text{ M}\Omega$$

$$R_{ON} = (1 + g_{m2} r_{o1}) r_{o2} \approx g_m r_o^2 = 1.6 \text{ M}\Omega$$

$$R_{o2} = r_{o1} \parallel \left(\frac{1}{g_{m2}} + \frac{R_{OP}}{g_m r_o} \right)$$

$$R_{o2} = r_{o1} \parallel \left(\frac{1}{g_{m2}} + r_o \right) \approx \frac{r_o}{2}$$


$$v_2 = -g_{m1} R_{o2} v_i = -\frac{g_{m1} r_o}{2} v_i$$

$$= -20 v_i$$

$$\frac{v_2}{v_i} = -20 \text{ V/V}$$

FOR $\frac{v_o}{v_i}$

NOTE

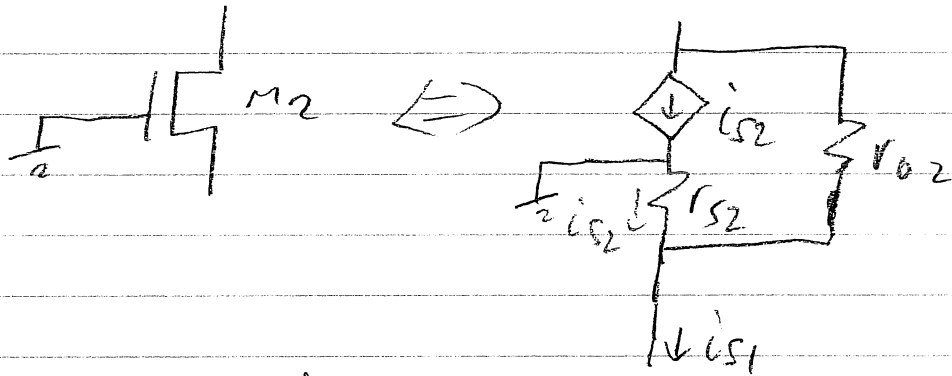

MOST OF i_{s1} GOES THROUGH r_{s2}
 SINCE $r_{o2} \gg r_{s2} = \frac{1}{g_{m2}}$

$$v_o = -g_{m1} \left(\frac{g_m r_o}{2} \right) v_i$$

$$\frac{v_o}{v_i} = - \frac{(g_m r_o)^2}{2} = - 800 \frac{V}{V}$$

ALTERNATIVE

FOR $\frac{N_o}{N_i}$


MSSA

$$N_o \approx q_{m2} (r_{o2} \parallel R_{op}) \approx q_{m2} r_{o2} N_2$$

$$\frac{N_o}{N_2} \approx q_{m2} r_{o2}$$

$$\begin{aligned} \frac{N_o}{N_i} &= \frac{N_o}{N_2} \times \frac{N_2}{N_i} = (q_{m2} r_{o2}) \left(-\frac{q_{m2} r_{o2}}{2} \right) \\ &= -\frac{(q_{m2} r_{o2})^2}{2} = -800 \frac{V}{V} \end{aligned}$$

EXAMPLE 2

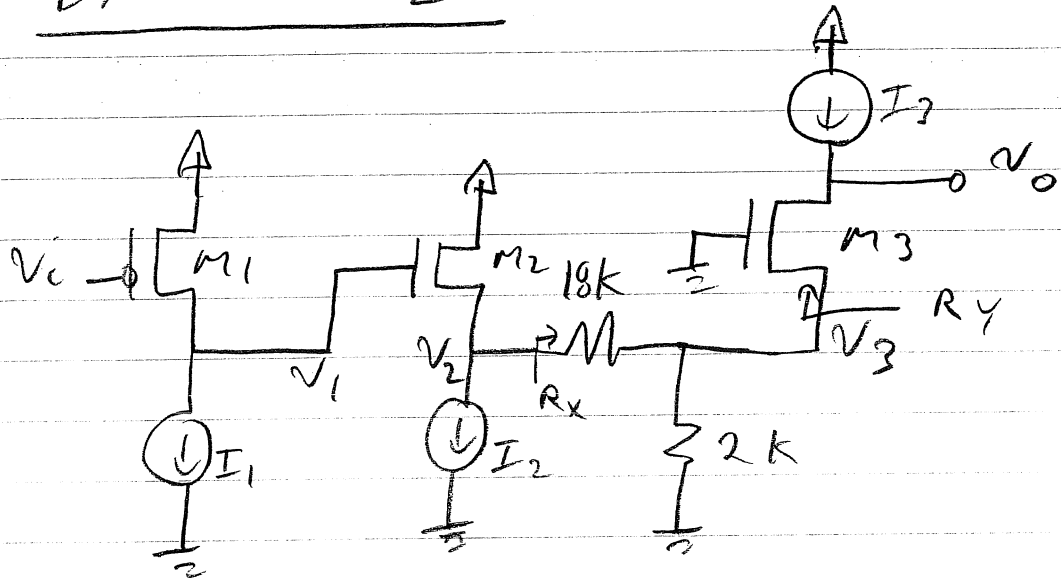

EACH TRANSISTOR HAS $g_m = 1 \text{ mA/V}$
 $r_o = 40 \text{ k}$

AND EACH CURRENT SOURCE
 HAS $r_o = 40 \text{ k}$

FIND $\frac{V_o}{V_c}$

$$\frac{V_1}{V_c} = -g_{m1} \left(\frac{r_o}{2} \right) = \underline{\underline{-20 \frac{V}{V}}}$$

$$\frac{V_2}{V_1} = \frac{r_o \parallel R_x}{r_o \parallel R_x + \frac{1}{g_{m2}}}$$

$R_y = \frac{2}{g_{m3}} = 2 \text{ k}$

$$R_x = 18 \text{ k} + \left[2 \text{ k} \parallel \left(\frac{1}{g_{m3}} + \frac{r_o}{g_{m3} r_{o3}} \right) \right]$$

1757

$$R_x = 18k + (2k \parallel 2k) = 19k$$

$$\frac{v_2}{v_1} = \frac{(40k \parallel 19k)}{(40k \parallel 19k) + 1k} = \frac{12.88}{13.88} = 0.928$$

$$\frac{v_2}{v_1} = \underline{\underline{0.928}} \quad \frac{V}{V}$$

$$\frac{v_3}{v_2} = \frac{(R_4 \parallel 2k)}{(R_4 \parallel 2k) + 18k} = \frac{1}{1 + 18k} = 0.0526$$

$$\frac{v_3}{v_2} = \underline{\underline{0.0526}}$$


$$\frac{v_0}{v_3} = g_{m3} \left(\frac{r_o}{2} \right) = \underline{\underline{20}} \quad \frac{V}{V}$$

$$\frac{v_0}{v_i} = \frac{v_1}{v_0} \times \frac{v_2}{v_1} \times \frac{v_3}{v_2} \times \frac{v_0}{v_3} = -19.53 \quad \frac{V}{V}$$


DERIVATIONS OF

(MSB)

MODELS

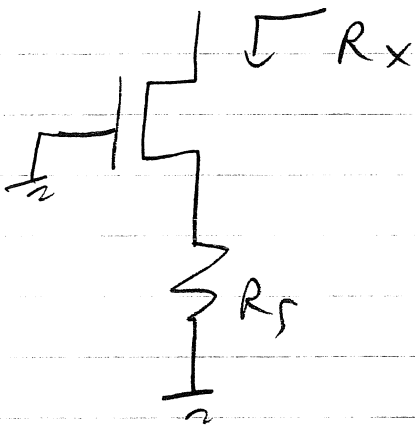
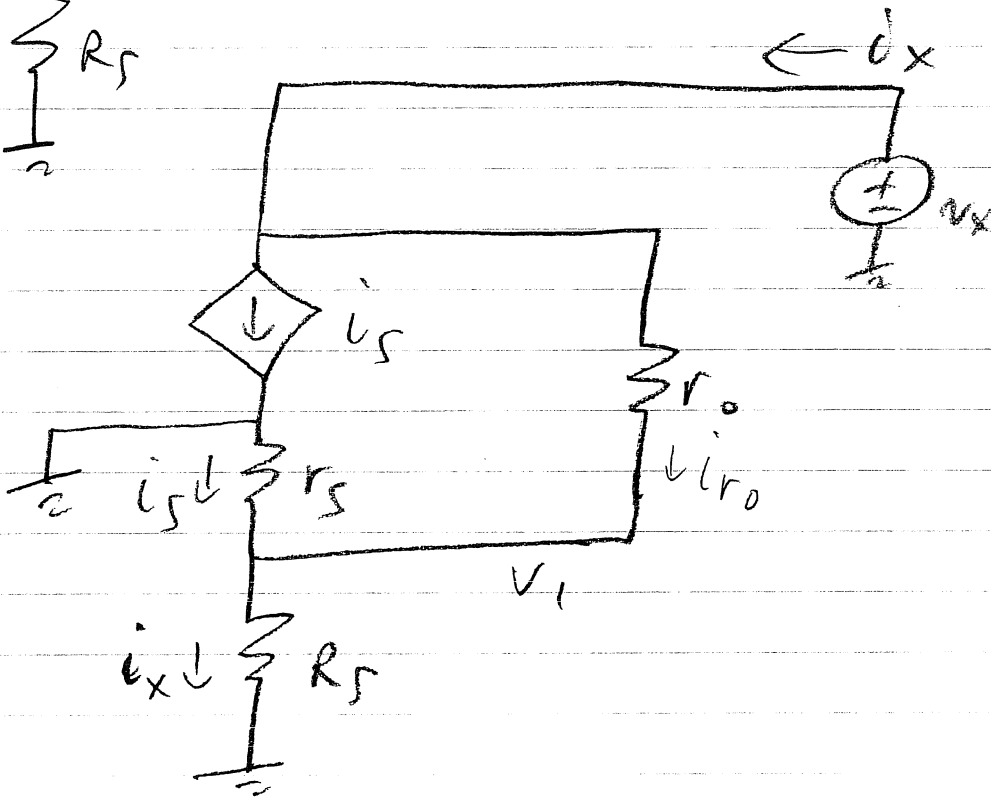
$$\text{FOR } R_x \equiv \frac{v_x}{i_x}$$



$$v_1 = i_x R_S \quad i_s = -\frac{v_1}{r_o} = -\frac{i_x R_S}{r_o}$$

$$i_{r_o} = \frac{v_x - v_1}{r_o} = \frac{v_x - i_x R_S}{r_o}$$

$$i_x = i_s + i_{r_o} = -\frac{i_x R_S}{r_o} + \frac{v_x - i_x R_S}{r_o}$$

M59

$$i_x \left(1 + \frac{R_S}{r_o} + \frac{R_S}{r_o} \right) = \left(\frac{1}{r_o} \right) v_x$$

SINCE $r_s = \frac{1}{g_m}$

$$R_x \equiv \frac{v_x}{i_x} = R_S + r_o + g_m r_o R_S$$


$$\underline{\underline{R_x = r_o + (1 + g_m r_o) R_S}}$$

FOR $g_m r_o \gg 1$

$$R_x \approx r_o + g_m r_o R_S$$

$$\underline{\underline{R_x \approx (1 + g_m R_S) r_o}}$$

FOR isc START WITH V_{oc}

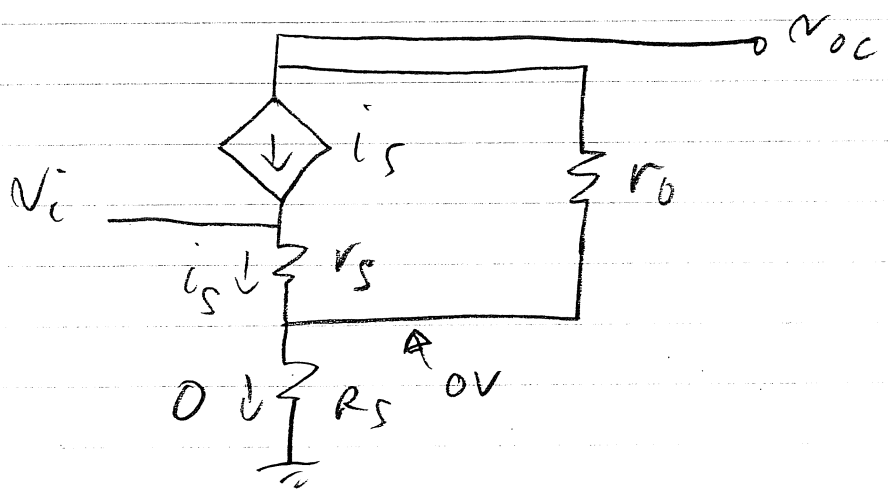

(MS10)

$$V_{oc} = - \frac{r_o}{r_s} v_i = -g_m r_o v_i$$



THEVENIN \Rightarrow NORTON

$$i_{sc} = \frac{V_{oc}}{R_x} v_i = \frac{-g_m r_o}{(1 + g_m r_s) r_o} v_i$$

$$= \frac{-g_m}{1 + g_m r_s} v_i$$

$$i_{sc} = \left(\frac{-1}{\frac{1}{g_m} + r_s} \right) v_i$$

M511

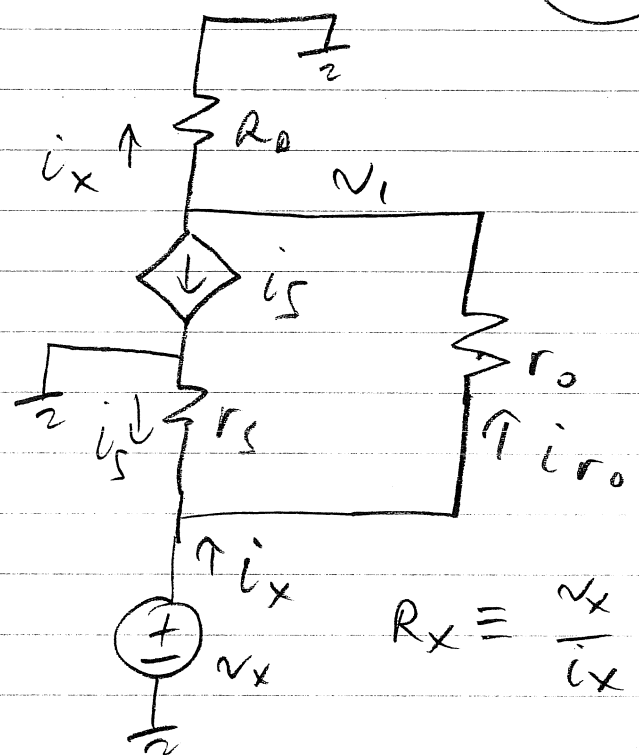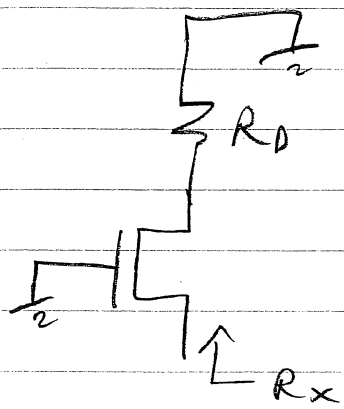

$$v_1 = i_x R_D$$

$$i_s = \frac{-v_x}{r_s} \quad i_{r_o} = \frac{v_x - v_1}{r_o} = \frac{v_x - i_x R_D}{r_o}$$

$$-i_s + i_{r_o} = i_x$$


$$\frac{v_x}{r_s} + \frac{v_x - i_x R_D}{r_o} = i_x$$

$$i_x \left(1 + \frac{R_D}{r_o} \right) = v_x \left(\frac{1}{r_s} + \frac{1}{r_o} \right)$$

$$R_x \equiv \frac{v_x}{i_x} = \frac{1 + \frac{R_D}{r_o}}{\frac{1}{r_s} + \frac{1}{r_o}} = \frac{r_o + R_D}{1 + g_m r_o}$$

$$R_x \approx \frac{r_o + R_D}{g_m r_o} = \frac{1}{g_m} + \frac{R_D}{g_m r_o}$$

FOR v_{oc}

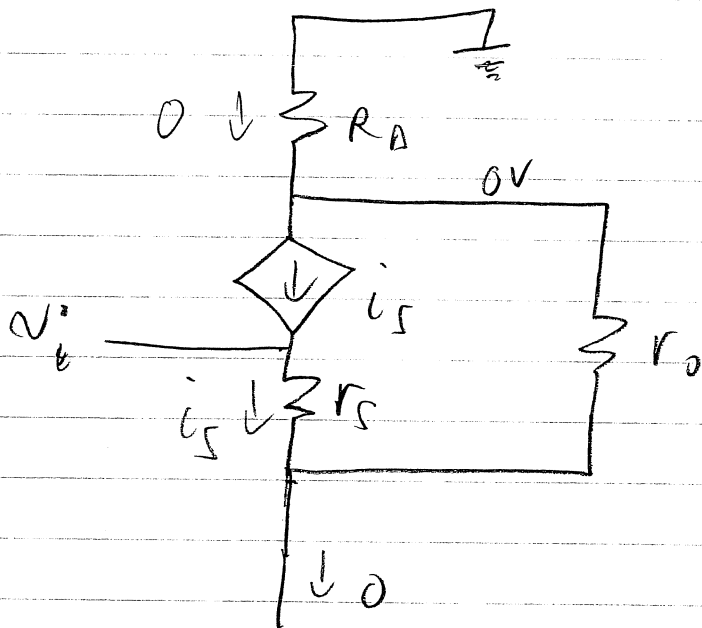

$$v_{oc} = \frac{r_o}{r_o + r_s} v_i$$

$$= \frac{g_m r_o}{g_m r_o + 1} v_i$$

$$\underline{\underline{v_{oc} \approx v_i}}$$