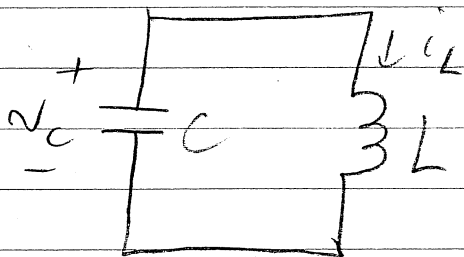


NEGATIVE RESISTANCE

- CAN CREATE NEGATIVE RESISTANCE USING FEEDBACK
- WHY?? => USEFUL FOR OSCILLATORS AND LATCHES

OSCILLATORS



IF IDEAL C & L
(NO RESISTANCES)


THEN IF INITIAL v_c (OR i_L)

WILL OSCILLATE AT


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

POLES AT $\pm j\omega_0$

s - PLANE

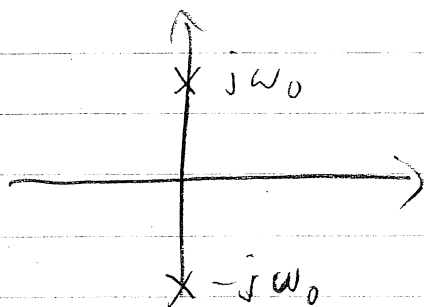


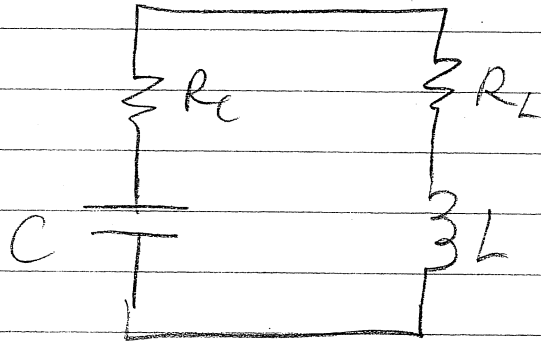HOWEVER, IN PRACTICE INDUCTOR HAS SERIES R_L & CAPACITOR HAS SERIES, R_C



R_C & R_L CAUSE DAMPING & POLES IN LEFT HALF PLANE


CAN MODEL ABOVE AS PARALLEL CIRCUIT

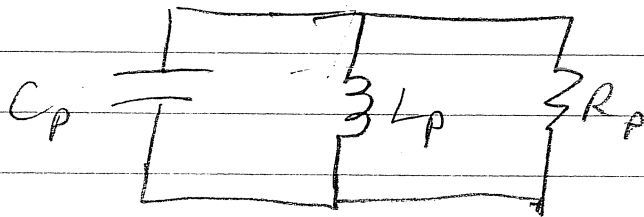

AT NARROWBAND FREQ NEAR OSC FREQ


(NOTE $C_p \neq C$
 $L_p \neq L$
 $R_p \neq R_C + R_L$)

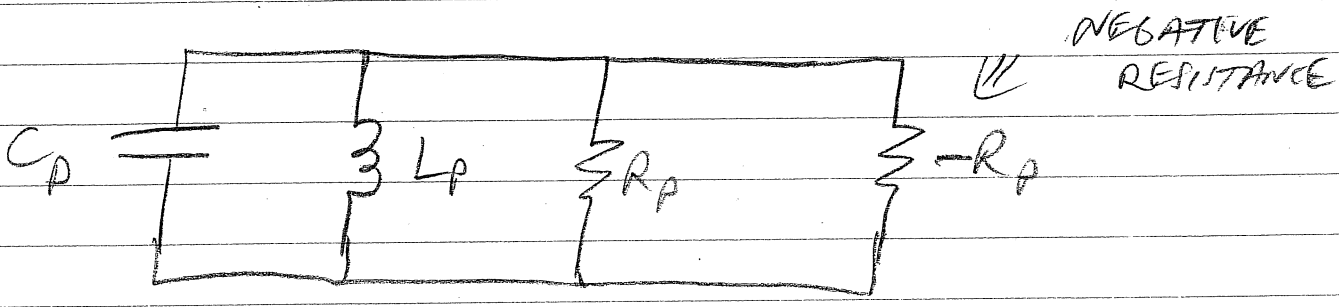SO TO CREATE AN OSCILLATOR
NEED NEGATIVE RESISTANCE



(MAKE $|-R_p| > R_p$ - SO OSCILLATION GROWS)
 THEN LET NON-LINEARITIES KEEP OSCILLATION
AMPLITUDE STABLE

USING MILLER EFFECT

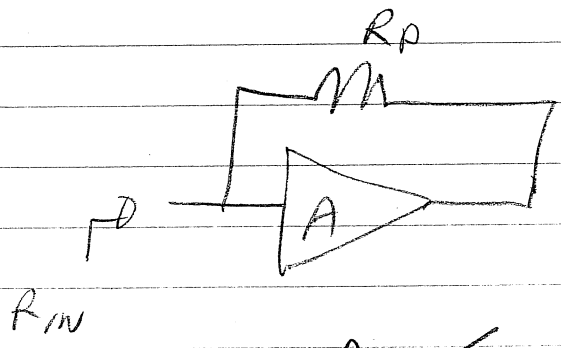


$$R_{in} = R_p / (1 - A) \quad \text{IF } A = -2$$


$$R_{in} = -R_p$$

MORE COMMON APPROACH


CROSS COUPLED TRANSISTORS

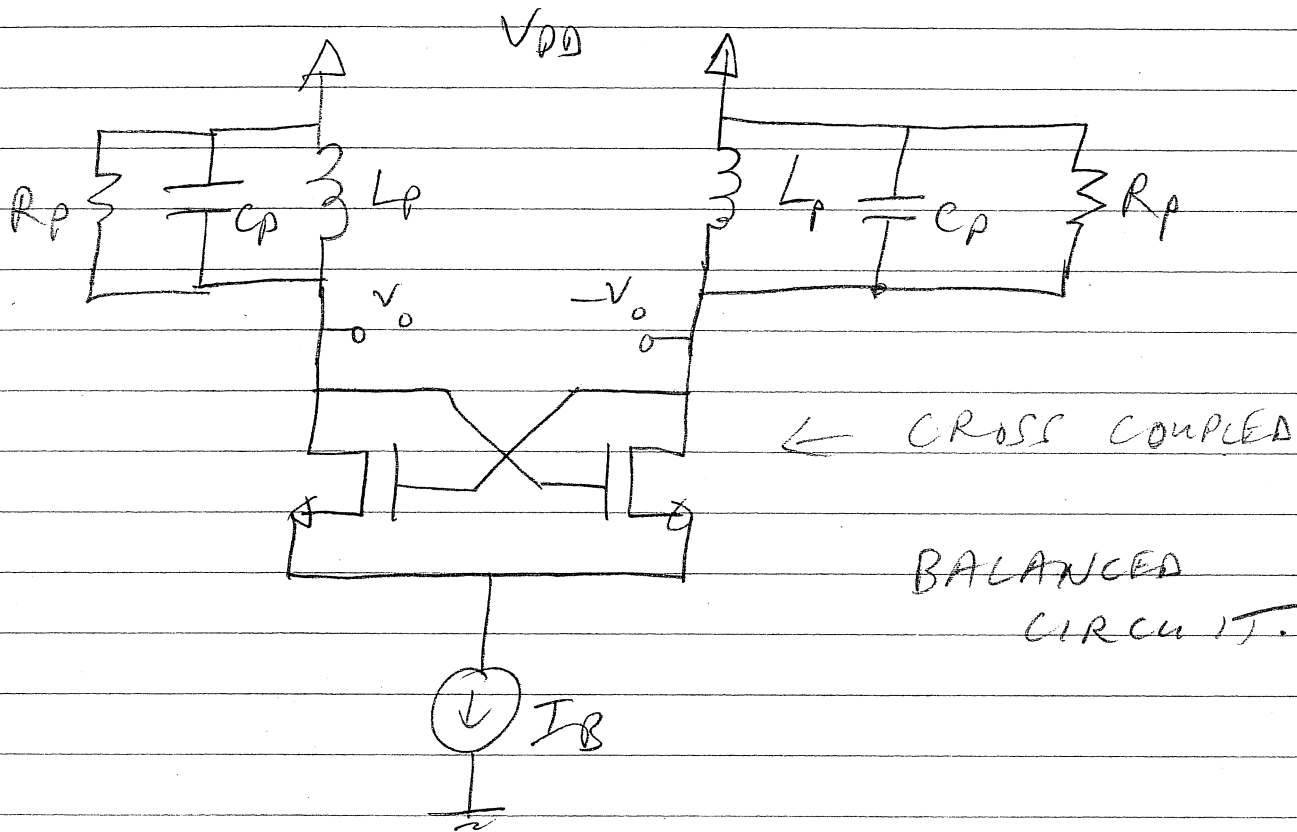

HALF CIRCUIT

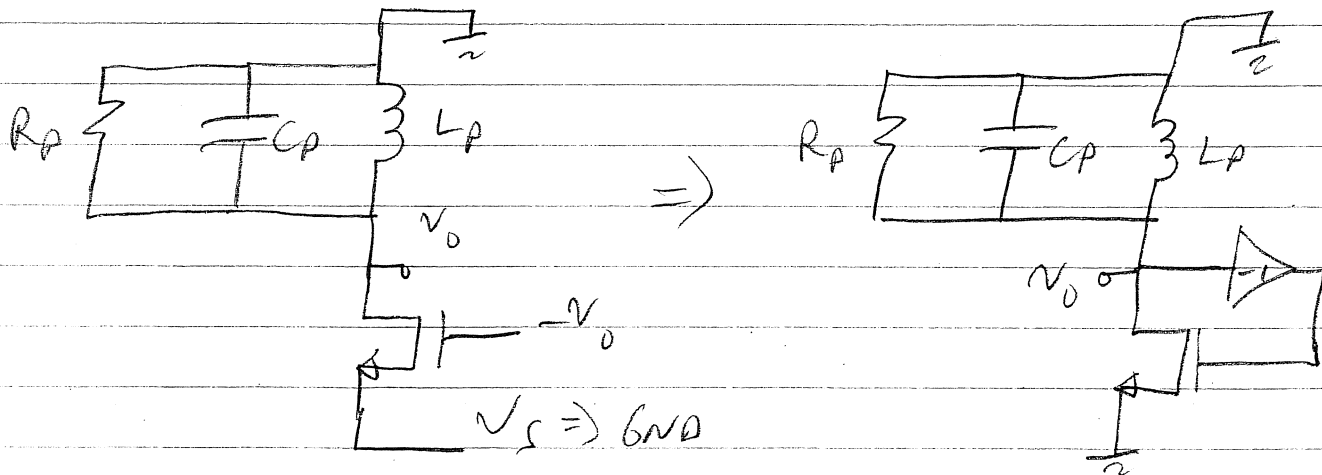

NR5

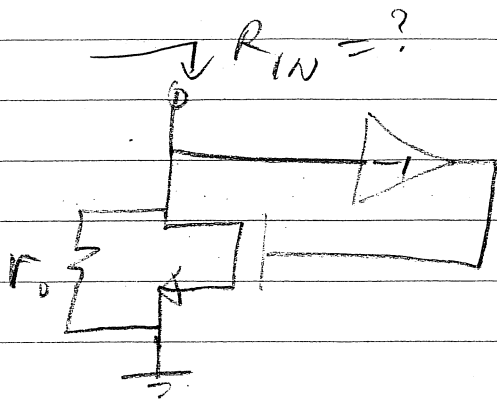

NOTE: -ive
SIGN



$$R_{p0} = r_o \quad L_S = 0 \quad L_o = -g_m r_o$$

$$R_{in} = R_{p0} \left[\frac{1 + L_S}{1 + L_o} \right]$$

$$R_{in} = \frac{r_o}{1 - g_m r_o} = r_o \parallel -\frac{1}{g_m}$$

$$\boxed{R_{in} = r_o \parallel -\frac{1}{g_m}} \quad \text{SET } R_{in} = -R_p$$