

POWER AMPLIFIERS

- DELIVERS SIGNIFICANT POWER TO OUTPUT LOAD
- SHOULD HAVE LOW OUTPUT IMPEDANCE
- USUALLY REQUIRES LOW THD (TOTAL HARMONIC DISTORTION)

$$THD = \frac{RMS \text{ OF HARMONICS}}{RMS \text{ OF FUNDAMENTAL}}$$

- SHOULD BE EFFICIENT

$$\eta = \frac{LOAD \text{ POWER } (P_L)}{SUPPLY \text{ POWER } (P_S)}$$

100% EFFICIENT ALL SUPPLY P_S GOES TO LOAD

50% EFFICIENT HALF OF P_S GOES TO LOAD

- USUALLY THERMAL DISSIPATION OF HEAT IN POWER TRANSISTORS IS IMPORTANT CONSIDERATION.

- CLASS A OUTPUT STAGE

- ⇒ OUTPUT TRANSISTOR ALWAYS CONDUCTING (100% CONDUCTING)
- ⇒ GOOD LINEARITY
POOR EFFICIENCY

- CLASS B

- ⇒ OUTPUT TRANSISTOR CONDUCTS ONLY WHEN $v_o > 0$ (50% CONDUCTING)
(A DIFFERENT OUTPUT TRANSISTOR CONDUCTS WHEN $v_o < 0$)
- ⇒ POORER LINEARITY
BETTER EFFICIENCY

- CLASS AB

- ⇒ SOME OVERLAP WHEN BOTH TRANSISTORS CONDUCTING (>50% CONDUCTING)
- ⇒ BETTER LINEARITY
EFFICIENCY BETTER THAN A
SLIGHTLY WORSE THAN B

A
= B
=

OTHER CLASSES (NOT COVERED)

- CLASS C $< 50^{\circ}$ CONDUCTING

⇒ INTO TUNED OUTPUT STAGE
(RF AMP)

- CLASS D HIGHLY EFFICIENT


USES PULSE-WIDTH MODULATION
OR PULSE DENSITY MODULATION

TRANSISTOR EITHER OFF OR ON
(USED AS A SWITCH)

REQUIRES FILTER TO REMOVE
HIGH FREQUENCY PULSE-FREQUENCY
HARMONICS

(PA3A)

RECALL FOR BJT

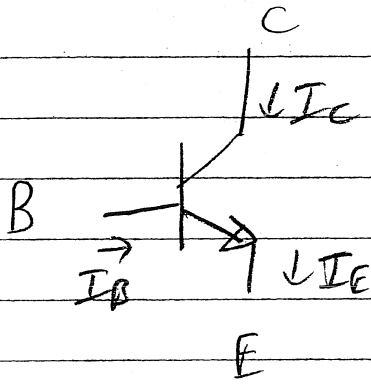

$$I_E = I_C + I_B$$

ACTIVE

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\alpha \equiv \frac{\beta}{\beta + 1}$$

$$I_C = \beta I_B$$


$$g_m = \frac{I_C}{V_T}$$

$$r_e = \frac{\alpha}{g_m} = \frac{V_T}{I_E}$$

SATURATION

$$V_{CE \text{ SAT}} \approx 0.2 \text{ V}$$

POWER DISSIPATION OF A CIRCUIT ELEMENT

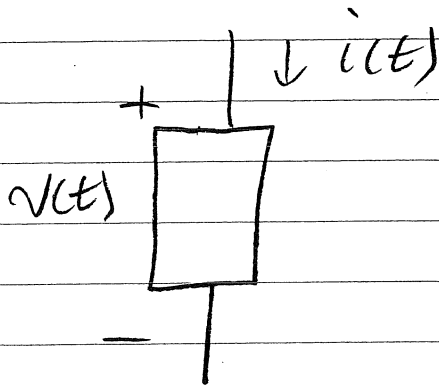

INSTANTANEOUS POWER
DISSIPATED

$$P(t) = v(t) i(t)$$

AVERAGE POWER DISSIPATED

$$P_D = \frac{1}{T} \int_0^T P(t) dt \quad \text{AS } T \rightarrow \infty$$

$$P_D = \frac{1}{T} \int_0^T v(t) i(t) dt$$

RESISTOR

IF CIRCUIT IS A RESISTOR $i(t) = \frac{v(t)}{R}$

$$P_R = \frac{1}{T} \int_0^T v(t) \frac{v(t)}{R} dt$$

$$= \frac{1}{R} \left[\frac{1}{T} \int_0^T v^2(t) dt \right]$$


← MEAN SQUARED VOLTAGE

$$= \frac{(V_{RMS})^2}{R}$$

IF $v(t) = \hat{V}_0 \sin(\omega t)$

$V_{RMS} = \frac{\hat{V}_0}{\sqrt{2}}$

IF $v(t) = V_{oc}$

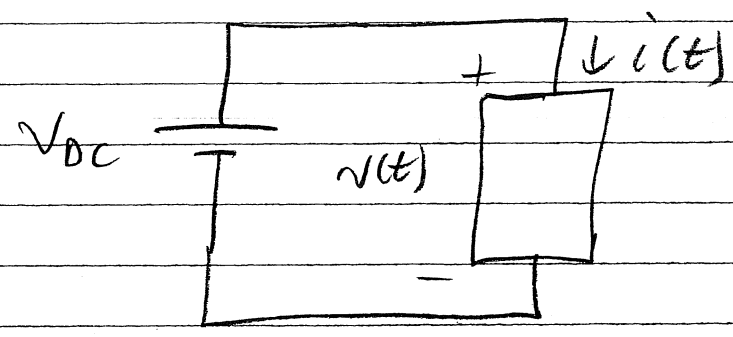


$P_D = \frac{1}{T} \int_0^T v(t) i(t) dt$

$= \frac{1}{T} \int_0^T V_{oc} i(t) dt$

$= V_{oc} \left[\frac{1}{T} \int_0^T i(t) dt \right]$

$P_D = V_{oc} I_{AVERAGE}$ $I_{AVERAGE} = \frac{1}{T} \int_0^T i(t) dt$

CLASS A

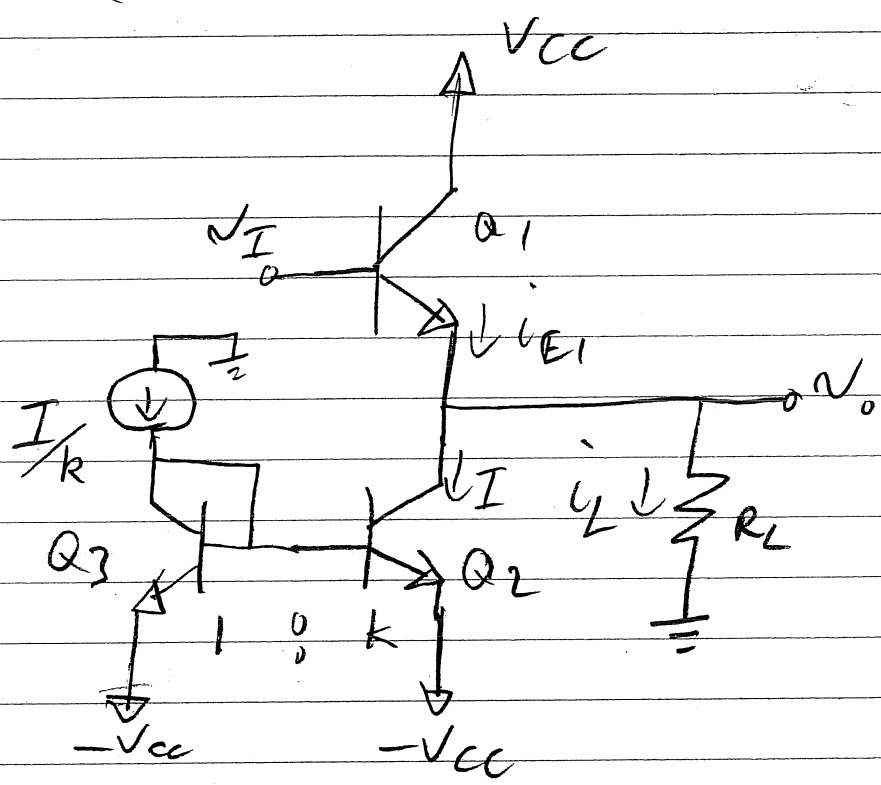

$$A_{BE2} = k \times A_{BE3}$$

$A_{BE} \Rightarrow$ AREA OF BASE EMITTER

Q_3 IS TO BIAS Q_2

ASSUME $k \gg 1$ SO CAN IGNORE $\frac{I}{k}$ CURRENT

PAS

$$V_o = V_I - N_{BE} I$$

$$V_{o \text{ MAX}} = V_{CC} - V_{CE1 \text{ SAT}} \quad \underline{\text{MAX } V_o}$$

$$V_{o \text{ MIN}} = -I R_L \quad \underline{\text{MIN } V_o}$$

OR

$$V_{o \text{ MIN}} = -V_{CC} + V_{CE2 \text{ SAT}}$$


$$\text{IF } I \geq \frac{|-V_{CC} + V_{CE2 \text{ SAT}}|}{R_L}$$

SIGNAL WAVEFORMS

ASSUME $V_{CE \text{ SAT}} = 0$ $V_{BE} = 0$

$$I = \frac{V_{CC}}{R_L}$$

$$V_{I} = V_{CC} \sin(\omega t)$$

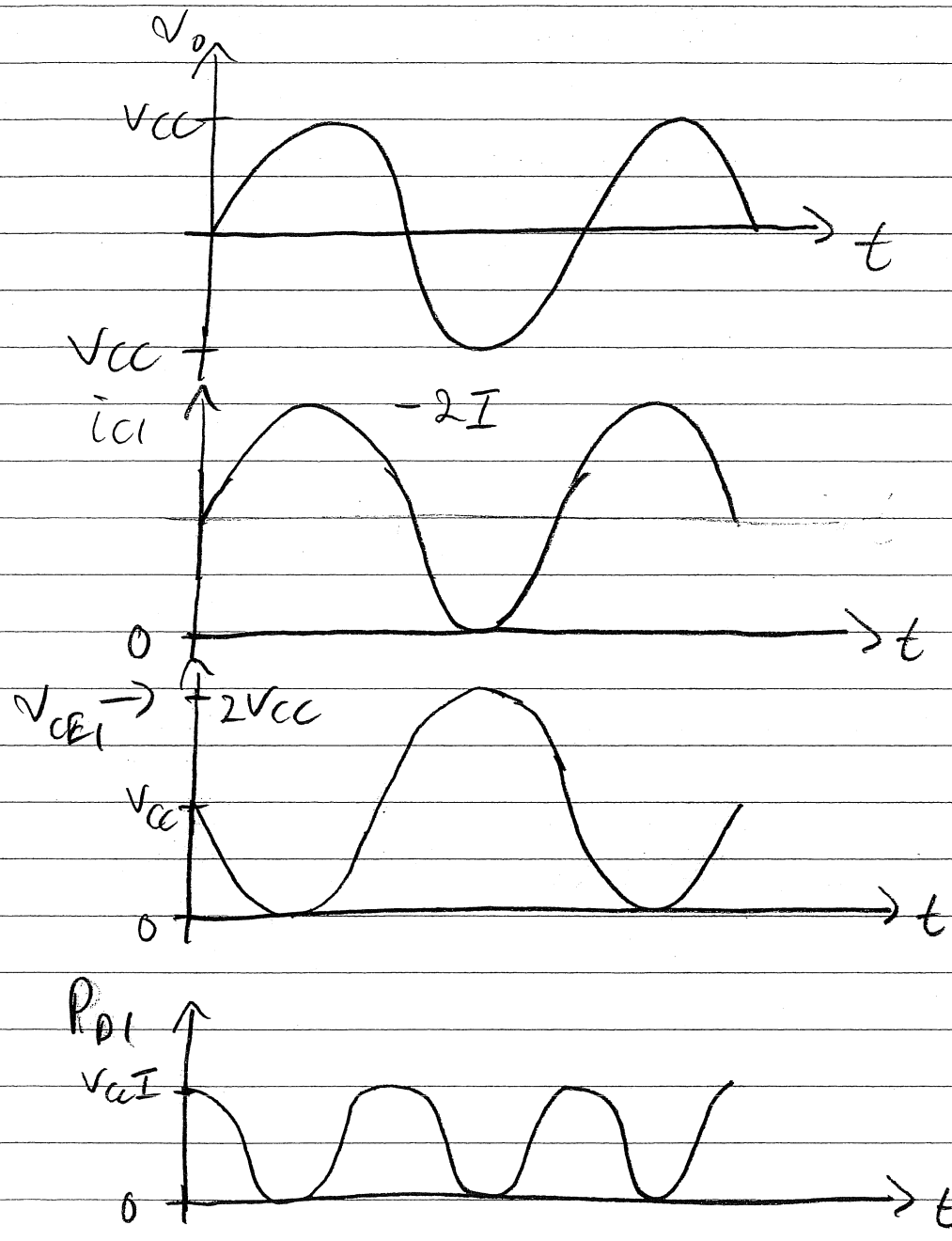

POWER DISSIPATED BY Q_1

$$P_{D1} \equiv V_{CE1} i_{C1}$$

INSTANTANEOUS POWER DISSIPATION IN Q_1

EFFICIENCY

$$\eta \equiv \frac{P_L}{P_L}$$

ASSUME $v_o = \hat{V}_o \sin(\omega t)$

$$P_L = \frac{(\hat{V}_o/\sqrt{2})^2}{R_L} = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$P_S = P_{S+} + P_{S-} = V_{CC} I + (-V_{CC})(-I)$$

$$P_S = 2V_{CC} I$$

$$\eta = \frac{P_L}{P_S} = \frac{1}{4} \left(\frac{\hat{V}_o}{IR_L} \right) \left(\frac{\hat{V}_o}{V_{CC}} \right)$$



SINCE $\hat{V}_o \leq V_{CC}$ & $\hat{V}_o \leq IR_L$

MAX η OCCURS WHEN $\hat{V}_o = V_{CC} = IR_L$

$$\eta_{\text{MAX}} = \frac{1}{4} = \underline{\underline{25\%}}$$


POOR EFFICIENCY

CLASS B

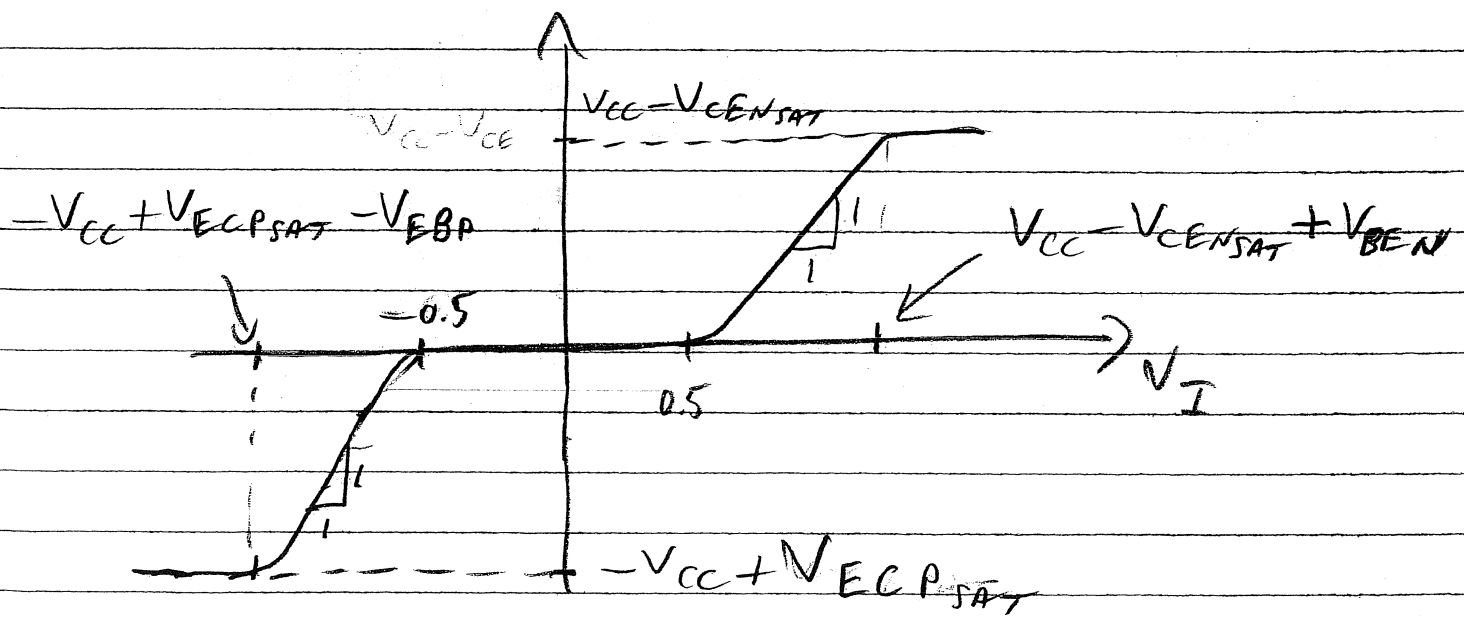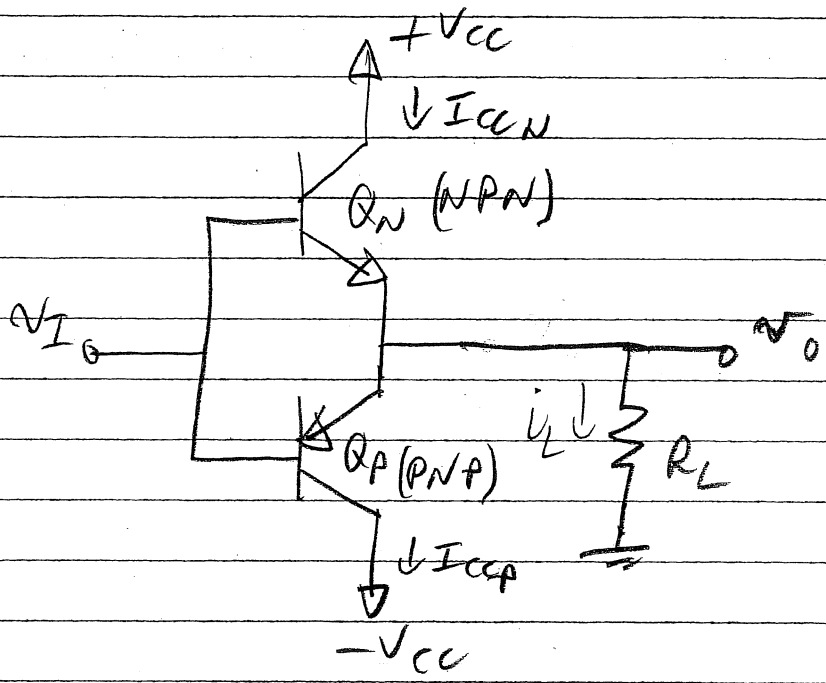


NOT TO SCALE

v_I

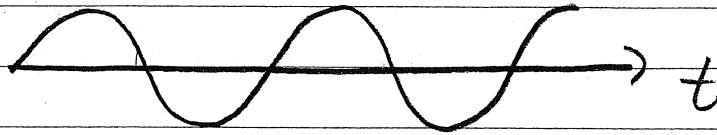

v_O

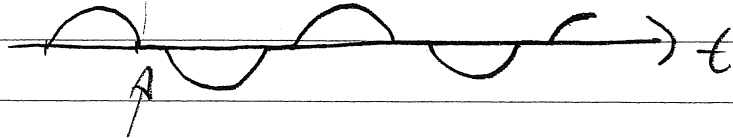

CROSS OVER

DISTORTION WHEN BOTH
 Q_N & Q_P OFF

POWER EFFICIENCY


IGNORING CROSSOVER DISTORTION

$V_{BE,N} \text{ \& } V_{BE,P} \approx 0$


$V_{CE,SAT} \approx 0$

$v_O = \hat{V}_O \sin(\omega t)$

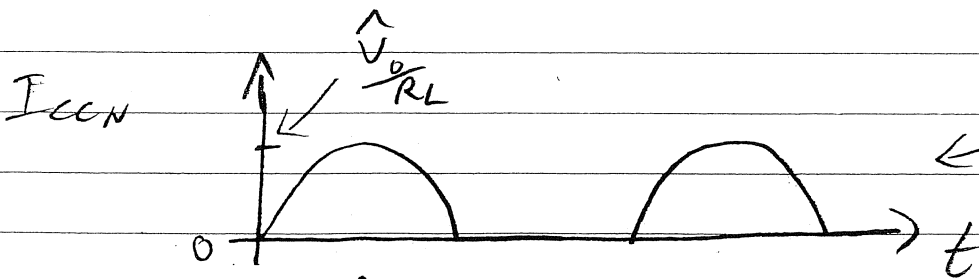$P_L = \frac{1}{2} \frac{\hat{V}_O^2}{R_L}$ FROM BEFORE



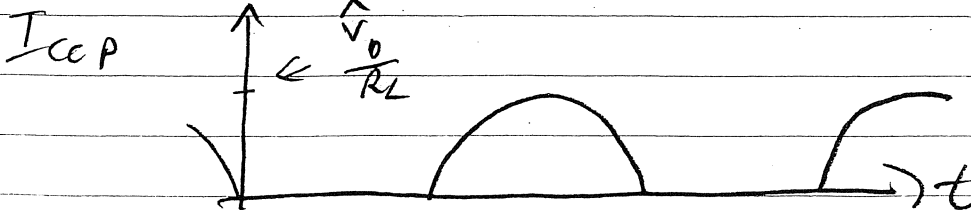$I_{CC,N-AVERAGE} = \frac{\hat{V}_O}{\pi R_L}$



$I_{CC,P-AVERAGE} = \frac{\hat{V}_O}{\pi R_L}$

PA10

$$P_{S+} = P_{S-} = \frac{1}{4} \frac{\hat{V}_o}{R_L} V_{CC}$$

$$P_S = P_{S+} + P_{S-} = \frac{2}{4} \frac{\hat{V}_o}{R_L} V_{CC}$$

EFFICIENCY

$$\eta = \frac{P_L}{P_S} = \frac{\frac{1}{4} \frac{\hat{V}_o}{R_L}}{\frac{2}{4} \frac{\hat{V}_o}{R_L} V_{CC}}$$

MAXIMUM EFFICIENCY WHEN $\hat{V}_o = V_{CC}$

$$\eta_{\text{MAX}} = \frac{\frac{1}{4}}{\frac{2}{4}} = \underline{\underline{78.5\%}}$$

$$\downarrow P_{L\text{MAX}} = \frac{1}{2} \frac{V_{CC}^2}{R_L} \quad \text{WHEN } \hat{V}_o = V_{CC}$$

(POWER DISSIPATED IN LOAD)

POWER DISSIPATION
OF OUTPUT STAGE, P_D

$$P_D = P_S - P_L$$

$$P_D = \frac{2}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} - \frac{1}{2} \frac{\hat{V}_o^2}{R_L} \quad (1)$$

$\frac{1}{2}$ POWER DISSIPATED IN Q_N

$\frac{1}{2}$ POWER DISSIPATED IN Q_P

TO FIND WORST CASE $P_{D \text{ MAX}}$

USED TO DETERMINE HOW MUCH HEAT NEEDS
TO BE DISSIPATED IN Q_N & Q_P

DIFFERENTIATE P_D WITH RESPECT TO \hat{V}_o
& SET TO ZERO


$$\frac{dP_D}{d\hat{V}_o} = \frac{2}{\pi} \frac{V_{CC}}{R_L} - \frac{\hat{V}_o}{R_L} = 0$$

$$\hat{V}_o = \frac{2}{\pi} V_{CC} \quad \text{PUT INTO (1)}$$

$$\Rightarrow P_{D \text{ MAX}} = \frac{2 V_{CC}^2}{\pi^2 R_L}$$

So $P_{PN\ MAX} = P_{DP\ MAX} = \frac{V_{CC}^2}{8RL}$

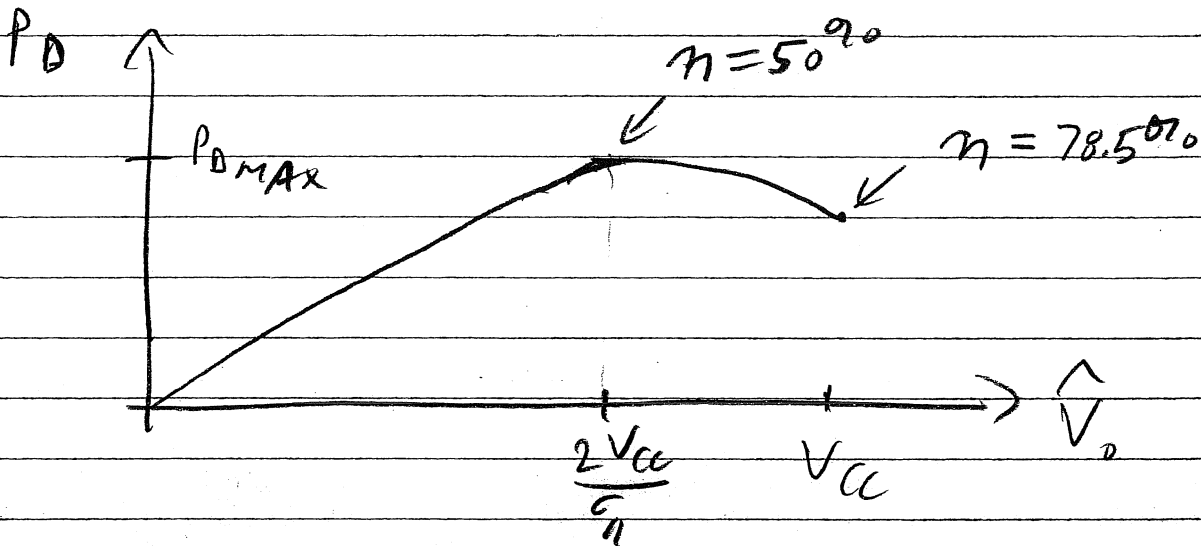$\eta = 50\%$ FOR $\hat{V}_o = \frac{2}{\sqrt{2}} V_{CC}$



EX DELIVER 20W INTO $R_L = 8\ \Omega$

$V_{CC} = 5V + V_{o\ PEAK}$ FIND $I_{CC-PEAK}$

$P_L = \frac{1}{2} \frac{V_o^2}{R_L}$

P_{S+}, P_{S-}

η

$P_{DN\ MAX}, P_{DP\ MAX}$

$20W = \frac{1}{2} \frac{V_o^2}{(8)} \Rightarrow \hat{V}_o = 17.9V$

$V_{CC} = 17.9 + 5 = 23V$

$I_{CC-PEAK} = \frac{\hat{V}_o}{R_L} = \frac{17.9}{8} = 2.24A$

PEAK TRANSISTOR
CURRENTS
AS WELL

PA13

$$P_{S+} = P_{S-} = \frac{1}{\eta} 2.24 \times 23 = 16.4 \text{ W}$$


$$P_S = 32.8 \text{ W} \quad P_L = 20 \text{ W}$$

$$\eta = \frac{20}{32.8} = 61\%$$

$$P_{DN \text{ max}} = P_{OP \text{ max}} = \frac{V_{CC}^2}{\eta^2 R_L} = 6.7 \text{ W}$$

$$\text{WHEN } \hat{V}_o = \frac{2}{\eta} V_{CC} = 14.64 \text{ V}$$


ONE WAY TO REDUCE CROSSOVER DISTORTION

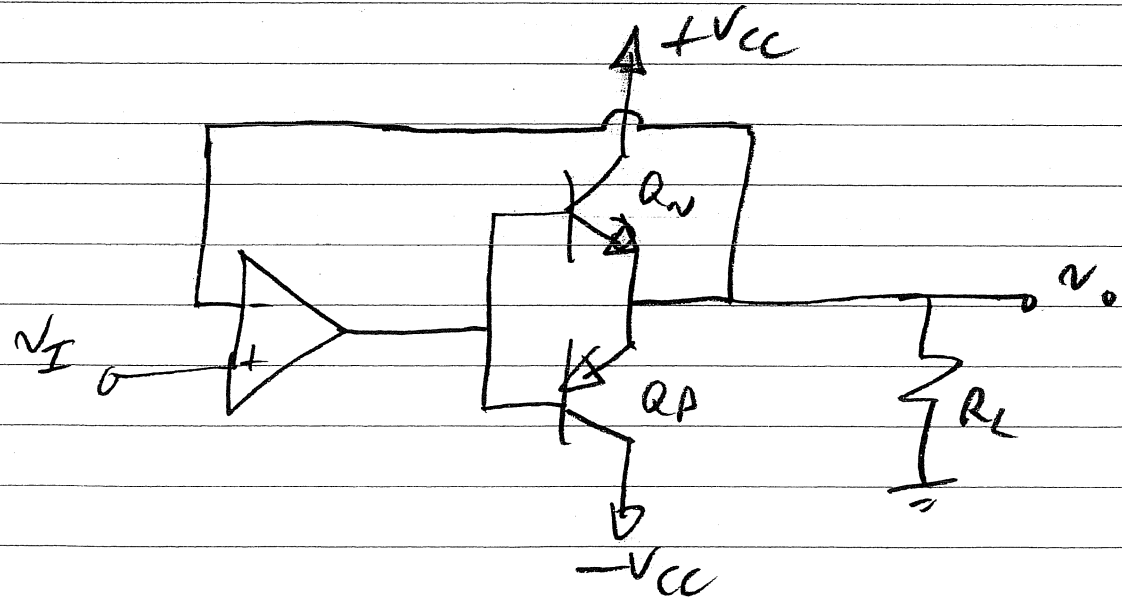

SLEW-RATE IN OPAMP MAY LIMIT PERFORMANCE

BETTER TO LEAVE TRANSISTORS BOTH ON WHEN $V_o \approx 0$

CLASS AB

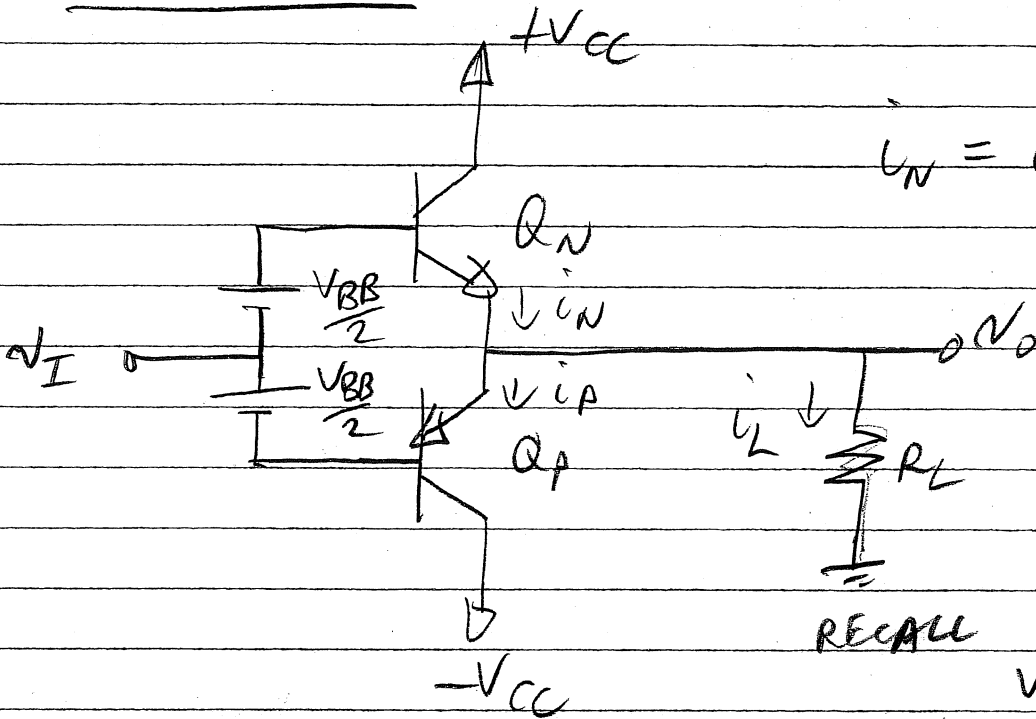

$$i_N = i_P + i_L$$

$$i_N = I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_{BE} = V_T \ln \frac{i_N}{I_S}$$

RECALL

FOR $v_I = v_O = 0$ & ASSUMING MATCHED DEVICES

$$i_N = i_P = I_Q = I_S e^{\frac{V_{BB}}{2V_T}} \quad (1)$$

V_{BB} SELECTED TO DETERMINE

QUIESCENT CURRENT I_Q

BOTH TRANSISTORS ON WITH $I_C = I_Q$ WHEN $v_O = 0$

PA15

AS $v_I > 0$

$$v_O = v_I + \frac{v_{BB}}{2} - v_{BEN}$$

SINCE $i_N = i_P + i_L$ (2) AS $i_N \uparrow$

$v_{BEN} \uparrow$

WHICH MEANS

$v_{EBA} \downarrow$

SINCE $v_{BEN} + v_{EBA} = v_{BB}$

FROM
①

$$V_T \ln \frac{i_N}{I_S} + V_T \ln \frac{i_P}{I_S} = 2V_T \ln \frac{I_Q}{I_S}$$


$$i_N i_P = I_Q^2 \quad (3)$$

COMBINE (2) & (3)

$$i_N^2 - i_L i_N - I_Q^2 = 0 \quad (4)$$

TO FIND i_N FOR A GIVEN i_L


PA16

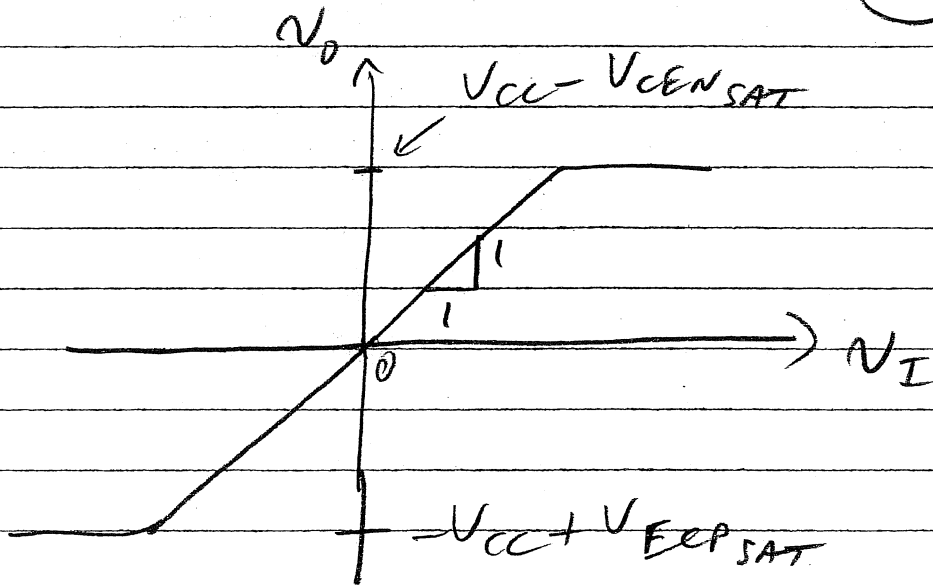

POWER RELATIONS ALMOST SAME
AS CLASS B

JUST ADD I_Q TO RESULTS
IN CLASS B
(USUALLY I_Q SMALL SO IT DOES
NOT CHANGE RESULTS MUCH)

OUTPUT RESISTANCE

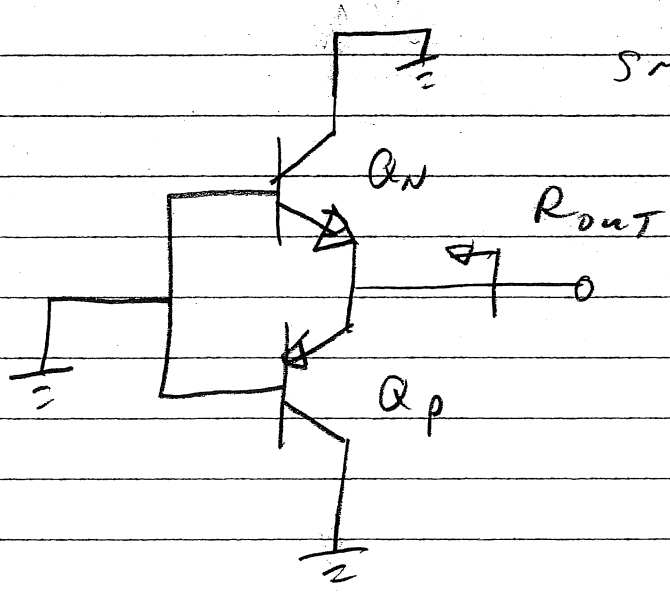

SMALL-SIGNAL MODEL

RECALL $r_e = \frac{V_T}{I_E}$

$V_T = \frac{kT}{q} \hat{=} 25 \text{ mV}$

$R_{OUT} = r_{eN} \parallel r_{eP}$

$r_{eN} = \frac{V_T}{i_N}$

$r_{eP} = \frac{V_T}{i_P}$

$R_{OUT} = \frac{V_T}{i_P + i_N}$

LARGEST R_{OUT} WHEN $i_P = i_N = I_Q$

AS $v_o > 0$ $\left. \begin{array}{l} i_N > I_Q \\ i_P < I_Q \end{array} \right\} R_{OUT} \text{ DECREASES}$

SIMILAR FOR $v_o < 0$

PA18

EXAMPLE CLASS AB

$$V_{CC} = 15 \text{ V} \quad I_Q = 2 \text{ mA} \quad R_L = 100 \Omega$$

$$Q_N \text{ \& } Q_P \text{ HAVE } I_S = 10^{-13} \text{ A}$$

1) FIND V_{BB}

2) FOR VARIOUS V_o VALUES

FIND i_L , i_N , i_P , v_I

ALSO FIND R_{out} \& $\frac{v_o}{v_i} \equiv \frac{R_L}{R_L + R_{out}}$
(SMALL-SIGNAL GAIN)

$$1) \text{ ①} \Rightarrow V_{BB} = 2 V_T \ln \left(\frac{I_Q}{I_S} \right) \quad V_T = 25 \text{ mV}$$

$$= 2(25 \text{ e-3}) \ln \left(\frac{2 \text{ e-3}}{1 \text{ e-13}} \right)$$

$$V_{BB} = 1.186 \text{ V}$$

2) TO FIND VALUES FOR v_o

1. ASSUME VALUE FOR v_o

2. $i_L = v_o / R_L$

3. $i_N^2 - i_L i_N - I_Q^2 = 0 \Rightarrow$ FIND i_N
 $i_N = i_L + i_p$

4. $V_{BEN} = V_T \ln\left(\frac{i_N}{I_S}\right)$

5. $v_I = v_o + V_{BEN} - \frac{V_{BB}}{2}$

$\frac{R_L}{R_L + R_{out}}$
 \downarrow


v_o	i_L	i_N	i_p	v_I	$\frac{v_o}{v_I}$	R_{out}	$\frac{v_o}{v_i}$
+10	100	100.04	0.04	10.1	0.99	0.25	1.00
+5	50	50.08	0.08	5.08	0.98	0.5	1.00
+0.5	5	5.7	0.7	0.526	0.95	4.03	0.96
0	0	2	2	0	-	6.25	0.94

SIMILAR FOR $v_o < 0$

i_L, i_N, i_p IN UNITS OF mA

BIASING CLASS AB CIRCUIT.

USING DIODES

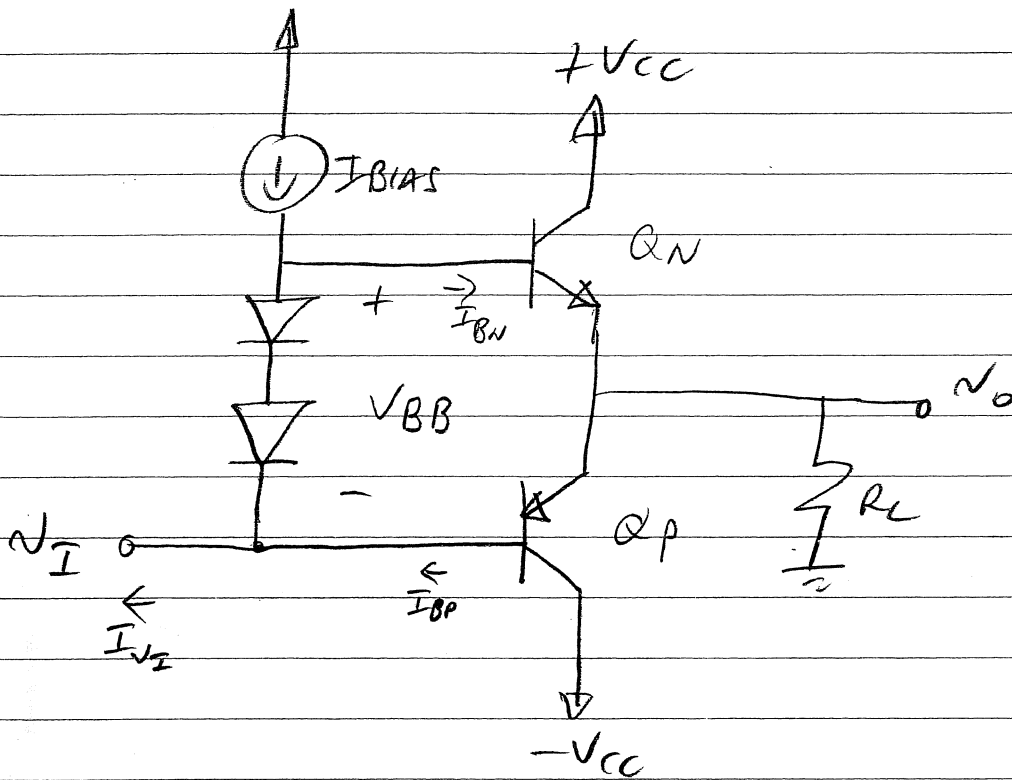

I_{NI} MUST SOURCE CURRENT OF

$$I_{NI} = I_{BIAS} - I_{BN} + I_{BP}$$

IF $\beta_N = \beta_P \Rightarrow I_{BN} = I_{BP}$ WHEN $v_o = 0$
OTHERWISE $I_{BN} \neq I_{BP}$

$A_{BE} = n A_D$ AREA BASE EMITTER = $n \times$ AREA DIODE

SO THAT $I_Q = n I_{BIAS}$

TYPICALLY $I_Q \approx 0.1 I_{C PEAK}$ (10% $I_{C PEAK}$)

BUT $I_{BN} = \frac{I_C}{\beta}$ & $\beta \approx 20 \rightarrow 40$ (SINCE POWER DEVICES)

& $I_{BIAS} > I_{BN}$ SO DIODE AREA

NOT MUCH SMALLER THAN BE AREA

$\Rightarrow n \lesssim 1$

DISADVANTAGE OF USING DIODES

ONE ADVANTAGE IS THERMAL STABILIZATION OF I_Q

RECALL RISE IN TEMP \Rightarrow DECREASE IN V_{BE}

$\approx -2mV/^\circ C$ IF I_C FIXED

IF V_{BB} CONSTANT $\Rightarrow I_C$ INCREASES

$I_C \uparrow \Rightarrow P_O \uparrow \Rightarrow TEMP \uparrow \Rightarrow I_C \uparrow$

ECT. THERMAL RUNAWAY IF GAIN GREATER THAN 1

IF DIODES USED & PLACED IN
THERMAL CONTACT WITH Q_N & Q_P

THEN AS

TEMP RISES \Rightarrow V_{BB} LOWERS

AND I_a ROUGHLY CONSTANT.

Ex

CLASS AB WITH DIODES

$$A_0 = \frac{A_{BE}}{3}$$

$$(n=3)$$

$$V_{CC} = 15 \text{ V}$$

$$R_L = 100 \Omega$$

$$v_o = 10 \sin(\omega t)$$

$$Q_N, Q_P \text{ HAS } I_S = 10^{-13} \text{ A} \quad \& \quad \beta = 50$$

FIND I_{BIAS} SUCH THAT $I_{O-MIN} = 1 \text{ mA}$ FIND I_Q , + P_{DQ} (QUIESCENT POWER DISSIPATION)FIND V_{BB} FOR $v_o = 0, +10 \text{ V}, -10 \text{ V}$ SOLN

$$I_{CN-MAX} = \frac{10}{100} = 100 \text{ mA}$$

$$I_{B-MAX} = \frac{I_{CN-MAX}}{\beta} = 2 \text{ mA}$$

$$\text{SO } I_{BIAS} = I_{B-MAX} + I_{O-MIN} = 3 \text{ mA}$$

$$\Rightarrow I_Q = n I_{BIAS} = 9 \text{ mA}$$

$$P_{DQ} = 2 \times V_{CC} \times I_Q = 270 \text{ mW}$$

PART 4

FOR $v_o = 0$ $I_E = 9 \text{ mA}$

$$I_B = \frac{I_E}{\beta + 1} = \frac{9}{51} = 0.18 \text{ mA}$$

So $I_{D1} = I_{BIAS} - I_{B1} = 2.82 \text{ mA}$

$$I_{S(D100E)} = \frac{1}{3} \times 10^{-13} \text{ A} \Rightarrow V_{BB} = 2V_T \ln \frac{2.82 \text{ mA}}{I_{S(D100E)}}$$

$$V_{BB} = 1.26 \text{ V}$$


$v_o = +10 \text{ V}$ $I_D = 1 \text{ mA}$

$$V_{BB} = 2V_T \ln \frac{1 \text{ mA}}{I_{S(D100E)}} = \underline{\underline{1.21 \text{ V}}}$$

$v_o = -10 \text{ V}$ $I_{Q2} \approx 0 \Rightarrow I_D = 3 \text{ mA}$

$$V_{BB} = 2V_T \ln \frac{3 \text{ mA}}{I_{S(D100E)}} \approx 1.26 \text{ V}$$

V_{BE} MULTIPLIER

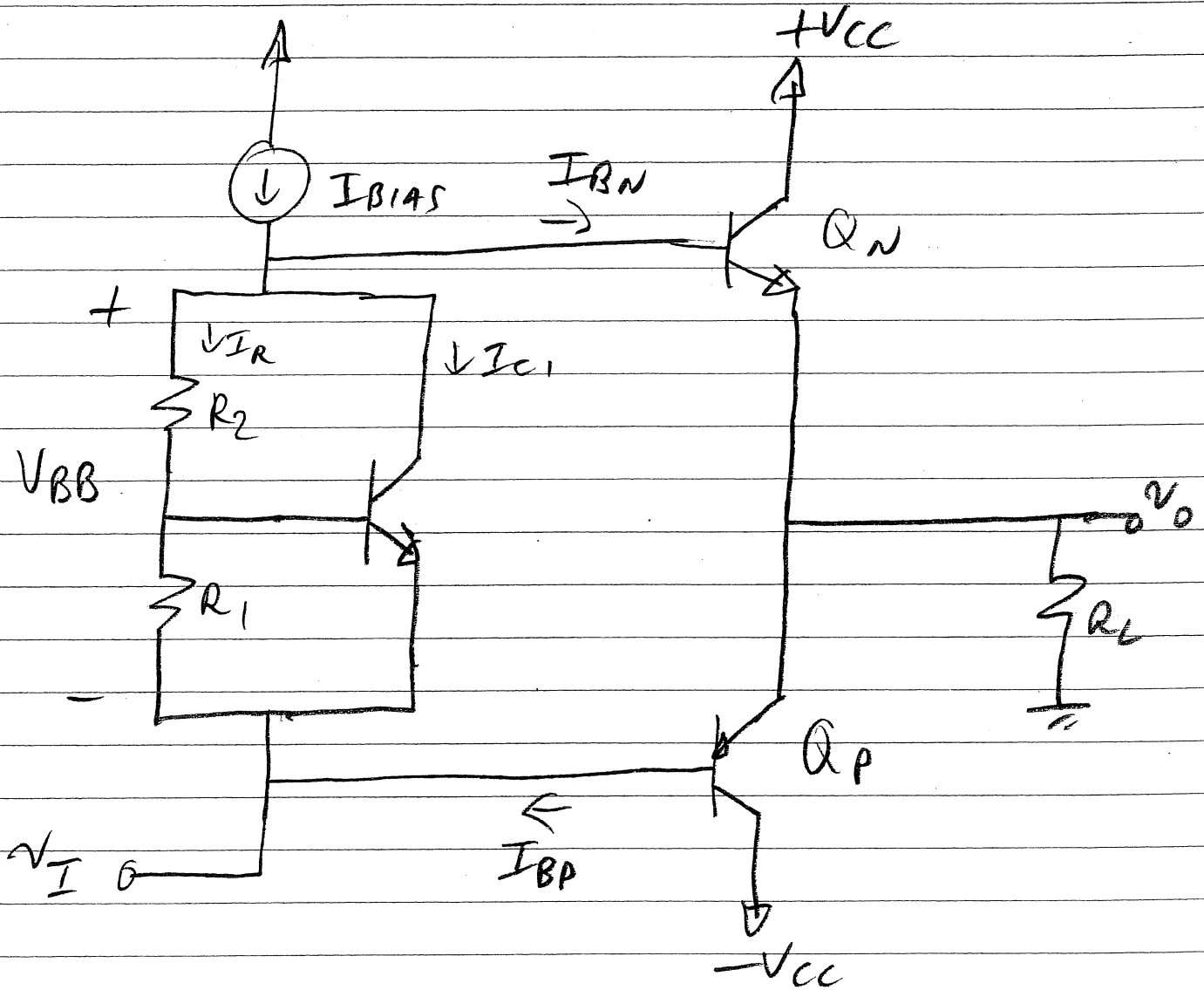

PA26

ASSUME $I_{B1} \approx 0$

$$I_R = \frac{V_{BE1}}{R_1}$$

$$V_{BB} = I_R (R_1 + R_2) =$$

$$V_{BB} = V_{BE} \left(1 + \frac{R_2}{R_1} \right)$$

$$I_{C1} = I_{BIAS} - I_{BN} = I_R \quad \& \quad V_{BE1} = V_T \ln \left(\frac{I_{C1}}{I_{S1}} \right)$$

IN DISCRETE DESIGN \Rightarrow ADJUST R_2, R_1 TO OBTAIN
DESIRED I_Q
(USUALLY THROUGH
POTENTIOMETER)

NOTE AS I_{BN} CHANGES $\Rightarrow I_{C1}$ CHANGES

$\Rightarrow V_{BE1}$ SLIGHTLY CHANGES

SO I_R REMAINS ABOUT SAME

$\Delta I_{BN} \Rightarrow$ RESULTS IN ΔI_{C1} CHANGE

BUT $I_R \approx$ CONSTANT $\&$

$V_{BB} \approx$ CONSTANT.

REPEAT EXAMPLE WITH VBE MULTIPLIER

WHERE $I_{S1} = 10^{-14}$ A (1/10 SIZE OF Q_N + Q_P)

DESIGN FOR $I_Q = 2$ mA

$I_{BN_MAX} = 2$ mA $\Rightarrow I_{BIAS} = 1$ mA + I_{BN_MAX}
 $I_{BIAS} = 3$ mA

I_Q DESIGN $I_{BN} = \frac{I_Q}{\beta + 1} \approx 0.04$ mA

$I_R + I_{C1} = I_{BIAS} - I_{BN} \approx 3$ mA

NEED TO DECIDE I_R + I_{C1} BREAKDOWN

WHEN $I_{BN_MAX} = 2$ mA $\Rightarrow I_R + I_{C1} = 1$ mA (MIN VALUE)

GIVE EACH 0.5 mA IN THIS CASE
 $\downarrow I_R$ WILL NOT VARY MUCH SO
FOR $V_o = 0$ CASE

$I_R = 0.5$ mA $I_{C1} = 2.5$ mA

SINCE $I_Q = 2$ mA $V_{BB} = 2V_T \ln\left(\frac{2 \text{ mA}}{10^{-13}}\right)$
 $= 1.19$ V

$$I_R = \frac{V_{BB}}{R_1 + R_2} \Rightarrow 0.5 = \frac{1.19}{R_1 + R_2}$$

$$\Rightarrow R_1 + R_2 = 2.38 \text{ k}\Omega$$

$$V_{BE1} = V_T \ln \frac{2.5 \text{ mA}}{10^{-14} \text{ A}} = 0.656 \text{ V}$$

$$I_R = \frac{V_{BE1}}{R_1} \Rightarrow R_1 = \frac{0.66}{0.5 \text{ mA}} = \underline{\underline{1.31 \text{ k}\Omega}}$$

$$R_2 = 2.38 - 1.32 = \underline{\underline{1.07 \text{ k}\Omega}}$$

$$\underline{V_o = +10 \text{ V}}$$

$$I_{C1} = 0.5 \text{ mA} \Rightarrow V_{BE1} = V_T \ln \left(\frac{0.5 \text{ mA}}{10^{-14}} \right) \\ = 0.616 \text{ V}$$

$$I_R = 0.47 \text{ mA} \approx 0.5 \text{ mA}$$

$$V_{BB} = V_{BE1} \left(1 + \frac{R_2}{R_1} \right) = V_{BE1} (1.817) \\ = 1.12 \text{ V}$$


$$\underline{V_o = -10 \text{ V}}$$

$$I_{C1} = 2.5 \text{ mA} \Rightarrow V_{BE1} = 0.656 \text{ V}$$

$$V_{BB} = V_{BE1} \left(1 + \frac{R_2}{R_1} \right) = 1.19 \text{ V}$$

CMOS CLASS AB OUTPUT STAGES

CLASSICAL - BASED ON BJT

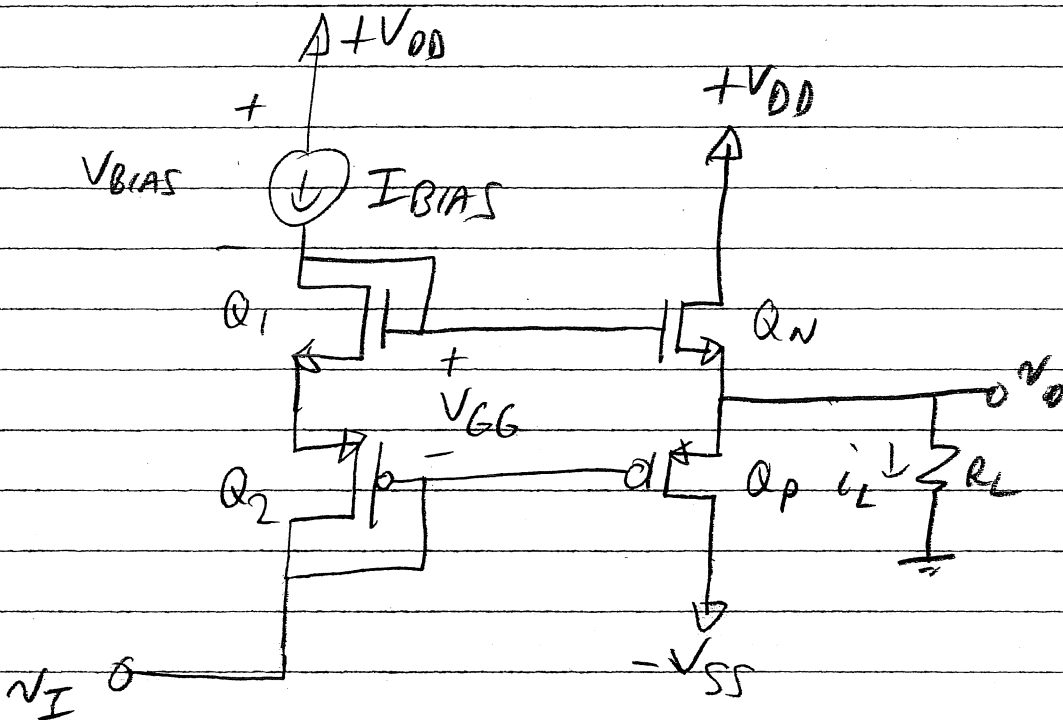

$$I_{D1} = I_{D2} = I_{BIAS} \quad \text{INDEPENDENT OF } I_{DN} \text{ \& } I_{DP}$$

 V_{GG} CONSTANT

I_Q

$$I_{D1} = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{thn})^2 \quad (1)$$

$$I_{D2} = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right)_2 (V_{SG2} - |V_{thp}|)^2 \quad (2)$$

$$V_{GG} = V_{GS1} + V_{SG2} = V_{thn} + |V_{thp}| + \sqrt{2I_{BIAS}} \left(\frac{1}{\sqrt{\mu_n C_{ox}} \left(\frac{W}{L}\right)_1} + \frac{1}{\sqrt{\mu_p C_{ox}} \left(\frac{W}{L}\right)_2} \right)$$

SIMILAR $V_{GG} = V_{GSN} + V_{SGP}$

CAN SHOW

$$I_Q = I_{BIAS} \left[\frac{1}{\sqrt{\mu_n C_{ox}} \left(\frac{W}{L}\right)_1} + \frac{1}{\sqrt{\mu_p C_{ox}} \left(\frac{W}{L}\right)_2} \right]^2$$

$$\left[\frac{1}{\sqrt{\mu_n C_{ox}} \left(\frac{W}{L}\right)_N} + \frac{1}{\sqrt{\mu_p C_{ox}} \left(\frac{W}{L}\right)_P} \right]^2$$

IF $Q_1 \neq Q_2$ MATCHED $\mu_p C_{ox} \left(\frac{W}{L}\right)_2 = \mu_n C_{ox} \left(\frac{W}{L}\right)_1$

\downarrow $Q_N \neq Q_P$ MATCHED

THEN

$$I_Q = I_{BIAS} \frac{(W/L)_N}{(W/L)_P}$$

PROBLEM WITH ABOVE CMOS OUTPUT STAGE IS SMALL OUTPUT SIGNAL RANGE

$$V_O = V_{DD} - V_{BIAS} - V_{GSN}$$

$$V_{O-MAX} = V_{DD} - V_{OV1BIAS} - (V_{TN} + V_{OVN})$$


V_{OVN} CAN BE LARGE WHEN $i_L = i_{LMAX}$

SIMILAR

$$V_{O-MIN} = -V_{SS} + V_{OV1I} + |V_{TP}| + |V_{OVP}|$$

V_{OV1I} IS OVERDRIVE VOLTAGE DUE TO INPUT.

CMOS PUSH-PULL OUTPUT STAGE

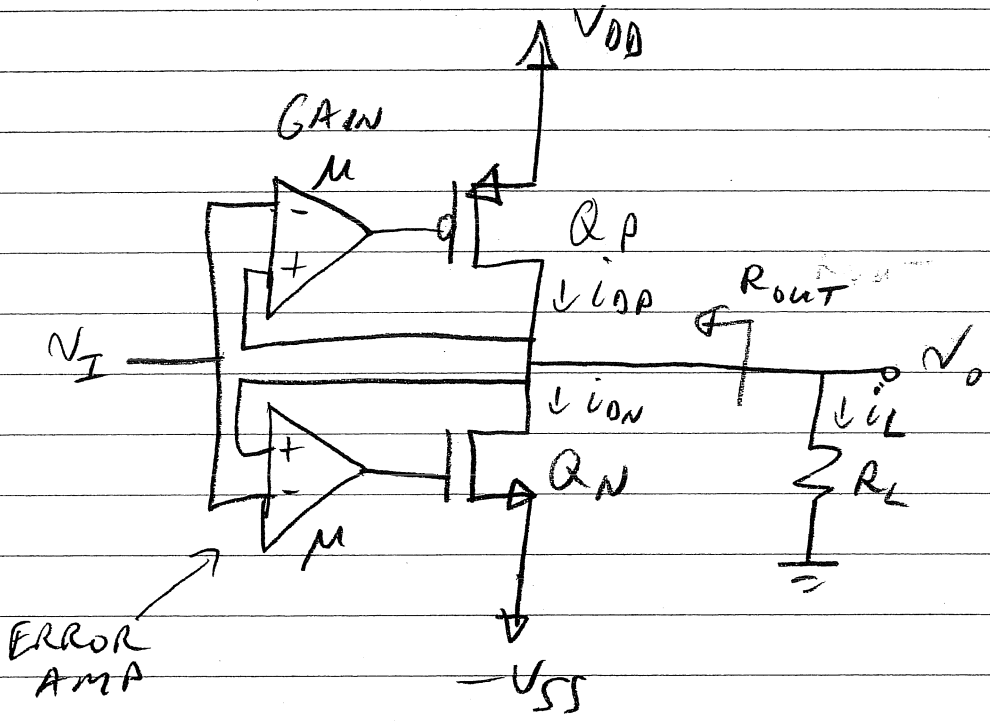


IF NO ERROR AMPLIFIERS \Rightarrow OUTPUT RESISTANCE WOULD BE HIGH

ERROR AMPS \Rightarrow FEEDBACK TO REDUCE OUTPUT RESISTANCE

ALSO $v_o \approx v_i$ DUE TO FEEDBACK

OUTPUT RESISTANCE

TOP HALF (SMALL-SIGNAL)

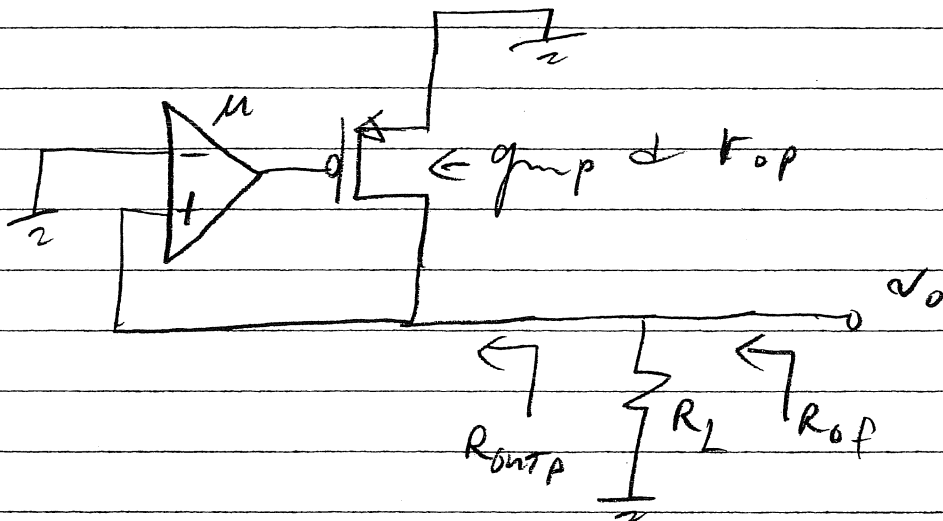

$$R_{of} = R_{p0} \left[\frac{1 + L_S}{1 + L_0} \right] \quad \begin{array}{l} L_S = 0 \\ L_0 = \mu g_{mp} (r_{op} \parallel R_L) \end{array}$$

$$R_{p0} = r_{op} \parallel R_L$$

$$R_{of} = \frac{r_{op} \parallel R_L}{1 + \mu g_{mp} (r_{op} \parallel R_L)} = R_{outp} \parallel R_L$$

$$R_{outp} = \left(\frac{1}{R_{of}} - \frac{1}{R_L} \right)^{-1}$$

$$R_{outp} = r_{op} \parallel \frac{1}{\mu g_{mp}} \approx \frac{1}{\mu g_{mp}}$$

SIMILARLY $R_{outN} \approx \frac{1}{n g_{mn}}$

COMBINING


$$R_{out} \approx \frac{1}{n (g_{mp} + g_{mn})}$$

LARGE SIGNAL v_o / v_i RELATIONSHIP

ASSUME $k \equiv \mu_n C_{ox} (\frac{W}{L})_n = \mu_p C_{ox} (\frac{W}{L})_p$

MATCHED DEVICES $Q_n \neq Q_p$

WHEN $v_i = 0$

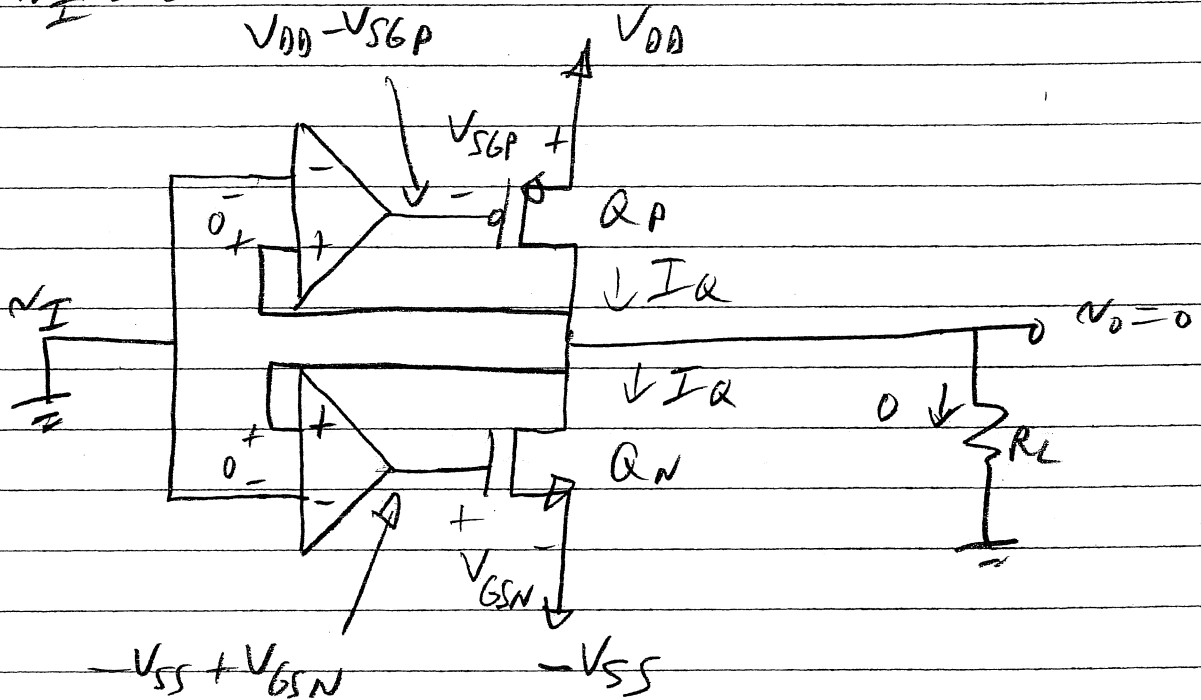


$$V_{SGP} = V_{ov} + |V_{tp}| \Rightarrow V_{ov} = V_{SGP} - |V_{tp}| \quad (1)$$

$$I_{Dp} = I_Q = \frac{1}{2} k (V_{SGP} - |V_{tp}|)^2 = I_n$$

$$I_Q = \frac{1}{2} k V_{ov}^2 \quad (2)$$

FOR $v_I \neq 0$

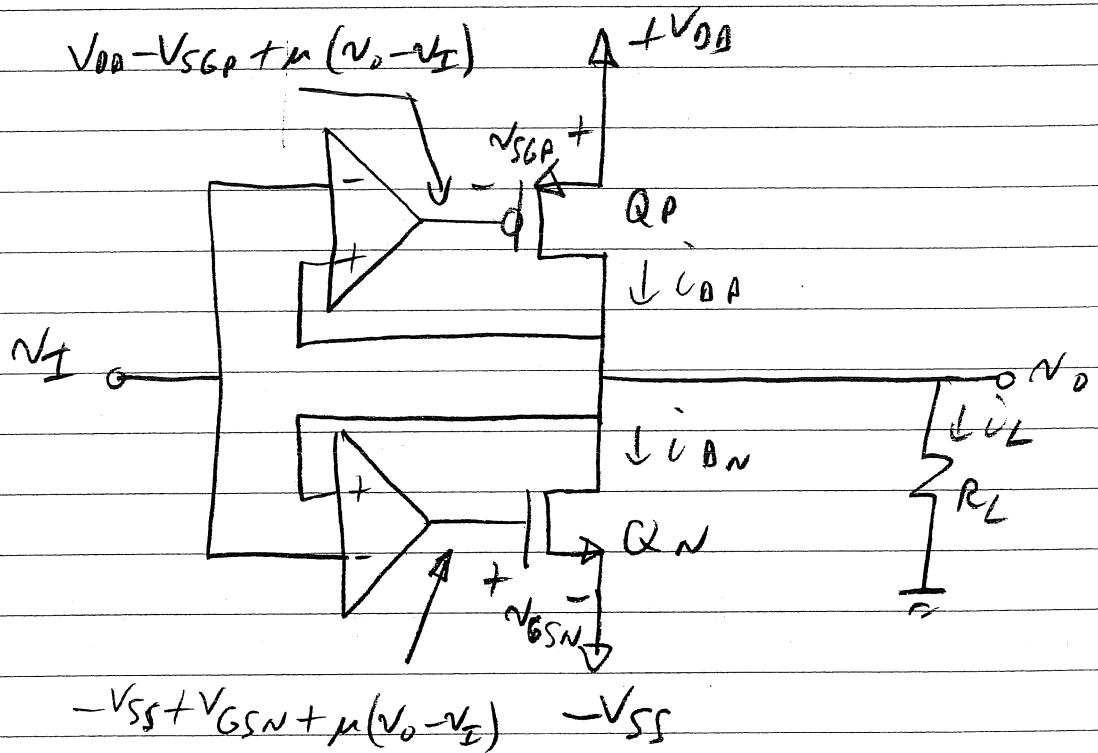OUTPUT OF ERROR AMP IS
ORIGINAL $v_I = 0$ VALUE + $\mu(v_O - v_I)$



$$v_{SGP} = V_{DD} - (V_{DD} - V_{SGP} + \mu(v_O - v_I))$$

$$v_{SGP} = V_{SGP} - \mu(v_O - v_I)$$

$$v_{SGP} = |V_{tp}| + V_{ov} - \mu(v_O - v_I) \quad \text{FROM ①}$$

$$i_{DP} = \frac{1}{2} k (v_{SGP} - |V_{tp}|)^2$$

$$= \frac{1}{2} k (V_{ov} - \mu(v_O - v_I))^2$$

$$i_{OP} = \frac{1}{2} k V_{OV}^2 \left(1 - \mu \frac{V_0 - V_I}{V_{OV}} \right)^2$$

PA37

$$i_{OP} = I_Q \left(1 - \mu \left(\frac{V_0 - V_I}{V_{OV}} \right) \right)^2 \quad \text{FROM (2)}$$

SIMILAR $i_{ON} = I_Q \left(1 + \mu \left(\frac{V_0 - V_I}{V_{OV}} \right) \right)^2$

$$i_L = i_{OP} - i_{ON} \quad \left(\text{NOTE SQUARE TERMS CANCEL} \right)$$

$$i_L = -4 I_Q \mu \frac{(V_0 - V_I)}{V_{OV}} \quad (3)$$

$$i_L = \frac{V_0}{R_L} \quad (4)$$

PUT (4) \rightarrow (3) & SOLVE FOR V_0

$$V_0 = \frac{V_I}{1 + \frac{V_{OV}}{4\mu I_Q R_L}}$$

FOR $\frac{V_{OV}}{4\mu I_Q R_L} \ll 1 \Rightarrow V_0 \approx V_I \left(1 - \frac{V_{OV}}{4\mu I_Q R_L} \right)$

GAIN ERROR IS $v_o - v_I = - \frac{v_{ov}}{A_{\mu} I_a R_L}$

↓ SINCE $g_m \equiv g_{m_n} = g_{m_p} = \frac{2I_a}{V_{ov}}$

$$\text{GAIN ERROR} = - \frac{1}{2\mu g_m R_L}$$

SO LARGE μ REDUCES GAIN ERROR & OUTPUT RESISTANCE

HOWEVER LARGE μ MAKE I_a HIGHLY VARIABLE DUE TO MISMATCH & OFFSETS

TYPICAL $\mu \approx 5 \rightarrow 10$

EXAMPLE

$$V_{DD} = -V_{SS} = 2.5V$$

$$V_{tn} = -V_{tp} = 0.5V$$

$$\mu_n C_{ox} = 2.5 \mu A/V^2 = 250 \mu A/V^2$$

LET $\mu = 10$ & $I_Q = 1mA$

AND $R_L = 100 \Omega$, V_{OV} BETWEEN 0.1 → 0.2V

FIND Q_N , Q_P SIZES & QUIESCENT OPERATING POINTS.

TO MINIMIZE GAIN ERROR & OUTPUT RESISTANCE

⇒ MAXIMIZE $g_m = \frac{2I_Q}{V_{OV}}$

SO CHOOSE $V_{OV} = 0.1V$

$$g_m = \frac{2(1mA)}{0.1V} = 20 mA/V$$

$$I_Q = \frac{1}{2} k (V_{OV})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_N (V_{OV})^2$$

$$1mA = \frac{1}{2} (250e-6) \left(\frac{W}{L}\right)_N (0.1)^2$$

$$\left(\frac{W}{L}\right)_N = \underline{\underline{800}}$$

PA 40

SIMILAR FOR $\left(\frac{W}{L}\right)_P$

$$1 \text{ mA} = \frac{1}{2} \left(\frac{250 \times 10^{-6}}{2.5} \right) \left(\frac{W}{L}\right)_P (0.1)^2$$

$$\left(\frac{W}{L}\right)_P = \underline{\underline{2000}}$$

$$R_{out} = \frac{1}{\mu (g_{mp} + g_{mn})} = \frac{1}{(10)(20 \times 10^{-3} + 20 \times 10^{-3})}$$
$$= 2.5 \Omega$$

