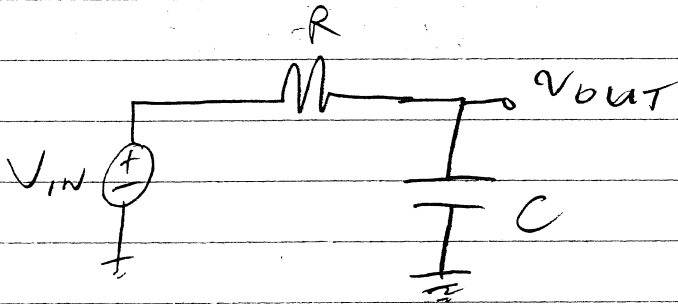


SINGLE TIME CONSTANT CIRCUITS



LOWPASS
SINGLE TIME CONSTANT
(STC)

$$T(s) = \frac{V_{OUT}}{V_{IN}} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} = \frac{1}{1 + sRC}$$

DEFINING $\tau = RC$ & $\omega_0 = \frac{1}{\tau} = \frac{1}{RC}$

$$T(s) = \frac{1}{1 + s\tau} = \frac{1}{1 + s/\omega_0}$$

IN GENERAL, A LOWPASS STC IS

$$T(s) = \frac{K}{1 + s/\omega_0}$$

WHERE $\omega_0 = \frac{1}{\tau} = \frac{1}{RC}$

IF RC IS USED
TO REALIZE IT

MAGNITUDE RESPONSE

$$|T(j\omega)| = \left| \frac{k}{1 + \frac{j\omega}{\omega_0}} \right|$$

$$= \frac{k}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

$$|T(j\omega)| \approx k \quad \text{FOR } \omega \ll \omega_0$$

$$|T(j\omega)| \approx \frac{k\omega_0}{\omega} \quad \text{FOR } \omega \gg \omega_0$$

$$|T(j\omega)| = \frac{k}{\sqrt{2}} \quad \text{FOR } \omega = \omega_0 \quad 3\text{dB FREQ.}$$

PHASE RESPONSE

$$\angle T(j\omega) = \angle k - \angle \left(1 + \frac{j\omega}{\omega_0}\right)$$


$$= 0 - \tan^{-1} \left(\frac{\omega}{\omega_0}\right)$$

$$\angle T(j\omega) \approx 0 \quad \text{FOR } \omega \ll \omega_0$$


$$\angle T(j\omega) \approx -90^\circ \quad \text{FOR } \omega \gg \omega_0$$

$$\angle T(j\omega) = -45^\circ \quad \text{FOR } \omega = \omega_0$$


$$20 \log \left| \frac{T(j\omega)}{K} \right| \text{ dB}$$

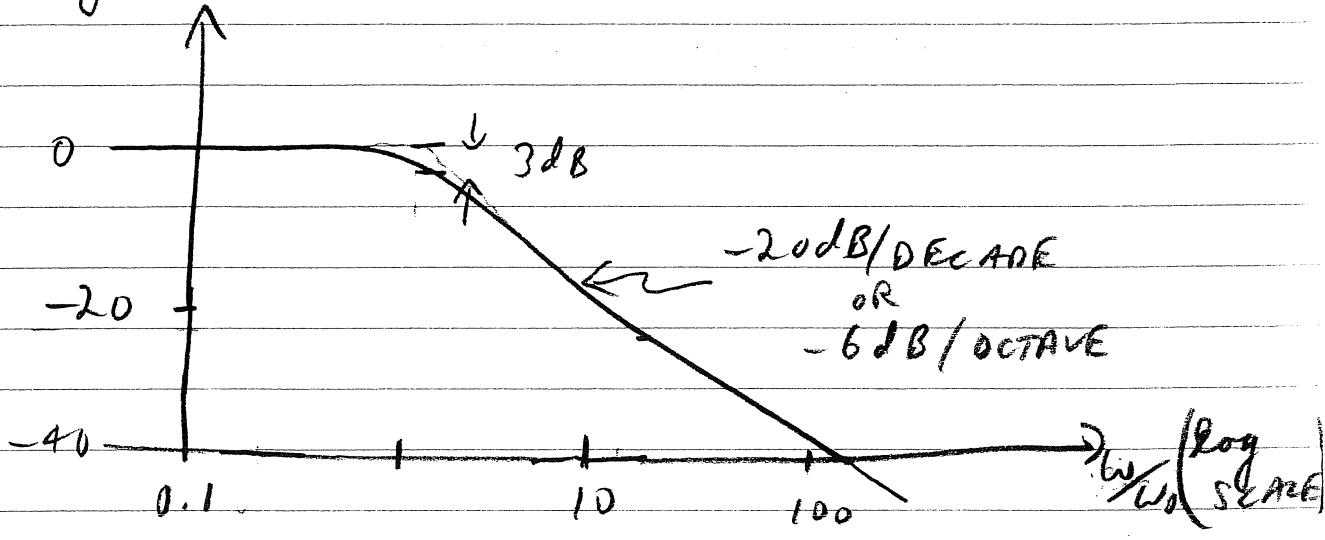

$$\angle T(j\omega)$$

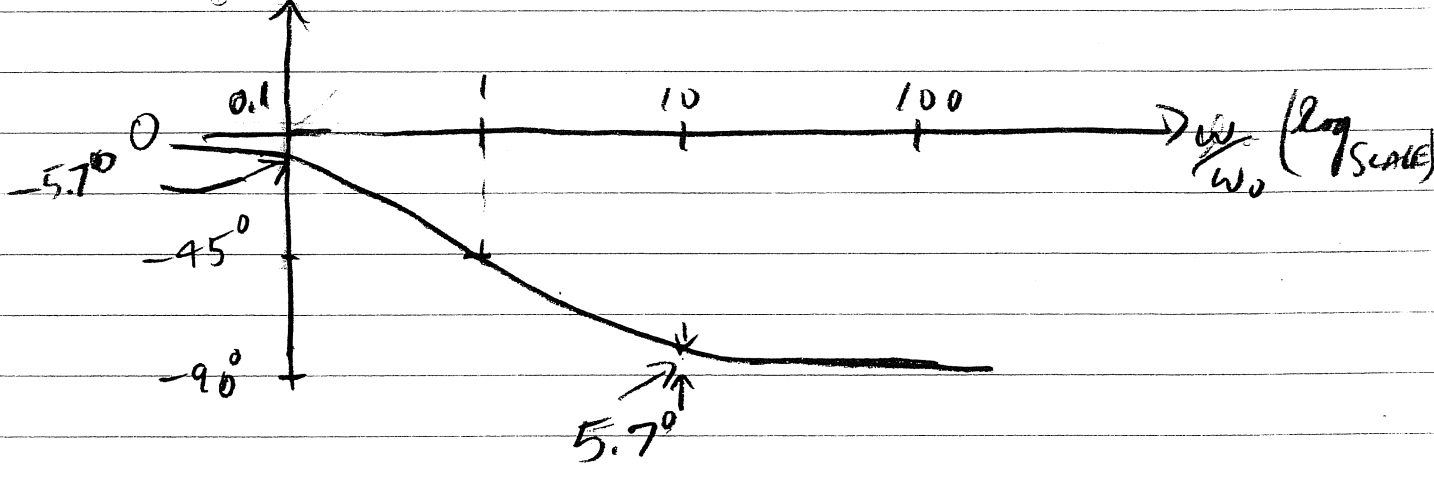

HIGHPASS

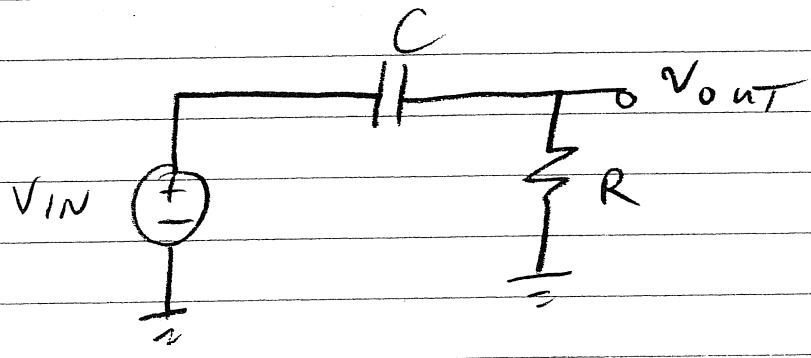

$$T(s) = \frac{V_{OUT}}{V_{IN}} = \frac{R}{\frac{1}{sC} + R} = \frac{sCR}{sCR + 1} = \frac{s}{s + \frac{1}{CR}}$$

DEFINING $\tau = RC$ & $\omega_0 = \frac{1}{\tau} = \frac{1}{RC}$.



$$T(s) = \frac{s}{s + \frac{1}{\tau}} = \frac{s}{s + \omega_0}$$

IN GENERAL, A HIGHPASS STC IS

$$T(s) = \frac{k s}{s + \omega_0} \quad \text{WHERE } \omega_0 = \frac{1}{\tau}$$

$$|T(j\omega)| = \frac{k \omega}{\sqrt{\omega^2 + \omega_0^2}} = \frac{k}{\sqrt{1 + \frac{\omega_0^2}{\omega^2}}}$$

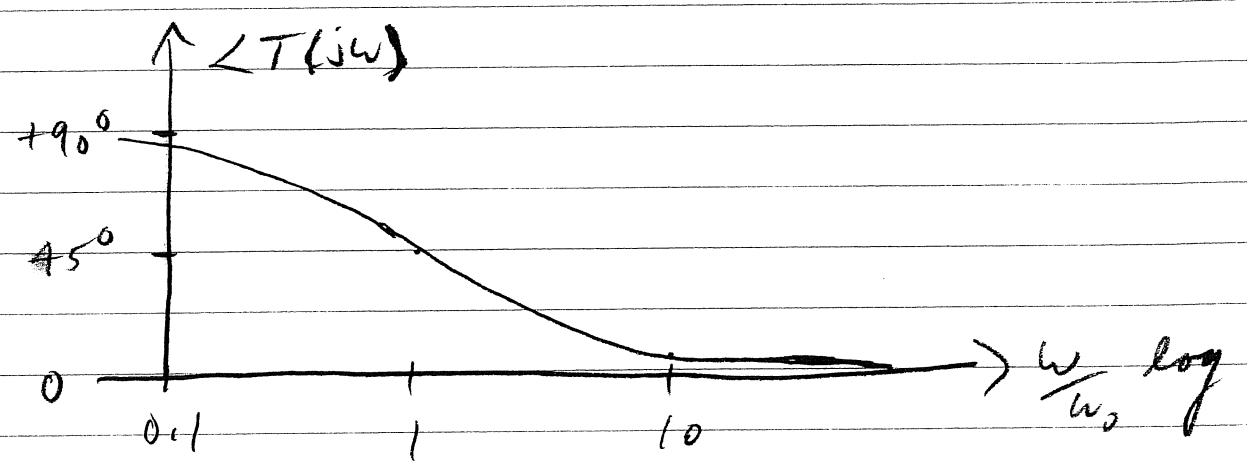
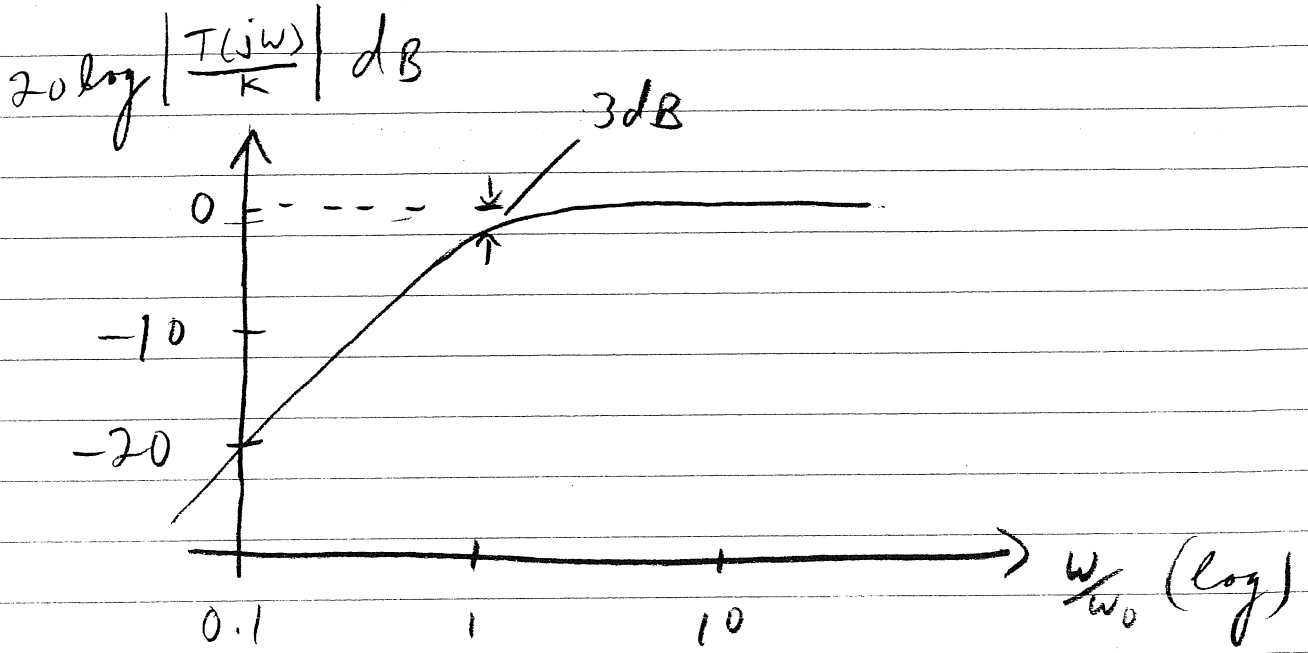
$$\angle T(j\omega) = \tan^{-1} \left(\frac{\omega_0}{\omega} \right)$$




STEP RESPONSE OF STC CIRCUITS

$$y(t) = Y_{\infty} - (Y_{\infty} - Y_{0+}) e^{-t/\tau}$$

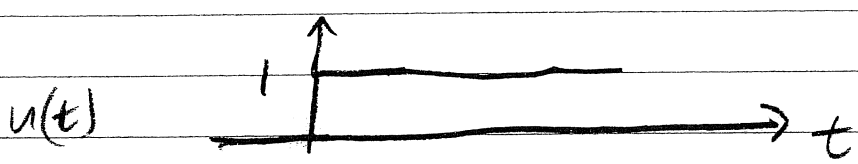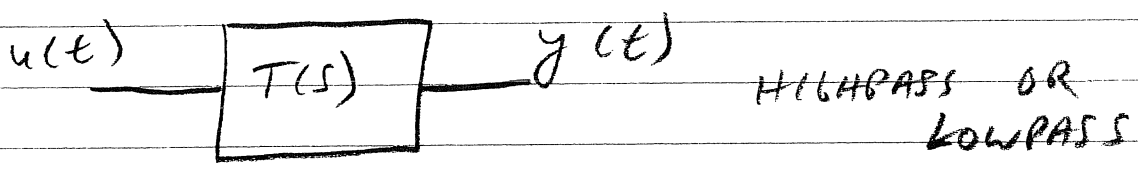WHERE Y_{∞} IS FINAL VALUE
 Y_{0+} IS INITIAL " "
 τ IS TIME CONSTANT



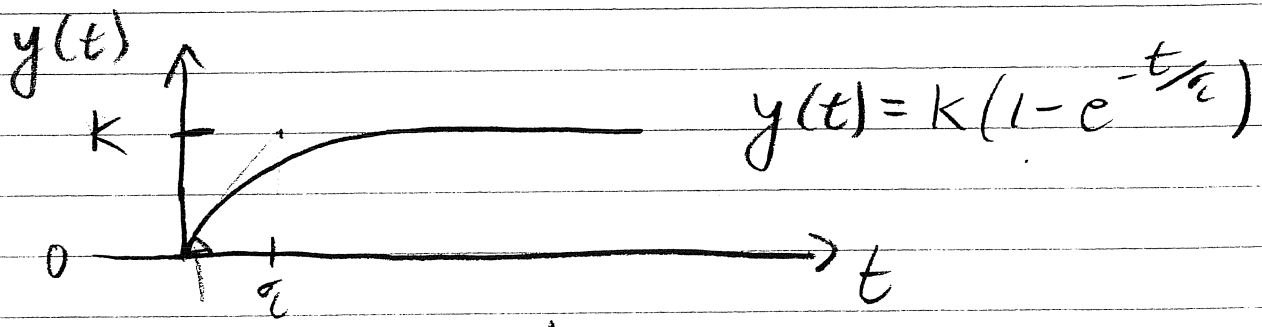
LOWPASS $T(s) = \frac{k}{1 + s/\omega_0}$ $\omega_0 = \frac{1}{\tau}$




INITIAL SLOPE = $\frac{k}{\tau}$

HIGH PASS
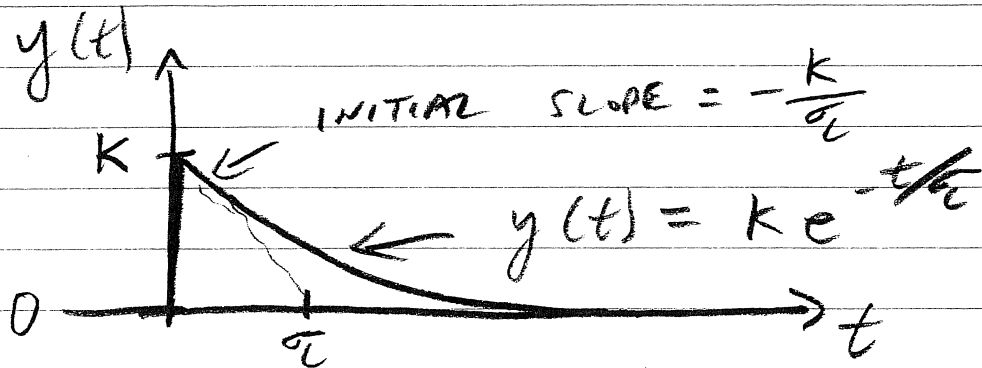
$$T(s) = \frac{Ks}{s + \omega_c} \quad \omega_c = \frac{1}{RC}$$





PULSE RESPONSES

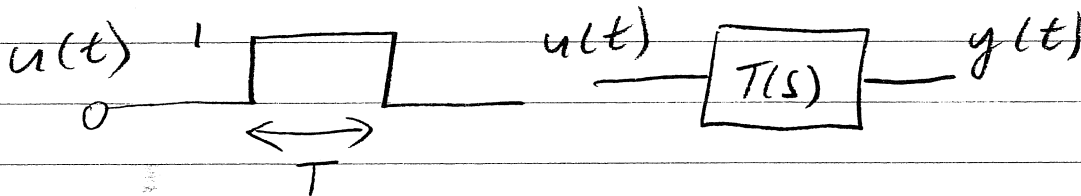


LOW PASS OUTPUT

$$\omega_c \ll T$$

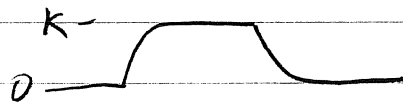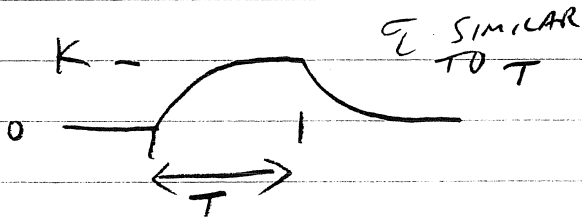


$$\omega_c \gg T$$

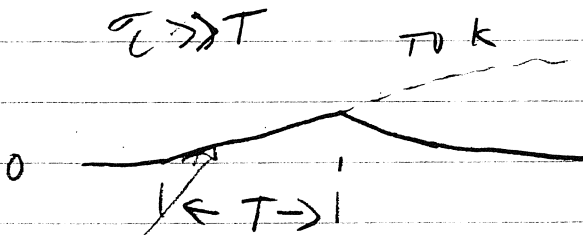


SLOPE = $\frac{K}{T}$

HIGH PASS OUTPUT

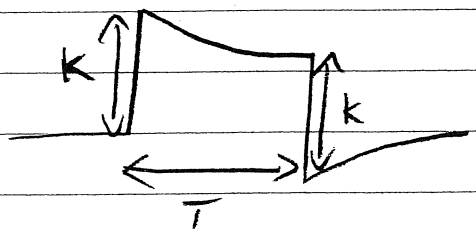

σ COMPARABLE TO T

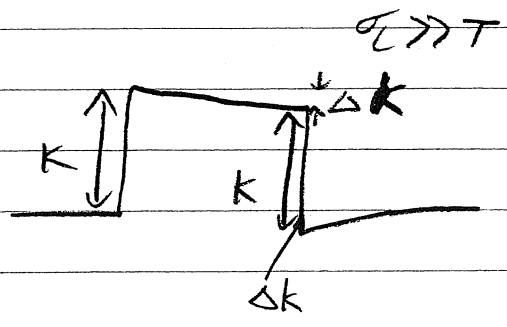


$$\Delta k \approx \frac{k}{\sigma} T$$

PERCENTAGE SAG

$$= \frac{\Delta k}{k} \times 100$$

$$\approx \frac{T}{\sigma} \times 100$$

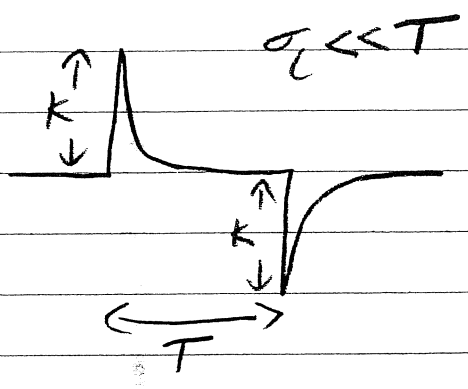


$\sigma \ll T$

FINDING τ FROM STC CIRCUITS WITH R'S + C'S

1) IF SINGLE CAPACITOR + MULTIPLE RESISTORS

- REDUCE INDEPENDENT SOURCES TO ZERO
- FIND EQUIVALENT RESISTANCE "SEEN" BY CAPACITOR

EXAMPLE

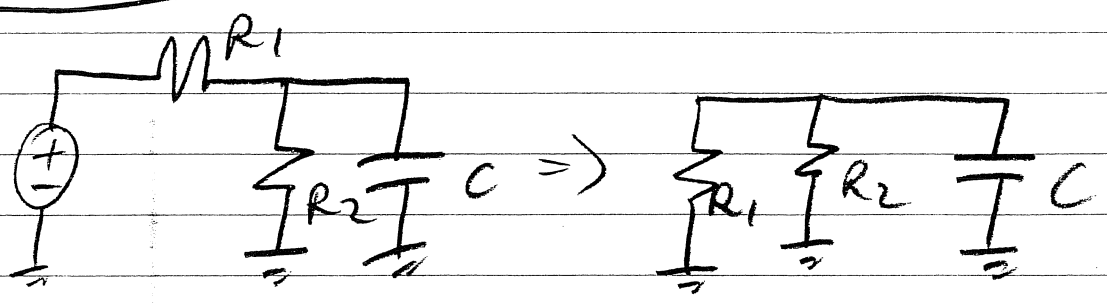


$$R_{eq} = R_1 \parallel R_2$$

$$\tau = R_{eq} C$$

$$= (R_1 \parallel R_2) C$$

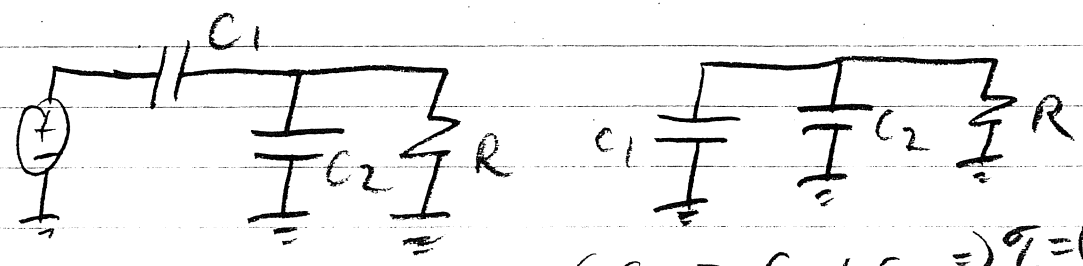
2) IF SINGLE RESISTOR + MULTIPLE CAPACITORS

- REDUCE INDEPENDENT SOURCES TO ZERO
- FIND EQUIV CAPACITANCE "SEEN" BY RESISTOR




$$C_{eq} = C_1 + C_2 \Rightarrow \tau = (C_1 + C_2) R$$

Ex

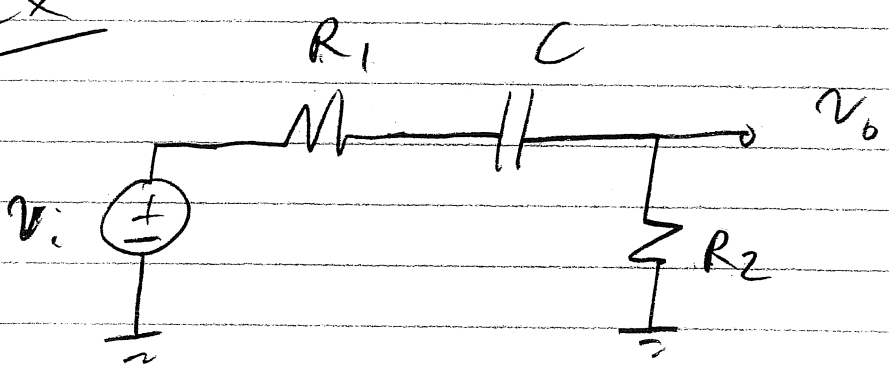

$$\tau_c = C(R_1 + R_2)$$


$$\omega_{3dB} = \frac{1}{C(R_1 + R_2)} \quad \left| \frac{v_o(j\omega)}{v_i} \right| = \frac{R_2}{R_1 + R_2}$$

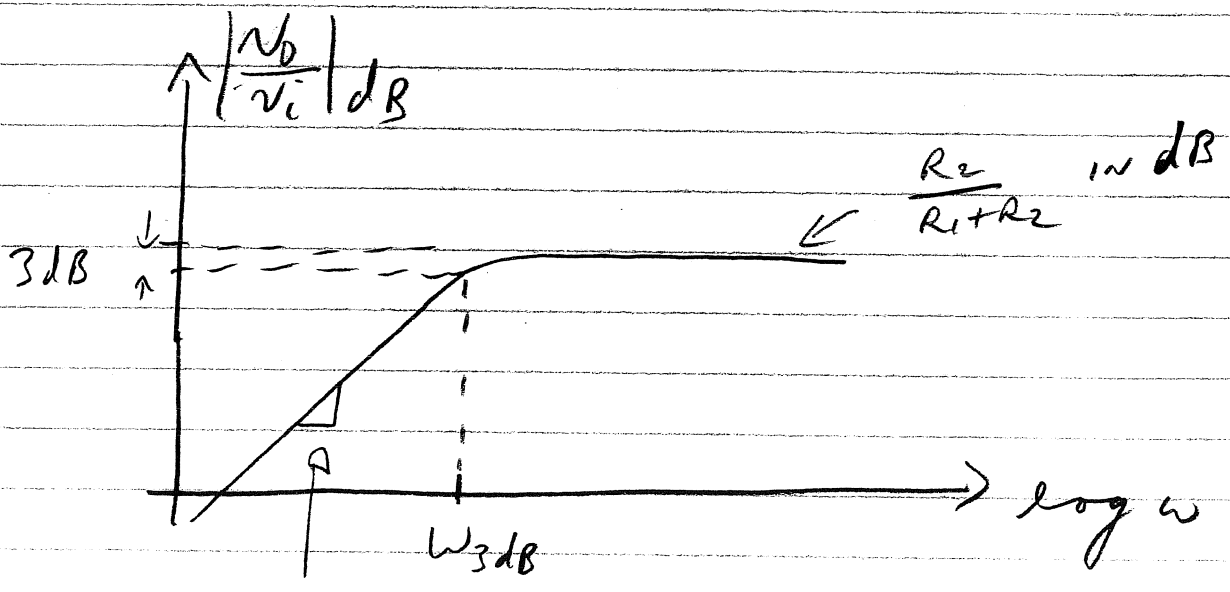

20 dB/DECADE

ST11


REAL-AXIS POLES & ZEROS BODE PLOT

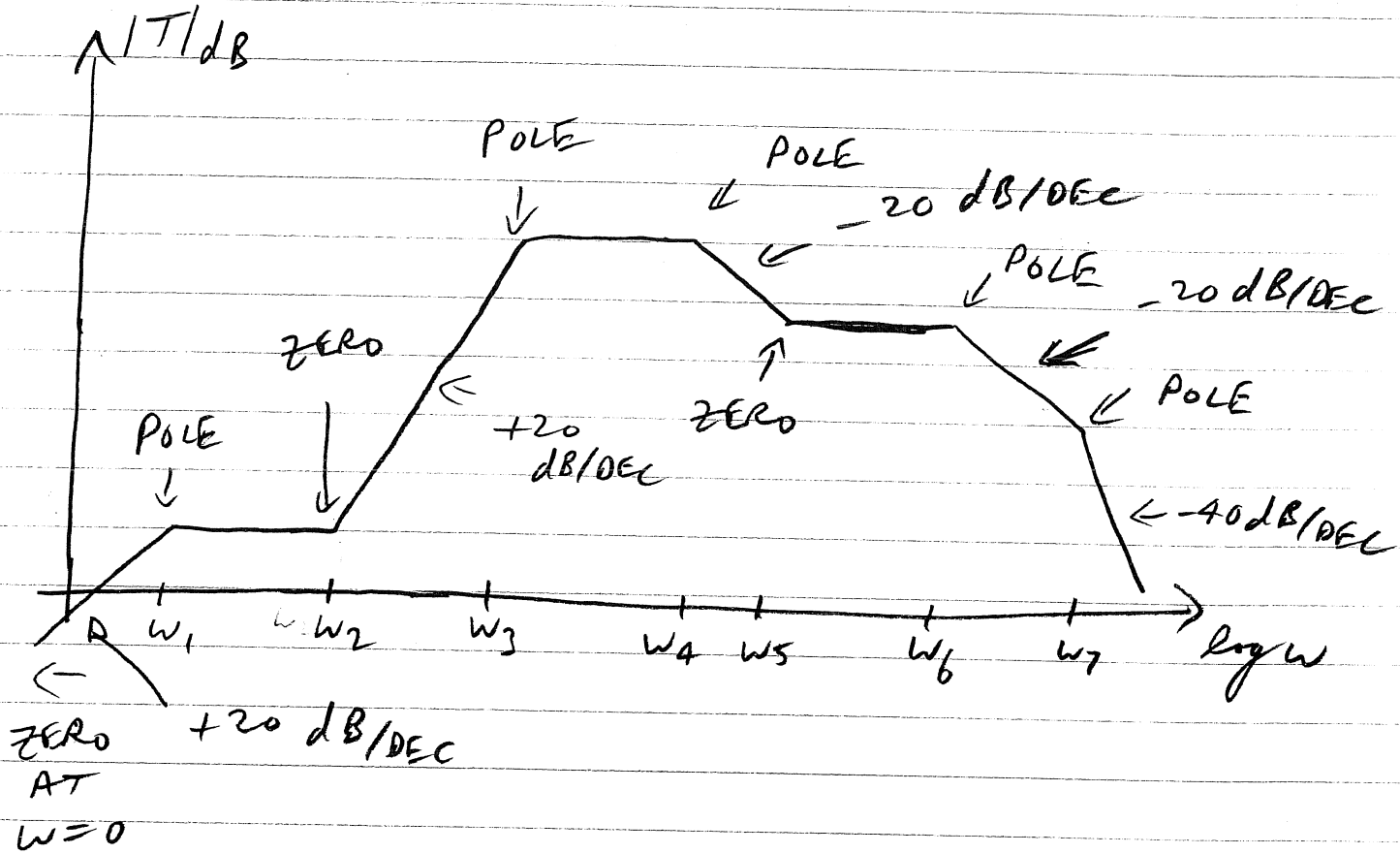

POLES CAN BE FOUND BY τ AND DO NOT DEPEND ON WHERE INPUT APPLIED OR OUTPUT TAKEN.

ZEROS REQUIRE ANALYSIS (OR EXPERIENCE)

EX

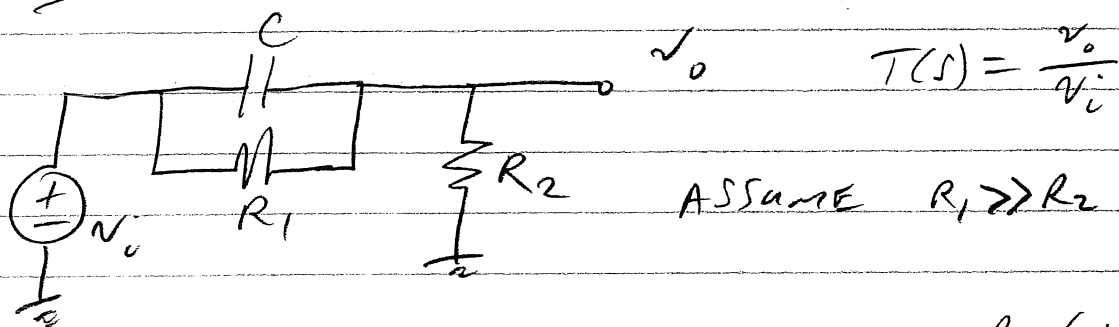

CAN SOLVE TO FIND $T(s) = \frac{R_2(1+sCR_1)}{(R_1+R_2+sCR_1R_2)}$

$$T(s) = \left(\frac{R_2}{R_1+R_2} \right) \left(\frac{1+sCR_1}{1+sC(R_1 \parallel R_2)} \right)$$


SO $T(s)$ HAS ZERO AT $\omega_z = \frac{1}{CR_1}$

AND POLE AT $\omega_p = \frac{1}{C(R_1 \parallel R_2)}$

FROM INSPECTION INSTEAD OF ANALYSIS

$$\tau_p = C(R_1 \parallel R_2) \Rightarrow \omega_p = \frac{1}{C(R_1 \parallel R_2)}$$


$\tau_z = CR_1 \Rightarrow \omega_z = \frac{1}{CR_1}$
 SINCE WHEN $\left| \frac{1}{sC} \parallel R_1 \right| = \frac{R_1}{\sqrt{2}} \leftarrow$ IMPEDANCE GOING TO ZERO

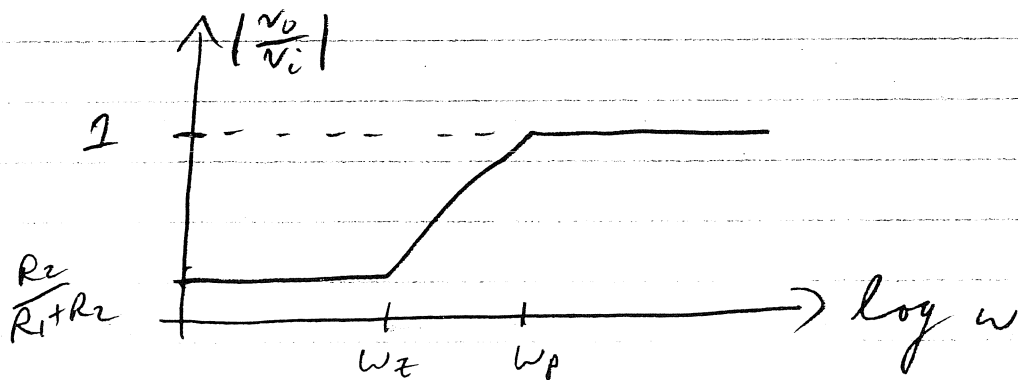

UNITY GAIN FREQ $f_t = \frac{\omega_t}{2\pi}$
OF A STC WHEN LOW FREQ GAIN $\gg 1$

CONSIDER
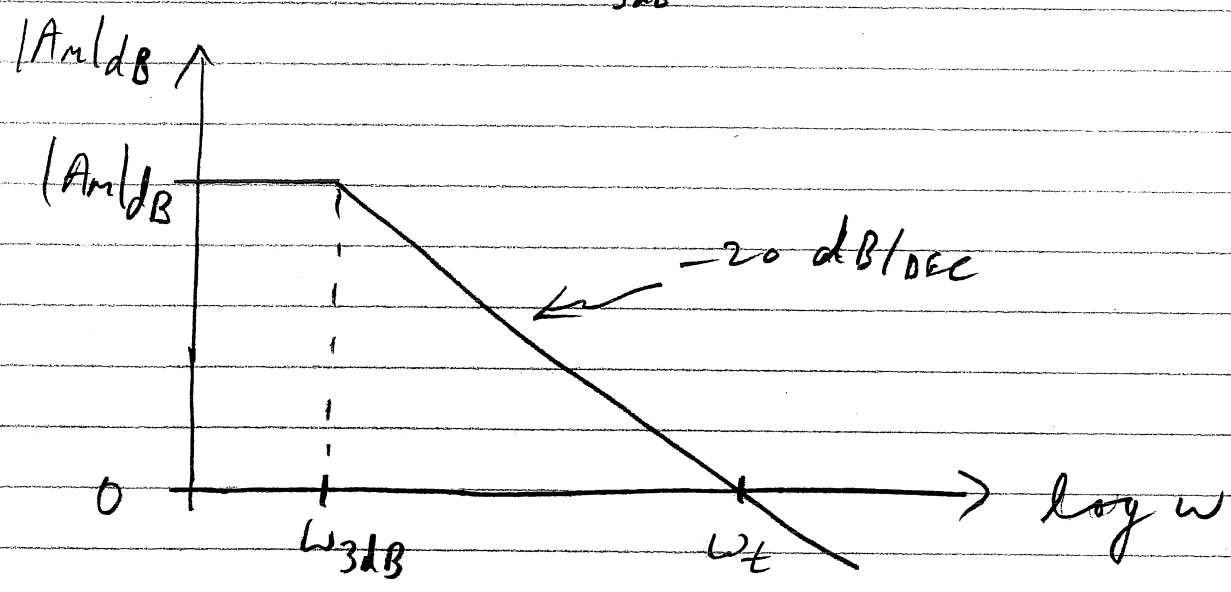
$$T(s) = \frac{A_M}{1 + s/\omega_{3dB}} \quad A_M \gg 1$$



ω_t OCCURS WHEN $|T(j\omega_t)| = 1$

$$\left| \frac{A_M}{1 + \frac{j\omega_t}{\omega_{3dB}}} \right| = 1$$

$\omega_t \gg \omega_{3dB}$ SINCE $A_M \gg 1$

$$\left| \frac{A_M}{\frac{j\omega_t}{\omega_{3dB}}} \right| \approx 1 \Rightarrow \omega_t \approx |A_M| \omega_{3dB}$$

OR $f_t \approx |A_M| f_{3dB}$