


(TRI)

TRANSISTOR REVIEW

MOSFET

N-CHANNEL \Rightarrow NMOS

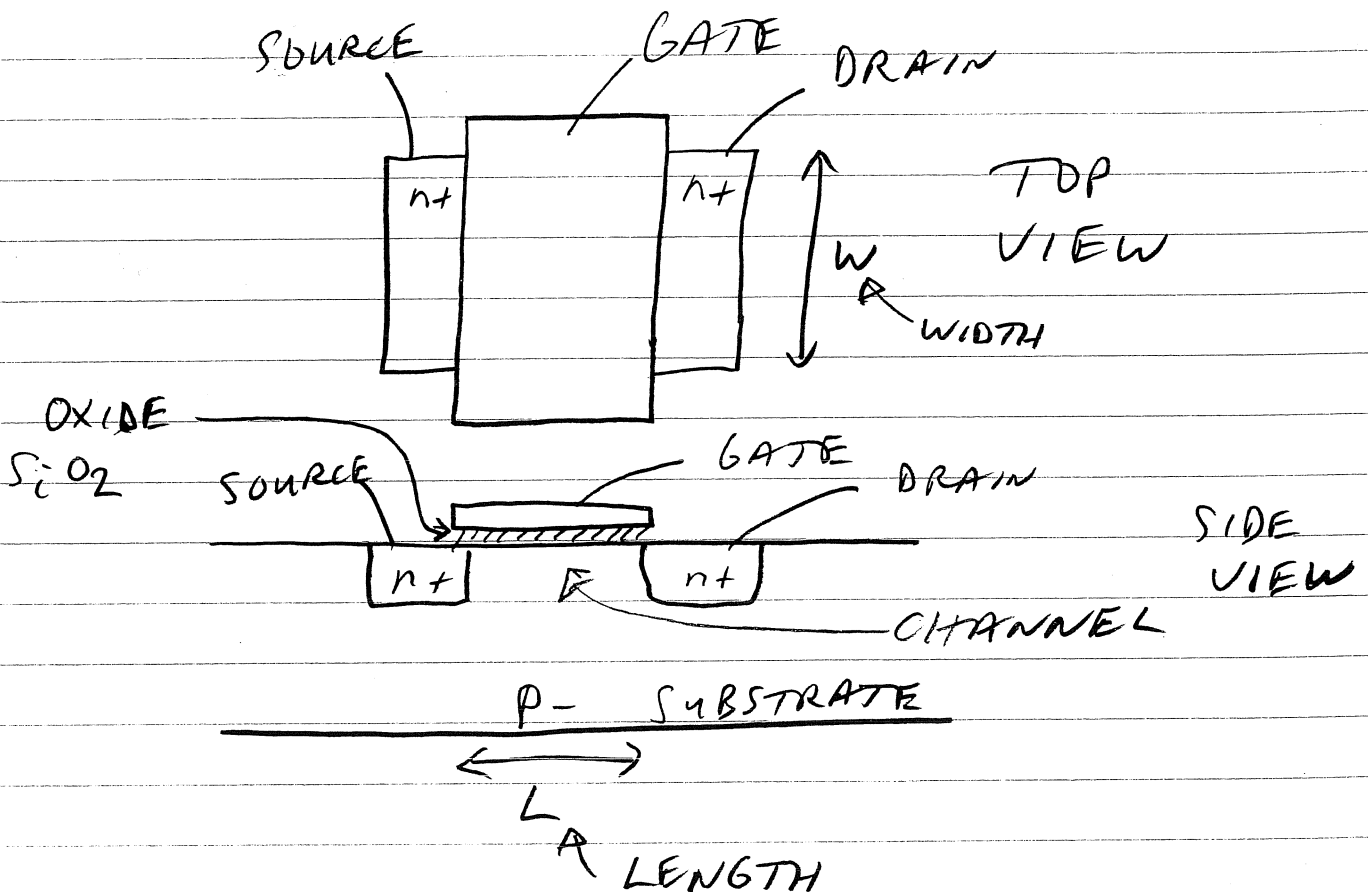METAL OXIDE SEMICONDUCTOR FIELD EFFECT TRANSISTOR




n+ SILICON WITH HIGHLY DOPED ARSENIC, As
OR PHOSPHORUS, P

P- SILICON WITH LIGHTLY DOPED BORON, B

TR2


MOSFET OPERATION

CUTOFF

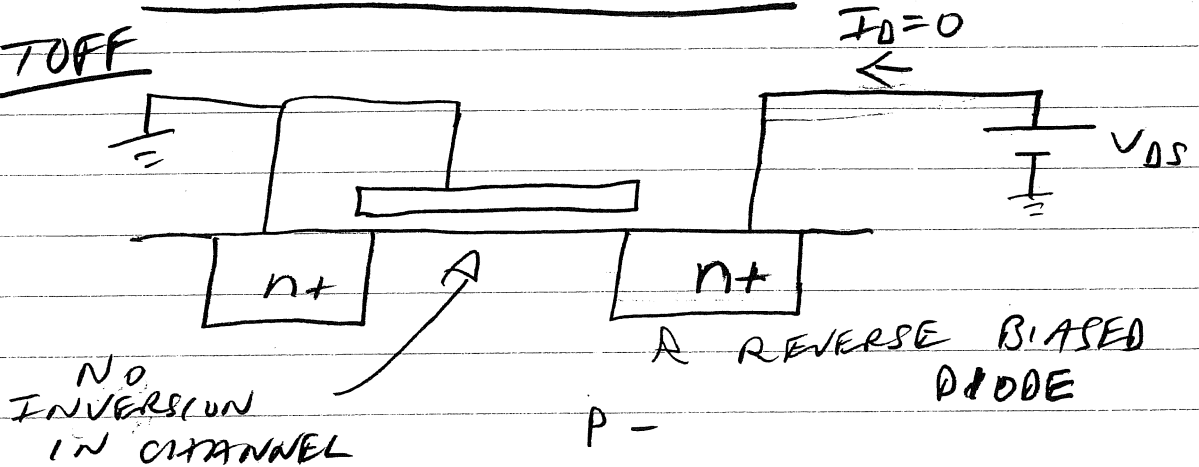

TRIODE

$V_{th} \Rightarrow$ THRESHOLD VOLTAGE

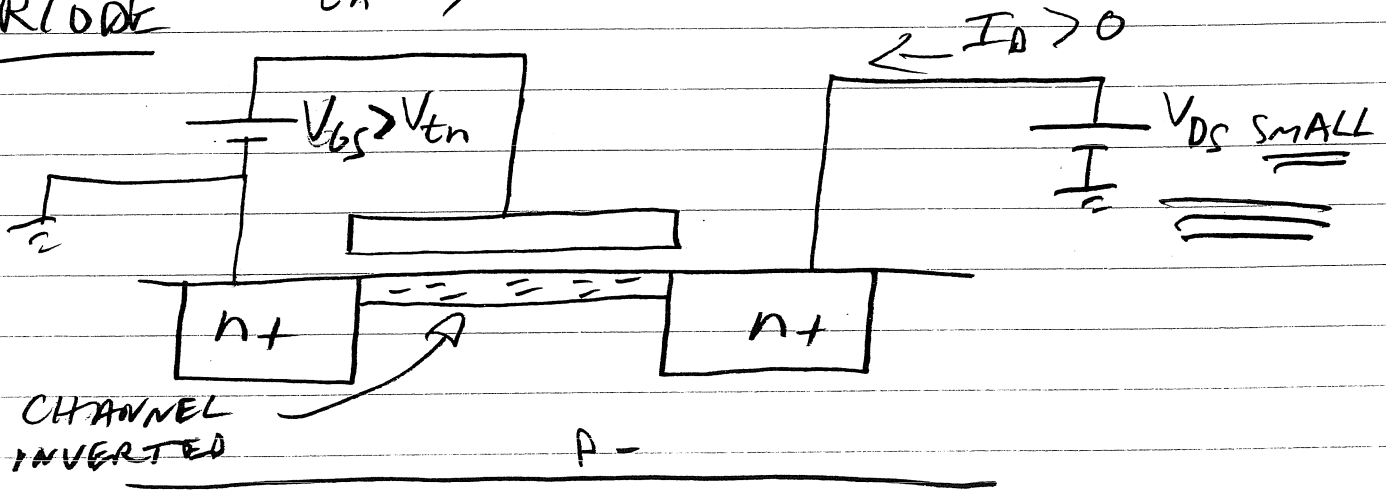


TO
n-TYPE

ELECTRONS ATTRACTED UNDER GATE
TO INVERT CHANNEL

TR3

TRLODE LARGER V_{DS}

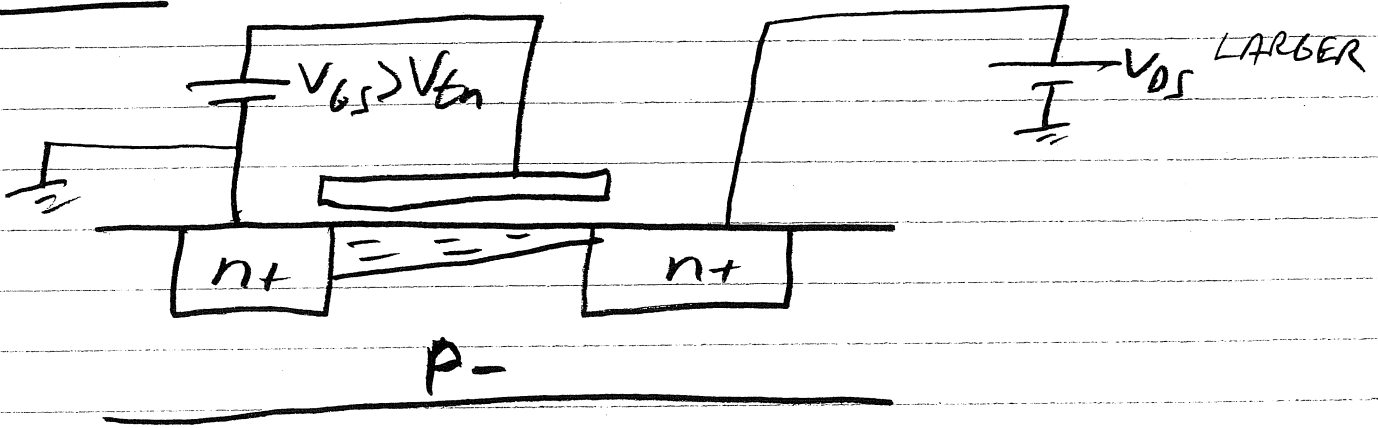

SMALLER CHANNEL NEAR DRAIN

SINCE $V_{GD} < V_{GS}$

AS V_{DS} INCREASES V_{GD} DECREASES


UNTIL $\Rightarrow V_{GD} < V_{Th}$ THEN

CHANNEL NOT INVERTED NEAR DRAIN

\Rightarrow PINCH-OFF

TRA

ACTIVE (OR SATURATION)

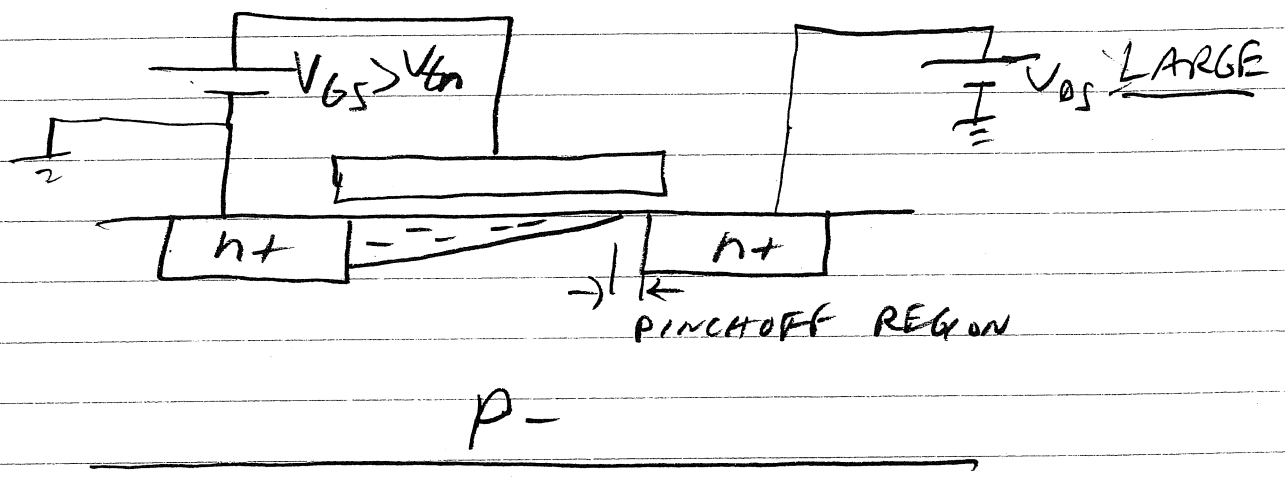

PINCH OFF OCCURS WHEN

$$V_{GD} \leq V_{Th}$$

$$V_{GS} - V_{DS} \leq V_{Th}$$

$$V_{DS} \geq V_{GS} - V_{Th}$$


PINCH-OFF OCCURS

AS $V_{DS} \uparrow$ PINCH-OFF REGION INCREASES
& I_D CONSTANT

(ELECTRONS SWEPT ACROSS PINCH-OFF REGION)


ACTUALLY I_D SMALL CHANGE DUE TO SMALLER CHANNEL \Rightarrow MODEL

WITH λ

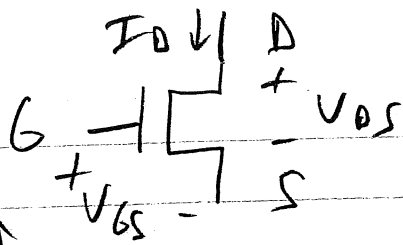


TR4A

$$\frac{I_D}{I_D} = 0$$

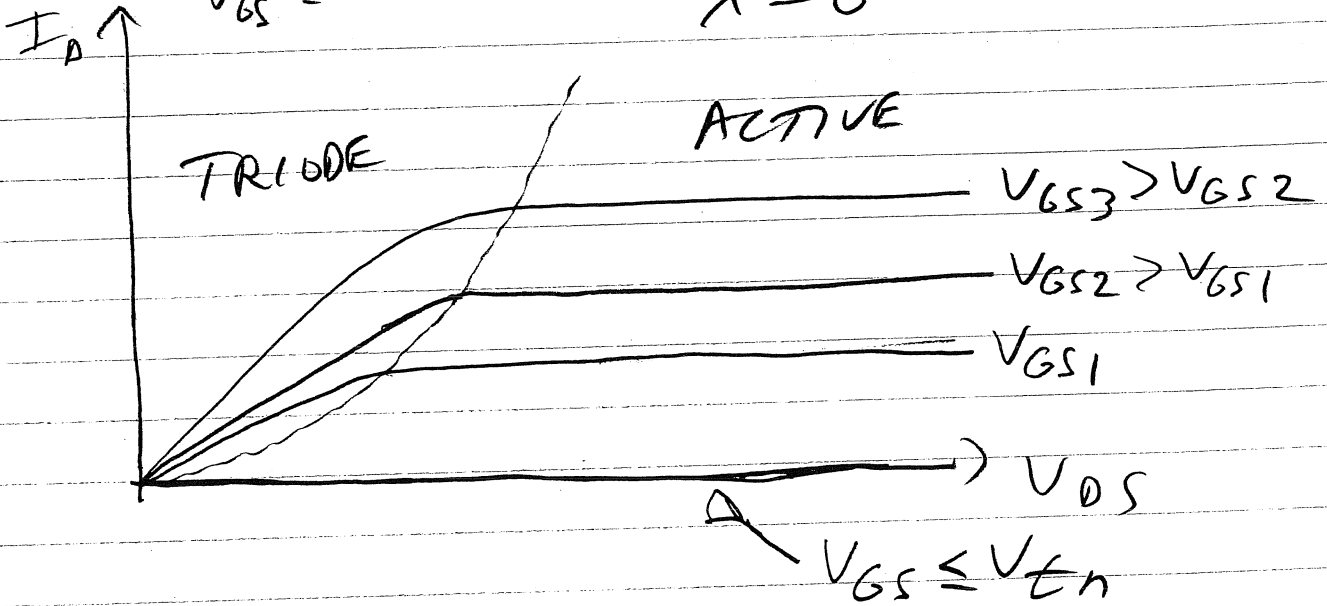



$$I_D \quad \lambda \neq 0$$

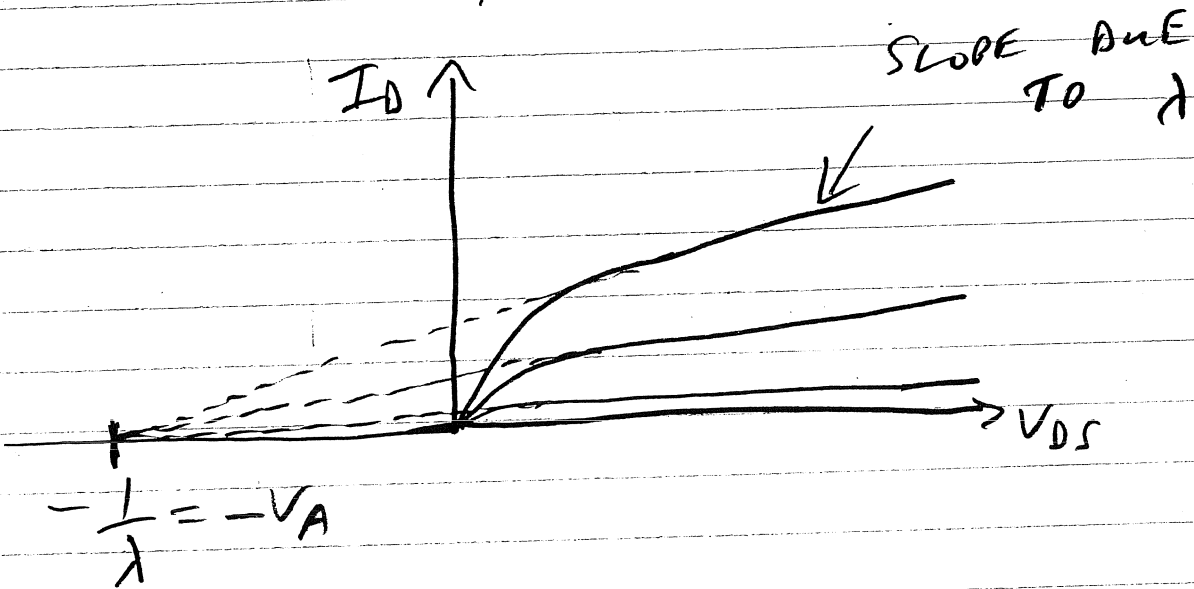

TRANSISTOR
REVIEW

MOSFET


NMOS

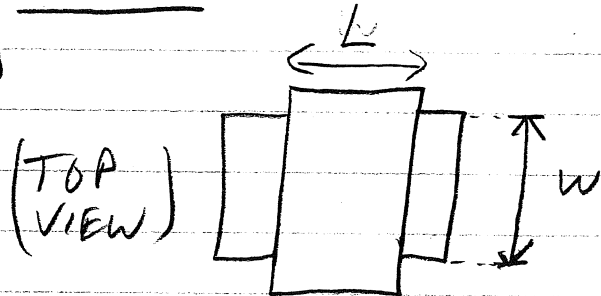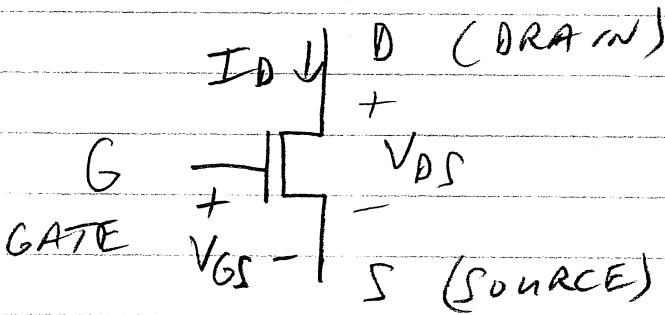

$V_{DS} \geq 0$

$I_D \geq 0$

(SIDE VIEW)

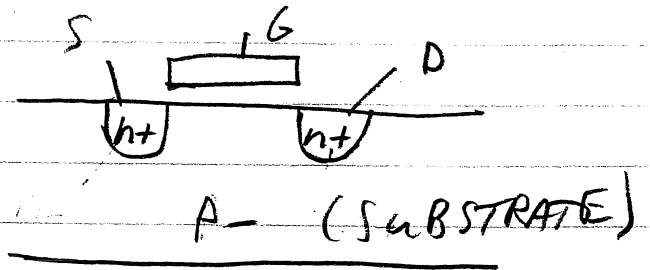

A MOSFET IS A SYMMETRICAL DEVICE

=> THE SOURCE IS THE n+ REGION WITH LOWER VOLTAGE

(IT COULD SWITCH DURING OPERATION)

DEFINE $V_{OV} \equiv V_{GS} - V_{th}$

V_{OV} => OVERDRIVE VOLTAGE

V_{th} => THRESHOLD VOLTAGE

$V_{th} > 0$ (ENHANCEMENT NMOS)

TR6

$W \Rightarrow$ WIDTH OF TRANSISTOR [m]

$L \Rightarrow$ LENGTH OF TRANSISTOR [m]

$\mu_n \Rightarrow$ ELECTRON MOBILITY IN CHANNEL [m²/V·s]

$C_{ox} \Rightarrow$ GATE OXIDE CAPACITANCE/AREA [F/m²]

$\lambda \Rightarrow$ CHANNEL LENGTH MODULATION PARAMETER [V⁻¹]

$\lambda = \frac{1}{V_A}$ V_A IS EARLY VOLTAGE

NMOS

3 REGIONS OF OPERATION

CUTOFF

$$V_{GS} \leq V_{th}$$

$$I_D = 0$$

TRIODE

$$V_{GS} \geq V_{th}, V_{DS} \leq V_{OV}$$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L}\right) \left(V_{OV} - \frac{V_{DS}}{2}\right) V_{DS}$$



ACTIVE

$$V_{GS} \geq V_{th}, V_{DS} \geq V_{OV}$$

$$I_D = \left(\frac{\mu_n C_{ox}}{2}\right) \left(\frac{W}{L}\right) V_{OV}^2 [1 + \lambda V_{DS}]$$

TR7

PMOS

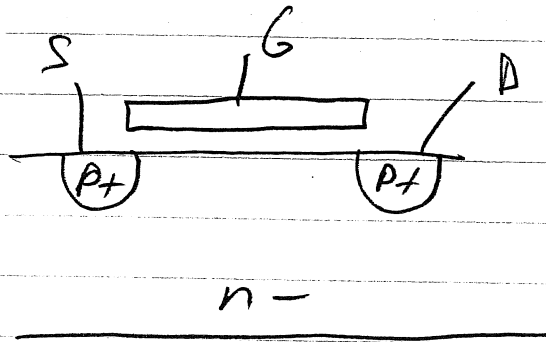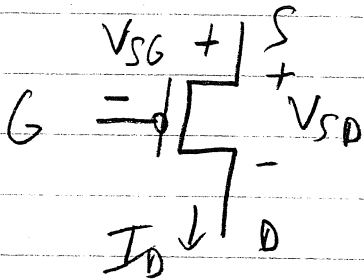

$$V_{SD} \geq 0$$

$$I_D \geq 0$$

SOURCE IS DRAIN / SOURCE JUNCTION
AT HIGHER VOLTAGE

$\mu_p \Rightarrow$ MOBILITY OF HOLES IN CHANNEL

$C_{ox} \Rightarrow$ SAME AS NMOS

$V_{tp} \Rightarrow$ THRESHOLD VOLTAGE, $V_{tp} < 0$

DEFINE V_{ov}

$$V_{ov} \equiv V_{SG} - |V_{tp}|$$

TR8

PMOS 3 REGIONS OF OPERATION

CUTOFF

$$V_{SG} \leq |V_{TP}|$$

$$I_D = 0$$

TRIODE

$$V_{SG} \geq |V_{TP}|, V_{SD} \leq V_{OV}$$

$$I_D = \mu_p C_{ox} \left(\frac{W}{L}\right) \left(V_{OV} - \frac{V_{SD}}{2}\right) V_{SD}$$

ACTIVE

$$V_{SG} \geq |V_{TP}|, V_{SD} \geq V_{OV}$$

$$I_D = \left(\frac{\mu_p C_{ox}}{2}\right) \left(\frac{W}{L}\right) V_{OV}^2 \left[1 + |\lambda| V_{SD}\right]$$

$\lambda < 0$ FOR PMOS

TR9

SMALL-SIGNAL MODELS

SAME FOR PMOS + NMOS

$$r_o = \frac{1}{\lambda |I_D|} \quad \text{WHERE } I_D' \text{ IS } I_D \\ \text{WHEN } \lambda = 0$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) V_{ov} \quad (\mu_p \text{ FOR PMOS})$$

$$g_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_D}$$

$$g_m = \frac{2 I_D}{V_{ov}}$$


$$r_s = \frac{1}{g_m}$$

NOTE λ IS CONSTANT FOR A GIVEN LENGTH, L
BUT AS $L \downarrow \lambda \uparrow$


$$\lambda = \frac{\lambda'}{L} \quad \text{WHERE } \lambda' \text{ IS} \\ \text{INDEPENDENT OF } L$$

TR10

π -MODEL

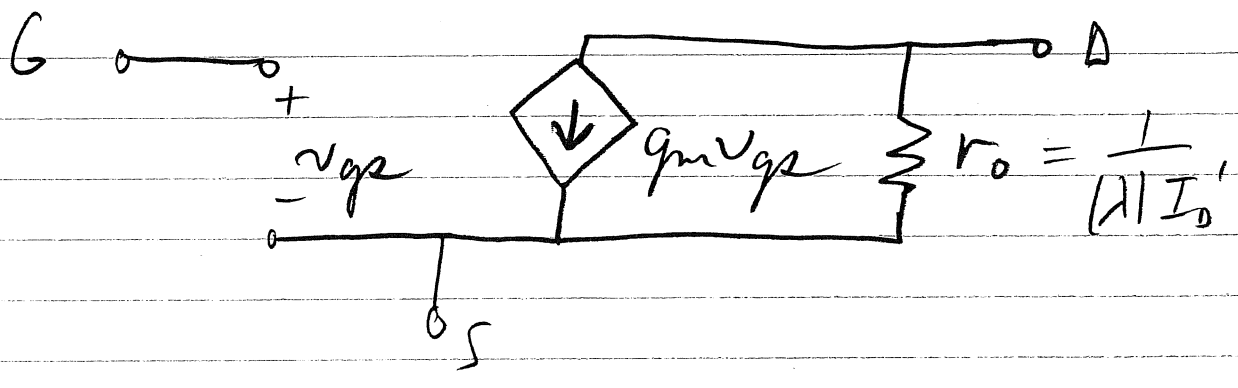

T-MODEL

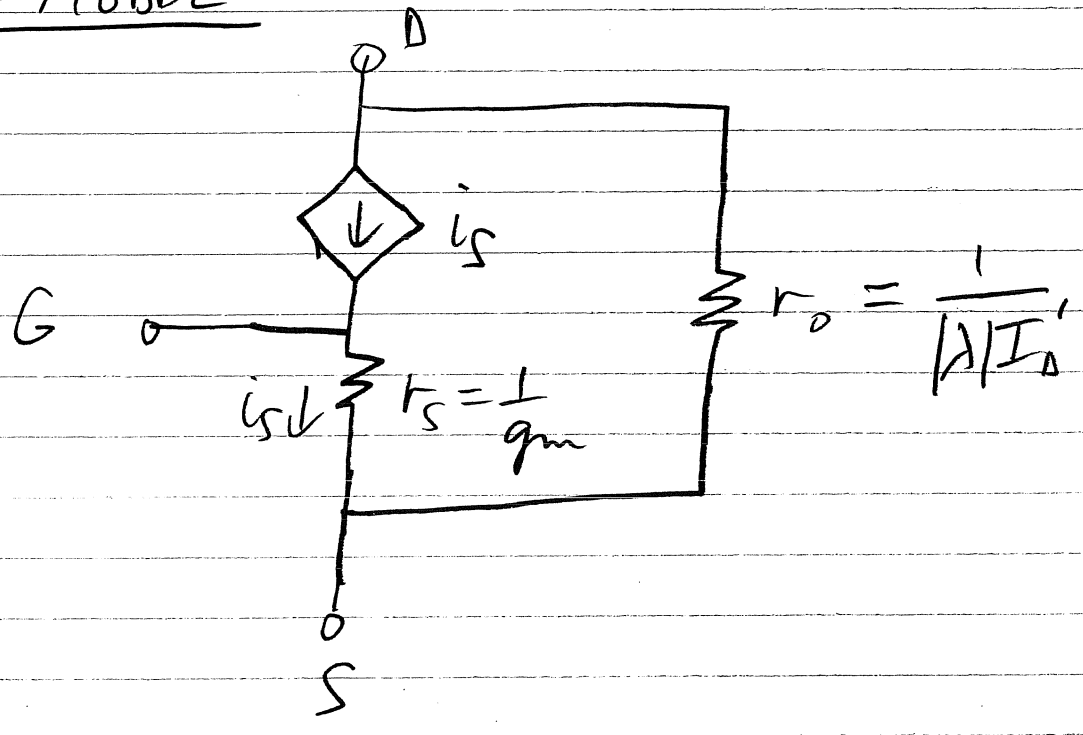

TR11

EXAMPLE 1

GIVEN

$$\mu_n C_{ox} = 120 \mu A/V^2$$

$$V_{tn} = 0.5V$$


$$W/L = 10$$

$$\lambda = 0.05 V^{-1}$$

FIND DC OPERATING POINTS +

$\frac{v_o}{v_i}$ SMALL SIGNAL

R_{in} & R_{out}

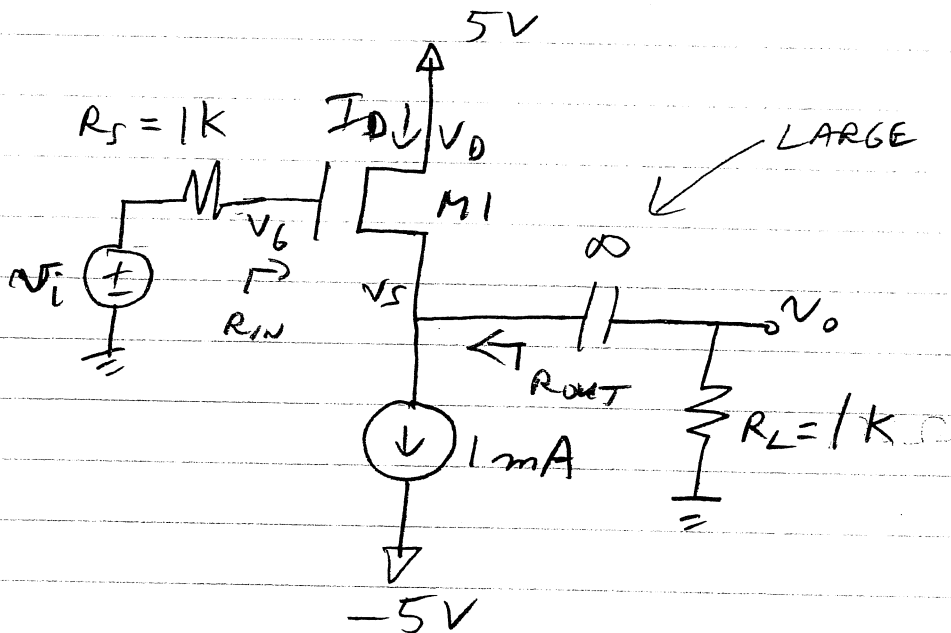

DC

$$I_G = 0 \Rightarrow \underline{v_G = 0}$$

$$I_D = 1mA \Rightarrow \text{ASSUME M1 ACTIVE}$$

$$I_D = \frac{\mu_n C_{ox} (W/L)}{2} (V_{OV})^2$$

$$1mA = \left(\frac{120e-6}{2} \right) (10) (V_{OV})^2$$

$$V_{OV} = 1.291 V$$

$$V_{ov} = 1.291 \Rightarrow V_{GS} - V_{tn} = V_{ov}$$

$$V_{GS} = V_{ov} + V_{tn} = 1.291 + 0.5$$

$$V_{GS} = 1.791 \text{ V}$$

$$\text{SINCE } V_B = 0 \Rightarrow V_{GS} = V_G - V_S = -V_S$$

$$V_S = V_G - V_{GS} = \underline{\underline{-1.791 \text{ V}}}$$

$$V_D = 5 \text{ V} \Rightarrow V_{DS} = 5 - (-1.791) = 6.791 \text{ V}$$

$V_{DS} > V_{GS} - V_{tn}$ SO ACTIVE IS (CORRECT)

$$g_m = \frac{2I_D}{V_{ov}} = \frac{2(1 \text{ mA})}{1.291} = 1.55 \text{ mA/V}$$

$$r_s = \frac{1}{g_m} = 646 \Omega$$

$$r_o = \frac{1}{\lambda I_D} = 20 \text{ k}$$

TR12A

IF ASSUME MI CUTOFF

$$I_G = 0 \Rightarrow V_G = 0$$

$$I_D = 0 \Rightarrow V_S = -5V$$

$$\text{So } V_{GS} = +5V \neq V_{GS} > V_{th}$$

So NOT CUTOFF X

IF ASSUME MI TRIODE

$$\text{So } \begin{cases} V_{GS} \geq V_{th} \\ V_{DS} \leq V_{OV} \end{cases}$$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L}\right) \left(V_{OV} - \frac{V_{DS}}{2}\right) V_{DS}$$

$$1e-3 = (120e-6)(10) \left(V_{OV} - \frac{V_{DS}}{2}\right) V_{DS}$$

$$\left(V_{OV} - \frac{V_{DS}}{2}\right) V_{DS} = 0.8333 \quad (1)$$

$$\downarrow V_{DS} = V_D - V_S \quad V_D = 5V$$

$$V_S = V_G - V_{GS} = V_G - (V_{OV} + V_{th})$$

$$V_S = 0 - (V_{OV} + 0.5) = -V_{OV} - 0.5$$

$$V_{DS} = 5 + V_{OV} + 0.5$$

$$V_{DS} = 5.5 + V_{OV} \quad (2)$$

COMBINE (1) & (2)

$$V_{DS} = 11.15$$

$$0.5V_{DS} - 5.5V_{DS} - 0.8333 = 0$$

OR -0.15


$$V_{DS} > V_{OV}$$

$$V_{DS} < 0 \quad X$$

X
NOT TRIODE

SMALL-SIGNAL

TR13

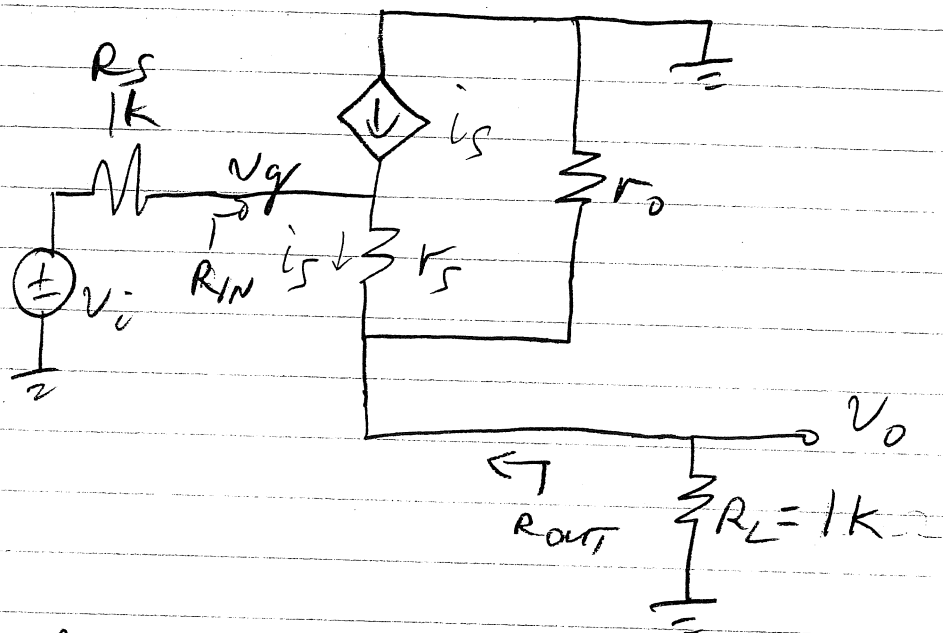

$R_{IN} \rightarrow \infty$ SINCE $i_g = 0$

$$v_g = \frac{R_{IN}}{R_{IN} + R_S} v_i = v_i \quad \text{SINCE } R_{IN} \rightarrow \infty$$

$$v_o = \frac{R_L \parallel r_o}{(R_L \parallel r_o) + R_S} v_g = \frac{(1k \parallel 20k)}{(1k \parallel (20k) + 646)} v_g$$

$$v_o = \frac{952}{952 + 646} v_g = 0.596 v_g$$


So $v_o = 0.596 v_i$ SINCE $v_g = v_i$

$$\underline{\underline{\frac{v_o}{v_i} = 0.596 \text{ V/V}}}$$

TR14

R_{out}

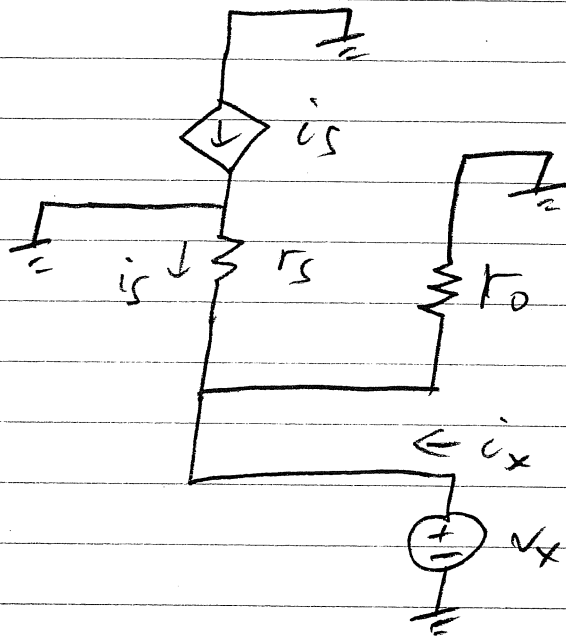SET $v_i = 0 \Rightarrow v_g = 0$
SINCE $i_g = 0$



$$R_{out} \equiv \frac{v_x}{i_x}$$

$$i_x = \frac{v_x}{r_s} + \frac{v_x}{r_o} \Rightarrow \frac{i_x}{v_x} = \frac{1}{r_s} + \frac{1}{r_o}$$

$$R_{out} = \left(\frac{1}{r_s} + \frac{1}{r_o} \right)^{-1} = r_s \parallel r_o$$

$$= \underline{\underline{626 \Omega}}$$

TR16

$$I_D = \frac{\mu_p C_{ox}}{2} \left(\frac{W}{L}\right) (V_{SG} - |V_{tp}|)^2$$

$$1 \text{ mA} = \frac{30 \times 10^{-6}}{2} (10) (V_{SG} - 0.6)^2$$

$$V_{SG} = \underline{3.182 \text{ V}} \quad \text{OR} \quad -1.982 \quad \left\{ \begin{array}{l} \text{NOT POSSIBLE} \\ \text{SINCE} \\ V_{SG} \geq |V_{tp}| \end{array} \right.$$

$$V_S = 0 + V_{SG} = 3.182 \text{ V} \quad V_{OV} = V_{SG} - |V_{tp}| = 2.582 \text{ V}$$

$$V_D = -5 + 3 = -2 \text{ V}$$


$$V_{SD} = 3.182 - (-2) = 5.182 \geq V_{OV} = 2.582$$

ACTIVE ✓

$$g_m = \frac{2I_D}{V_{OV}} = \frac{2(1 \text{ e-3})}{2.582} = 0.775 \text{ mA/V}^2$$

$$r_s = \frac{1}{g_m} = 1.291 \text{ k}$$
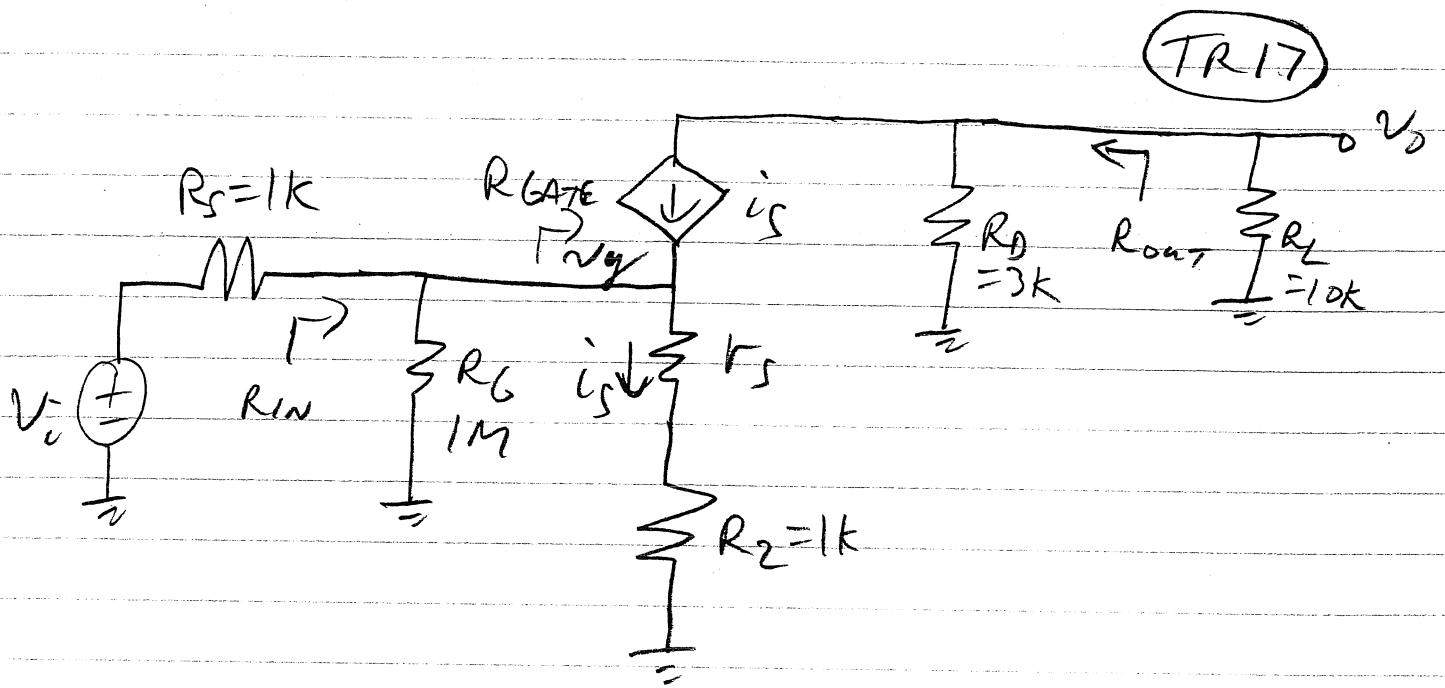
$$r_o \Rightarrow \infty \quad \text{SINCE } \lambda = 0$$



$$R_{IN} = R_G \parallel R_{GATE} \quad \downarrow \quad R_{GATE} \rightarrow \infty$$

$$= R_G = 1M\Omega$$

$$R_{out} = R_D = 3k \quad \text{SET } v_i = 0 \text{ WHEN FINDING } R_{out}$$

$$v_g = \frac{R_G}{R_G + R_S} v_i = \frac{1M}{1M + 1k} v_i = 0.999 v_i \approx v_i$$

$$i_s = \frac{v_g}{r_s + R_2} \quad v_o = -i_s (R_D \parallel R_L)$$

$$v_o = \frac{-(R_D \parallel R_L)}{r_s + R_2} v_g = \frac{-(3k \parallel 10k)}{1.291k + 1k} v_g$$

$$v_o \approx -v_g \Rightarrow \frac{v_o}{v_i} \approx -1 \frac{V}{V}$$

BIPOLAR TRANSISTORS

NPN & PNP TRANSISTORS


NPN

E - EMITTER


B - BASE

C - COLLECTOR

TOP VIEW

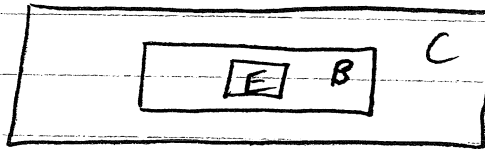



SIDE VIEW

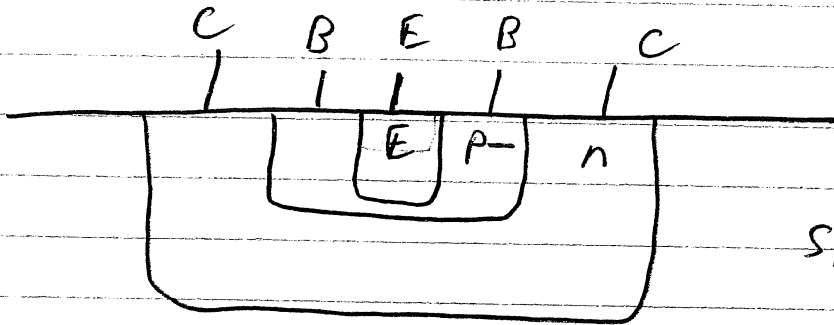

NOT SYMMETRICAL

CB JUNCTION MUCH LARGER AREA THAN BE JUNCTION. MORE POWER DISSIPATED IN CB JUNCTION.

BASE IS LIGHTLY DOPED

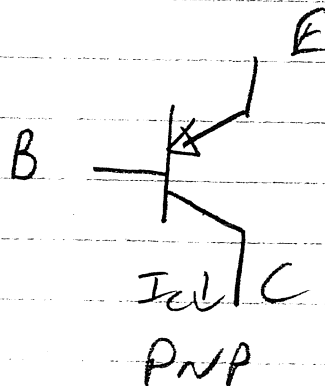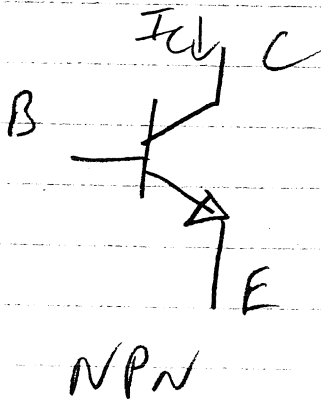

$$I_E = I_B + I_C$$

TR19

3 MODES OF OPERATION

MODE	EJT (EB JUNCTION)	CJT (CB JUNCTION)	TYPICAL USE
CUTOFF	REVERSE	REVERSE	OFF SWITCH
ACTIVE	FORWARD	REVERSE	AMPLIFIER
SATURATION	FORWARD	FORWARD	ON SWITCH

FORWARD WHEN $V_J \gtrsim 0.5 V$

REVERSE WHEN $V_J \lesssim 0.5 V$

WHEN FORWARD BIASED ASSUME

$$V_{BE} \approx 0.7 V$$

$$V_{BC} \approx 0.5 V \text{ SINCE MUCH LARGER}$$

SO IF IN SATURATION $V_{CE} \approx 0.2 V$

$$\begin{aligned} V_{CE} &= V_{CB} - V_{EB} = -V_{BC} - (-V_{BE}) = -V_{BC} + V_{BE} \\ &= 0.7 - 0.5 = \underline{\underline{0.2 V}} \end{aligned}$$

SO $V_{CE} \approx 0.2 V$ IN SATURATION

TR20

CUTOFF EBJ + CBJ REVERSE

$$I_B \approx 0 \quad I_C \approx 0$$

SATURATION EBJ + CBJ FORWARD

$$V_{CE} \approx 0.2V \quad \left(\begin{array}{l} \text{ACTUALLY } V_{CE \text{ SAT}} \\ \text{VOLTAGE} \end{array} \right)$$

ACTIVE EBJ FORWARD + CBJ REVERSE

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left[1 + \frac{V_{CE}}{V_A} \right]$$

SUGGESTS $V_{BE} \approx 0.7V$

I_S SCALE CURRENT + IS PROPORTIONAL TO BEJ AREA

V_T THERMAL VOLTAGE $V_T = \frac{kT}{q} \approx 26 \text{ mV}$
AT ROOM TEMP

V_A EARLY VOLTAGE

TR 21

$$i_c = \beta i_b$$

$\beta \approx 100$
DEPENDS ON DOPING LEVELS
BASE WIDTH, ETC.

$$i_e = (\beta + 1) i_b$$

SINCE $i_e = i_b + i_c$


$$\alpha \equiv \frac{\beta}{\beta + 1}$$

$$i_c = \alpha i_e$$

$\alpha \approx 1$ (0.99 IF $\beta = 100$)


SMALL-SIGNAL

π-MODEL =

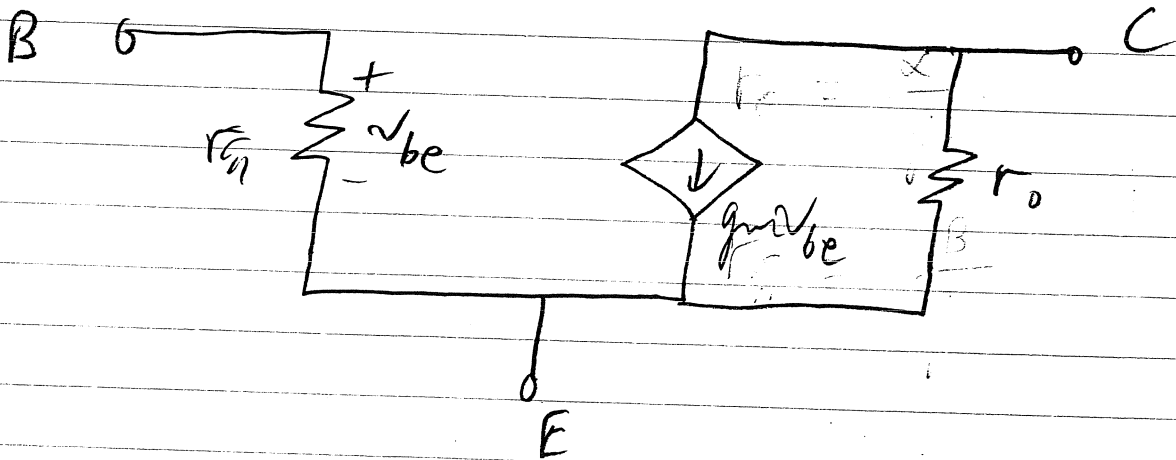

TR22

T-MODEL

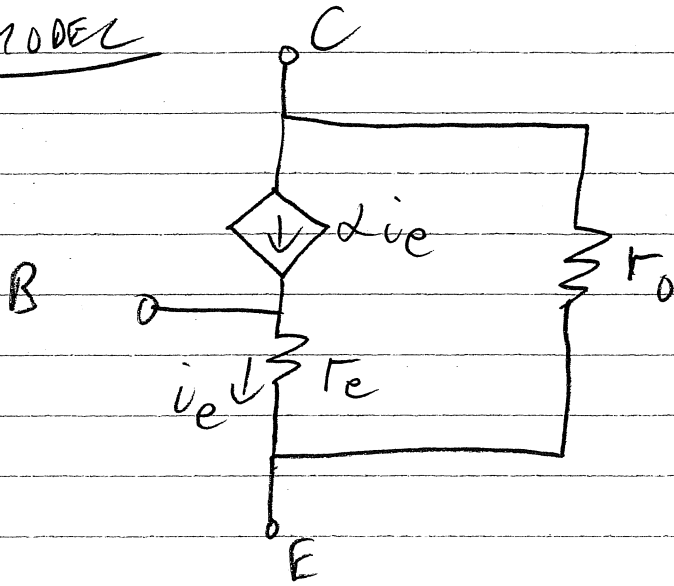


$$g_m = \frac{I_c}{V_T}$$

$$V_T = \frac{kT}{q} \approx 26 \text{ mV}$$


$$r_e = \frac{\alpha}{g_m} = \frac{V_T}{I_E}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

$$r_o = \frac{|V_A|}{I_c}$$

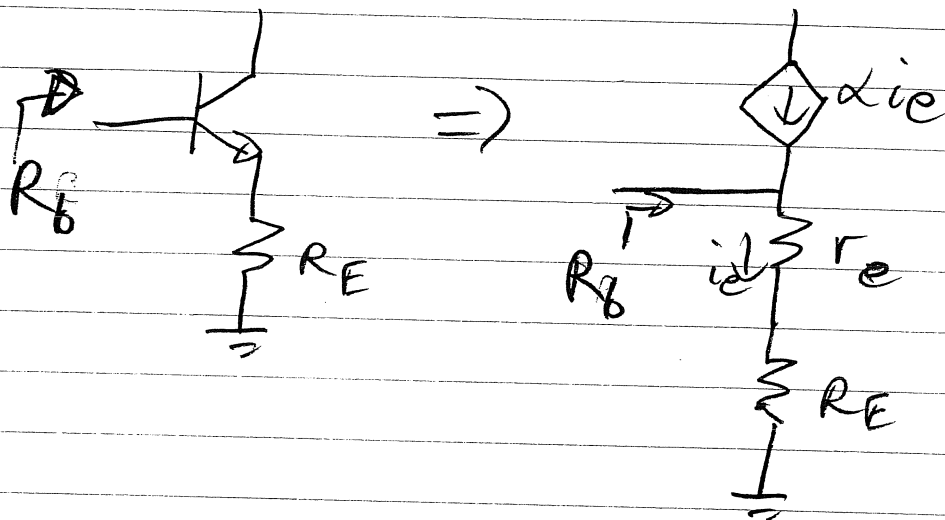IMPEDANCE RULES FOR BJT
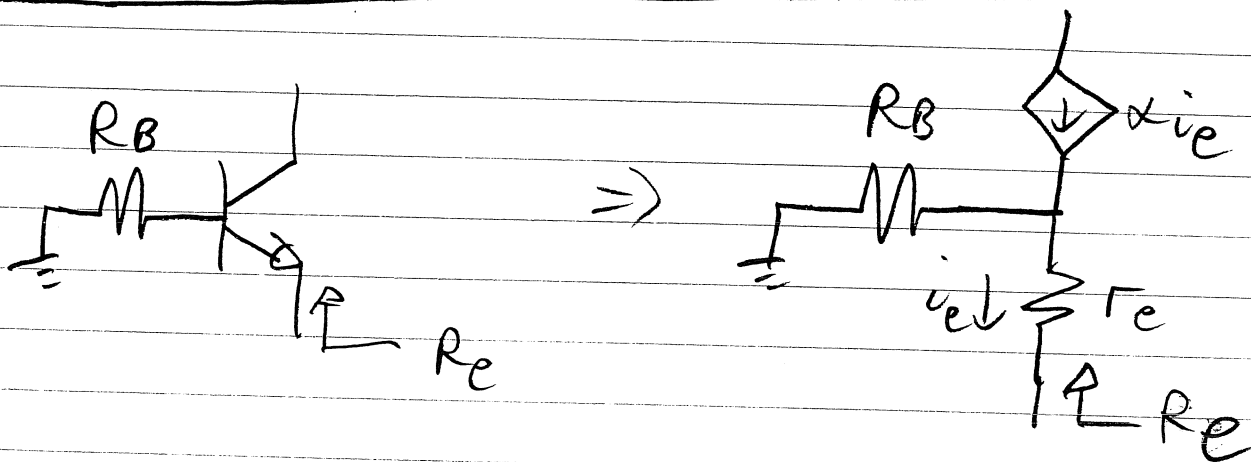
$$R_b = (\beta + 1)(r_e + R_E) = r_{\pi} + (\beta + 1)R_E$$



$$R_e = \frac{R_B}{\beta + 1} + r_e = \frac{R_B + r_{\pi}}{\beta + 1}$$