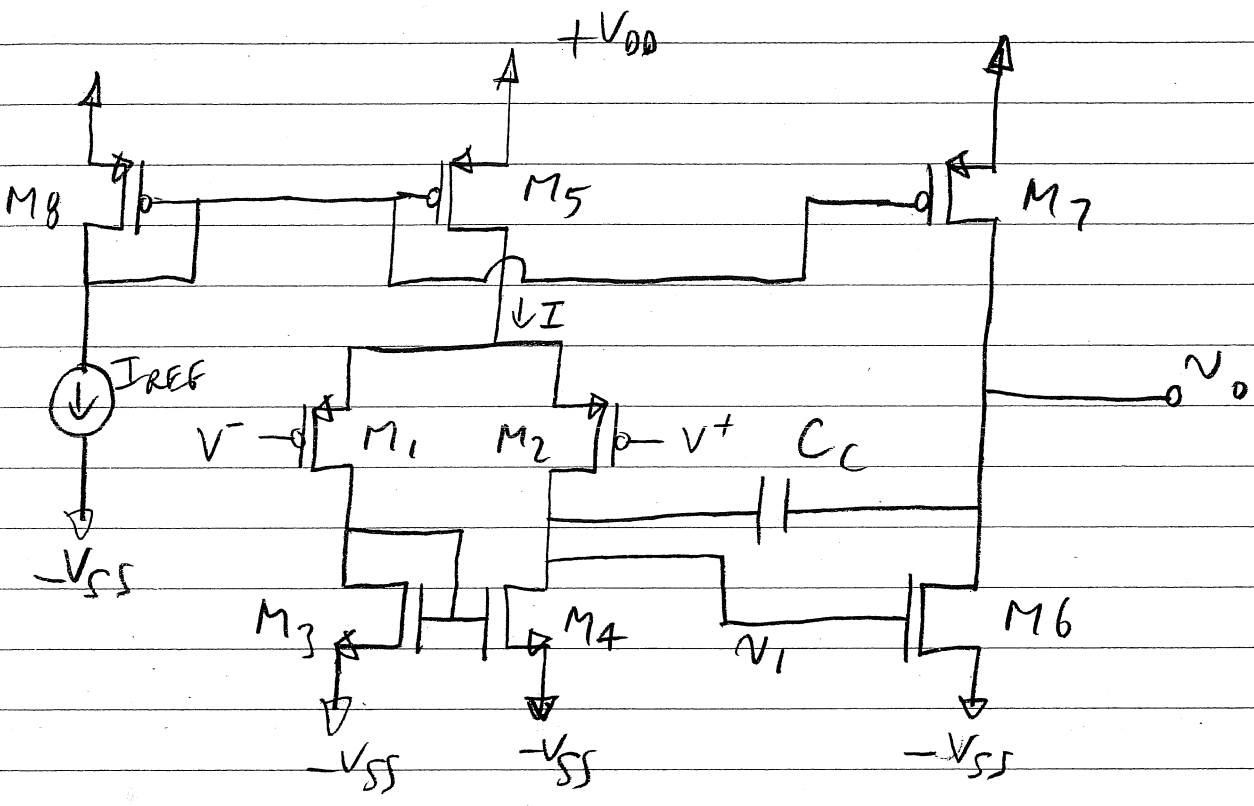


TWO-STAGE CMOS OPAMP




FOR 0 SYSTEMATIC dc OFFSET

(FROM BEFORE)

$$\frac{(W/L)_6}{(W/L)_4} = 2 \frac{(W/L)_7}{(W/L)_5}$$

RECALL FOR ACTIVE REGION

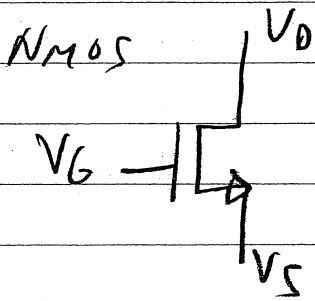


$$V_{DS} \geq V_{GS} - V_{tn}$$

$$V_D \geq V_G - V_{tn}$$

$$V_G \leq V_D + V_{tn}$$

PMOS

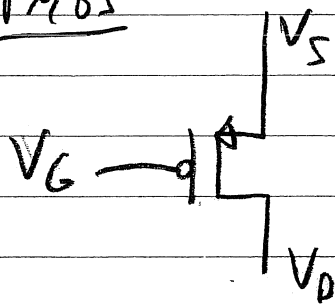

$$V_{SD} \geq V_{SG} - |V_{tp}|$$

$$-V_D \geq -V_G - |V_{tp}|$$

$$V_G \geq V_D - |V_{tp}|$$

INPUT COMMON-MODE RANGE

TIE V^+ TO V^- + CONNECT TO V_{ICM}

MIN $V_{ICM} \Rightarrow$ KEEP $M1$ & $M2$ ACTIVE

$$V_{ICM} \geq -V_{SS} + V_{tn} + V_{ov3} - |V_{tp}| \quad (1)$$

MAX $V_{ICM} \Rightarrow$ KEEP $M5$ ACTIVE

$$V_{ICM} + |V_{tp}| + |V_{ov1}| \leq V_{DD} - |V_{ov5}| \quad (2)$$

(753)

COMBINING ① & ② WE HAVE

$$-V_{SS} + V_{tn} + V_{ov3} - |V_{tp}| \leq V_{ICM} \leq V_{DD} - |V_{tp}| - |V_{ov1}| - |V_{ov5}|$$

$$\text{IF } V_{tn} \approx |V_{tp}|$$

$$-V_{SS} + V_{ov3} \leq V_{ICM} \leq V_{DD} - |V_{tp}| - |V_{ov1}| - |V_{ov5}|$$

CAN BE CLOSER TO $-V_{SS}$ THAN V_{DD}

OUTPUT VOLTAGE SWING

$$-V_{SS} + V_{ov6} \leq v_o \leq V_{DD} - |V_{ov7}|$$

WITHIN ONE V_{ov} OF EACH POWER SUPPLY.

TS4

VOLTAGE GAIN

$$v_{id} \equiv v^+ - v^-$$

$$A_v \equiv \frac{v_o}{v_{id}} = -g_{m1} (r_{o2} \parallel r_{o4})$$

WHERE $g_{m1} = \frac{2I_D}{V_{ov1}} = \frac{2(I/2)}{V_{ov1}} = \frac{I}{V_{ov1}}$

$$r_{o2} = \frac{|V_{A2}|}{(I/2)} \quad r_{o4} = \frac{|V_{A4}|}{(I/2)}$$

$$A_v = - \frac{\left(\frac{2}{V_{ov1}} \right)}{\left(\frac{1}{|V_{A2}|} \right) + \left(\frac{1}{|V_{A4}|} \right)}$$

FOR A GIVEN $I \Rightarrow$ TO INCREASE A_v ,

DECREASE V_{ov1} (LARGER W/L) $\&$ INCREASE $|V_{A2}| + |V_{A4}|$ (LONGER L)

TSS

$$A_2 \equiv \frac{v_o}{v_i} = -g_{m6} (r_{o6} \parallel r_{o7})$$

WHERE $g_{m6} = \frac{2I_{D6}}{V_{OV6}}$

$$r_{o6} = \frac{V_{A6}}{I_{D6}} \quad r_{o7} = \frac{|V_{A7}|}{I_{D6}} \quad \text{SINCE } I_{D7} = I_{D6}$$

$$A_2 = \frac{-\frac{2}{V_{OV6}}}{\left(\frac{1}{V_{A6}}\right) + \left(\frac{1}{|V_{A7}|}\right)}$$

TO INCREASE $A_2 \Rightarrow$ DECREASE V_{OV6}
(LARGE W/L)

INCREASE V_{A6}, V_{A7}
(LONGER L)

$$A_v = A_1 A_2$$

$$A_v = g_{m1} (r_{o2} \parallel r_{o4}) g_{m6} (r_{o6} \parallel r_{o7})$$

TSC

OUTPUT RESISTANCE

$$R_o = r_{o6} \parallel r_{o7}$$

IF IN FEEDBACK WITH $\beta = 1$


THEN

$$R_{of} = \frac{R_o}{1 + A_v \beta} \approx \frac{r_{o6} \parallel r_{o7}}{g_{m1}(r_{o1} \parallel r_{o2}) g_{m6}(r_{o6} \parallel r_{o7})}$$

$$R_{of} \approx \frac{1}{g_{m6} g_{m1}(r_{o1} \parallel r_{o2})}$$

FREQ RESPONSE

CAN MODEL OPAMP AS

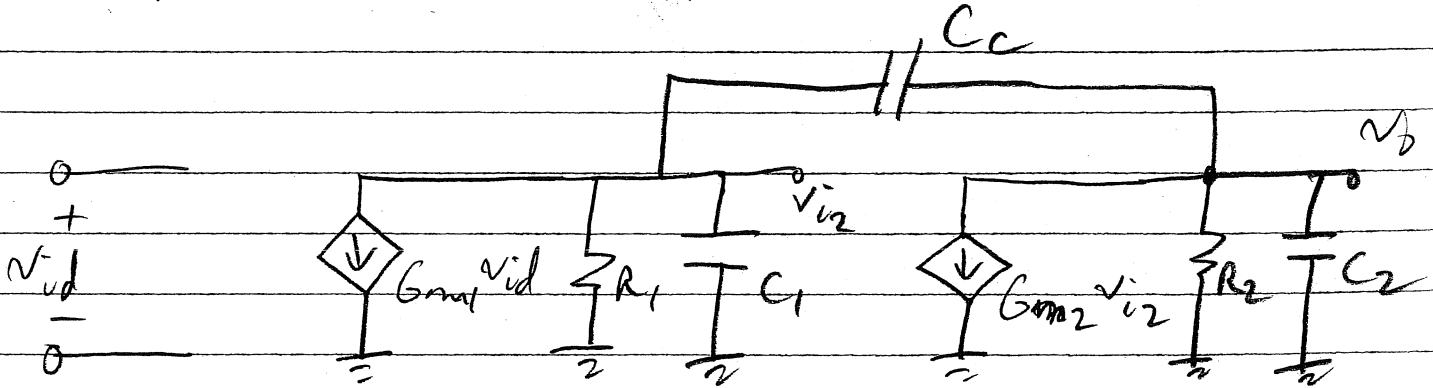

$$G_{m1} = g_{m1} \quad G_{m2} = g_{m6}$$

$$R_1 = r_{o2} \parallel r_{o4} \quad R_2 = r_{o6} \parallel r_{o7}$$

$$C_1 = C_{gd2} + C_{db2} + C_{gd4} + C_{db4} + C_{gs6}$$

$$C_2 = C_{db6} + C_{db7} + C_{gd7} + C_L$$

C_c ADDED COMPENSATION CAPACITOR THAT INCLUDES C_{gd6}

(T58)

FROM BEFORE WE FOUND

$$f_{p1} \cong \frac{1}{2\pi R_1 G_{m2} R_2 C_c}$$

DOMINANT POLE

$$f_{p2} \cong \frac{G_{m2}}{2\pi C_2}$$

NON-DOMINANT POLE

$$f_z \cong \frac{G_{m2}}{2\pi C_c}$$

ZERO

$$\star f_t \cong |A_v| f_{p1} = \frac{G_{m1}}{2\pi C_c} \quad \begin{array}{l} \text{UNITY} \\ \text{GAIN FREQ} \end{array}$$

TO ENSURE REASONABLE STABILITY WITH $\beta=1$

REQUIRE $f_t \leq f_{p2} \star f_t \leq f_z$



SO $\frac{G_{m1}}{C_c} \leq \frac{G_{m2}}{C_2}$ (f_{p2} REQUIREMENT)

AND $G_{m1} \leq G_{m2}$ (f_z REQUIREMENT)

TS9

PHASE MARGIN (ASSUME $\beta=1$)

$$L = AB = A$$

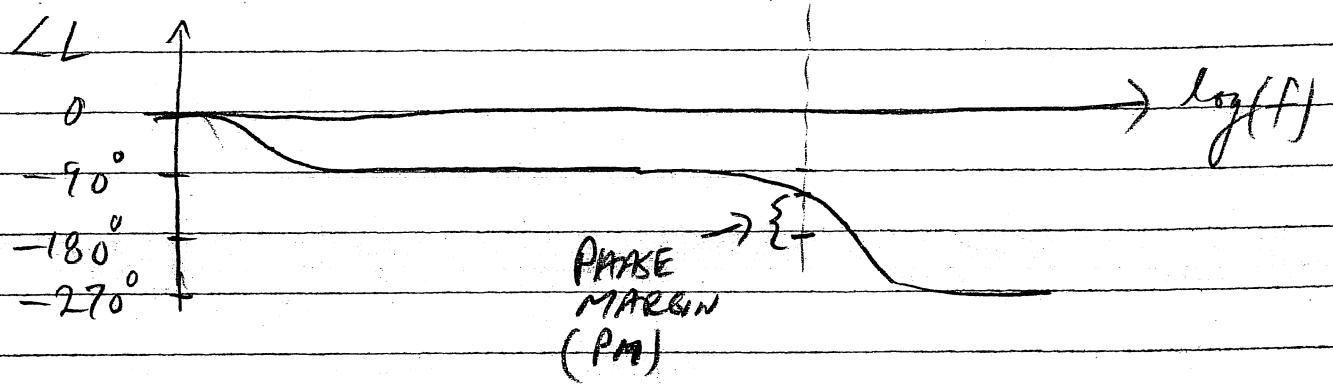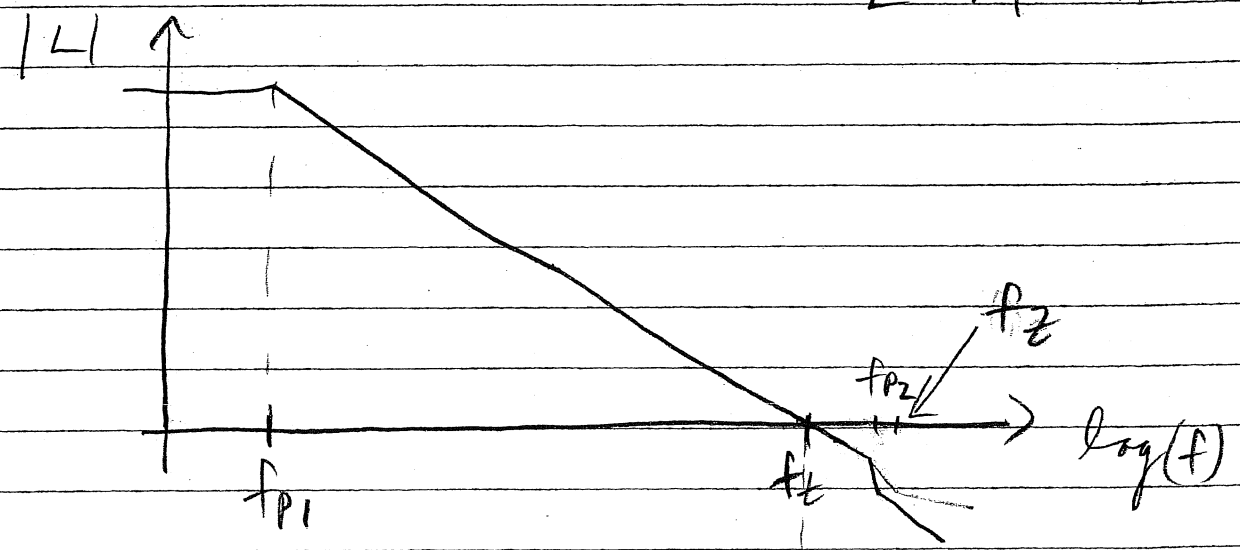

f_{p2} LEFT HALF PLANE POLE $\Rightarrow -90^\circ$ (PHASE LAG)

f_z RIGHT HALF PLANE ZERO $\Rightarrow -90^\circ$ (PHASE LAG)

$$\phi_{p2} = -\tan^{-1}\left(\frac{f_t}{f_{p2}}\right) \quad \leftarrow \text{AT } f_t \text{ DUE TO } f_{p2}$$

$$\phi_z = -\tan^{-1}\left(\frac{f_t}{f_z}\right) \quad \leftarrow \text{AT } f_t \text{ DUE TO } f_z$$

TS10

SO PHASE \angle AT $f_t \Rightarrow \phi_{TOTAL}$

$$\phi_{TOTAL} = -90^\circ - \tan^{-1}\left(\frac{f_t}{f_{p2}}\right) - \tan^{-1}\left(\frac{f_t}{f_z}\right)$$

$$\begin{aligned} \text{PHASE MARGIN } PM &= -\phi_{TOTAL} - (-180^\circ) \\ &= 180 + \phi_{TOTAL} \end{aligned}$$

$$PM = 90 - \tan^{-1}\left(\frac{f_t}{f_{p2}}\right) - \tan^{-1}\left(\frac{f_t}{f_z}\right)$$

SO RIGHT HALF PLANE ZERO CAUSES
WORSE PHASE MARGIN

(NOTE A LEFT HALF PLANE ZERO
WOULD HELP IMPROVE PHASE MARGIN)

LHP & RHP ZERO

TS10A

CONSIDER NUMERATOR ROOT

$$\left(1 + \frac{s}{\omega_z}\right) \Rightarrow s = -\omega_z$$

IF $\omega_z > 0$ LHP ZERO


$$\angle \left(1 + \frac{j\omega}{\omega_z}\right) = \angle \tan^{-1} \left(\frac{\omega}{\omega_z}\right)$$

IF $\omega = \omega_z \Rightarrow$ PHASE = 45°
($\tan^{-1}(1)$)

IF $\omega_z < 0$ RHP ZERO

$$\angle \left(1 + \frac{j\omega}{\omega_z}\right) = \angle \tan^{-1} \left(\frac{\omega}{\omega_z}\right)$$

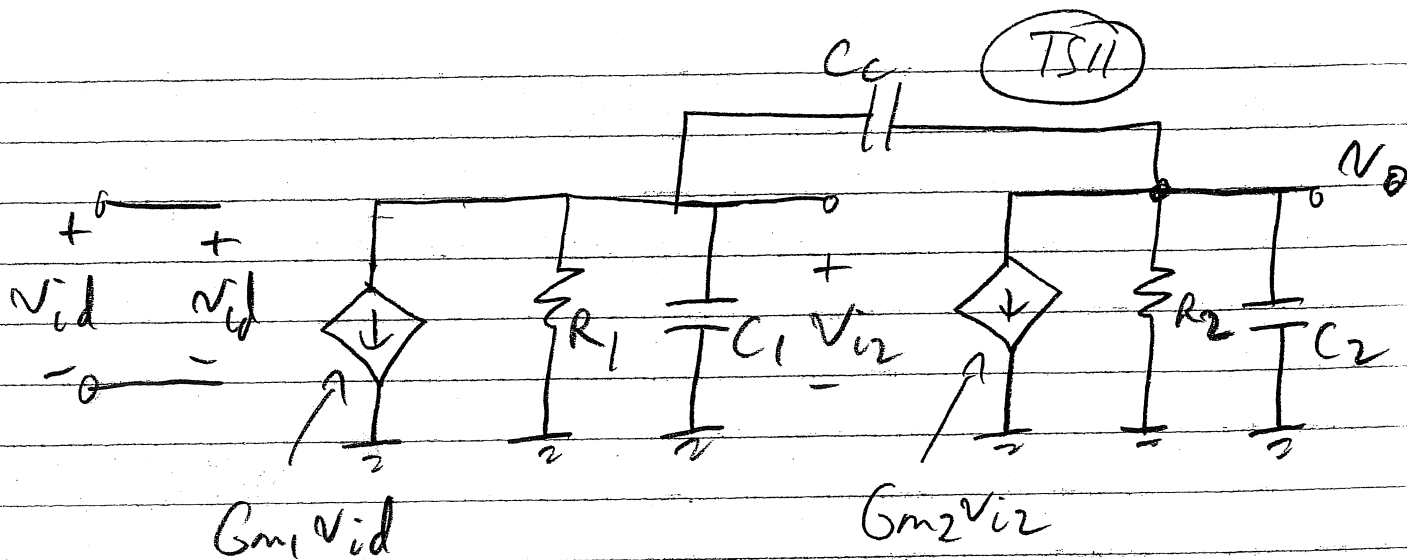IF $\omega = -\omega_z \Rightarrow$ PHASE = -45°
($\tan^{-1}(-1)$)



ZERO OCCURS WHERE $\frac{v_o}{v_{id}} = 0$

SO TO FIND ZERO CAN ASSUME $v_o = 0$

AND WRITE


$$\frac{v_{i2}}{\frac{1}{sC_c}} = G_{m2}v_{i2} \Rightarrow s = \frac{1}{C_c \left(\frac{1}{G_{m2}}\right)}$$

RHP $\omega_z = \frac{1}{C_c \left(\frac{1}{G_{m2}}\right)}$

$$f_z = \frac{1}{2\pi C_c \left(\frac{1}{G_{m2}}\right)}$$

TS12

INTRODUCE R IN SERIES WITH Cc

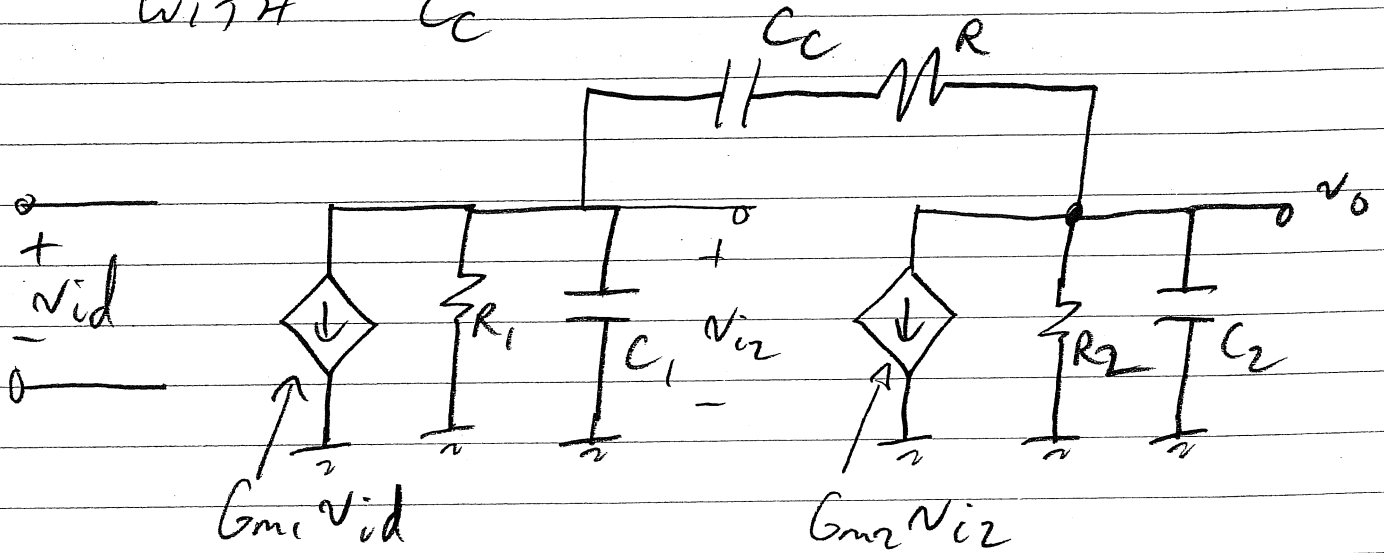

Now
$$\frac{V_{i2}}{R + \frac{1}{sC_c}} = G_{m2} V_{i2}$$

$$\Rightarrow s = \frac{1}{C_c \left(\frac{1}{G_{m2}} - R \right)} \Rightarrow \omega_z = \frac{1}{C_c \left(\frac{1}{G_{m2}} - R \right)}$$

IF $R = \frac{1}{G_{m2}} \quad \omega_z \rightarrow \infty$

MUCH BETTER PHASE MARGIN



IF $R > \frac{1}{G_{m2}}$ ZERO IN LEFT HALF PLANE

AND IMPROVES PHASE MARGIN

(LIMIT TO THIS AS THERE ARE OTHER POLES AS WELL)

TS13

SIMPLIFIED HIGH FREQ MODEL

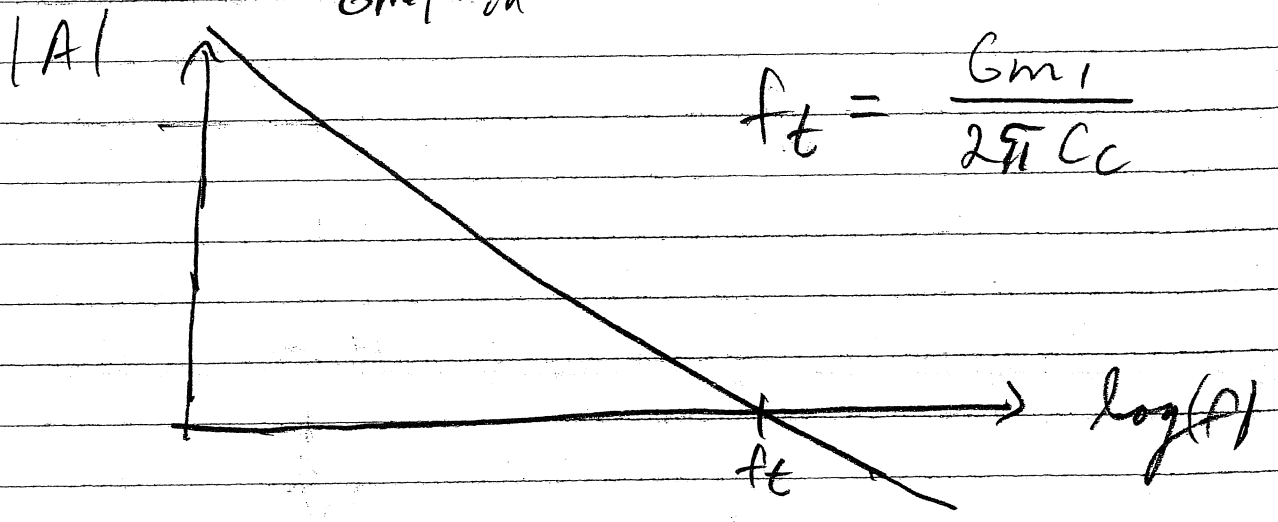
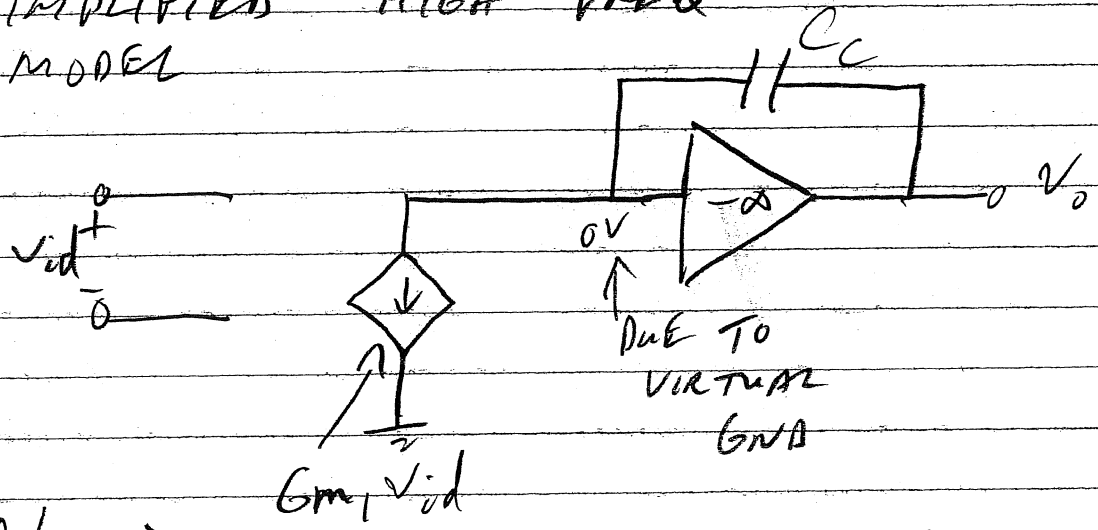


$$f_t = \frac{G_{m1}}{2\pi C_c}$$

VALID FOR $f \gg f_{p1}$

(BUT NOT REALISTIC OUTPUT IMPEDANCE)


SLEW-RATE

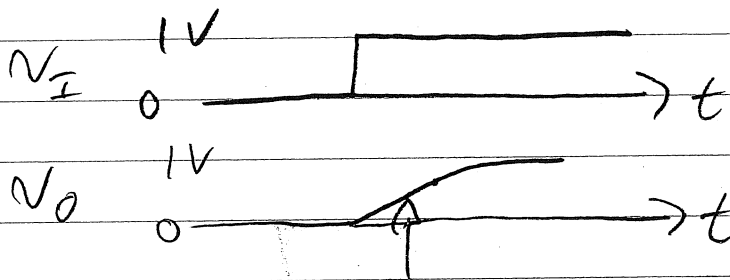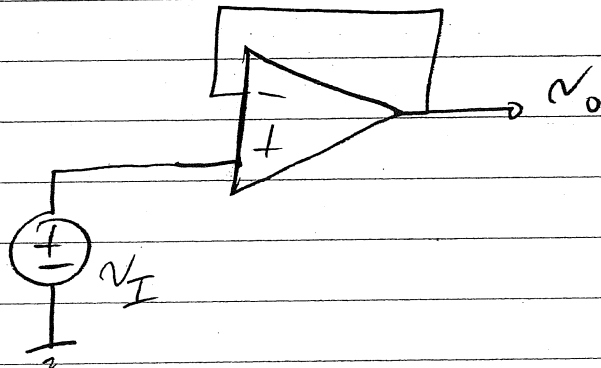

SLEW-RATE LIMITED MAX $\frac{dV_O}{dt}$

SLEW-RATE LIMIT OCCURS WHEN $\frac{I}{C_C}$
 OF INPUT DIFF PAIR ALL GOES ONE
 SIDE OF DIFF PAIR AND CHARGE/DISCHARGES
 C_C

TS15

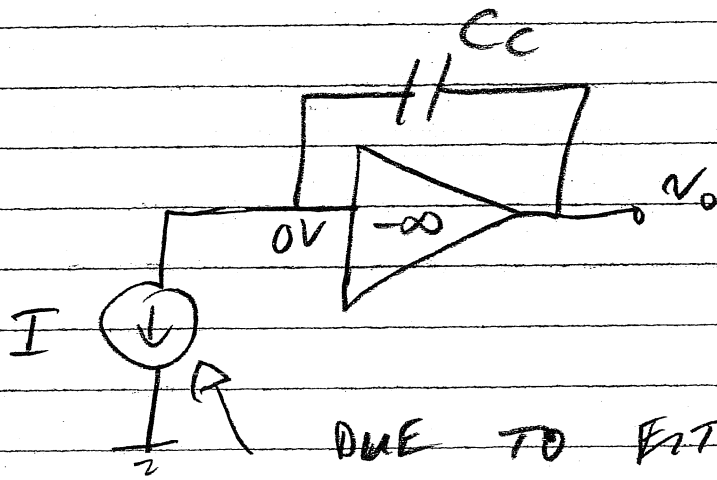

DUE TO EITHER $\begin{cases} i_{d4} = I \\ i_{d2} = 0 \end{cases}$

OR $\begin{cases} i_{d2} = I \\ i_{d4} = 0 \end{cases}$

$$q = CV \Rightarrow \frac{dq}{dt} = C \frac{dv}{dt} \Rightarrow I = C \frac{\Delta V}{\Delta t}$$

HERE

$$v_o(t) = \frac{I}{C_c} t$$

$$SR = \frac{I}{C_c}$$

(TS16)

RELATIONSHIP BETWEEN SR & f_t

$$G_{m1} = g_{m1} = \frac{2I_{D1}}{V_{ov1}} = \frac{2\left(\frac{I}{2}\right)}{V_{ov1}} = \frac{I}{V_{ov1}}$$

$$I = G_{m1} V_{ov1}$$

$$SR = \frac{G_{m1} V_{ov1}}{C_c} \quad \& \quad f_t = \frac{G_{m1}}{2\pi C_c}$$

$$\Rightarrow G_{m1} = 2\pi f_t C_c$$

$$SR = 2\pi f_t V_{ov1} \quad \& \quad W_t = 2\pi f_t$$

$$SR = W_t V_{ov1}$$

SO TO OBTAIN A HIGH SLEW-RATE

INCREASE V_{ov1} & W_t

SHOULD CHOOSE PMOS INPUT STAGE

f_{p2} DUE TO NMOS \Rightarrow INCREASES W_t

V_{ov1} HIGHER FOR SAME I

FINALLY RECALL FROM CHAPTER 2

IF OUTPUT STEP SIZE IS \hat{V}_0

THEN WILL NOT SLEW-RATE

LIMIT IF

$$W_t \hat{V}_0 \leq SR = W_t V_{ov1}$$

IF STEP OUTPUT HAS

$$\hat{V}_0 \leq V_{ov1}$$

THEN WILL NOT
SLEW-RATE LIMIT.

& WILL SETTLE
AS EXPONENTIAL