

**D.8** Consider the exponential response of an STC low-pass circuit to a 10-V step input. In terms of the time constant  $\tau$ , find the time taken for the output to reach 5 V, 9 V, 9.9 V, and 9.99 V.

**D.9** The high-frequency response of an oscilloscope is specified to be like that of an STC LP circuit with a 100-MHz corner frequency. If this oscilloscope is used to display an ideal step waveform, what rise time (10% to 90%) would you expect to observe?

**E.1** Find the transfer function  $T(s) = V_o(s)/V_i(s)$  of the circuit in Fig. PE.1. Is this an STC network? If so, of what type? For  $C_1 = C_2 = 0.5 \mu\text{F}$  and  $R = 100 \text{ k}\Omega$ , find the location of the pole(s) and zero(s), and sketch Bode plots for the magnitude response and the phase response.

**D\*E.2** (a) Find the voltage transfer function  $T(s) = V_o(s)/V_i(s)$ , for the STC network shown in Fig. PE.2.

(b) In this circuit, capacitor  $C$  is used to couple the signal source  $V_s$  having a resistance  $R_s$  to a load  $R_L$ . For  $R_s = 10 \text{ k}\Omega$ , design the circuit, specifying the values of  $R_L$  and  $C$  to only one significant digit to meet the following requirements:

- (i) The load resistance should be as small as possible.
- (ii) The output signal should be at least 70% of the input at high frequencies.
- (iii) The output should be at least 10% of the input at 10 Hz.

**E.7** An amplifier has a voltage transfer function  $T(s) = 10^6 s / (s + 10)(s + 10^3)$ . Convert this to the form convenient for constructing Bode plots [that is, place the denominator factors in the form  $(1 + s/a)$ ]. Provide a Bode plot for the magnitude response, and use it to find approximate values for the amplifier gain at 1, 10,  $10^2$ ,  $10^3$ ,  $10^4$ , and  $10^5$  rad/s.

**E.9** A transfer function has the following zeros and poles: one zero at  $s = 0$  and one zero at  $s = \infty$ ; one pole at  $s = -100$  and one pole at  $s = -10^6$ . The magnitude of the transfer function at  $\omega = 10^4$  rad/s is 100. Find the transfer function  $T(s)$  and sketch a Bode plot for its magnitude.

**E.10** Sketch Bode plots for the magnitude and phase of the transfer function

$$T(s) = \frac{10^4(1 + s/10^5)}{(1 + s/10^3)(1 + s/10^4)}$$

From your sketches, determine approximate values for the magnitude and phase at  $\omega = 10^6$  rad/s.

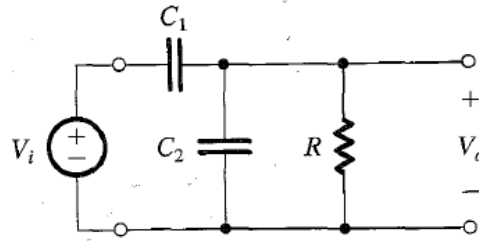


FIGURE PE.1

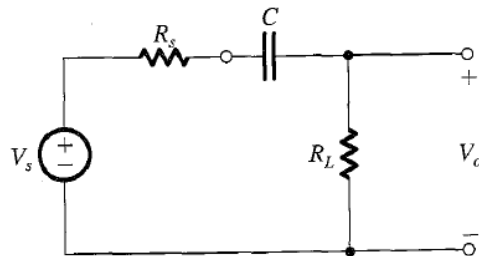


FIGURE PE.2

**D 9.1** The amplifier in Fig. P9.1 is biased to operate at  $g_m = 1 \text{ mA/V}$ . Neglecting  $r_o$ , find the midband gain. Find the value of  $C_S$  that places  $f_L$  at 20 Hz.

**9.3** The NMOS transistor in the discrete CS amplifier circuit of Fig. P9.3 is biased to have  $g_m = 5 \text{ mA/V}$ . Find  $A_{Mf}$ ,  $f_{P1}$ ,  $f_{P2}$ ,  $f_{P3}$ , and  $f_L$ .

**D 9.4** Consider the low-frequency response of the CS amplifier of Fig. 9.2(a). Let  $R_{sig} = 0.5 \text{ M}\Omega$ ,  $R_G = 2 \text{ M}\Omega$ ,  $g_m = 3 \text{ mA/V}$ ,  $R_D = 20 \text{ k}\Omega$ , and  $R_L = 10 \text{ k}\Omega$ . Find  $A_{Mf}$ . Also, design the coupling and bypass capacitors to locate the three low-frequency poles at 50 Hz, 10 Hz, and 3 Hz. Use a minimum total capacitance, with capacitors specified only to a single significant digit. What value of  $f_L$  results?

