

D 11.15 Design the quiescent current of a class AB BJT output stage so that the incremental voltage gain for v_i in the vicinity of the origin is in excess of 0.98 V/V for loads larger than 100 Ω . Assume that the BJTs have V_{BE} of 0.7 V at a current of 100 mA and determine the value of V_{BB} required.

***11.18** A class AB output stage, resembling that in Fig. 11.11 but utilizing a single supply of +10 V and biased at $V_i = 6$ V, is capacitively coupled to a 100- Ω load. For transistors for which $|V_{BE}| = 0.7$ V at 1 mA and for a bias voltage $V_{BB} = 1.4$ V, what quiescent current results? For a step change in output from 0 to -1 V, what input step is required? Assuming transistor saturation voltages of zero, find the largest possible positive-going and negative-going steps at the output.

D 11.19 Consider the diode-biased class AB circuit of Fig. 11.14. For $I_{BIAS} = 100 \mu\text{A}$, find the relative size (n) that should be used for the output devices (in comparison to the biasing devices) to ensure that an output resistance of 10 Ω or less is obtained in the quiescent state. Neglect the resistance of the biasing diodes.

D *11.20 A class AB output stage using a two-diode bias network as shown in Fig. 11.14 utilizes diodes having the same junction area as the output transistors. For $V_{CC} = 10$ V, $I_{BIAS} = 0.5$ mA, $R_L = 100 \Omega$, $\beta_N = 50$, and $|V_{CEsat}| = 0$ V, what is the quiescent current? What are the largest possible positive and negative output signal levels? To achieve a positive peak output level equal to the negative peak level, what value of β_N is needed if I_{BIAS} is not changed? What value of I_{BIAS} is needed if β_N is held at 50? For this value, what does I_Q become?

****11.23** A V_{BE} multiplier is designed with equal resistances for nominal operation at a terminal current of 1 mA, with half the current flowing in the bias network. The initial design is based on $\beta = \infty$ and $V_{BE} = 0.7$ V at 1 mA.

- Find the required resistor values and the terminal voltage.
- Find the terminal voltage that results when the terminal current increases to 2 mA. Assume $\beta = \infty$.
- Repeat (b) for the case the terminal current becomes 10 mA.

 


Fig. 11.11

 


Fig. 11.14

D 11.25 (a) For the circuit in Fig. 11.17 in which Q_1 and Q_2 are matched, and Q_N and Q_P are matched, show that the small-signal voltage gain at the quiescent condition is given by

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + (2/g_m)}$$

where g_m is the transconductance of each of Q_N and Q_P and where channel-length modulation is neglected.

(b) For the case $I_{BIAS} = 0.1$ mA, $R_L = 1$ k Ω , $k_n = k_p = nk_1 = nk_2$, where $k = \mu C_{ox}(W/L)$, and $k_1 = 20$ mA/V², find the ratio n that results in an incremental gain of 0.98. Also find the quiescent current I_Q .

D 11.26 Design the circuit of Fig. 11.17 to operate at $I_Q = 1$ mA with $I_{BIAS} = 0.1$ mA. Let $\mu_n C_{ox} = 250$ μ A/V², $\mu_p C_{ox} = 100$ μ A/V², $V_{tn} = -V_{tp} = 0.45$ V, and $V_{DD} = V_{SS} = 2.5$ V. Design so that Q_1 and Q_2 are matched and Q_N and Q_P are matched, and that in the quiescent state each operates at an overdrive voltage of 0.2 V.

- Specify the W/L ratio for each of the four transistors.
- In the quiescent state with $v_O = 0$, what must v_I be?
- If Q_N is required to supply a maximum load current of 10 mA, find the maximum allowable output voltage. Assume that the transistor supplying I_{BIAS} needs a minimum of 0.2 V to operate properly.

D 11.29 It is required to design the circuit of Fig. 11.19 to drive a load resistance of 50 Ω while exhibiting an output resistance, around the quiescent point, of 2.5 Ω . Operate Q_N and Q_P at $I_Q = 1.5$ mA and $|V_{OV}| = 0.15$ V. The technology utilized is specified to have $k'_n = 250$ μ A/V², $k'_p = 100$ μ A/V², $V_{tn} = -V_{tp} = 0.5$ V, and $V_{DD} = V_{SS} = 2.5$ V.

- Specify (W/L) for each of Q_N and Q_P .
- Specify the required value of μ .
- What is the expected error in the stage gain?
- In the quiescent state, what dc voltage must appear at the output of each of the error amplifiers?
- At what value of positive v_O will Q_P be supplying all the load current? Repeat for negative v_O and Q_N supplying all the load current.
- What is the linear range of v_O ?

 


Fig. 11.17

 


Fig. 11.19