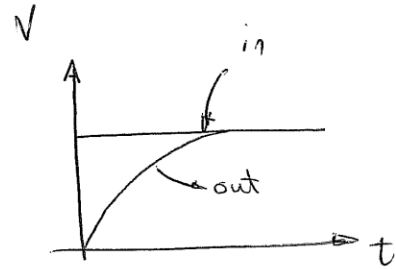


Problem 5

(1)

D. 8

$$\begin{aligned} V_{out}(t) &= V_{final} + (V_{initial} - V_{final}) e^{-t/\tau} \\ &= 10 + (0 - 10) e^{-t/\tau} \\ &= 10 - 10 e^{-t/\tau} \end{aligned}$$



$$\Rightarrow e^{-t/\tau} = \frac{10 - V_{out}(t)}{10} \Rightarrow \frac{t}{\tau} = \ln\left(\frac{10}{10 - V_{out}(t)}\right)$$

$$\Rightarrow t = \tau \cdot \ln\left(\frac{10}{10 - V_{out}(t)}\right)$$

$V_{out}(t)$	5(V)	9(V)	9.9(V)	9.99(V)
t	$\tau \ln(2)$	$\tau \ln(10)$	4.6τ	6.9τ

U.1

$$f_{3db} = 100 \text{ MHz} = f_0$$

$$\Rightarrow \omega_0 = 2\pi f_0 = \frac{1}{\tau} = \frac{1}{RC} \Rightarrow \tau = \frac{1}{2\pi \times 100 \times 10^6} = 1.59 \text{ ns}$$

$$V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}}) e^{-t/\tau} = V_{\text{out}}(t)$$

assume $V_{\text{initial}} = 0$,

$$V_{\text{final}} = V_f$$

$$\Rightarrow V_{\text{out}}(t) = V_f - V_f e^{-t/\tau}$$

$$\Rightarrow t = \tau \ln \left(\frac{V_f}{V_f - V_{\text{out}}(t)} \right)$$

$$V_{\text{out}}(t_1) = 0.1 V_f$$

$$\Rightarrow t_1 = \tau \ln \left(\frac{1}{0.9} \right) = 0.105 \tau$$

$$V_{\text{out}}(t_2) = 0.9 V_f$$

$$\Rightarrow t_2 = \tau \ln \left(\frac{1}{0.1} \right) = 2.303 \tau$$

$$\Delta t = t_{\text{rise}} = t_2 - t_1 = 2.2 \tau \approx 3.5 \text{ ns}$$

1.1

(3)

$$R \parallel \frac{1}{sC_2} = \left(\frac{1}{R} + sC_2 \right)^{-1} = \frac{R}{1 + sRC_2}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{R}{1 + sRC_2}}{\frac{1}{sC_1} + \frac{R}{1 + sRC_2}} = \frac{R}{\frac{1 + sRC_2 + sRC_1}{sC_1}}$$



$$= \frac{sRC_1}{1 + s(RC_1 + RC_2)} = \frac{RC_1}{RC_1 + RC_2} \cdot \frac{s}{\frac{1}{R(C_1 + C_2)} + s}$$

$$= \frac{C_1}{C_1 + C_2} \cdot \frac{s}{\frac{1}{R(C_1 + C_2)} + s}$$

It is a HPF. $\omega_0 = \frac{1}{\tau} = (R(C_1 + C_2))^{-1} = 10 \text{ Hz} \rightarrow \text{pole}$

$$k = \frac{C_1}{C_1 + C_2} = \frac{1}{2}$$

We have a zero at 0.

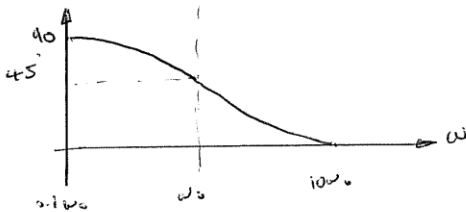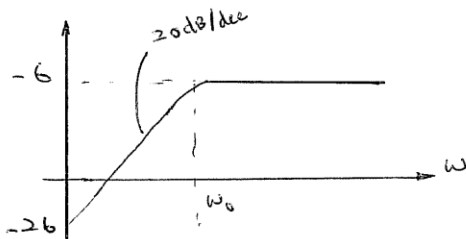

The bode plot not drawn to scale.

E.2 a)

$$T(s) = \frac{R_L}{R_L + R_s + \frac{1}{sC}} = \frac{R_L sC}{1 + sC(R_L + R_s)}$$
$$= \frac{R_L C}{C(R_L + R_s)} \cdot \frac{s}{\frac{1}{C(R_L + R_s)} + s} = \frac{R_L}{R_L + R_s} \cdot \frac{s}{\frac{1}{C(R_L + R_s)} + s}$$

b) at high frequencies:

$$\frac{V_o(s)}{V_i(s)} = \frac{R_L}{R_L + R_s} = \frac{R_L}{R_L + 10^k} > 0.7 \quad \text{--- I}$$

$$|T(j\omega)| = \frac{R_L}{R_L + R_s} \cdot \sqrt{\frac{\omega^2}{\omega^2 + \frac{1}{C^2(R_L + R_s)^2}}}$$

at 10 Hz, $\omega = 2\pi \times 10 = 62.8 \text{ rad/s}$

$$\Rightarrow \frac{R_L}{R_L + 10^k} \cdot \sqrt{\frac{1}{3947 + \frac{1}{C^2(R_L + R_s)^2}}} \cdot 62.8 =$$

$$\frac{62.8 \cdot R_L \cdot C}{\sqrt{1 + 3947 C^2 (R_L + R_s)^2}} > 0.1 \quad \text{--- II}$$


Smallest value of R_L to satisfy I is: $R_L = 23.3 \text{ k}$

Substituting R_L into II:

$$C = 6.89 \times 10^{-8} \text{ F} = 68.9 \text{ nF}$$

$$T(s) = \frac{10^6 \cdot s}{(s+10)(s+10^3)} = \frac{10^2 \cdot s}{\left(1 + \frac{s}{10}\right)\left(1 + \frac{s}{10^3}\right)}$$

(5)


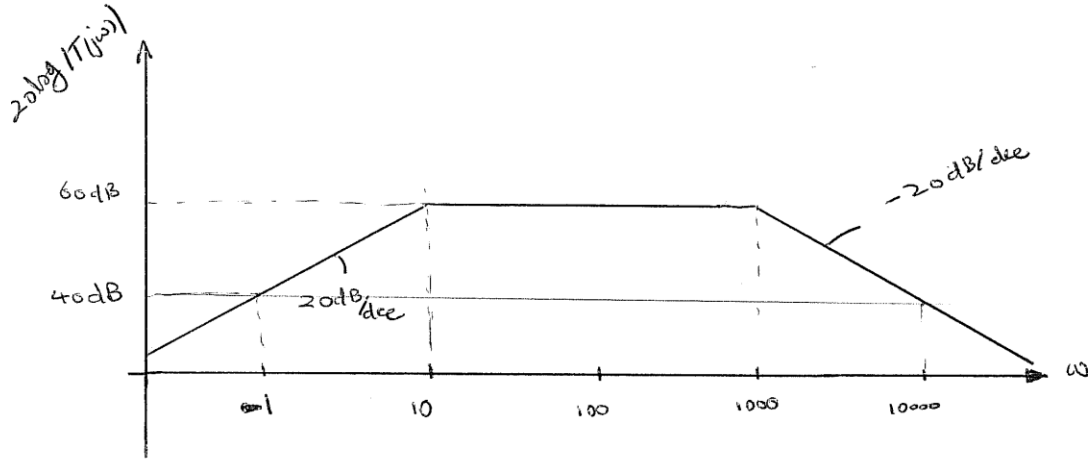


freq.	1	10	10 ²	10 ³	10 ⁴	10 ⁵
magn. tude	20	40	40	40	20	0

2

$$T(s) = \frac{s \times A}{\left(1 + \frac{s}{100}\right) \left(1 + \frac{s}{10^6}\right)}$$

to find A: $\frac{A\omega}{\omega} \approx |T(j\omega)|_{\omega=10^4} \Rightarrow A=1$ (6)

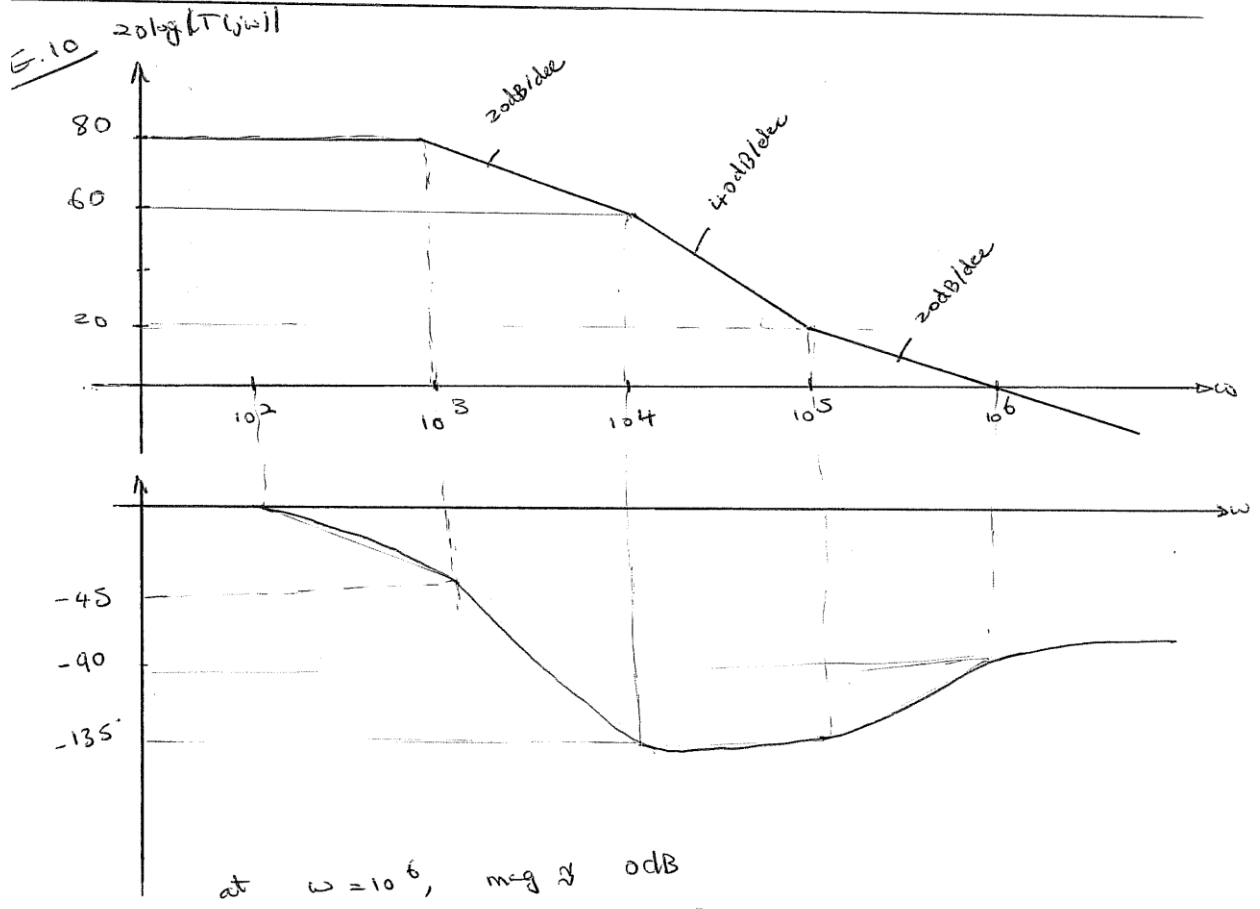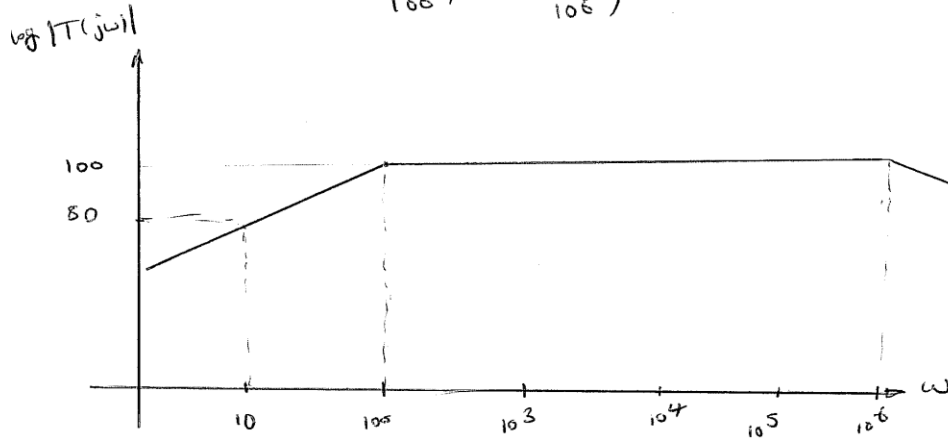

9.1 Using eq. $A_{VO} = \frac{-g_m R_D}{1 + g_m R_S}$

$$A_M = \frac{-g_m \cdot R_D}{1 + g_m \cdot R_S} = \frac{-1 \text{ mA/V} \cdot 10 \text{ k}\Omega}{1 + 1 \text{ mA/V} \cdot 6 \text{ k}\Omega}$$

$$= \frac{-10}{1 + 6}$$

$$A_M = 1.43 \text{ V/V}$$

$$f_L = \frac{1}{2\pi \left(\frac{1}{g_m} \parallel R_S \right) \cdot C_S} = 20 \text{ Hz}$$

$$C_S = \frac{1}{2\pi \cdot 20(1 \text{ k}\Omega \parallel 6 \text{ k}\Omega)} = 9.3 \text{ }\mu\text{F}$$

9.2 $f_{C_{C2}} = \frac{1}{2\pi \cdot C_{C2}(R_L + R_D \parallel r_D)}$
 $\leq 10 \text{ Hz}$

$$\Rightarrow C_{C2} \geq \frac{1}{10 \cdot 2\pi (10 \text{ k}\Omega + 10 \text{ k}\Omega \parallel 100 \text{ k}\Omega)}$$

$$C_{C2} \geq 0.83 \text{ }\mu\text{F}$$

If I_D is doubled with both r_D and R_D halved

$$f_{C_{C2}} = \frac{1}{2\pi \cdot 0.83 \text{ }\mu\text{ (} 10 \text{ k}\Omega + 5 \text{ k}\Omega \parallel 50 \text{ k}\Omega)}$$

$$= 13.18 \text{ Hz}$$

For higher power designs, where I_D is incremented and r_o and R_D are reduced, eventually $r_o \parallel R_D \ll R_L$ then R_L becomes dominant in determining the corner frequency:

$$f_{C_{C2}} = \frac{1}{2\pi \cdot C_{C2} \cdot R_L} = 19.17 \text{ Hz}$$

9.3 Refer to Fig. P. 9.3: $g_m = 5 \text{ mA/V}$

$$A_M = \frac{-R_G}{R_G + R_{sig}} \cdot g_m (R_D \parallel R_L) \text{ where}$$

$$R_G = 47 \text{ M}\Omega \parallel 10 \text{ M}\Omega = 8.25 \text{ M}\Omega$$

$$A_M = \frac{-8.25}{8.25 + 0.1} \cdot 5 \times 10^{-3} \cdot (4.7 \parallel 10) \cdot 10^3$$

$$= -15.79 \text{ V/V}$$

$$f_{P1} = \frac{1}{2\pi \cdot C_{C1}(R_G + R_{sig})} \text{ (Eq. 9.2)}$$

$$f_{P1} = \frac{1}{2\pi \cdot 0.01 \times 10^{-6} \cdot (8.25 + 0.1) \times 10^6}$$

$$= 1.9 \text{ Hz}$$

$$f_{P2} = \frac{1}{2\pi \cdot C_S \cdot \left(R_S \parallel \frac{1}{g_m} \right)}$$

$$= \frac{1}{2\pi \cdot 10 \times 10^{-6} \left(2 \text{ k}\Omega \parallel \frac{1}{5} \text{ k}\Omega \right)} = 87.5 \text{ Hz}$$

$$f_{P3} = \frac{1}{2\pi \cdot C_{C2} \cdot (R_D + R_L)}$$

$$= \frac{1}{2\pi \cdot 0.1 \times 10^{-6} (4.7 + 10) \times 10^3} = 108.3 \text{ Hz}$$

$$f_L \approx 108.3 \text{ Hz}$$

9.4 $A_M = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$

$$= -\frac{2 \times 3}{2 + 0.5} (20 \text{ k}\Omega \parallel 10 \text{ k}\Omega), (r_o = \infty)$$

$$A_M = -16 \text{ V/V}$$

$$f_{P1} = \frac{1}{2\pi C_{C1}(R_G + R_{sig})} \Rightarrow 3 \text{ Hz}$$

$$= \frac{1}{2\pi \cdot C_{C1}(2 + 0.5) \times 10^6}$$

$$\Rightarrow C_{C1} = 21.2 \text{ nF}$$

$$f_{P2} = \frac{g_m}{2\pi C_S} \Rightarrow 50 \text{ Hz} = \frac{3 \times 10^{-3}}{2\pi \times C_S}$$

$$\Rightarrow C_S = 9.6 \text{ }\mu\text{F}$$

$$f_{P3} = \frac{1}{2\pi C_{C2}(R_D + R_L)}$$

$$\Rightarrow 10 \text{ Hz} = \frac{1}{2\pi C_{C2}(10 \text{ k}\Omega + 20 \text{ k}\Omega)}$$

$$\Rightarrow C_{C2} = 0.5 \text{ }\mu\text{F}$$

$$f_L = 50 \text{ Hz}$$

9.5 Refer to Fig. 9.1

$$g_m = 5 \text{ mA/V}, R_{sig} = 200 \text{ k}\Omega, R_G = 10 \text{ M}\Omega,$$

$$R_D = 3 \text{ k}\Omega, R_L = 5 \text{ k}\Omega$$

If $C_{C1} = C_{C2} = C_S = 1 \text{ }\mu\text{F}$ then from Eq 9.2,

9.4, 9.6

$$f_{P1} = \frac{1}{2\pi \cdot C_{C1}(R_G + R_{sig})}$$

$$= \frac{1}{2\pi \cdot 1 \times 10^{-6} (10 + 0.2) \times 10^6} = 15.6 \text{ mHz}$$

$$f_{P2} = \frac{g_m}{2\pi \cdot C_S} = \frac{5 \times 10^{-3}}{2\pi \cdot 10^{-6}} = 795.8 \text{ Hz}$$

$$f_{P3} = \frac{1}{2\pi \cdot C_{C2}(R_D + R_L)}$$

$$= \frac{1}{2\pi \cdot 10^{-6} (3 + 5) \times 10^3} = 19.9 \text{ Hz}$$

From highest to lowest :

$$f_{P2} = 795.8 \text{ Hz}, f_{P3} = 19.9 \text{ Hz}, f_{P1} = 15.6 \text{ mHz}$$

$$\frac{f_{P2}}{f_{P3}} = 39.5, \frac{f_{P3}}{f_{P1}} = 1275.6$$

If $f_{P2} = 10 \text{ Hz}$

$$\Rightarrow C_S = \frac{5 \times 10^{-3}}{2\pi \cdot 10} = 79.6 \text{ }\mu\text{F}$$