

Q1 CONT

(2)

$$\frac{v_o}{v_1} = \frac{(R_{53} \parallel r_{o3} \parallel R_x)}{(R_{53} \parallel r_{o3} \parallel R_x) + r_{53}} = 0.932$$

$$\frac{v_2}{v_1} = \frac{(R_1 \parallel R_x)}{(R_1 \parallel R_x) + R_2} = 0.0526$$

$$\frac{v_r}{v_2} = g_m (R_{o1} \parallel r_{o1}) = 50$$

$$L \equiv \frac{v_r}{v_1} = 50 \times 0.932 \times 0.0526 \times 50 = \underline{\underline{122.6}}$$

A_∞ $L \rightarrow \infty \Rightarrow v_2 = v_5 \downarrow i_{D1} = 0$

$$v_5 = \frac{R_1}{R_1 + R_2} v_o$$

$$A_\infty \equiv \left. \frac{v_o}{v_5} \right|_{L \rightarrow \infty} = \frac{R_1 + R_2}{R_1} = \underline{\underline{10}}$$

$$\frac{v_o}{v_5} = A_\infty \left(\frac{L}{1+L} \right) + d \left(\frac{1}{1+L} \right) \quad d \approx 0 \text{ (GIVEN)}$$

$$\frac{v_o}{v_5} = (10) \left(\frac{122.6}{122.6+1} \right) = \underline{\underline{9.92}} \text{ } \checkmark \checkmark$$

3

Q1 CONT

$$R_{out} = R_{i^0} \left(\frac{1+L_s}{1+L_o} \right) \quad L_s = 0$$

$$L_o = L = 122.6$$

$$R_{i^0} = r_{S3} \parallel R_{S3} \parallel R_x = 0.94 \text{ k}\Omega$$

$$R_{out} = 0.94 \left(\frac{1}{1+122.6} \right) = \underline{\underline{7.6 \Omega}}$$

(4)

Q2 DC ANALYSIS

$$V_{ov} = \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} \quad V_{ov1} = V_{ov2} = V_{ov3} = 0.2887 \text{ V}$$


$$g_{m1} = g_{m2} = g_{m3} = \frac{2I_D}{V_{ov}} = 693 \text{ mA/V} = \frac{1}{r_{s1}}$$

$$g_{m4} = 2.078 \text{ mA/V}$$

$$g_{m5} = 1.96 \text{ mA/V} \Rightarrow r_{s5} = 511 \Omega$$

$$r_{o1} = r_{o2} = r_{o3} = \frac{V_A' L}{I_D} = 240 \text{ k}$$
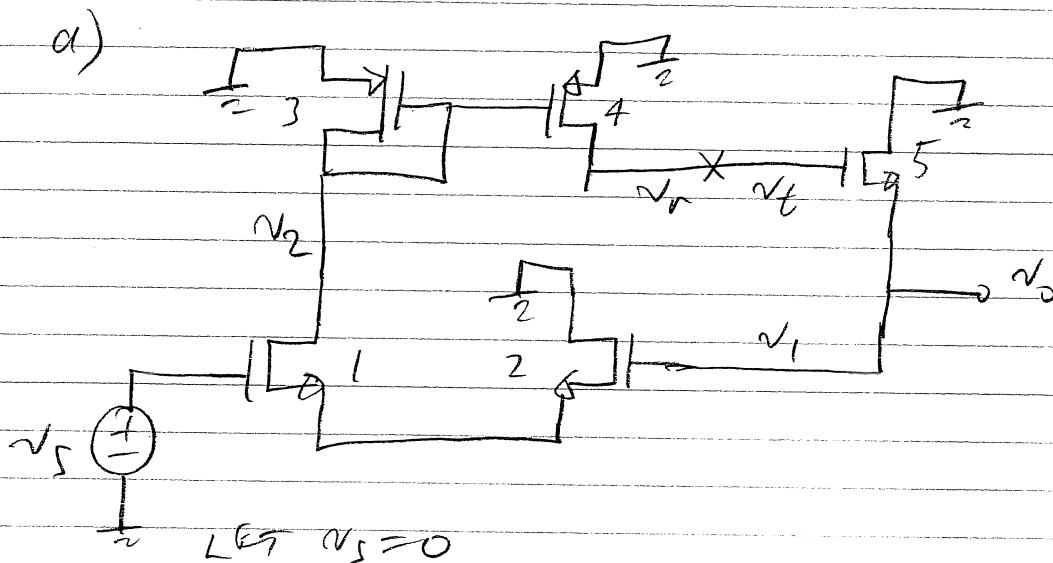
$$r_{o4} = 80 \text{ k} \quad r_{o5} = 30 \text{ k}$$



$$\frac{v_1}{v_t} = \frac{r_{o5}}{r_{o5} + r_{s5}} = 0.98$$

$$\frac{v_2}{v_1} \approx \frac{\frac{1}{g_{m3}}}{r_{s1} + r_{s2}} = 0.5$$

$$\frac{v_r}{v_2} = -g_{m4} r_{o4} = -166.2$$

$$\underline{\underline{L}} = 0.98 \times 0.5 \times 166.2 = \underline{\underline{81.4}}$$

(5)

A_{∞} INSERT GAIN A_{∞} AS "X"

$$\text{AS } A_{\infty} \rightarrow \infty \Rightarrow v_r \rightarrow 0$$

$$v_r \rightarrow 0 \Rightarrow v_2 \rightarrow 0 \Rightarrow i_{o1} \rightarrow 0$$

$$\Rightarrow v_1 \rightarrow v_s$$

$$A_{\infty} = 1$$

d $d = 0$

$$\frac{v_o}{v_s} = A_{\infty} \left(\frac{L}{1+L} \right) + d \left(\frac{1}{1+L} \right) = \frac{L}{1+L} = 0.988 \frac{V}{V}$$


b) $R_{out} = R_{p0} \left(\frac{1+L_s}{1+L_o} \right)$ $L_s = 0$
 $L_o = 81.4$

$$R_{p0} = r_{s5} \parallel r_{o5} = 0.502 \text{ k}$$

$$R_{out} = 0.502 \left(\frac{1}{1+L} \right) = 6.1 \Omega$$

6

Q-3

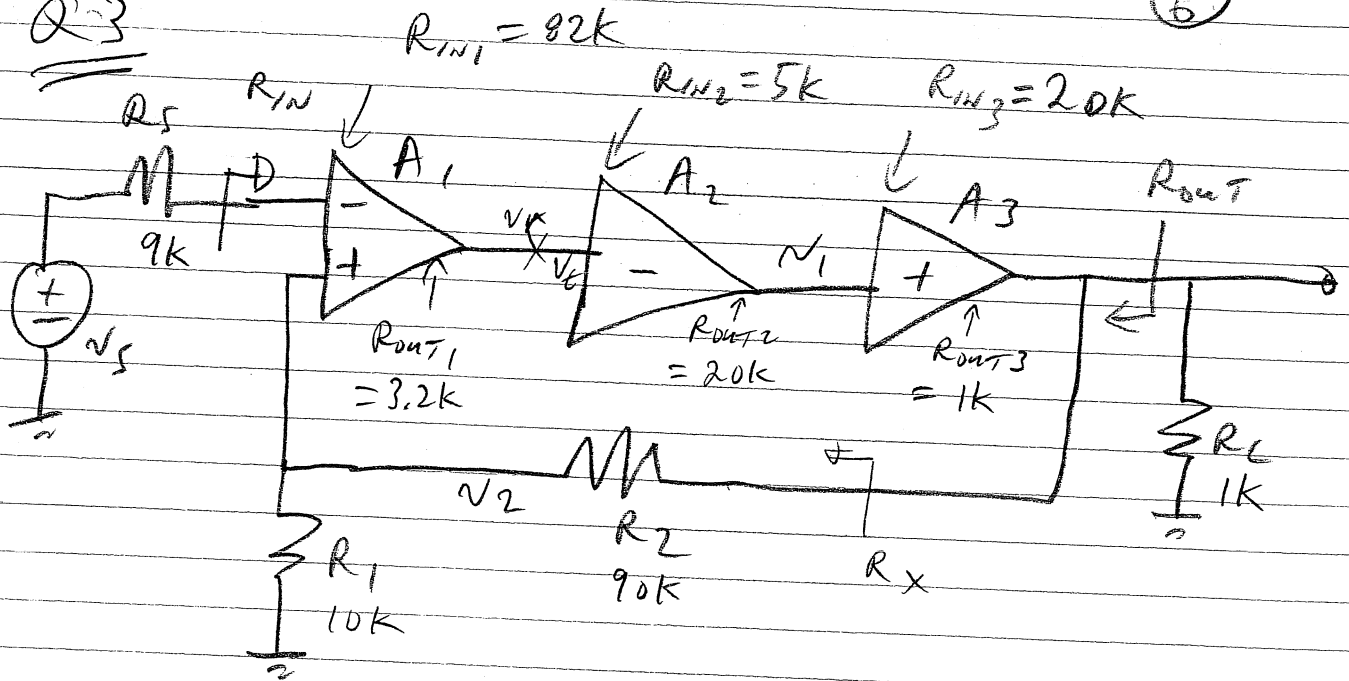

$$A_1 = 20 \frac{V}{V}$$

$$A_2 = 20 \text{ mA/V}$$

$$A_3 = 1 \frac{V}{V}$$

$$R_x \equiv R_2 + [R_1 \parallel (R_{in1} + R_5)] = 99 \text{ k}$$

$$\frac{v_1}{v_t} = -A_2 \times (R_{out2} \parallel R_{in3}) = (-20 \text{ mA/V})(10 \text{ k}) = -200 \frac{V}{V}$$

$$\frac{v_o}{v_1} = A_3 \frac{(R_L \parallel R_x)}{(R_L \parallel R_x) + R_{out3}} = 0.5 \frac{V}{V}$$

$$\frac{v_2}{v_o} = \frac{R_1 \parallel (R_{in1} + R_5)}{[R_1 \parallel (R_{out1} + R_5)] + R_2} = \frac{9}{9 + 90} = 0.091 \frac{V}{V}$$

Q3 CONT

⑦

$$\frac{V_r}{V_2} = \left(\frac{R_{IN1}}{R_{IN1} + R_S} \right) A_1 \left(\frac{R_{IN2}}{R_{IN2} + R_{OUT1}} \right)$$

$$= \left(\frac{82}{82 + 9} \right) (20) \left(\frac{5}{5 + 3.2} \right)$$


$$= 11 \frac{V}{V}$$

$$L = - \frac{V_r}{V_t} = 200 \times 0.5 \times 0.091 \times 11$$

$$L = 100 \frac{V}{V}$$

d_{20} GIVEN

A_o

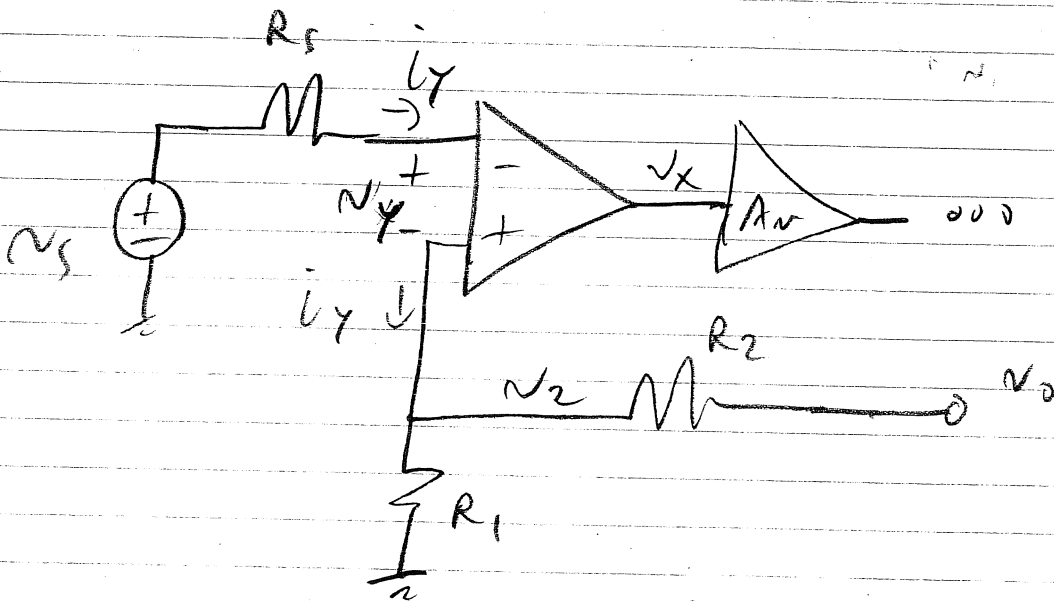

$$A_o \rightarrow \infty \Rightarrow V_Y \rightarrow 0 \text{ \& } i_Y \rightarrow 0$$

Q3 CONT

8


$$v_y \rightarrow 0 \text{ \& } i_y \rightarrow 0 \Rightarrow v_2 = v_5$$

$$v_5 = \frac{R_1}{R_1 + R_2} v_o$$

$$A_\infty \equiv \left. \frac{v_o}{v_5} \right|_{L \rightarrow \infty} = \frac{R_1 + R_2}{R_1} = 10$$

$$\frac{v_o}{v_5} = A_\infty \left(\frac{L}{1+L} \right) + d \left(\frac{1}{1+L} \right)$$
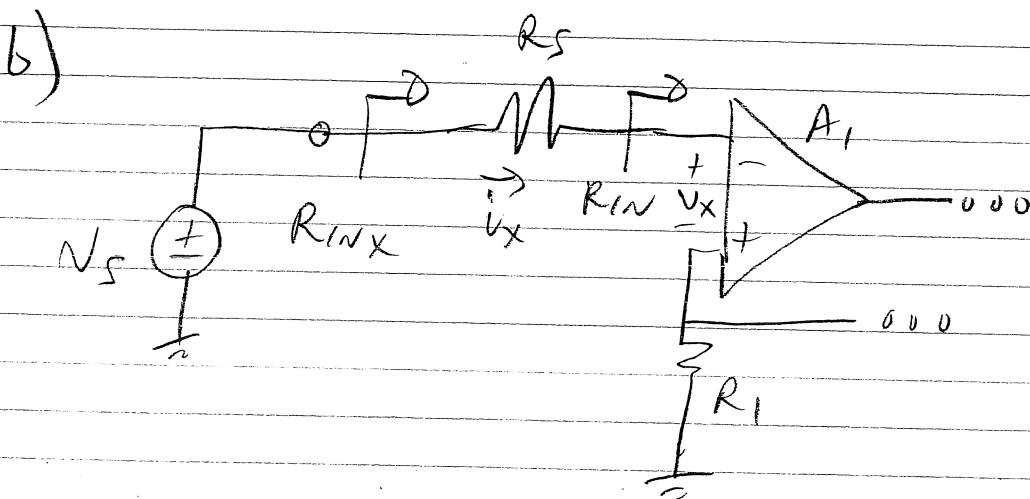
$$= (10) \left(\frac{100}{1+100} \right) = \underline{\underline{9.9}}$$



EASIER TO FIND R_{inx} THAN R_{in}

$$\downarrow R_{inx} = R_{in} + R_S$$

Q3 CONT

(9)

$$R_{inX} = R_{i^0} \left(\frac{1+L_S}{1+L_0} \right) \quad \begin{array}{l} L_S = L = 100 \\ L_0 = 0 \end{array}$$

$$\left(L_0 = 0 \quad \text{SINCE} \quad i_x = 0 \Rightarrow v_x = 0 \right)$$

$$\begin{aligned} R_{i^0} &= R_S + R_{in1} + \left[R_1 \parallel \left(R_2 + (R_L \parallel R_{out3}) \right) \right] \\ &= 100 \text{ K} \end{aligned}$$

$$R_{inX} = (100 \text{ K})(1+100) = 10.1 \text{ M}\Omega$$

$$R_{inX} = R_{in} + R_S \Rightarrow R_{in} = R_{inX} - R_S$$

$$\underline{\underline{R_{in} = 10.1 \text{ M}\Omega}}$$

R_{out}

$$R_{out} = R_{i^0} \left(\frac{1+L_S}{1+L_0} \right) \quad \begin{array}{l} L_S = 0 \\ L_0 = L = 100 \end{array}$$

$$R_{i^0} = R_{out3} \parallel R_L \parallel \left[R_2 + (R_1 \parallel (R_{in1} + R_S)) \right]$$

$$R_{i^0} = 500 \Omega$$

$$R_{out} = \frac{500}{1+100} \hat{=} \underline{\underline{5 \Omega}}$$