

11.1

Refer to Fig 11.2. The upper limit of the output voltage is determined by the saturation of Q_1 as

$$\begin{aligned} v_{Omax} &= V_{CC} - V_{CEsat} \\ &= 5 - 0.3 = 4.7 \text{ V} \end{aligned}$$

The corresponding input is

$$v_i = 4.7 + 0.7 = 5.4 \text{ V}$$

The bias current I is

$$\begin{aligned} I &= \frac{0 - (-V_{CC} + V_{BE2})}{R} \\ &= \frac{5 - 0.7}{1} = 4.3 \text{ mA} \end{aligned}$$

The lower limit of v_o is determined by either Q_1 cutting off,

$$\frac{-v_o}{R_L} = I \Rightarrow v_o = -4.3 \text{ V}$$

or by Q_2 saturating,

$$v_o = -V_{CC} + V_{CEsat} = -4.7 \text{ V}$$

Obviously, $v_{Omin} = -4.3 \text{ V}$

and the corresponding input is

$$v_i = -4.3 + 0.7 = -3.6 \text{ V}$$

If the emitter-base junction area of Q_3 is 14 made twice as large as that of Q_2 , I becomes one half its previous value,

$$I = \frac{4.3}{2} = 2.15 \text{ mA}$$

and thus the lower limit of v_o changes to

$$v_{Omin} = -IR_L = -2.15 \text{ V}$$


The corresponding value of v_i is

$$v_i = -2.15 + 0.7 = -1.45 \text{ V}$$

The upper limit does not change.

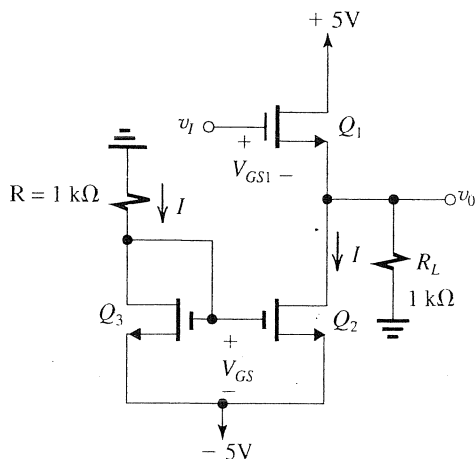11.2

First we determine the bias current I as follows:



$$I = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

But $V_{GS} = 5 - IR$

$$= 5 - I$$

Thus

$$I = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (5 - I - V_t)^2$$

$$I = 10(5 - I - 1)^2$$

$$\Rightarrow I^2 - 8.1I + 16 = 0$$

$$I = 3.416 \text{ mA and } V_{GS} = 1.584 \text{ V}$$

The upper limit on v_o is determined by Q_1 leaving the saturation region (and entering the triode region). This occurs when v_i exceeds V_{DI} by V_t volts,

$$v_{Imax} = 5 + 1 = +6 \text{ V}$$

To obtain the corresponding value of v_o we must find the corresponding value of V_{GS1} , as follows:

$$v_o = v_i - V_{GS1}$$

$$i_L = \frac{v_o}{R_L} = \frac{v_i - V_{GS1}}{1}$$

$$= v_i - V_{GS1} = 6 - V_{GS1}$$

$$i_1 = I + i_L$$

$$= 3.416 + 6 - V_{GS1}$$

$$= 9.416 - V_{GS1}$$

$$\text{But } i_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_t)^2$$

$$\text{Thus, } 9.416 - V_{GS1} = 10(V_{GS1} - 1)^2$$

$$\Rightarrow V_{GS1}^2 - 1.9 V_{GS1} + 0.0584 = 0$$

$$V_{GS1} = 1.869 \text{ V}$$

$$v_{Omax} = 6 - 1.869$$

$$= +4.131 \text{ V}$$

The lower limit of v_o is determined either by Q_1 cutting off,

$$v_o = -IR_L = -3.416 \times 1 = -3.416 \text{ V}$$

or by Q_2 leaving saturation,

$$v_o = V_{GS} - V_t$$

$$= -5 + 1.584 - 1 = -4.416 \text{ V}$$

Thus, $v_{Omin} = -3.416 \text{ V}$

The corresponding value of v_i is determined by moving that since Q_1 is on the verge of cut-off,

$$V_{GS1} = V_t = 1 \text{ V and}$$

$$v_i = -3.416 + 1 = -2.416 \text{ V}$$


11.3

Refer to Fig. 11.2. With $V_{CC} = +9\text{ V}$, the upper limit on v_o is 8.7 V, which is greater than the required value of +7 V. To obtain a lower limit of -7V we select I so that

$$IR_L = 7$$

$$\Rightarrow I = 7\text{ mA}$$

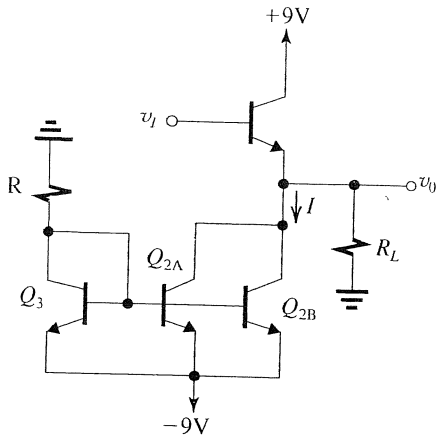Since we are provided with four devices, we can minimize the total supply current by paralleling two devices to form Q_2 as shown below.



The resulting supply current will be $3 \times \frac{I}{2}$ rather than $2I$ which is the value obtained in the circuit of Fig. 11.2. Then the supply current is 10.5 mA. The value of R is found from

$$R = \frac{8.3\text{ V}}{3.5\text{ mA}} = 2.37\text{ k}\Omega$$

In a practical design we would select a standard value for R that results in I somewhat larger than 7 mA. Say, $R=2.2\text{k}\Omega$

11.4

Refer to Fig. 11.2. For a load resistance of 100 Ω and v_o ranging between -5 V and +5 V, the maximum current through Q_1 is

$$I + \frac{5}{0.1} = I + 50, \text{ mA}$$

$$\text{and the minimum current is } I - \frac{5}{0.1} = I - 50, \text{ mA.}$$

For a current ratio of 10,

$$\frac{I + 50}{I - 50} = 10$$

$$\Rightarrow I = 61.1\text{ mA}$$

$$R = \frac{9.3\text{ V}}{61.1\text{ mA}} = 152\ \Omega$$

The incremental voltage gain is $A_v = \frac{R_L}{R_L + r_{e1}}$

For $R_L = 100\ \Omega$;

$$\text{At } v_o = +5\text{ V}, I_{E1} = 61.1 + 50 = 111.1\text{ mA}$$

$$r_{e1} = \frac{25}{111.1} = 0.225\ \Omega$$

$$A_v = \frac{100}{100 + 0.225} = 0.998\text{ V/V}$$

$$\text{At } v_o = 0\text{ V}, I_{E1} = 61.1\text{ mA}$$

$$r_{e1} = \frac{25}{61.1} = 0.409\ \Omega$$

$$A_v = \frac{100}{100.409} = 0.996\text{ V/V}$$

$$\text{At } v_o = -5\text{ V}, I_{E1} = 61.1 - 50 = 11.1\text{ mA}$$

$$r_{e1} = \frac{25}{11.1} = 2.25\ \Omega$$


$$A_v = \frac{100}{102.25} = 0.978\text{ V/V}$$

Thus the incremental gain changes by $0.998 - 0.978 = 0.02$ or about 2% over the range of v_o .

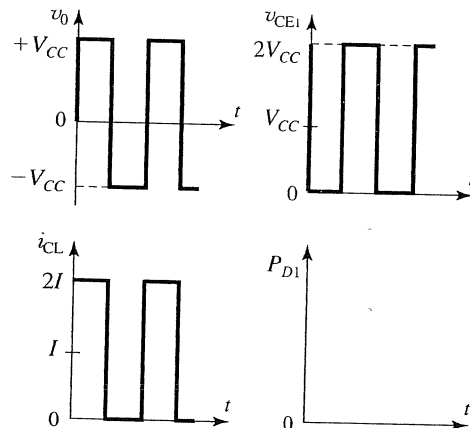11.5

Refer to Fig. 11.2 and 11.4

For v_o being a square wave of $\pm V_{CC}$ levels:




$$P_{D1}|_{\text{average}} = 0 \text{ For the corresponding sine wave}$$

$$\text{curve [Fig. 11.4], } P_{D1}|_{\text{avg}} = \frac{1}{2}V_{CC}I$$

For v_o a square wave of $\pm V_{CC}/Z$ levels :

11.10

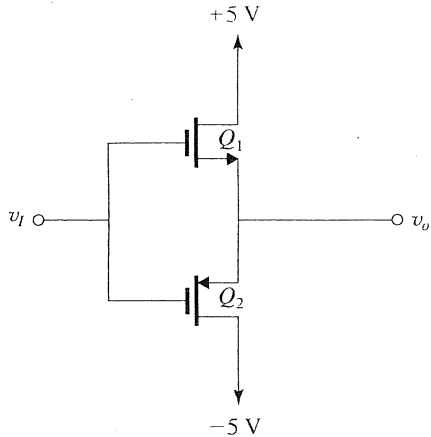

Devices have $|V_t| = 0.5 \text{ V}$

$$\mu C_{ox} \frac{W}{L} = 2 \text{ mA/V}^2$$

For $R_L = \infty$, the current is normally zero, so


$$V_{GS} = V_t$$

$$\therefore v_o = v_i - V_{GS1} = 5 - 0.5 = 4.5 \text{ V}$$

The peak output voltage will be 4.5 V

$$\sin \theta = \frac{0.5}{5} \Rightarrow \theta = 5.74^\circ$$

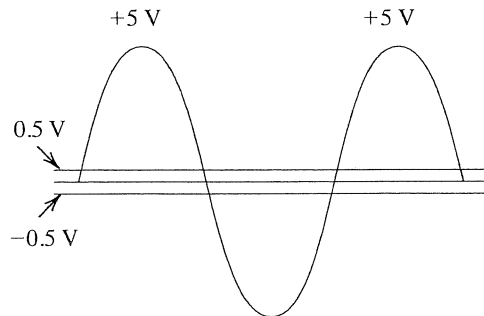
$$\begin{aligned} \text{Crossover interval} &= 4\theta = 22.96^\circ \\ &= \frac{22.96}{360} \times 100 \\ &= 6.4\% \end{aligned}$$



For $v_i = 5 \text{ V}$, $v_o = 2.5 \text{ V}$

$$\therefore V_{GS} = 5 - 2.5 = 2.5 \text{ V}$$
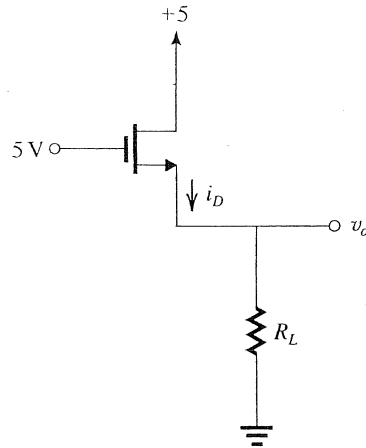
$$\begin{aligned} i_D &= \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \\ &= \frac{1}{2} \times 2 \times (2.5 - 0.5)^2 \end{aligned}$$



$$i_D = 4 \text{ mA and } R_L = \frac{2.5 \text{ V}}{4 \text{ mA}} = 625 \Omega$$

11.11

For $V_{CC} = 10 \text{ V}$ and $R_L = 100 \Omega$, the maximum

sine-wave output power occurs when $\hat{V}_o = V_{CC}$

$$\begin{aligned} \text{and is } P_{L\max} &= \frac{1}{2} \frac{V_{CC}^2}{R_L} \\ &= \frac{1}{2} \times \frac{100}{100} = 0.5 \text{ W} \end{aligned}$$

Correspondingly,

$$\begin{aligned} P_{S+} = P_{S-} &= \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC} \\ &= \frac{1}{\pi} \times \frac{10}{100} \times 10 = 0.318 \text{ W} \end{aligned}$$

For a total supply power of

$$P_s = 2 \times 0.318 = 0.637 \text{ W}$$

The power conversion efficiency η is

$$\eta = \frac{P_L}{P_s} \times 100 = \frac{0.5}{0.637} \times 100 = 78.5\%$$

For $\hat{V}_o = 5 \text{ V}$,

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L} = \frac{1}{2} \times \frac{25}{100} = \frac{1}{8} \text{ W}$$

$$P_{S+} = P_{S-} = \frac{1}{\pi} \frac{\hat{V}_o}{R_L} V_{CC}$$

$$= \frac{1}{\pi} \times \frac{5}{100} \times 10 = \frac{1}{2\pi}$$

$$P_{S'} = \frac{1}{\pi} \text{ W} = 0.318 \text{ W}$$

$$\eta = \frac{1/8}{1/\pi} \times 100 = \frac{\pi}{8} \times 100 = 39.3\%$$

11.12

$$V_{CC} = 5 \text{ V}$$

For maximum η ,

$$\hat{V}_o = V_{CC} = 5 \text{ V}$$

The output voltage that results in maximum device dissipation is given by Eq. (12.20),

$$\begin{aligned} \hat{V}_o &= \frac{2}{\pi} V_{CC} \\ &= \frac{2}{\pi} \times 5 = 3.18 \text{ V} \end{aligned}$$

If operation is always at full output voltage, $\eta = 78.5\%$ and thus

$$\begin{aligned} P_{\text{dissipation}} &= (1 - \eta)P_s \\ &= (1 - \eta)\frac{P_L}{\eta} = \frac{1 - 0.785}{0.785}P_L = 0.274P_L \end{aligned}$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \times 0.274P_L = 0.137P_L$$

For a rated device dissipation of 1 W, and using a factor of 2 safety margin,

$$\begin{aligned} P_{\text{dissipation/device}} &= 0.5 \text{ W} \\ &= 0.137P_L \end{aligned}$$

$$\Rightarrow P_L = 3.65 \text{ W}$$

$$3.65 = \frac{1}{2} \times \frac{25}{R_L}$$

$$\Rightarrow R_L = 3.425 \Omega \text{ (i.e., } R_L \geq 3.425 \Omega \text{)}$$

The corresponding output power (i.e., greatest possible output power) is 3.65 W.

If operation is allowed at $\hat{V}_o = \frac{1}{2}V_{CC} = 2.5 \text{ V}$,

$$\begin{aligned} \eta &= \frac{\pi \hat{V}_o}{4 V_{CC}} \text{ (Eq. 12.15)} \\ &= \frac{\pi}{4} \times \frac{1}{2} = 0.393 \end{aligned}$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \frac{1 - \eta}{\eta} P_L = 0.772P_L$$

$$0.5 = 0.772P_L$$

$$\Rightarrow P_L = 0.647 \text{ W}$$

$$= \frac{1}{2} \frac{2.5^2}{R_L}$$

$$\Rightarrow R_L = 4.83 \Omega \text{ (i.e., } \geq 4.83 \Omega \text{)}$$

11.13

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$100 = \frac{1}{2} \frac{\hat{V}_o^2}{16}$$

$$\hat{V}_o = 56.6 \text{ V}$$

$$V_{CC} = 56.6 + 4 = 60.6 \rightarrow 61 \text{ V}$$

$$\begin{aligned} \text{Peak current from each supply} &= \frac{\hat{V}_o}{R_L} = \frac{56.6}{16} \\ &= 3.54 \text{ A} \end{aligned}$$

$$P_{s+} = P_{s-} = \frac{1}{\pi} \times 3.54 \times 61$$

$$\begin{aligned} \text{Thus, } P_s &= \frac{2}{\pi} \times 3.54 \times 61 \\ &= 137.4 \text{ W} \end{aligned}$$

$$\eta = \frac{P_L}{P_s} = \frac{100}{137.4} = 73\%$$

Using Eq. (12.22),

$$\begin{aligned} P_{DN \text{ max}} = P_{DP \text{ max}} &= \frac{V_{CC}^2}{\pi^2 R_L} = \frac{61^2}{\pi^2 \times 16} \\ &= 23.6 \text{ W} \end{aligned}$$

11.14

$$P_L = \frac{\hat{V}_o^2}{R_L}$$

$$P_{s+} = P_{s-} = \frac{1}{2} \left(\frac{\hat{V}_o}{R_L} \right) V_{SS}$$

$$P_s = \frac{\hat{V}_o}{R_L} V_{SS}$$

$$\eta = \frac{P_L}{P_s} = \frac{\hat{V}_o^2 / R_L}{\hat{V}_o V_{SS} / R_L} = \frac{\hat{V}_o}{V_{SS}}$$

$$\eta_{\text{max}} = 1 (100\%), \text{ obtained for } \hat{V}_o = V_{SS}$$

$$P_{L \text{ max}} = \frac{V_{SS}^2}{R_L}$$

$$P_{\text{dissipation}} = P_s - P_L$$

$$= \frac{\hat{V}_o}{R_L} V_{SS} - \frac{\hat{V}_o^2}{R_L}$$

$$\frac{\partial P_{\text{dissipation}}}{\partial \hat{V}_o} = \frac{V_{SS}}{R_L} - \frac{2\hat{V}_o}{R_L}$$

$$= 0 \text{ for } \hat{V}_o = \frac{V_{SS}}{2}$$

$$\text{Correspondingly, } \eta = \frac{V_{SS}/2}{V_{SS}} = \frac{1}{2} \text{ or } 50\%$$

11.15

$$A_v = \frac{R_L}{R_L + R_{\text{out}}} \text{ and } R_{\text{out}} = \frac{r_e}{2} = \frac{V_T}{2I_Q}$$

Now $A_v \geq 0.98$ for $R_L \geq 100 \Omega$

$$\therefore 0.98 = \frac{100}{100 + R_{\text{out}}}$$

$$\Rightarrow R_{\text{out}} \simeq 2 \Omega$$

$$R_{\text{out}} = 2 = \frac{V_T}{2I_Q}$$