

11.12

$$V_{CC} = 5 \text{ V}$$

For maximum η ,

$$\hat{V}_o = V_{CC} = 5 \text{ V}$$

The output voltage that results in maximum device dissipation is given by Eq. (12.20),

$$\begin{aligned} \hat{V}_o &= \frac{2}{\pi} V_{CC} \\ &= \frac{2}{\pi} \times 5 = 3.18 \text{ V} \end{aligned}$$

If operation is always at full output voltage, $\eta = 78.5\%$ and thus

$$\begin{aligned} P_{\text{dissipation}} &= (1 - \eta)P_s \\ &= (1 - \eta)\frac{P_L}{\eta} = \frac{1 - 0.785}{0.785}P_L = 0.274P_L \end{aligned}$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \times 0.274P_L = 0.137P_L$$

For a rated device dissipation of 1 W, and using a factor of 2 safety margin,

$$\begin{aligned} P_{\text{dissipation/device}} &= 0.5 \text{ W} \\ &= 0.137P_L \end{aligned}$$

$$\Rightarrow P_L = 3.65 \text{ W}$$

$$3.65 = \frac{1}{2} \times \frac{25}{R_L}$$

$$\Rightarrow R_L = 3.425 \Omega \text{ (i.e. } R_L \geq 3.425 \Omega \text{)}$$

The corresponding output power (i.e., greatest possible output power) is 3.65W.

If operation is allowed at $\hat{V}_o = \frac{1}{2}V_{CC} = 2.5 \text{ V}$,

$$\begin{aligned} \eta &= \frac{\pi}{4} \frac{\hat{V}_o}{V_{CC}} \text{ (Eq. 12.15)} \\ &= \frac{\pi}{4} \times \frac{1}{2} = 0.393 \end{aligned}$$

$$P_{\text{dissipation/device}} = \frac{1}{2} \frac{1 - \eta}{\eta} P_L = 0.772P_L$$

$$0.5 = 0.772P_L$$

$$\Rightarrow P_L = 0.647 \text{ W}$$

$$= \frac{1}{2} \frac{2.5^2}{R_L}$$

$$\Rightarrow R_L = 4.83 \Omega \text{ (i.e., } \geq 4.83 \Omega \text{)}$$

11.13

$$P_L = \frac{1}{2} \frac{\hat{V}_o^2}{R_L}$$

$$100 = \frac{1}{2} \frac{\hat{V}_o^2}{16}$$

$$\hat{V}_o = 56.6 \text{ V}$$

$$V_{CC} = 56.6 + 4 = 60.6 \rightarrow 61 \text{ V}$$

$$\begin{aligned} \text{Peak current from each supply} &= \frac{\hat{V}_o}{R_L} = \frac{56.6}{16} \\ &= 3.54 \text{ A} \end{aligned}$$

$$P_{s+} = P_{s-} = \frac{1}{\pi} \times 3.54 \times 61$$

$$\begin{aligned} \text{Thus, } P_s &= \frac{2}{\pi} \times 3.54 \times 61 \\ &= 137.4 \text{ W} \end{aligned}$$

$$\eta = \frac{P_L}{P_s} = \frac{100}{137.4} = 73\%$$

Using Eq. (12.22),

$$\begin{aligned} P_{DN \text{ max}} = P_{DP \text{ max}} &= \frac{V_{CC}^2}{\pi^2 R_L} = \frac{61^2}{\pi^2 \times 16} \\ &= 23.6 \text{ W} \end{aligned}$$

11.14

$$P_L = \frac{\hat{V}_o^2}{R_L}$$

$$P_{s+} = P_{s-} = \frac{1}{2} \left(\frac{\hat{V}_o}{R_L} \right) V_{SS}$$

$$P_s = \frac{\hat{V}_o}{R_L} V_{SS}$$

$$\eta = \frac{P_L}{P_s} = \frac{\hat{V}_o^2 / R_L}{\hat{V}_o V_{SS} / R_L} = \frac{\hat{V}_o}{V_{SS}}$$

$$\eta_{\text{max}} = 1 (100\%), \text{ obtained for } \hat{V}_o = V_{SS}$$

$$P_{L \text{ max}} = \frac{V_{SS}^2}{R_L}$$

$$P_{\text{dissipation}} = P_s - P_L$$

$$= \frac{\hat{V}_o}{R_L} V_{SS} - \frac{\hat{V}_o^2}{R_L}$$

$$\frac{\partial P_{\text{dissipation}}}{\partial \hat{V}_o} = \frac{V_{SS}}{R_L} - \frac{2\hat{V}_o}{R_L}$$

$$= 0 \text{ for } \hat{V}_o = \frac{V_{SS}}{2}$$

$$\text{Correspondingly, } \eta = \frac{V_{SS}/2}{V_{SS}} = \frac{1}{2} \text{ or } 50\%$$

11.15

$$A_v = \frac{R_L}{R_L + R_{\text{out}}} \text{ and } R_{\text{out}} = \frac{r_e}{2} = \frac{V_T}{2I_Q}$$

Now $A_v \geq 0.98$ for $R_L \geq 100 \Omega$

$$\therefore 0.98 = \frac{100}{100 + R_{\text{out}}}$$

$$\Rightarrow R_{\text{out}} \approx 2 \Omega$$

$$R_{\text{out}} = 2 = \frac{V_T}{2I_Q}$$

(table is for 11.16)

v_o (V)	i_L (mA)	i_N (mA)	i_p (mA)	V_{BEN} (V)	V_{EBR} (V)	V_i (V)	V_j/V	R_{out} (Ω)	V_j/V	i_i	R_{in} (Ω)
+10.0	100	100.04	0.04	0.691	0.495	10.1	0.99	0.25	1.00	2	5050
+5.0	50	50.08	0.08	0.673	0.513	5.08	0.98	0.50	1.00	1	5080
+1.0	10	10.39	0.39	0.634	0.552	1.041	0.96	2.32	0.98	0.2	5205
+0.5	5	5.70	0.70	0.619	0.567	0.526	0.95	4.03	0.96	0.1	5260
+0.2	2	3.24	1.24	0.605	0.581	0.212	0.94	5.58	0.95	0.04	5300
+0.1	1	2.56	1.56	0.599	0.587	0.106	0.94	6.07	0.94	0.02	5300
0	0	2	2	0.593	0.593	0	-	6.25	0.94		
-0.1	-1	1.56	2.56	0.587	0.599	-0.106	0.94	6.07	0.94	-0.02	5300
-0.2	-2	1.24	3.24	0.581	0.605	-0.212	0.94	5.58	0.95	-0.04	5300
-0.5	-5	0.70	5.70	0.567	0.619	-0.526	0.95	4.03	0.96	-0.1	5260
-1.0	-10	0.39	10.39	0.552	0.634	-1.041	0.96	2.32	0.98	-0.2	5205
-5.0	-50	0.08	50.08	0.513	0.673	-5.08	0.98	0.50	1.00	-1	5080
-10.0	-100	0.04	100.04	0.495	0.691	-10.1	0.99	0.25	1.00	-2	5050

$$I_Q = \frac{V_T}{4} = \frac{25 \times 10^{-3}}{4} = 6.25 \text{ mA}$$

$$V_{BB} = 2V_{BE} = 2 \left[0.7 + V_T \ln \left(\frac{6.25}{100} \right) \right]$$

$$= 1.26 \text{ V}$$

11.16The current i_i can be obtained as

$$i_i = \frac{i_N}{\beta_N + 1} - \frac{i_p}{\beta_P + 1} = \frac{i_L}{\beta + 1}$$

$$\therefore \beta_N = \beta_P = \beta = 49$$

Using values of v_i from the table one can evaluate R_{in}

$$\therefore R_{in} = \frac{v_i}{i_i}$$

Using resistance reflection rule

$$R_{in} \cong \beta R_L = 49 \times 100$$

$$= 4900 \Omega$$

For large input signal the two values of R_{in} are somewhat same. For the small values of v_o , the calculated value in the table is larger.**11.17**

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + R_{out}} \text{ and}$$

$$R_{out} = \frac{V_T}{i_p + i_N} = \frac{V_T}{I_Q + I_Q} \text{ at } v_o = 0$$

$$a. \epsilon = 1 - \frac{v_o}{v_i} \Big|_{v_o=0}$$

$$= 1 - \frac{R_L}{R_L + R_{out}} = 1 - \frac{R_L}{R_L + \frac{V_T}{2I_Q}} = \frac{V_T/2I_Q}{R_L + (V_T/2I_Q)}$$

$$\epsilon = \frac{V_T/2I_Q}{R_L + (V_T/2I_Q)} = \frac{V_T}{2R_L I_Q + V_T}$$

If $2I_Q R_L \gg V_T$

$$\epsilon = \frac{V_T}{2I_Q R_L}$$

b. Quiescent Power Dissipation = $2V_{CC} I_Q = P_D$ c. $\epsilon \times$ Quiescent Power Dissipation =

$$\frac{V_T}{2I_Q R_L} \times 2V_{CC} I_Q = V_T \times \left(\frac{V_{CC}}{R_L} \right)$$

$$\therefore \epsilon P_D = V_T \left(\frac{V_{CC}}{R_L} \right)$$

$$d. \epsilon P_D = V_T \frac{V_{CC}}{R_L} = 25 \times 10^{-3} \times \frac{15}{100}$$

$$= 3.75 \text{ mW}$$

$$P_D = \frac{3.75 \times 10^{-3}}{\epsilon}$$

ϵ	P_D in mW
0.05	75
0.02	187.5
0.01	375

11.18

$$I_Q = 1 \text{ mA}$$

$$\text{For output of } -1 \text{ V, } i_L = -\frac{1}{100} = -10 \text{ mA}$$

Using Eq. (11.27)

$$i_N^2 - i_L i_N - I_Q^2 = 0$$

$$i_N^2 + 10i_N - 1 = 0$$

$$i_N = 0.1 \text{ mA}$$

$$i_P = 10.1 \text{ mA}$$

$$\text{Thus } v_{EB_P} \text{ increases by } V_T \ln \frac{10.1}{1} = 0.06 \text{ V}$$

and the input step must be -1.06 V

Largest possible positive output from 6 to 10, i.e., 4 V

Largest negative output from 6 to 0, i.e., 6 V

11.19

$$R_{\text{out}} = r_e / 2 = 10 \Omega$$

$$\Rightarrow r_e = 20 \Omega$$

$$I_Q = \frac{V_T}{r_e} = \frac{25}{20} = 1.25 \text{ mA}$$

$$\text{Thus, } \eta = \frac{1.25}{0.1} = 12.5$$

11.20

$I_Q \approx I_{\text{bias}} = 0.5 \text{ mA}$, neglecting the base current of Q_N . More precisely,

$$I_Q = I_{\text{bias}} \frac{I_Q}{\beta + 1}$$

$$\Rightarrow I_Q = \frac{I_{\text{bias}}}{1 + \frac{1}{\beta + 1}} \approx 0.98 \times 0.5 = 0.49 \text{ mA}$$

The largest positive output is obtained when all of I_{bias} flows into the base of Q_N , resulting in

$$v_o = (\beta_N + 1) I_{\text{bias}} R_L = 51 \times 0.5 \times 100 \Omega = 2.55 \text{ V}$$

The largest possible negative output voltage is limited by the saturation of

$$Q_P \text{ to } -10 + V_{\text{ECSat}} = -10 \text{ V}$$

To achieve a maximum positive output of 10 V without changing I_{bias} , β_N must be

$$10 = (\beta_N + 1) \times 0.5 \times 100 \Omega \\ \Rightarrow \beta_N = 199$$

Alternatively, if β_N is held at 50, I_{bias} must be increased so that

$$10 = 51 \times I_{\text{bias}} \times 100 \Omega \\ \Rightarrow I_{\text{bias}} = 1.96 \text{ mA}$$

for which,

$$I_Q = \frac{I_{\text{bias}}}{1 + \frac{1}{\beta + 1}} = 1.92 \text{ mA}$$

11.21

$$\text{At } 20^\circ\text{C, } I_Q = 1 \text{ mA} = I_S e^{(0.6/0.025)}$$

$$\Rightarrow I_S \text{ (at } 20^\circ\text{C)} = 3.78 \times 10^{-11} \text{ mA}$$

$$\text{At } 70^\circ\text{C, } I_S = 3.78 \times 10^{-11} (1.14)^{50}$$

$$= 2.64 \times 10^{-8} \text{ mA}$$

$$\text{At } 70^\circ\text{C, } V_T = 25 \frac{273 + 70}{273 + 20} = 29.3 \text{ mV}$$

$$\text{Thus, } I_Q \text{ (at } 70^\circ\text{C)} = 2.64 \times 10^{-8} e^{0.6/0.0293} \\ = 20.7 \text{ mA}$$

$$\text{Additional current} = 20.7 - 1 = 19.7 \text{ mA}$$

$$\text{Additional power} = 2 \times 20 \times 19.7 = 788 \text{ mW}$$

$$\text{Additional temperature rise} = 10 \times 0.788 = 7.9^\circ\text{C,}$$

At 77.9°C :

$$V_T = \frac{25}{293} (273 + 77.9) = 29.9 \text{ mV}$$

$$I_Q = 3.78 \times 10^{-11} \times (1.14)^{57.9} e^{(0.6/0.0299)} \\ = 37.6 \text{ mA}$$

etc., etc.

11.22

Since the peak positive output current is 200 mA , the base current of Q_N can be as high as

$$\frac{200}{\beta_N + 1} = \frac{200}{51} \approx 4 \text{ mA. We select}$$

$I_{\text{bias}} = 5 \text{ mA}$, thus providing the multiplier with a minimum current of 1 mA .

Under quiescent conditions ($v_o = 0$ and $i_L = 0$) the base current of Q_N can be neglected.

Selecting $I_R = 0.5 \text{ mA}$ leaves $I_{C1} = 4.5 \text{ mA}$. To obtain a quiescent current of 2 mA in the output transistors, V_{BB} should be

$$V_{BB} = 2V_T \ln \frac{2 \times 10^{-3}}{10^{-15}} = 1.19 \text{ V}$$

Thus

$$R_1 + R_2 = \frac{V_{BB}}{I_R} = \frac{1.19}{0.5} = 2.38 \text{ k}\Omega$$

At a collector current of 4.5 mA , Q_1 has

$$V_{BE1} = V_T \ln \frac{4.5 \times 10^{-3}}{10^{-14}} = 0.671 \text{ V}$$

The value of R_1 can now be determined as

$$R_1 = \frac{0.671}{0.5} = 1.34 \text{ k}\Omega \text{ and}$$

$$R_2 = 2.58 - 1.34 = 1.04 \text{ k}\Omega$$

11.23

(a) $V_{BE} = 0.7 \text{ V}$ at 1 mA

At 0.5 mA ,

$$V_{BE} = 0.7 + 0.025 \ln \frac{0.5}{1} = 0.683 \text{ V}$$

$$\text{Thus } R_1 = \frac{0.683}{0.5} = 1.365 \text{ k}\Omega$$

$$\text{and } R_2 = 1.365 \text{ k}\Omega$$

(b) For $I_{\text{bias}} = 2 \text{ mA}$, I_C increases to nearly 1.5 mA for which

$$V_{BE} = 0.7 + 0.025 \ln \frac{1.3}{1} = 0.710 \text{ V}$$

$$\text{Note that } I_R = \frac{0.710}{1.365} = 0.52 \text{ mA is very nearly}$$

equal to the assumed value of 0.50 mA, Thus no further iterations are required.

$$V_{BB} = 2V_{BE} = 1.420 \text{ V}$$

(c) For $I_{\text{bias}} = 10 \text{ mA}$, assume that I_R remains constant at 0.5 mA, thus $I_{C1} = 9.5 \text{ mA}$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.5}{1} = 0.756 \text{ V}$$

at which

$$I_R = \frac{0.755}{1.365} = 0.554 \text{ mA}$$

Thus,

$$I_{C1} = 10 - 0.554 = 9.45 \text{ mA}$$

$$\text{and } V_{BE} = 0.7 + 0.025 \ln \frac{9.45}{1} = 0.756 \text{ V}$$

$$\text{Thus } V_{BB} = 2 \times 0.756 = 1.512 \text{ V}$$

(d) Now for $\beta=100$,

$$I_{R1} = \frac{0.756}{1.365} = 0.554 \text{ mA}$$

$$I_{R2} = 0.554 + \frac{9.45}{101} = 0.648 \text{ mA}$$

$$I_C = 10 - 0.648 = 9.352 \text{ mA}$$

$$\text{Thus, } V_{BE} = 0.7 + 0.025 \ln \frac{9.352}{1} = 0.756 \text{ V}$$

$$V_{BB} = 0.756 + I_{R2} R_2$$

$$= 0.756 + 0.648 \times 1.365$$

$$= 1.641 \text{ V}$$

11.24

a. From Figure 11.17

$$R_{\text{out}} = R_{\text{OQN}} \parallel R_{\text{OQP}}$$

$$R_{\text{OQM}} = \frac{1}{g_{mN}} \parallel r_{\text{ON}} \approx \frac{1}{g_{mN}}$$

$$R_{\text{OQP}} = \frac{1}{g_{mP}} \parallel r_{\text{OP}} \approx \frac{1}{g_{mP}}$$

$$R_{\text{out}} = \frac{1}{g_{mN}} \parallel \frac{1}{g_{mP}} = \frac{1}{\frac{g_{mN}}{1} + \frac{g_{mP}}{1}} = \frac{1}{g_{mN} + g_{mP}}$$

$$= \frac{1}{2g_m} \text{ for matched devices } g_{mN} = g_{mP} = g_m$$

$$\text{b. } R_{\text{out}} = 10 = \frac{1}{2g_m} \Rightarrow g_m = \frac{1}{20}$$

$$g_m = \frac{2I}{V_{ov}} = \frac{2}{V_{ov}} \times \frac{1}{2} k' \left(\frac{W}{L} \right) V_{ov}^2 = k' \left(\frac{W}{L} \right) V_{ov}$$

$$\therefore \frac{1}{20} = k' \left(\frac{W}{L} \right) V_{ov} = 200 \times 10^{-3} \times V_{ov}$$

$$\Rightarrow V_{ov} = 0.25 \text{ V}$$


$$\text{But } V_{ov} = V_{GS} - V_t$$

$$0.25 = V_{GS} - 0.7$$

$$\text{So } V_{GS} = 0.95 \text{ V}$$

$$V_{GG} = V_{GS1} + V_{GS2} = 2 V_{GS} = 1.9$$

11.25

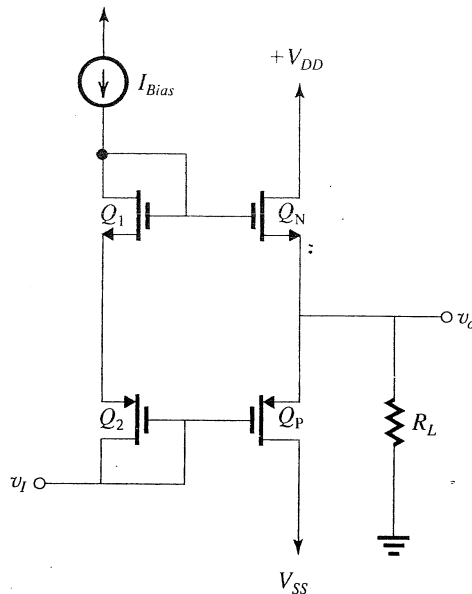

a. under quiescent condition

$$\text{Voltage gain} = \frac{v_O}{v_i} = \frac{R_L}{R_L + R_{\text{out}}}$$

As shown in problem 11.24, for matched transistors

$$R_{\text{out}} = \frac{1}{2g_m}$$

Substitute for R_{out} above for $\frac{v_O}{v_i}$

$$\frac{v_O}{v_i} = \frac{R_L}{R_L + \frac{1}{2g_m}}$$

$$\text{b. Voltage gain} = 0.98 = \frac{R_L}{R_L + \frac{1}{2g_m}}$$

$$0.98 = \frac{1000}{1000 + \frac{1}{2g_m}}$$

$$\Rightarrow g_m = 24.5 \text{ mA/V}$$

For Q_1 , $I_{\text{Bias}} = I_D$

$$\therefore 0.1 = \frac{1}{2} k_1 V_{OV}^2$$

$$0.1 = \frac{1}{2} \times 20 \times V_{ov}^2$$

$$\Rightarrow V_{ov} = 0.1 \text{ V}$$

For Q_N

$$g_m = k_n V_{ov}$$

$$24.5 = k_n \times 0.1$$

$$k_n = 245 \text{ mA/V}^2$$

$$n = \frac{k_n}{k_1} = \frac{245}{20}$$


$$= 12.25$$

and $I_Q = nI_{bias}$

$$= 12.25 \times 0.1$$

$$= 1.225 \text{ mA}$$

11.26

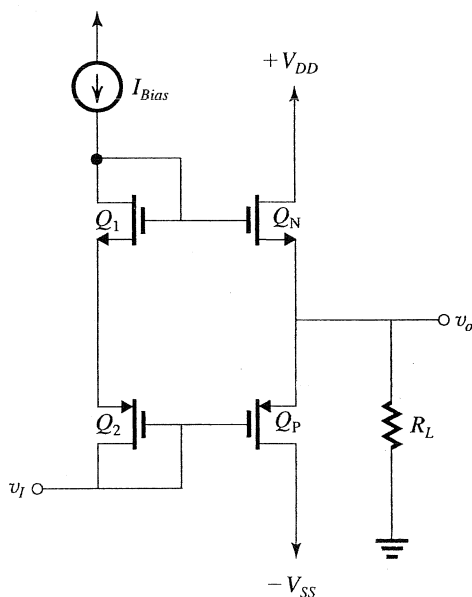

a. Equation 11.43

$$I_Q = I_{Bias} \frac{(W/L)_n}{(W/L)_1}$$

$$1 = 0.1 \frac{(W/L)_n}{(W/L)_1}$$

$$\frac{(W/L)_n}{(W/L)_1} = 10$$

$$Q_1: I_{Bias} = \frac{1}{2} k_n' \left(\frac{W}{L}\right)_1 V_{ov}^2$$

$$0.1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_1 \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_1 = 20$$

$$Q_2: 0.1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_2 \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_2 = 50$$

$$Q_N: 1 = \frac{1}{2} \times 0.250 \times \left(\frac{W}{L}\right)_N \times (0.2)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_N = 200$$

$$Q_P: 1 = \frac{1}{2} \times 0.100 \times \left(\frac{W}{L}\right)_P \times (0.2)^2$$

$$\left(\frac{W}{L}\right)_P = 500$$

b. From the circuit we get $-v_i + V_{GSP} + v_o = 0$

Since $v_o = 0$

$$v_i = V_{GSP}$$

$$V_{SGP} = |V_{ov}| + |V_t|$$

$$= 0.2 + 0.45$$

$$= -0.65 \text{ V}$$

$$\therefore v_i = V_{GSP} = -0.65 \text{ V}$$

c. Using equation 11.4

$$v_{o\max} = V_{DD} - V_{ov}|_{Bias} - V_{GSN}$$

To find V_{GSN} ,

$$i_{DN\max} = \frac{1}{2} k_n' \frac{W}{L} (V_{GSN} - V_t)^2$$

$$10 = \frac{1}{2} \times 0.250 \times 200 (V_{GSN} - V_t)^2$$

$$\Rightarrow V_{GSN} - V_t = 0.63 \text{ V}$$

$$V_{GSN} = V_t + 0.63 = 0.45 + 0.63 \approx 1.1 \text{ V}$$

$$\therefore v_{o\max} = 2.5 - 0.2 - 1.1 = 1.2 \text{ V}$$

11.27

Refer to Figure 11.19

$$I_Q = 3 \text{ mA}, |V_{ov}| = 0.15 \text{ V}$$

$$g_{mn} = g_{mp} = \frac{2I_D}{V_{ov}} = \frac{2 \times 3}{0.15} = 0.04 \text{ A/V}$$

$$= 40 \text{ mA/V}$$

Using equation 11.57

$$R_{out} = \frac{1}{\mu(g_{mp} + g_{mn})} = \frac{1}{5(0.04 + 0.04)}$$

$$= 2.5 \Omega$$

11.28

a. From equation 11.68

$$|\text{Gain Error}| = \frac{1}{2\mu g_m R_L}$$

From equation 11.57

$$R_{out} \approx \frac{1}{\mu(g_{mp} + g_{mn})}$$

$$= \frac{1}{2\mu g_m} \text{ when } g_{mp} = g_{mn} = g_m$$

$$\therefore |\text{Gain Error}| = \frac{1}{2\mu g_m} \times \frac{1}{R_L}$$

$$= \frac{R_{out}}{R_L}$$

b. Again equation 11.68

$$|\text{Gain Error}| = \frac{1}{2\mu g_m R_L}$$

$$0.05 = \frac{1}{2 \times 10 \times g_m \times 100}$$

$$g_m = 0.01 \text{ A/V} = 10 \text{ mA/V}$$

Equation 11.67

$$g_m = \frac{2I_Q}{V_{ov}}$$

$$V_{ov} = \frac{2I_Q}{g_m} = \frac{2 \times 1}{10}$$

$$V_{ov} = 0.2 \text{ V}$$

11.29

$$\text{a. } I_Q = \frac{1}{2} k_n' \frac{W}{L} V_{ov}^2$$

$$1.5 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right)_P (0.15)^2$$

$$\Rightarrow \left(\frac{W}{L}\right)_P \approx 1333.3$$

$$\left(\frac{W}{L}\right)_N = \frac{(W/L)_P}{(k_n'/k_{Q_p}')} = \frac{1333.3}{(250/100)}$$

$$= 533.3$$

$$\text{b. } g_m = \frac{2I_Q}{V_{ov}} = \frac{2 \times 1.5}{0.15} = 20 \text{ mA/V}$$

$$= 0.02 \text{ A/V}$$

$$R_{out} = \frac{1}{2\mu g_m} \quad g_{mp} = g_{mn} = g_m$$

$$2.5 = \frac{1}{2\mu \times 0.02}$$

$$\mu = \frac{1}{2.5 \times 2 \times 0.02}$$

$$\mu = 10$$

$$\text{c. Gain Error} = -\frac{V_{ov}}{4\mu I_Q R_L}$$

$$= -\frac{0.15}{4 \times 10 \times 1.5 \times 10^{-3} \times 50}$$

$$= -0.05$$

$$\text{Gain Error} = 5\%$$

d. In the quiescent state $v_o = 0$

The voltage at the output of each amplifier will be $= \mu (v_o - v_i) = -\mu v_i$

e. Q_N turn off when the voltage at its gate drops from quiescent value of -1.85 V to -2 V , at which point $V_{GSN} = V_{NS}$, and an equal change of -0.15 V appear at the output of the top amplifier.

$$i_P = \frac{1}{2} k_P \left(\frac{W}{L}\right)_P (0.3)^2$$

$$= \frac{1}{2} \times 0.100 \times 1333.3 \times 0.3^2$$

$$i_P = 6 \text{ mA}$$

$$v_o = 6 \times 10^{-3} \times 50 \Omega = 0.3 \text{ V}$$

So for $v_o > 0.3 \text{ V}$, Q_P conducts all the current.
f. the situation at $v_o = v_{o,max}$ will occur when Q_P will go from saturation to triode region and it will be approximately 2 V .

Linear range of v_o from 2 to -2 V

11.30

$$\text{Power rating} = \frac{130 - 30}{2} = 50 \text{ W}$$

$$I_{Cav} \leq \frac{50}{20} = 2.5 \text{ A}$$

11.31

$$\theta_{JA} = \frac{150 - 25}{0.2} = 625^\circ \text{C/W} = 0.625^\circ \text{C/mW}$$

At 70°C , Power rating

$$= \frac{150 - 70}{0.625} = 128 \text{ mW}$$

$$T_J = 50 + 0.625 \times 100 = 112.5^\circ \text{C}$$

11.32

$$T_J \leq 50 + 3 \times 30 = 140^\circ \text{C}$$

$$V_{BE} = 800 - 2 \times (140 - 25) = 570 \text{ mV}$$

$$= 0.57 \text{ V}$$

It will reduce thermal resistance and maximum power dissipation.

11.33

$$\text{(a) } \theta_{JA} = \frac{T_{Jmax} - T_{AO}}{P_{DO}}$$

$$= \frac{100 - 25}{2} = 37.5^\circ \text{C/W}$$

(b) At $T_A = 50^\circ \text{C}$

$$P_{Dmax} = \frac{T_{Jmax} - T_A}{\theta_{JA}}$$

$$= \frac{100 - 50}{37.5} = 1.33 \text{ W}$$

(c) $T_J = 25^\circ + 37.5 \times 1 = 62.5^\circ \text{C}$

11.34

$$T_C - T_A = \theta_{CA} P_D$$

$$= (\theta_{CS} + \theta_{SA}) P_D$$

$$\Rightarrow P_D = \frac{T_C - T_A}{\theta_{CS} + \theta_{SA}} = \frac{90 - 30}{0.5 + 0.1} = 100 \text{ W}$$

$$T_J - T_C = \theta_{JC} P_D$$

$$130 - 90 = \theta_{JC} \times 100$$

$$\Rightarrow \theta_{JC} = 0.4^\circ \text{C/W}$$