


FIRST AND SECOND ORDER FILTERS

WHY SO IMPORTANT?

A N<sup>TH</sup> ORDER H(S) CAN BE FACTORED INTO 1<sup>st</sup> ORDER TRANSFER-FUNCTIONS

$$H(S) = H_1(S) H_2(S) \dots H_N(S)$$

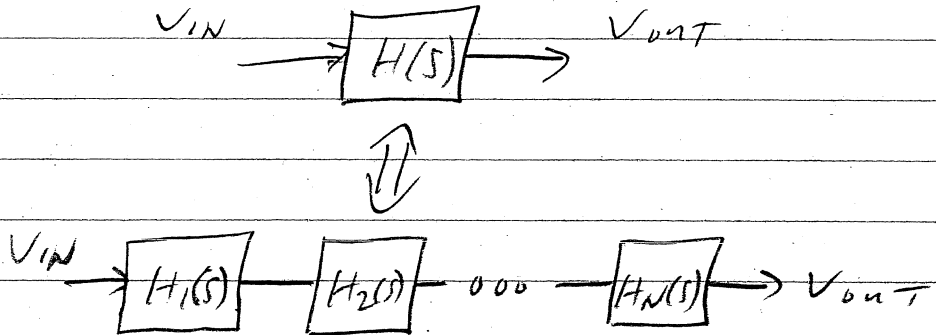WHERE H<sub>i</sub>(S) ARE 1<sup>st</sup> ORDER



BUT IF H(S) HAS COMPLEX ZEROS OR POLES THEN THOSE H<sub>i</sub>(S) HAVE COMPLEX COEFFICIENTS ⇒ NOT EASILY REALIZED

HOWEVER, IF WE GROUP COMPLEX-CONJUGATE PAIRS OF POLES AND ZEROS INTO 2nd ORDER SECTIONS THEN ALL COEFFICIENTS BECOME REAL

SPECIFICALLY, IF  $H(s) = \frac{[s - (x_1 + jy_1)][s - (x_1 - jy_1)] \dots}{[s - (x_2 + jy_2)][s - (x_2 - jy_2)] \dots}$

$x_1, y_1$  ALL REAL  
 $x_2, y_2$  REAL

$T_1(s)$        $T_2(s)$   
 $H_{BQ_1}(s)$

$$H(s) = \frac{[s^2 - 2x_1s - (x_1^2 + y_1^2)] \dots}{[s^2 - 2x_2s - (x_2^2 + y_2^2)] \dots}$$

$H_{BQ_1}(s) \leftarrow$  BIQUAD (BIQUADRATIC)

CAN ALWAYS WRITE  $H(s)$  IN FACTORED FORM CONTAINING BIQUADS (WITH ONLY REAL COEFF) AND POSSIBLY ONE BIQUADR (1st ORDER WITH REAL COEFF)

(A) 1st order  $H(s) = \frac{a_1s + a_0}{s + b_0} \triangleq \frac{a_1s + a_0}{s + \omega_0}$



$\omega_0 \rightarrow$  POLE FREQUENCY  $\omega_0 = b_0$

NATIVE POLE AT  $s = -\omega_0$   $\omega_0 > 0$  FOR STABILITY


TRANSMISSION ZERO AT  $s = -\frac{a_0}{a_1}$

DC  $s=0$   $H(0) = \frac{a_0}{\omega_0}$       AT HF  $s \rightarrow \infty$   $H(\infty) = a_1$

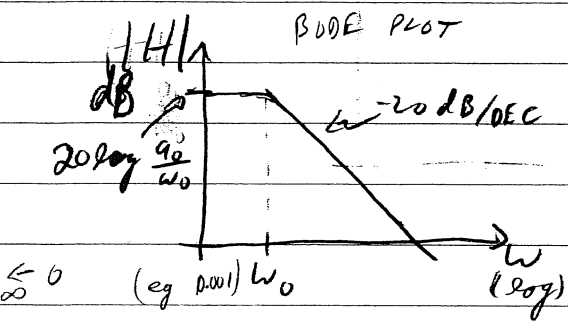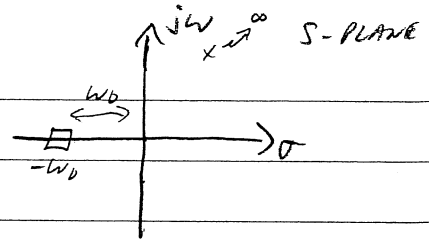a) LOW PASS  $H(s) = \frac{a_0}{s + \omega_0}$




PASSIVE REALIZATION

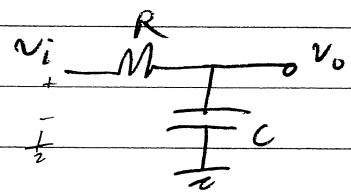

$CR = \frac{1}{\omega_0}$   
DC GAIN = 1



ACTIVE REALIZATION

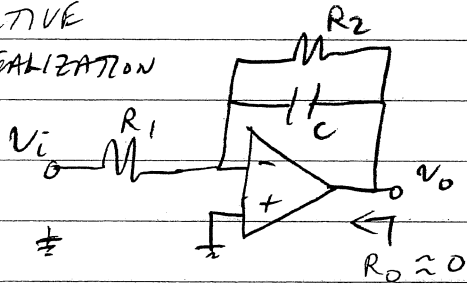


$CR_2 = \frac{1}{\omega_0}$   
DC GAIN =  $-\frac{R_2}{R_1}$

SO CAN CASCADE CIRCUITS WITH LITTLE INTERACTION

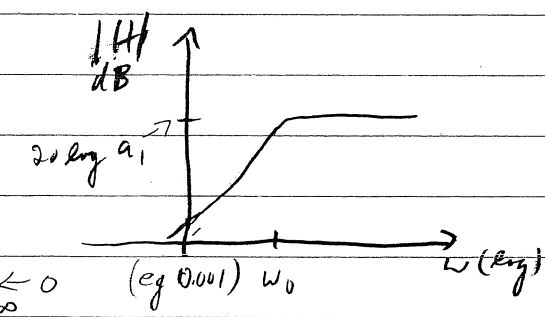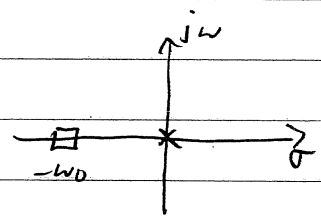b) HIGH-PASS  $H(s) = \frac{a_1 s}{s + \omega_0}$




PASSIVE

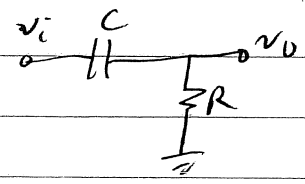

$CR = \frac{1}{\omega_0}$   
HF GAIN = 1

ACTIVE

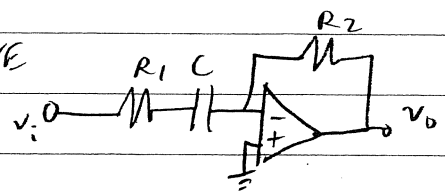

$CR_1 = \frac{1}{\omega_0}$   
HF GAIN =  $-\frac{R_2}{R_1}$

SEE TEXT FOR GENERAL & ALL-PASS CASES.

(B) BIQUADRATIC  $H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0} \triangleq \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$

POLES

$\omega_0 = \sqrt{b_0}$

POLE FREQUENCY

$Q = \frac{\sqrt{b_0}}{b_1}$

POLE QUALITY FACTOR (OR Q FACTOR)  
OR POLE-Q

WRITING  $s^2 + \frac{\omega_0}{Q}s + \omega_0^2 = (s - e_1)(s - e_2)$  (ie SOLVING FOR ROOTS)


$e_1, e_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{4Q^2}}$

FOR  $\frac{1}{4Q^2} < 1$  OR  $Q > 0.5$   $e_1, e_2$  ARE COMPLEX-CONJUGATE

$|e_1| = |e_2| = \omega_0$  &  $REAL[e_1] = REAL[e_2] = -\frac{\omega_0}{2Q}$

GRAPHICALLY

FOR  $Q > 0.5$

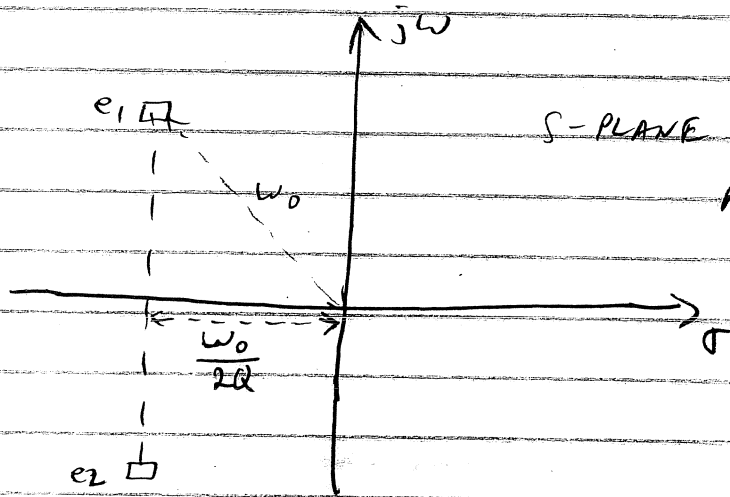


AS  $Q \rightarrow \infty$

$e_1, e_2$  APPROACH  $j\omega$  AXIS


$Q \rightarrow 0.5$

$e_1, e_2$  APPROACH REAL AXIS

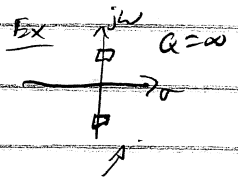

FOR  $Q < 0.5$   
 $Q > 0$  FOR STABILITY

$e_1, e_2$  ARE ON THE REAL AXIS

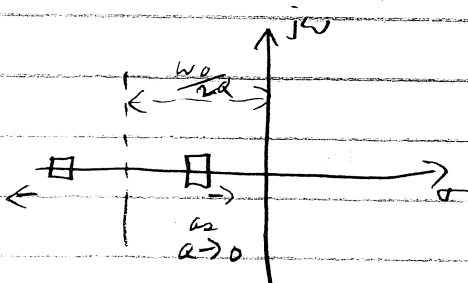

TRANSMISSION ZEROS  
 $a_2 s^2 + a_1 s + a_0$



LP  $\Rightarrow a_0$       HP  $\Rightarrow a_2 s^2$

BP  $\Rightarrow a_1 s$       NOTCH  $\Rightarrow a_2 s^2 + a_0$

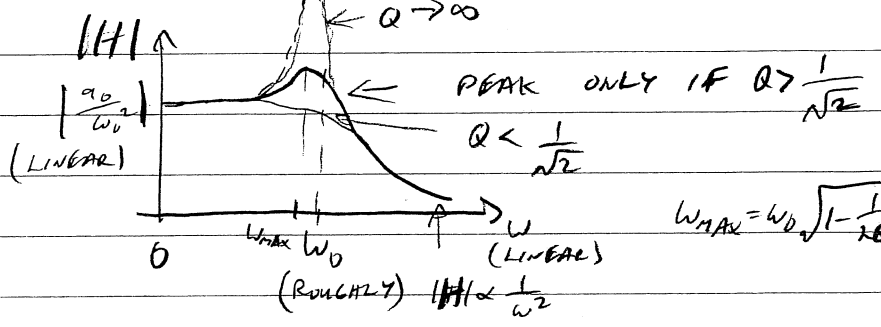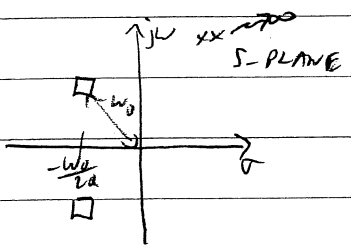a) LOW PASS

$$H(s) = \frac{a_0}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



DC GAIN  $\Rightarrow T(0) = \frac{a_0}{\omega_0^2}$



b) HIGH PASS



$$H(s) = \frac{a_2 s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

HF GAIN  $\Rightarrow H(\infty) = a_2$

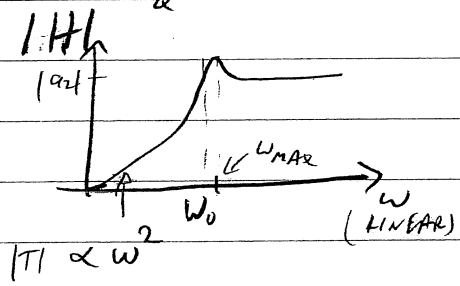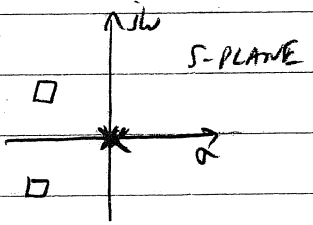

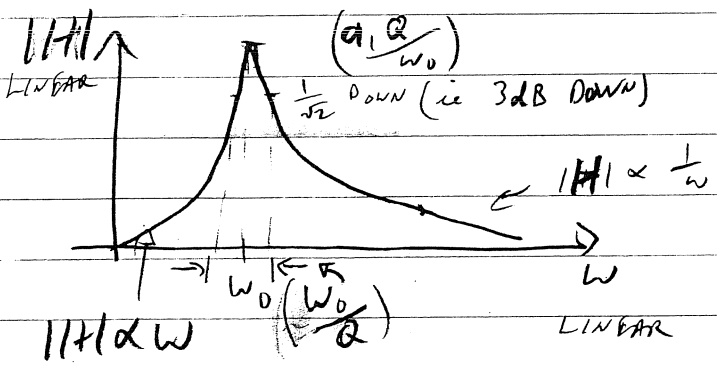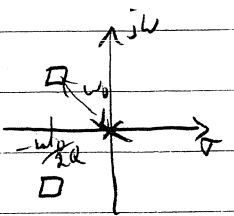c) BAND PASS

$$H(s) = \frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$





WIDTH OF 3dB BANDWIDTH  $BW = \frac{\omega_0}{Q}$

[ 3dB BANDWIDTH  $= \omega_2 - \omega_1$  WHERE  $|H(\omega_2)| = |H(\omega_1)| = \frac{1}{\sqrt{2}}$  PEAK VALUE ]

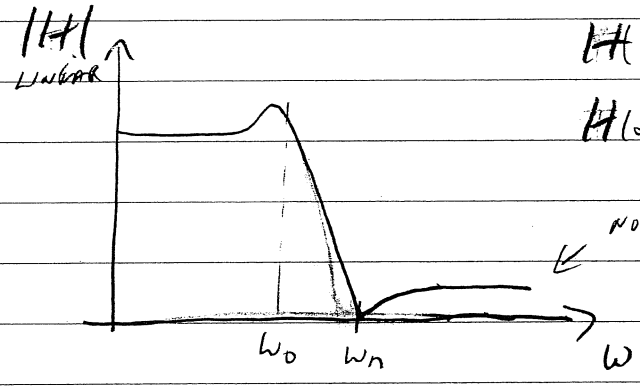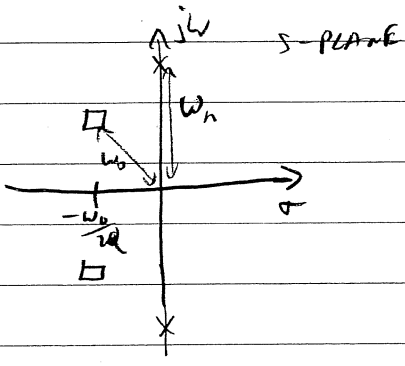d) LOW PASS NOTCH (LPN)

$$H(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \omega_n \geq \omega_0$$





$$H(0) = \frac{a_2 \omega_n^2}{\omega_0^2}$$

$$H(\infty) = a_2$$

NOTE  $\neq 0$

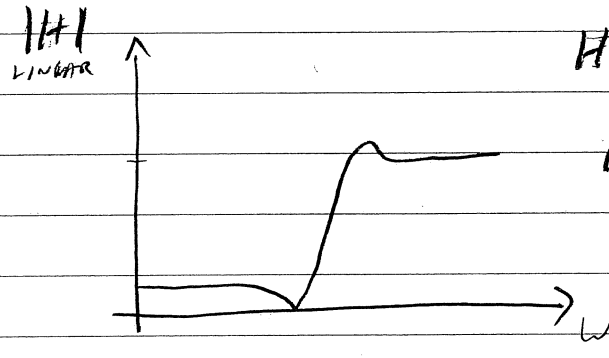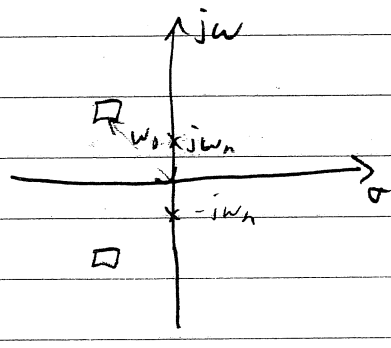e) HIGH PASS NOTCH (HPN)

$$H(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \omega_n \leq \omega_0$$






$$H(0) = \frac{a_2 \omega_n^2}{\omega_0^2}$$

$$H(\infty) = a_2$$

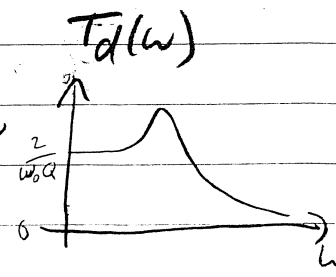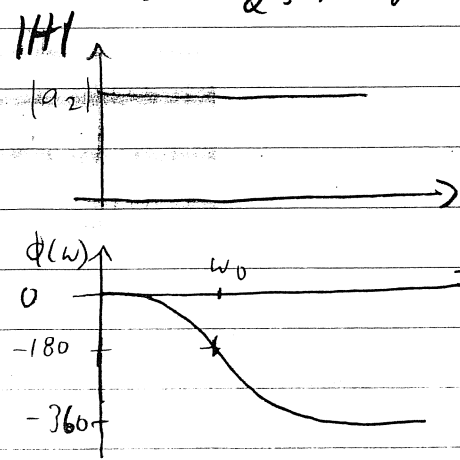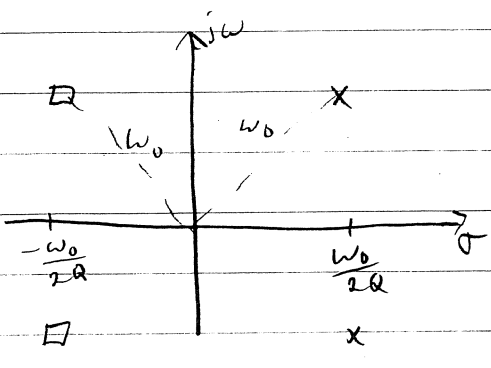
f) ALL-PASS

$$H(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$




NOTE

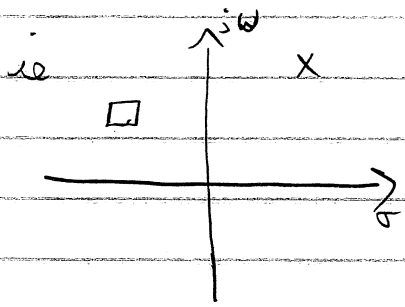FOR PHASE - THE EFFECT OF A ZERO IN THE RHP IS THE SAME AS A MIRROR IMAGE POLE IN LHP




SAME PHASE AS

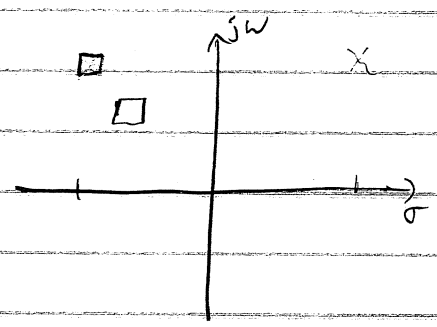

17 2ND ORDER LCR RESONATOR

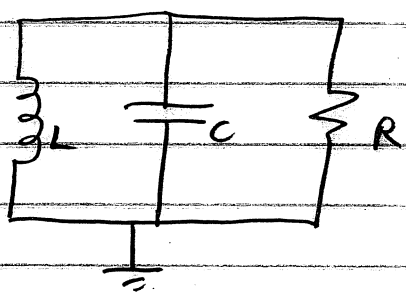THE POLES OF A BIQUAD CAN BE REALIZED WITH THE FOLLOWING LCR CIRCUIT



SHALL SEE THAT

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 CR$$

IF THE INPUT IS APPLIED OR OUTPUT TAKEN SUCH THAT IT DOES NOT AFFECT THE NATURAL RESONANCE, THEN THE POLES CAN BE FOUND AS THE DENOMINATOR OF THE TRANSFER-FUNCTION POLYNOMIAL.