


FIRST AND SECOND ORDER FILTERS

WHY SO IMPORTANT?

A NTH ORDER H(S) CAN BE FACTORED INTO 1st ORDER TRANSFER-FUNCTIONS

$$H(S) = H_1(S) H_2(S) \dots H_N(S)$$

WHERE H_i(S) ARE 1st ORDER

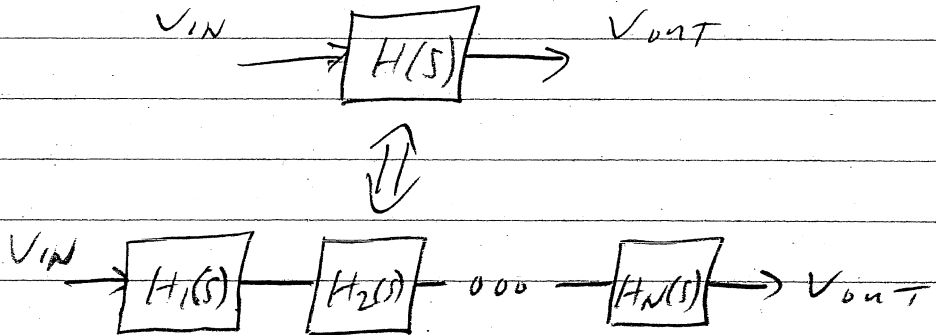

BUT IF H(S) HAS COMPLEX ZEROS OR POLES
 THEN THOSE H_i(S) HAVE COMPLEX
 COEFFICIENTS ⇒ NOT EASILY REALIZED

HOWEVER, IF WE GROUP COMPLEX-CONJUGATE PAIRS OF POLES AND ZEROS INTO 2nd ORDER SECTIONS THEN ALL COEFFICIENTS BECOME REAL

SPECIFICALLY, IF $H(s) = \frac{[s - (x_1 + jy_1)][s - (x_1 - jy_1)] \dots}{[s - (x_2 + jy_2)][s - (x_2 - jy_2)] \dots}$

x_1, y_1 ALL REAL
 x_2, y_2 REAL

$T_1(s)$ $T_2(s)$
 $H_{BQ_1}(s)$

$$H(s) = \frac{[s^2 - 2x_1s - (x_1^2 + y_1^2)] \dots}{[s^2 - 2x_2s - (x_2^2 + y_2^2)] \dots}$$

$H_{BQ_1}(s) \leftarrow$ BIQUAD (BIQUADRATIC)

CAN ALWAYS WRITE $H(s)$ IN FACTORED FORM CONTAINING BIQUADS (WITH ONLY REAL COEFF) AND POSSIBLY ONE BILINEAR (1st ORDER WITH REAL COEFF)

(A) 1st order $H(s) = \frac{a_1s + a_0}{s + b_0} \triangleq \frac{a_1s + a_0}{s + \omega_0}$



$\omega_0 \rightarrow$ POLE FREQUENCY $\omega_0 = b_0$

NATIVE POLE AT $s = -\omega_0$ $\omega_0 > 0$ FOR STABILITY


TRANSMISSION ZERO AT $s = -\frac{a_0}{a_1}$

DC $s=0$ $H(0) = \frac{a_0}{\omega_0}$ AT HF $s \rightarrow \infty$ $H(\infty) = a_1$

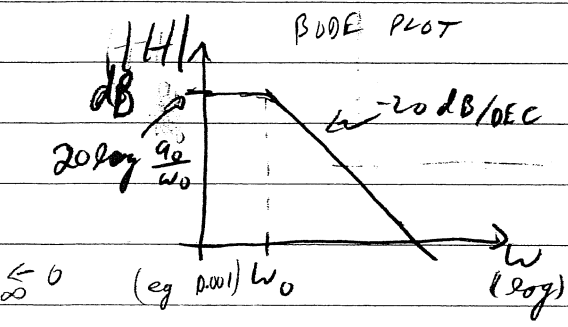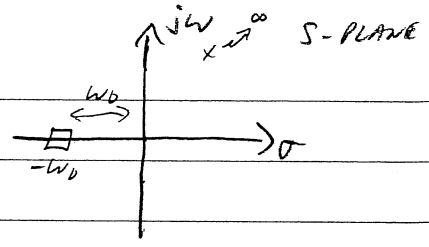a) LOW PASS $H(s) = \frac{a_0}{s + \omega_0}$




PASSIVE REALIZATION

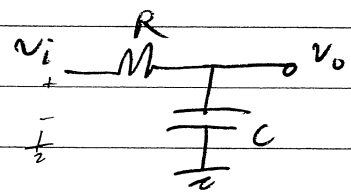

$CR = \frac{1}{\omega_0}$
DC GAIN = 1



ACTIVE REALIZATION

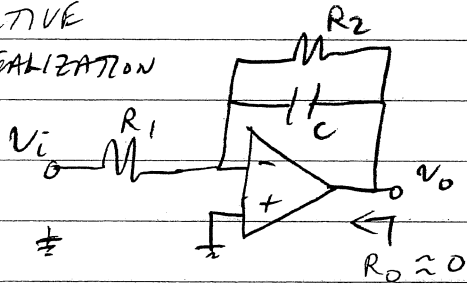


$CR_2 = \frac{1}{\omega_0}$
DC GAIN = $-\frac{R_2}{R_1}$

SO CAN CASCADE CIRCUITS WITH LITTLE INTERACTION

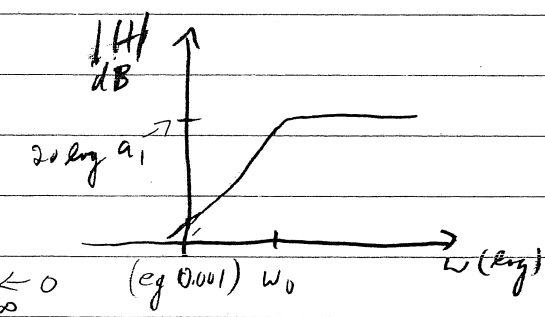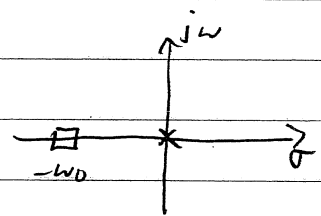b) HIGH-PASS $H(s) = \frac{a_1 s}{s + \omega_0}$




PASSIVE

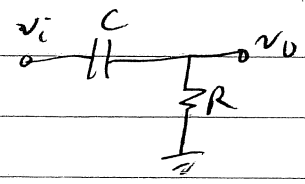

$CR = \frac{1}{\omega_0}$
HF GAIN = 1

ACTIVE

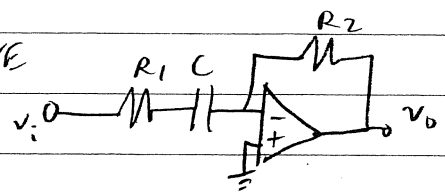

$CR_1 = \frac{1}{\omega_0}$
HF GAIN = $-\frac{R_2}{R_1}$

SEE TEXT FOR GENERAL & ALL-PASS CASES.

(B) BIQUADRATIC $H(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0} \triangleq \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$

POLES

$\omega_0 = \sqrt{b_0}$ POLE FREQUENCY

$Q = \frac{\sqrt{b_0}}{b_1}$ POLE QUALITY FACTOR (OR Q FACTOR) OR POLE-Q

WRITING $s^2 + \frac{\omega_0}{Q}s + \omega_0^2 = (s - e_1)(s - e_2)$ (ie SOLVING FOR ROOTS)


$e_1, e_2 = -\frac{\omega_0}{2Q} \pm j\omega_0 \sqrt{1 - \frac{1}{4Q^2}}$

FOR $\frac{1}{4Q^2} < 1$ OR $Q > 0.5$ e_1, e_2 ARE COMPLEX-CONJUGATE

$|e_1| = |e_2| = \omega_0$ & $REAL[e_1] = REAL[e_2] = -\frac{\omega_0}{2Q}$


GRAPHICALLY

FOR $Q > 0.5$

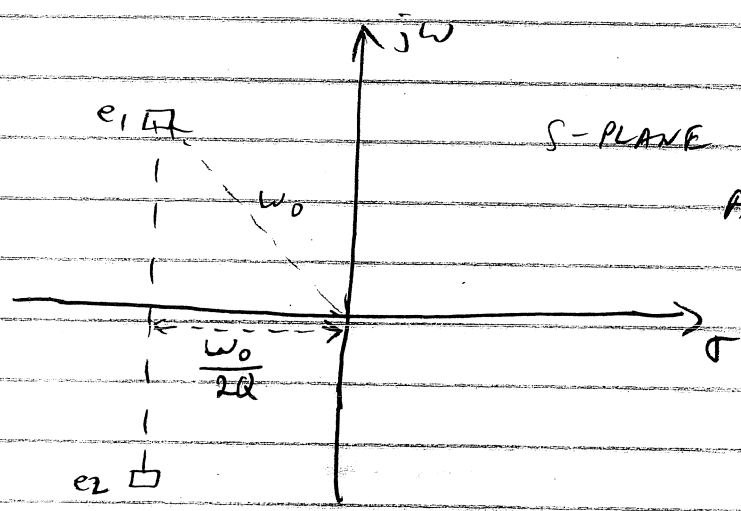


AS $Q \rightarrow \infty$
 e_1, e_2 APPROACH jw AXIS

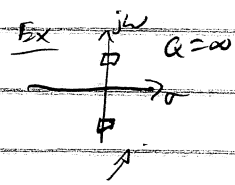$Q \rightarrow 0.5$
 e_1, e_2 APPROACH REAL AXIS



FOR $Q < 0.5$
 $Q > 0$ FOR STABILITY

e_1, e_2 ARE ON THE REAL AXIS

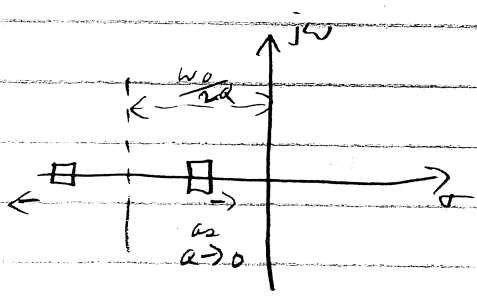

TRANSMISSION ZEROS
 $a_2 s^2 + a_1 s + a_0$



LP $\Rightarrow a_0$ HP $\Rightarrow a_2 s^2$

BP $\Rightarrow a_1 s$ NOTCH $\Rightarrow a_2 s^2 + a_0$

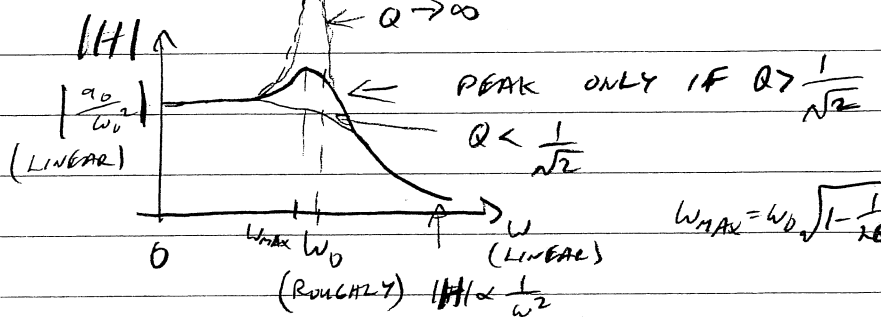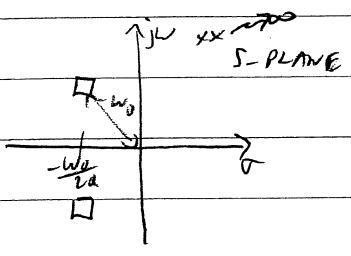a) LOW PASS

$$H(s) = \frac{a_0}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



DC GAIN $\Rightarrow T(0) = \frac{a_0}{\omega_0^2}$



b) HIGH PASS

$$H(s) = \frac{a_2 s^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



HF GAIN $\Rightarrow H(\infty) = a_2$

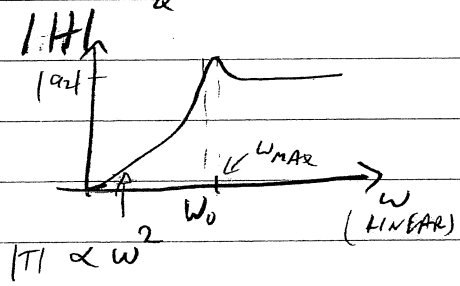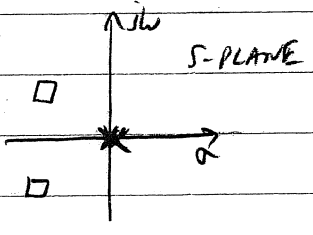

~~omega_max = omega_0 * sqrt(1 - 1/(2Q^2))~~

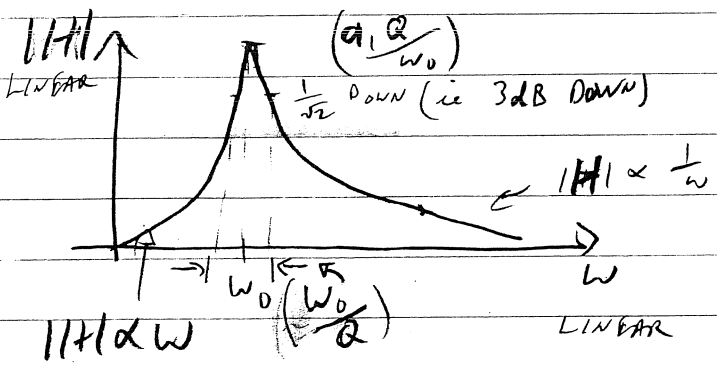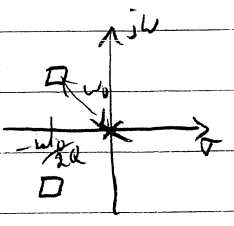c) BAND PASS

$$H(s) = \frac{a_1 s}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$





WIDTH OF 3dB BANDWIDTH $BW = \frac{\omega_0}{Q}$

[3dB BANDWIDTH $= \omega_2 - \omega_1$ WHERE $|H(\omega_2)| = |H(\omega_1)| = \frac{1}{\sqrt{2}}$ PEAK VALUE]

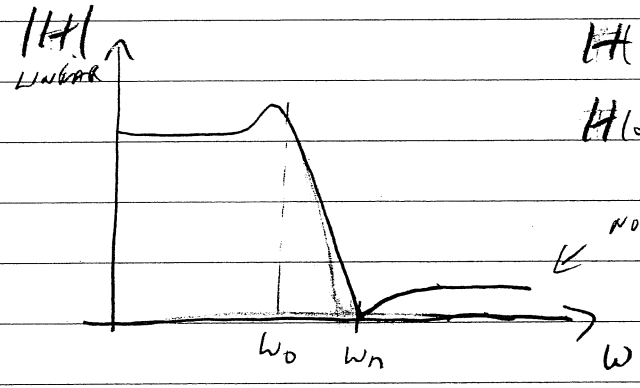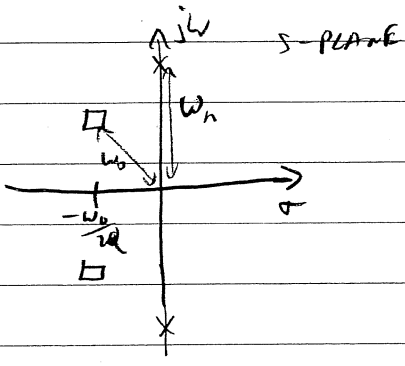d) LOW PASS NOTCH (LPN)

$$H(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \omega_n \geq \omega_0$$





$$H(0) = \frac{a_2 \omega_n^2}{\omega_0^2}$$

$$H(\infty) = a_2$$

NOTE $\neq 0$

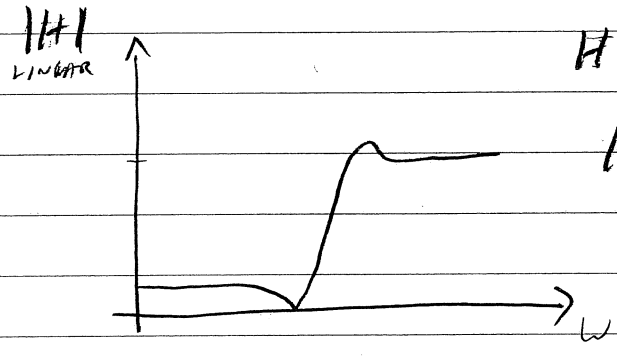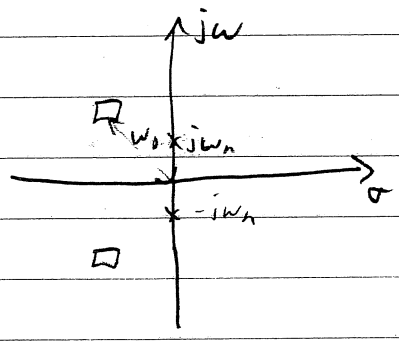e) HIGH PASS NOTCH (HPN)

$$H(s) = a_2 \frac{s^2 + \omega_n^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \omega_n \leq \omega_0$$






$$H(0) = \frac{a_2 \omega_n^2}{\omega_0^2}$$


$$H(\infty) = a_2$$

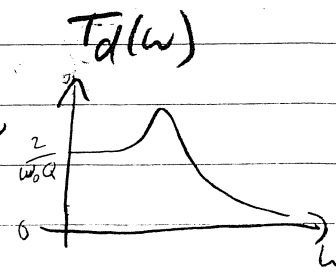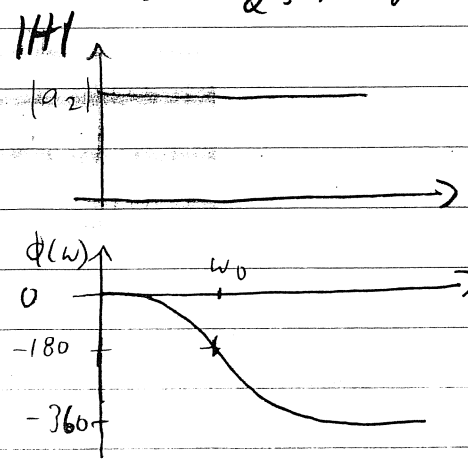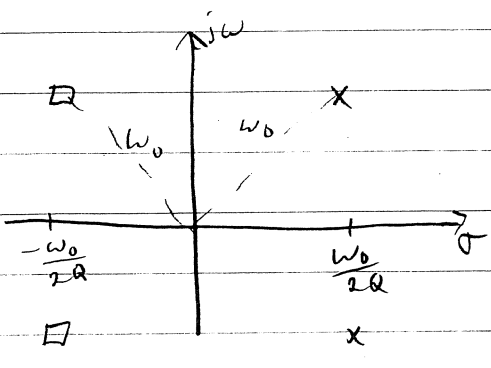f) ALL-PASS


$$H(s) = a_2 \frac{s^2 - s \frac{\omega_0}{Q} + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$



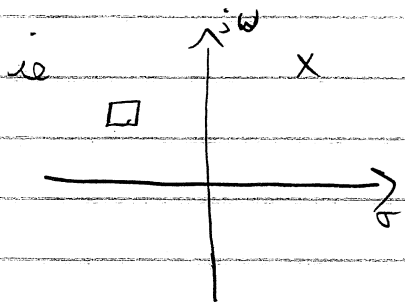NOTE FOR PHASE - THE EFFECT OF A ZERO IN THE RHP IS THE SAME AS A MIRROR IMAGE POLE IN LHP




SAME PHASE AS

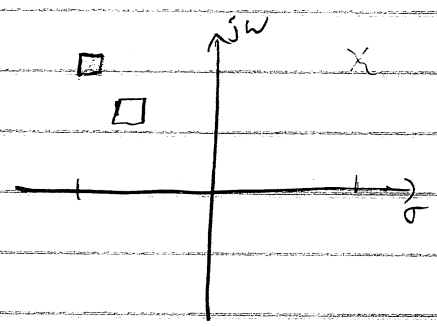

17 2ND ORDER LCR RESONATOR

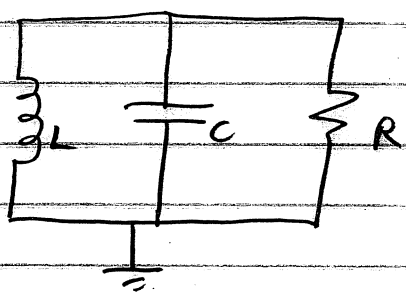THE ~~POLES~~ POLES OF A BIQUAD CAN BE REALIZED WITH THE FOLLOWING LCR CIRCUIT



SHALL SEE THAT

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 CR$$

IF THE INPUT IS APPLIED OR OUTPUT TAKEN SUCH THAT IT DOES NOT AFFECT THE NATURAL RESONANCE, THEN THE POLES CAN BE FOUND AS THE DENOMINATOR OF THE TRANSFER-FUNCTION POLYNOMIAL.