

# BIQUAD DESIGN

CASCADES-OF-BIQUADS ARE THE MOST COMMON DESIGN APPROACH FOR BOTH ANALOG AND DIGITAL FILTERS.

WHY?  $\Rightarrow$  PERFORMANCE IS GOOD (THOUGH NOT EXCELLENT) BUT TESTING IS SIMPLE (TEST INDIVIDUAL BIQUADS SEPARATELY). DESIGN IS ALSO RELATIVELY STRAIGHT FORWARD.

STEPS IN DESIGNING A CASCADE-OF-BIQUADS.

1) CHOOSE APPROPRIATE POLE-ZERO PAIRING

2) CHOOSE A SUITABLE CASCADE-ORDERING

3) REALIZE EACH BIQUAD SECTION IN DESIRED TECHNOLOGY (ACTIVE-RC, DIGITAL FILTERS, SWITCHED-CAPACITORS)

CAN BE DONE IN OPPOSITE ORDER  $\updownarrow$

4) SCALE APPROPRIATE SIGNAL NODES TO OBTAIN MAXIMUM DYNAMIC RANGE.

LETS LOOK AT EACH OF THESE STEPS USING ACTIVE-RC FOR EXAMPLES AND THE FOLLOWING TRANSFER-FUNCTION:

BTH ORDER BANDPASS FILTER  $\rightarrow$  EQUIRIPPLE PASSBAND FROM 1KHZ TO 1.4 KHZ (0.4 dB RIPPLE) PEAK GAIN OF 0 dB

T(S)

POLES:	$P_1, P_1^*$	$\omega_{01} = 0.7106$	$Q = 15.256$
	$P_2, P_2^*$	$\omega_{02} = 0.7911$	$Q = 6.192$
	$P_3, P_3^*$	$\omega_{03} = 0.9188$	$Q = 6.743$
	$P_4, P_4^*$	$\omega_{04} = 1.0048$	$Q = 19.113$

NORMALIZED WITH RESPECT TO  $2\pi \times 1.4$  K RAD/S


IS COMPLEX CONJUGATE OF  $P_1$

ZEROS:  $z_1, z_1^* \pm j 0.3996$   
 $z_2, z_2^* \pm j 1.2561$   
 $z_3, z_4 \quad 0, 0$   
 $z_5, z_6 \quad \infty, \infty$

NORMALIZED WRT  
 $2\pi \times 1.4 \text{ K RAD/S}$

DYNAMIC RANGE IN GENERAL

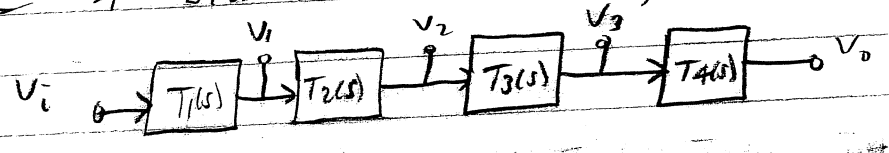
FOR THIS 8TH ORDER BANDPASS FILTER, THERE WILL BE A BIQUAD FILTERS;  $T_1(s), T_2(s), T_3(s), T_4(s)$



$$\frac{V_1}{V_i} = T_1(s) \quad \frac{V_2}{V_i} = T_1(s) T_2(s) \quad \frac{V_3}{V_i} = T_1(s) T_2(s) T_3(s)$$

$$\frac{V_o}{V_i} = T(s) = T_1(s) T_2(s) T_3(s) T_4(s)$$

DEFINE  $\|T_i(s)\|_\infty = \max(|T_i(j\omega)|, 0 \leq \omega < \infty)$  ← L<sub>∞</sub> NORM CALLED AN

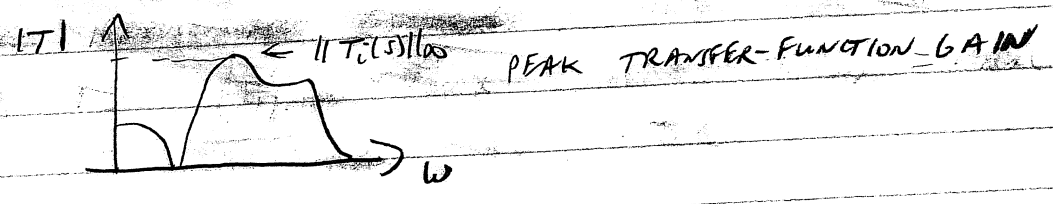

ASSUMING  $V_1, V_2, V_3, V_o$  ALL CLIP AT THE SAME LEVEL THEN WE SHOULD SCALE  $\|T_1\|_\infty, \|T_1 T_2\|_\infty, \|T_1 T_2 T_3\|_\infty$  SUCH THAT

$$\|T\|_\infty = \|T_1\|_\infty = \|T_1 T_2\|_\infty = \|T_1 T_2 T_3\|_\infty$$

THAT WAY, FOR A SWEEP SINUSOID INPUT OF SAY 1 VPP, EACH OUTPUT,  $V_1, V_2, V_3, V_o$  WILL ATTAIN THE SAME PEAK VOLTAGE LEVEL (THOUGH AT DIFFERENT FREQUENCIES PERHAPS). THUS DYNAMIC RANGE IS OPTIMIZED IN AN L<sub>∞</sub> SENSE. FOR A GIVEN SET OF  $T_1, T_2, T_3, T_4$

WHY? DYNAMIC RANGE IS DETERMINED BY THE RATIO OF LARGEST USEFUL SIGNAL TO THE SMALLEST USEFUL SIGNAL.

LARGEST USEFUL SIGNAL → DETERMINED BY MAXIMUM VOLTAGE LEVELS POSSIBLE WITHOUT SEVERE DISTORTION. (ie CLIPPING)

SMALLEST USEFUL SIGNAL → DETERMINED BY NOISE CONSIDERATIONS. THERMAL NOISE, INTERFERENCE, ETC.


TO MAXIMIZE DYNAMIC RANGE, KEEP ALL INTERNAL SIGNALS AS LARGE AS POSSIBLE WITHOUT DISTORTING.

WHILE STEP 4) SCALES FOR DYNAMIC RANGE FOR A GIVEN  $T_1, T_2, T_3, T_4$  THE CHOICE OF  $T_1, T_2, T_3, T_4$  & THEIR ORDERING


ALSO AFFECT DYNAMIC RANGE PERFORMANCE.

FOR FLAT PASSBANDS,

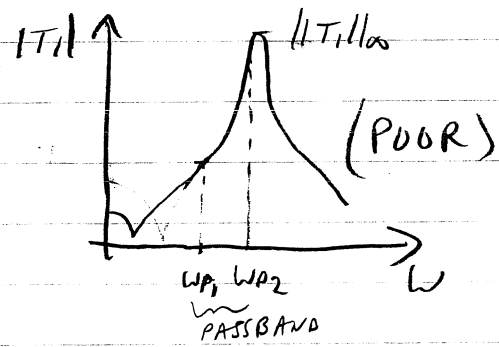TO SEE THIS CONSIDER TWO POSSIBLE CHOICES FOR  $T_1(s)$



NOT VERY FLAT

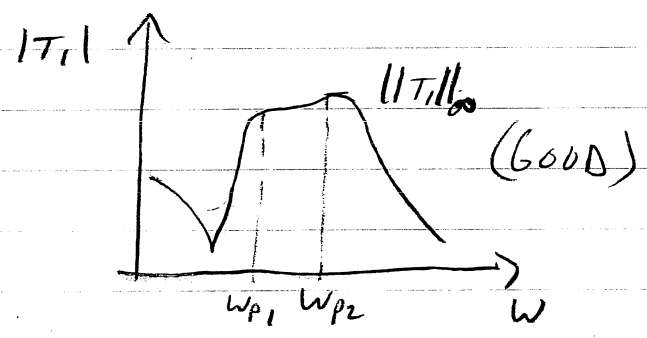

FLAT NEAR PASSBAND OF FILTER

DYNAMIC RANGE POOR

FOR FREQ NEAR  $w_{p1}$

(A GAIN LATER ON MUST COMPENSATE FOR THIS LOSS NEAR  $w_{p1}$ )

IN SUMMARY, CHOOSE  $T_1, T_2, T_3, T_4$  TO RESULT IN AS FLAT TRANSFER-FUNCTIONS AS POSSIBLE AROUND FILTER'S PASSBAND. (FOR FLAT PASSBANDS)

POLE-ZERO PAIRING  $\rightarrow$  EACH BIQUAD NEEDS A PAIR OF POLES AND A PAIR OF ZEROS


NEED 4 BIQUADS  $\Rightarrow$   $k_1 \frac{(s-z_1)(s-z_1^*)}{(s-p_1)(s-p_1^*)}$  OR  $k_1 \frac{(s-z_2)(s-z_2^*)}{(s-p_2)(s-p_2^*)}$  etc.  
(KEEP COMPLEX-CONJUGATES TOGETHER)

IN GENERAL,  $\left(\frac{N}{2}\right)!$  DIFFERENT POLE-ZERO PAIRING POSSIBILITIES

TO GET AS FLAT TRANSFER-FUNCTIONS AS POSSIBLE  
NOTE HIGH Q POLES CAUSE MOST DEVIATION IN PASSBAND  
& HAVING ZEROS CLOSE BY POLES IMPLY CANCELLATION AS  $|T(j\omega)|$  MOVE AWAY FROM PAIR. SYSTEMATIC PROCEDURES ARE AVAILABLE BUT A GOOD APPROXIMATION IS:

RULE-OF-THUMB FOR POLE-ZERO PAIRING

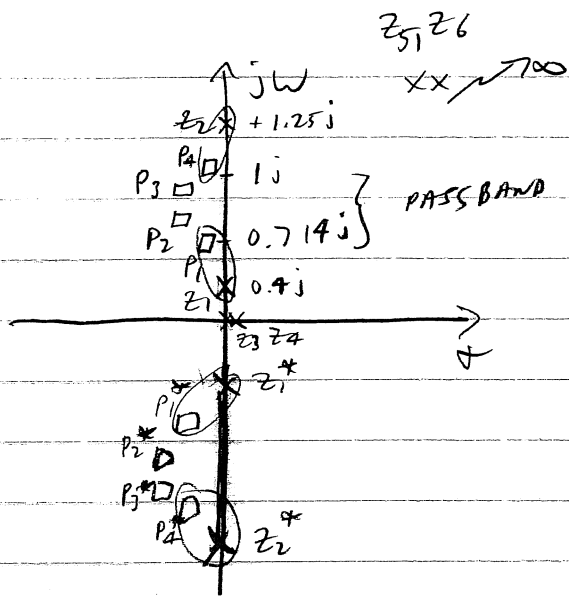POLES SHOULD BE PAIRED WITH THEIR NEAREST ZEROS WITH HIGH POLE Q'S TAKING PRIORITY. OTHER CHOICES DEPEND ON REALIZATION (eg. OFTEN BP PREFERRED OVER HP & LP DUE TO EASE OF TUNING)



$P_4$  IS HIGHEST  $Q \Rightarrow z_2 + P_4 \Rightarrow T_1 = \frac{k_1 (s^2 + 1.2501^2)}{s^2 + \frac{1.0048}{1.9113} s + 1.0048^2}$   
 $P_1$  IS NEXT HIGHEST  $Q \Rightarrow z_1 + P_1 \Rightarrow T_2 = \frac{k_2 (s^2 + 0.3896^2)}{s^2 + \frac{0.7106}{15.256} s + 0.7106^2}$   
 LAST TWO BP

$$T_3 = \frac{k_3 s}{s^2 + \frac{0.7911}{6.192} s + 0.7911^2}$$

$$T_4 = \frac{k_4 s}{s^2 + \frac{0.9188}{6.743} s + 0.9188^2}$$

OR LP & HP

$$T_3 = \frac{k_3 s^2}{s^2 + \frac{0.7911}{6.192} s + 0.7911^2}$$

$$T_4 = \frac{k_4}{s^2 + \frac{0.9188}{6.743} s + 0.9188^2}$$

CHOICE #1

CHOICE #2

NOTE:  $T_1 \Rightarrow$  LPN  
 $T_2 \Rightarrow$  HPN  
 $T_3, T_4 \Rightarrow$  BP

OR

$T_1 \Rightarrow$  LPN  
 $T_2 \Rightarrow$  HPN  
 $T_3 \Rightarrow$  HP  
 $T_4 \Rightarrow$  LP

CASCADE-ORDERING → NEED TO FIND A GOOD ORDERING FOR CASCADE-OF-BIQUADS.

$T_1 \rightarrow T_2 \rightarrow T_3 \rightarrow T_4$  OR  $T_3 \rightarrow T_2 \rightarrow T_4 \rightarrow T_1$  OR etc.

IN GENERAL  $(\frac{N}{2})!$  DIFFERENT ORDERING POSSIBILITIES

GOAL ⇒ KEEP TRANSFER-FUNCTIONS FLAT.

SYSTEMATIC PROCEDURE AVAILABLE BUT ...

RULE-OF-THUMB FOR CASCADE ORDERING

ALTERNATE HP & LP SECTIONS AND PLACE HIGH-Q SECTIONS IN THE MIDDLE WITH LOW Q AT EITHER END.

HP & LP ALTERNATING ⇒ ~~FLATTENS~~ FLATTENS OUT RESPONSE  
HIGH-Q SECTIONS TOGETHER ⇒ FLATTEN OUT EACH OTHER IN MIDDLE FOR SYMMETRY.

IN ABOVE EXAMPLE CHOICE #1.

ONE OF :  $T_3 T_1 T_2 T_4$   
 $T_4 T_2 T_1 T_3$

← SINCE  $T_3$  PEAKS AT 0.7911 - THEN CHOOSE  $T_1$  NEXT WHICH PEAKS AROUND 1.0048  
( $T_2$  PEAKS AROUND 0.7106 +)  
BUMPS WOULD ADD

CHOICE #2

$T_3 T_1 T_2 T_4 \Rightarrow$  HP, LPN, HPN, LP  
 $T_4 T_2 T_1 T_3 \Rightarrow$  LP, HPN, LPN, HP

## REALIZING BIQUAD SECTIONS (ACTIVE-RC)

3 MAIN CLASSES FOR REALIZING ACTIVE-RC BIQUADS.  
(i.e. ACTIVE-RC 2<sup>nd</sup> ORDER TRANSFER-FUNCTIONS)

- SINGLE-AMPLIFIER BIQUADS ( $SAB_1$ )

- ONE OP-AMP,  $\leftarrow$  POPULAR IN 70's AND AS ANTI-ALIASING FILTERS ON SOME IC's
- WORSE DYNAMIC RANGE
- MORE SUSCEPTIBLE TO NON-IDEAL EFFECTS OF AMPLIFIER

- TWO-INTEGRATOR-LOOP BIQUADS

- KHN AND TOW-THOMAS ARE 2 POPULAR TYPES

- TYPICALLY 3 OP-AMPS REQUIRED (SOMETIMES 4)

- GOOD DYNAMIC RANGE  $\leftarrow$  LESS SENSITIVE TO NON-IDEAL OP-AMPS THAN  $SAB_1$

- GENERALIZED-IMPEDANCE-CONVERTER (GIC) BASED

- ONLY 2 OP-AMPS REQUIRED (SOMETIMES 3)

- DEVELOPED BY TWO CANADIAN EE PROFS (ANTONIU & BRUTON)


- GOOD DYNAMIC RANGE  $\leftarrow$  LESS SENSITIVE TO NON-IDEAL OP-AMPS THAN ( $SAB_1$ )

- COULD OSCILLATE IF LARGE STRAY CAPACITANCES (MIGHT REQUIRE COMPENSATION)

# TWO-INTEGRATOR-LOOP BIQUADS


BASED ON A DIRECT-FORM REALIZATION FOR  $N=2$
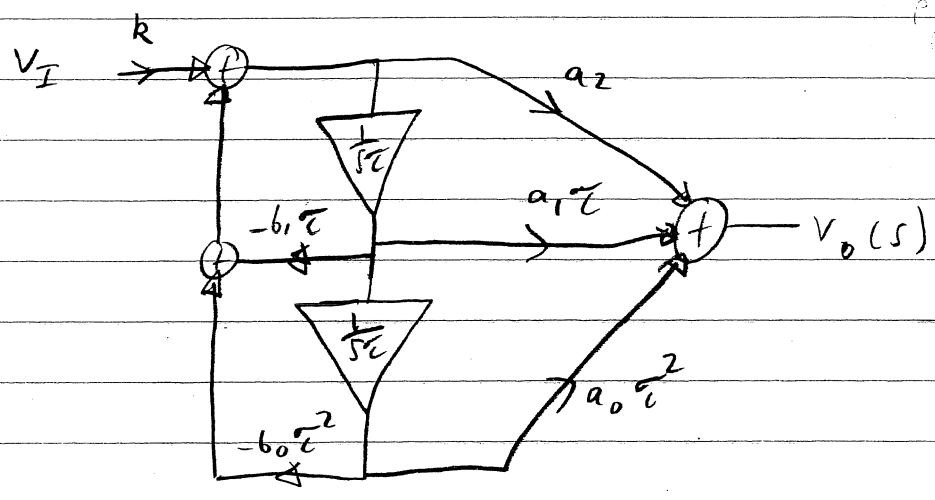
## KHN (KERWIN-HUELSMAN-NEWCOMB) BIQUAD (ALSO KNOWN AS THE STATE-VARIABLE BIQUAD)




$$T(s) \triangleq \frac{V_o}{V_I} = k \frac{a_2 s^2 + a_1 s + a_0}{s^2 + b_2 s + b_0} \triangleq k \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

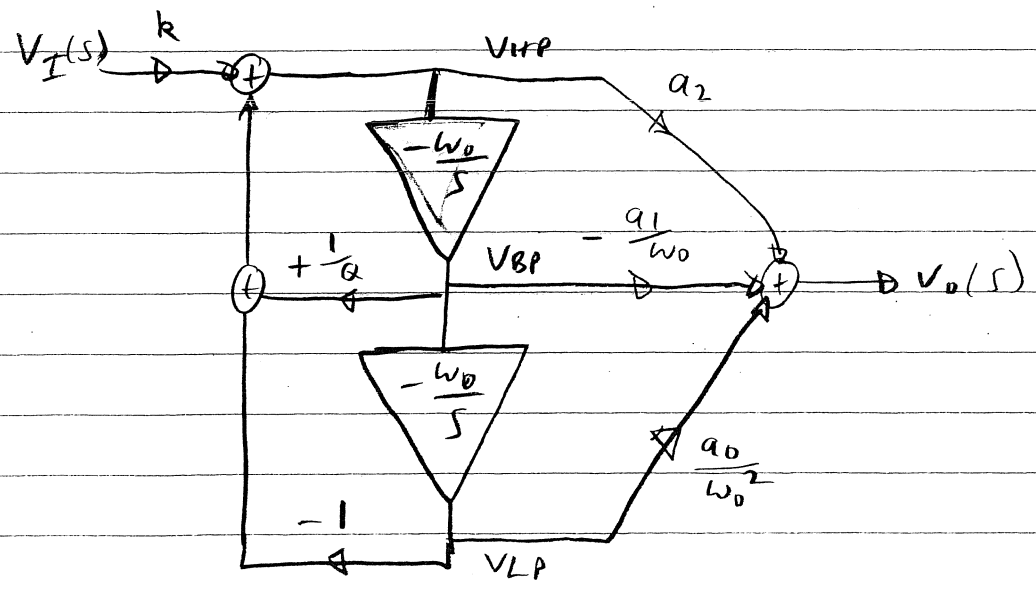AND USE NEGATIVE INTEGRATORS WITH  $\tau_c = \frac{1}{\omega_0}$  RESULTS IN





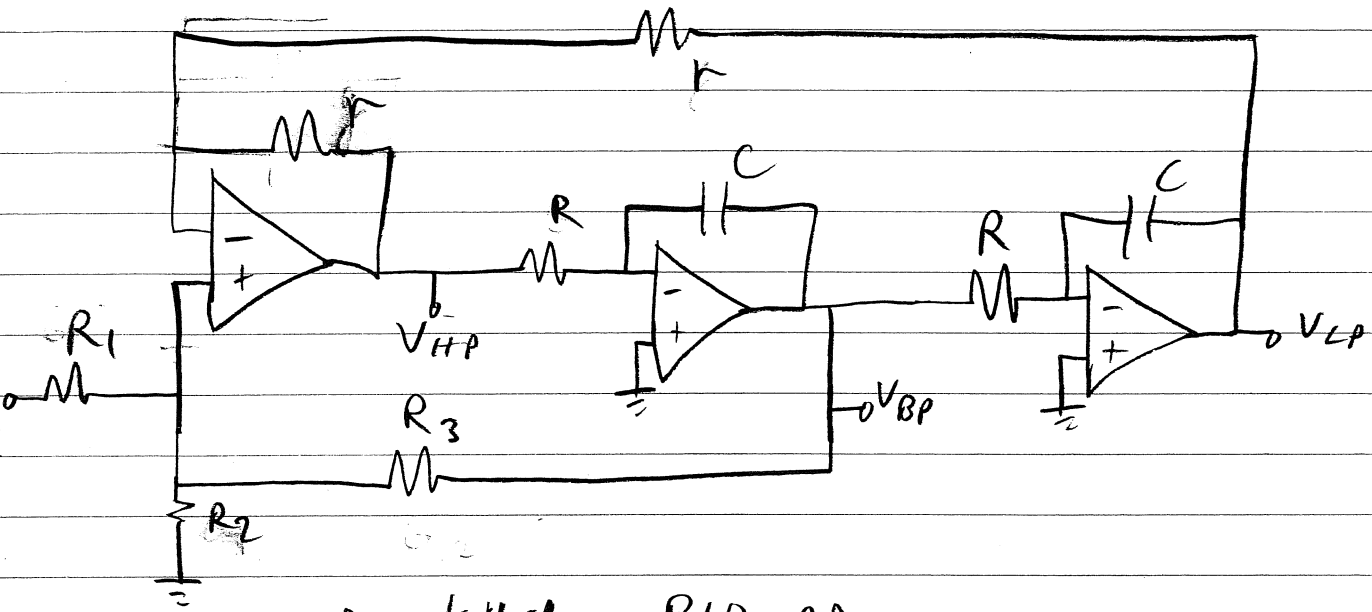WE CAN REALIZE THIS BLOCK DIAGRAM WITH THE FOLLOWING ACTIVE-RC CIRCUIT.



A KHN BIQUAD

IN ABOVE CIRCUIT,  $RC = \tau = \frac{1}{\omega_0}$

$$RC = \frac{1}{\omega_0}$$


USING SUPERPOSITION FOR SUMMER

$$V_{HP} = -V_{LP} + \underbrace{\left(1 + \frac{R}{r}\right)}_2 \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3}\right) V_{BP} + \underbrace{\left(1 + \frac{R}{r}\right)}_2 \left(\frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1}\right) V_i$$

$$\therefore \boxed{2 \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3} = \frac{1}{Q}} \quad \neq \quad \boxed{2 \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} = k}$$

2 EQUATIONS  $\Rightarrow$  3 unknowns  $\Rightarrow$  CAN CHOOSE SIZE OF RESISTORS.  
(ie 1k, 100k OR 1M)

THEN OUTPUT IS

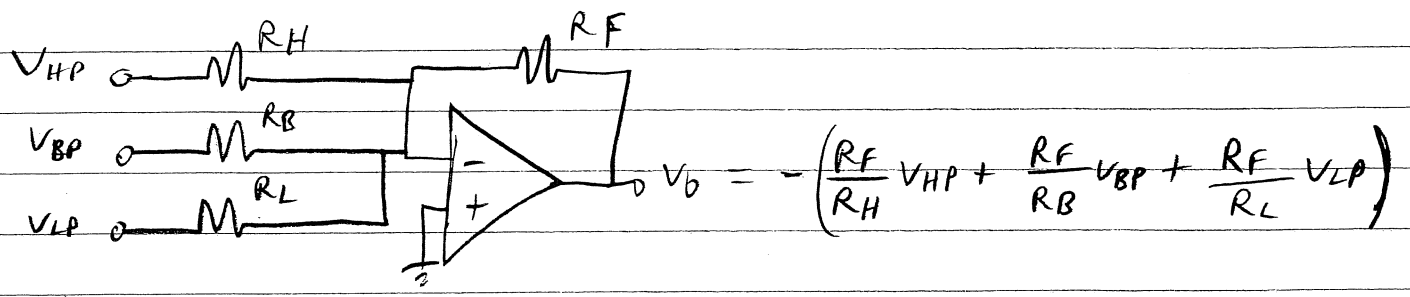

$$V_0 = - \left( \frac{R_F}{R_H} V_{HP} + \frac{R_F}{R_B} V_{BP} + \frac{R_F}{R_L} V_{LP} \right)$$

$\frac{R_F}{R_H} = a_2$      
  $\frac{R_F}{R_B} = -\frac{a_1}{\omega_0}$      
  $\frac{R_F}{R_L} = \frac{a_0}{\omega_0^2}$

AND



$$T(s) = -k \frac{a_2 s^2 + a_1 s + a_0}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$

IF  $R_H = R_E = R_F$  &  $R_B = R_F Q$  THEN AN ALL-PASS FUNCTION IS REALIZED.

$$T(s) = -k \frac{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2}$$


TOW-THOMAS BIQUAD

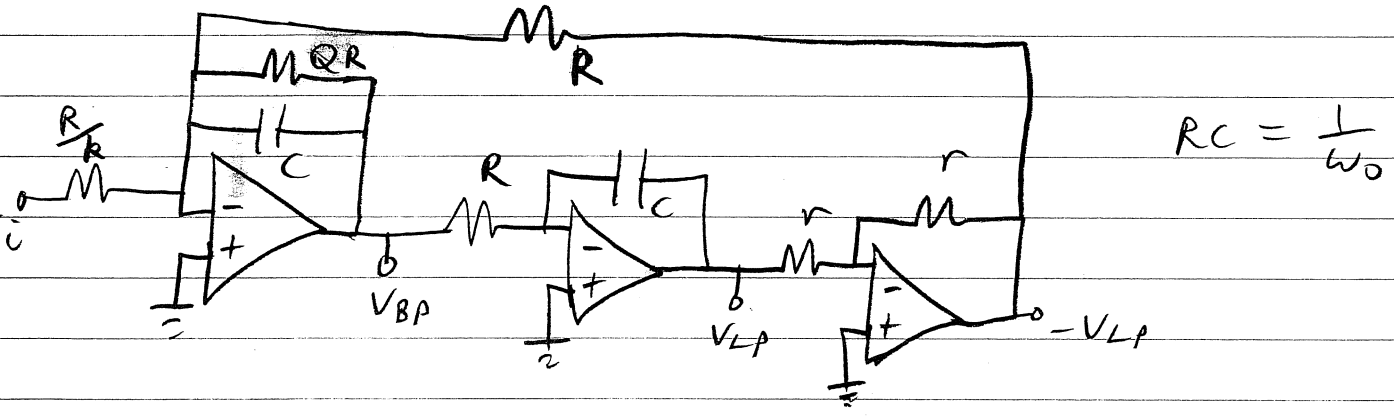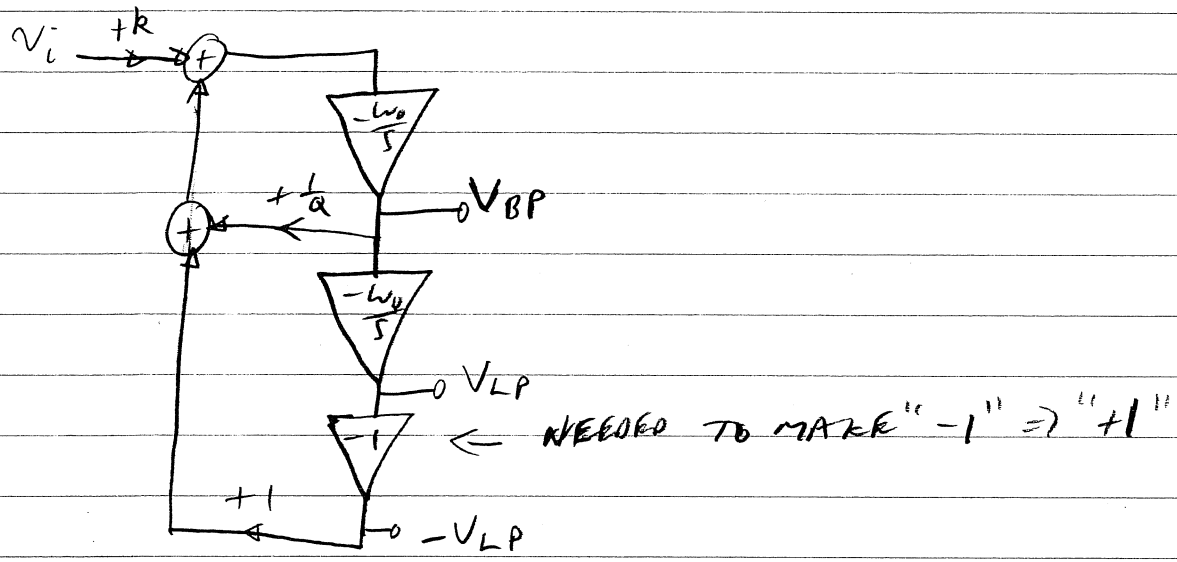ELIMINATE THE  $V_{HP}$  AS AN OP-AMP OUTPUT BY MAKING ALL COEFFICIENTS INTO IT '+ive'



FOR FINITE ZEROS  $\rightarrow$  CAN USE FEED-IN ELEMENTS.

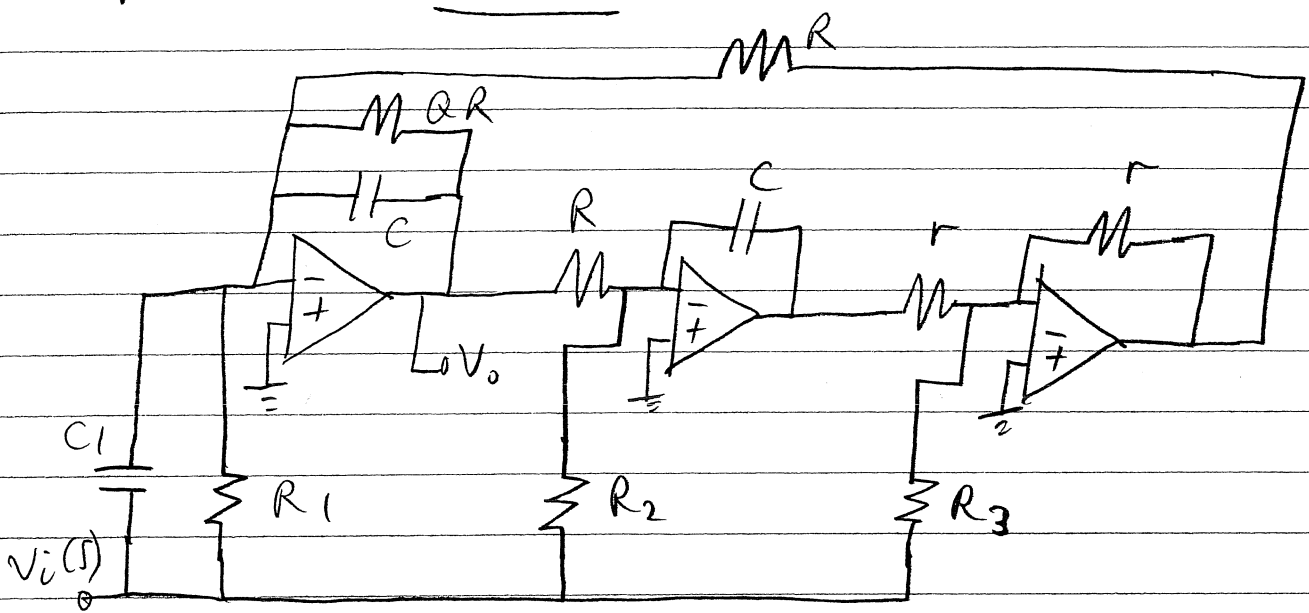TOW - THOMAS BIQUAD USING INPUT ELEMENTS TO REALIZE FINITE ZEROS



$$H(s) = \frac{V_o}{V_i} = \frac{s^2 \left(\frac{C_1}{C}\right) + s \left(\frac{1}{C}\right) \left(\frac{1}{R_1} - \frac{r}{RR_3}\right) + \frac{1}{RR_2 C^2}}{s^2 + \frac{1}{RC} s + \frac{1}{C^2 R^2}}$$

$$\omega_0 = \frac{1}{CR}$$

LOWPASS  $\Rightarrow C_1 = 0 \quad R_1 = R_3 \rightarrow \infty$

BANDPASS  $\Rightarrow C_1 = 0 \quad R_2 = R_3 \rightarrow \infty$  (NEG BP)


HIGH PASS  $\Rightarrow R_1 = R_2 = R_3 \rightarrow \infty$

LPN, HPN  $\Rightarrow R_1 = R_3 \rightarrow \infty \quad C_1 = \frac{C}{G} \quad R_2 = \frac{R \left(\frac{\omega_0}{\omega N}\right)^2}{G}$

"G" = HIGH FREQ GAIN

71A
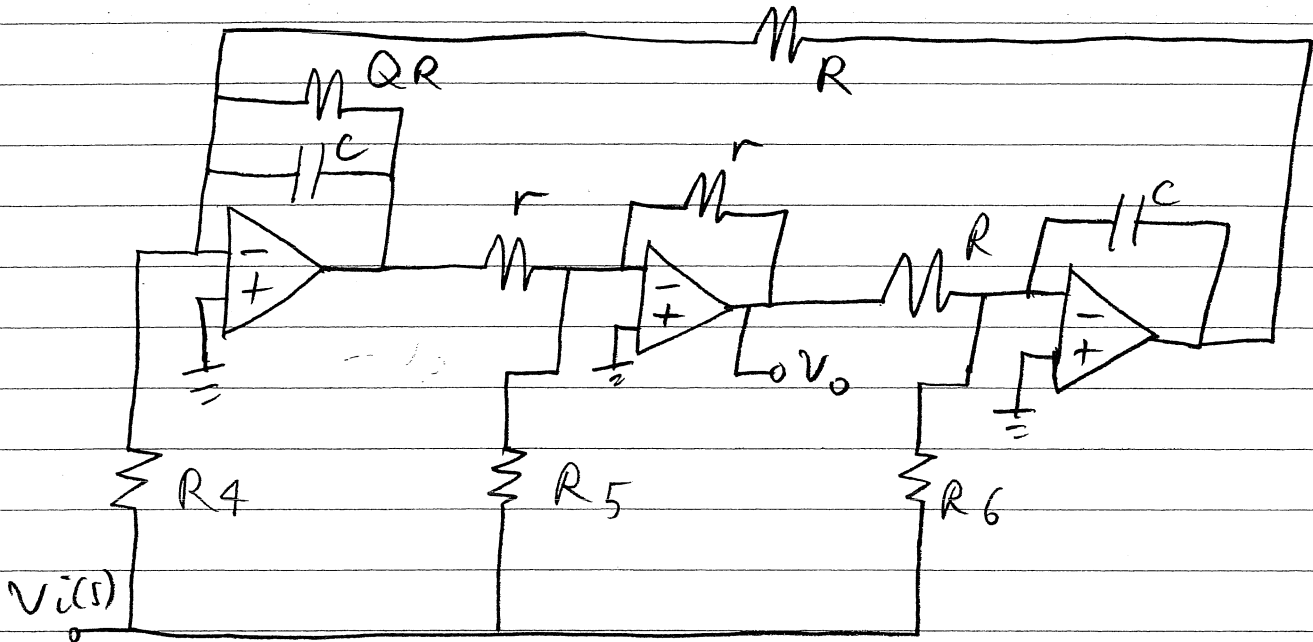
### ALTERNATE TOW-THOMAS WITH FINITE ZEROS



$$H(s) = - \frac{\left(\frac{r}{R_5}\right) s^2 + \frac{1}{RC} \left(\frac{r}{R_5} - \frac{QR}{R_4}\right) s + \frac{1}{QR_6 C^2}}{s^2 + \frac{1}{RC} s + \frac{1}{C^2 R^2}}$$

$$\omega_0 = \frac{1}{CR}$$

LOWPASS  $\Rightarrow R_4 = R_5 \rightarrow \infty$

BANDPASS  $\Rightarrow R_5 = R_6 \rightarrow \infty$

HIGH PASS  $\Rightarrow R_6 \rightarrow \infty \quad R_4 = \frac{QR}{G} \quad R_5 = \frac{r}{G}$

"G" HIGH PASS GAIN