

University of Toronto

Final Exam

Date - Dec. 15, 2009

Duration: 2.5 hrs

ECE512 — Analog Signal Processing

Lecturer - D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

1. Both programmable and non-programmable calculators allowed.
2. Equation sheet on last page of this test.
3. Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.

Last Name: SOLUTIONS

First Name: _____

Student #: _____

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

(max grade = 36)

[6] Question 1: Consider the following transfer-function, $H(s)$.

$$H(s) = \frac{2(s^2 + 9)}{s^4 + 1.3s^3 + s^2 + 0.75s + 1}$$

a) Determine the gain in dB at dc.

$$H(0) = \frac{2(9)}{1} = 18$$

$$H_{dB}(0) = 20 \log(18) = \underline{\underline{25.1 \text{ dB}}}$$

b) Calculate the rate of attenuation increase in dB per decade at high frequencies.

$$H(j\omega) \propto \frac{1}{s^2}$$

SO FALLS OFF AT 40 dB/DECADE

c) At which frequencies is the attenuation infinite?

ATTEN INFINITE WHERE $|H(j\omega)| = 0$
OCCURS AT $s^2 + 9 = 0$

$$(j\omega)^2 + 9 = 0 \Rightarrow -\omega^2 + 9 = 0$$

$$\omega = \underline{\underline{3 \text{ RAD/S}}}$$

AND AS $\omega \rightarrow \infty$

[6] Question 2:

a) For the following lowpass filter specifications:

$$f_p = 1 \text{ MHz} \quad \text{passband ripple} = 1 \text{ dB} \quad \leftarrow A_{\text{max}} = 1 \text{ dB}$$

$$f_s = 4 \text{ MHz} \quad \text{Min stopband atten} = 60 \text{ dB} \quad A_{\text{min}} = 60 \text{ dB}$$

Find the required filter order, N , to realize a Butterworth filter that meets this spec.

$$1 \text{ dB} = 20 \log \sqrt{1 + \epsilon^2} \Rightarrow \epsilon^2 = 0.2589$$

$$60 \leq 10 \log \left[1 + \epsilon^2 \left(\frac{4}{1} \right)^{2N} \right]$$

$$\epsilon^2 4^{2N} \geq (10^6 - 1) \approx 10^6 \Rightarrow 4^{2N} \geq \frac{10^6}{\epsilon^2} = 3.863e6$$

$$2N \log(4) \geq \log(3.863e6)$$

$$N \geq 5.47 \quad \text{so} \quad \underline{\underline{N = 6}}$$

b) Repeat part a) but assume a Chebyshev filter and find N .

$$\epsilon^2 = 0.2589$$

$$60 \leq 10 \log \left[1 + \epsilon^2 \cosh^2 \left(N \cosh^{-1} \left(\frac{\omega_s}{\omega_p} \right) \right) \right]$$

$$3.863e6 \leq \cosh^2 \left(N \cosh^{-1}(4) \right)$$

$$1.965e3 \leq \cosh \left(2.063 N \right)$$

$$2.063 N \geq 8.2766$$

$$N \geq 4.012 \quad \text{so} \quad \underline{\underline{N = 5}}$$

c) Show that for frequencies much greater than the passband frequency of lowpass filters, an N th-order Chebyshev filter has $6(N-1)$ dB more attenuation than an N th-order Butterworth filter.

$$C_0 = \cos(0) = 1$$

$$C_1 = \cos(\cos^{-1}(w)) = w$$

$$C_2 = 2wC_1 - C_0 = 2w^2 - 1$$

$$C_3 = 4w^3 - 3w$$

$$C_4 = 8w^4 - 8w^2 + 1$$

$$C_N = 2^{N-1} w^N + \dots$$

BUTTERWORTH FOR $w_p = 1 \gg 1$ $F(w^2) = \epsilon^2 w^{2N}$

FOR $w \gg 1$ $|H(jw)|_B^2 \approx \frac{1}{\epsilon^2 w^{2N}}$

CHEBYSHEV FOR $w_p = 1$ $F(w) = \epsilon^2 C_N^2(w)$

FOR $w \gg 1$ $|H(jw)|_C^2 \approx \frac{1}{\epsilon^2 2^{2(N-1)} w^{2N}}$

$$\frac{|H(jw)|_C^2}{|H(jw)|_B^2} = \frac{1}{2^{2(N-1)}}$$

$$10 \log \left[2^{2(N-1)} \right] = 20(N-1) \log(2)$$


$$= 6(N-1) \text{ dB}$$

MORE ATTENUATION

[6] Question 3:

(in μV_{RMS})

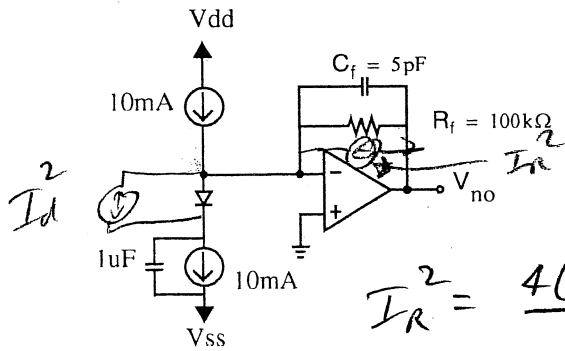a) Find the total output noise for the circuit shown below where the opamp and current sources are ideal and noiseless.



$$I_d^2 = 2qI_D \quad I_D = 10\text{mA}$$

$$I_R^2 = \frac{4kT}{R_f}$$

$$I_d^2 = (2)(1.6 \times 10^{-19})(10\text{mA}) = 3.2 \times 10^{-11} \quad [\text{A}^2/\text{Hz}]$$

$$I_R^2 = \frac{4(1.38 \times 10^{-23})(300)}{100 \times 10^3} = 1.66 \times 10^{-25} \quad [\text{A}^2/\text{Hz}]$$

$$V_{no}^2 = (I_d^2 + I_R^2) R_f^2 \left[\frac{\pi}{2} \right] \left[\frac{1}{2\pi R_f C_f} \right]$$

$$= (3.2 \times 10^{-11}) \left(\frac{1}{4(100 \times 10^3)(5 \times 10^{-12})} \right) = 1.6 \times 10^{-5}$$

$$V_{no} = \underline{\underline{4 \text{ mV}_{\text{RMS}}}}$$

v_1^2 v_2^2

b) Find the total output noise (in dBm) if 2 noise sources of sizes -60 dBm and -66 dBm are added together?

$$-60 \text{ dBm} = 10 \log \frac{v_1^2}{(50)(1 \times 10^{-3})} \Rightarrow v_1^2 = 5 \times 10^{-8}$$


$$-66 \text{ dBm} = 10 \log \frac{v_2^2}{(50)(1 \times 10^{-3})} \Rightarrow v_2^2 = 1.256 \times 10^{-8}$$

$$v_1^2 + v_2^2 = 6.256 \times 10^{-8}$$

$$10 \log \frac{6.256 \times 10^{-8}}{(50)(1 \times 10^{-3})} = \underline{\underline{-59.0 \text{ dBm}}}$$

[6] Question 4:

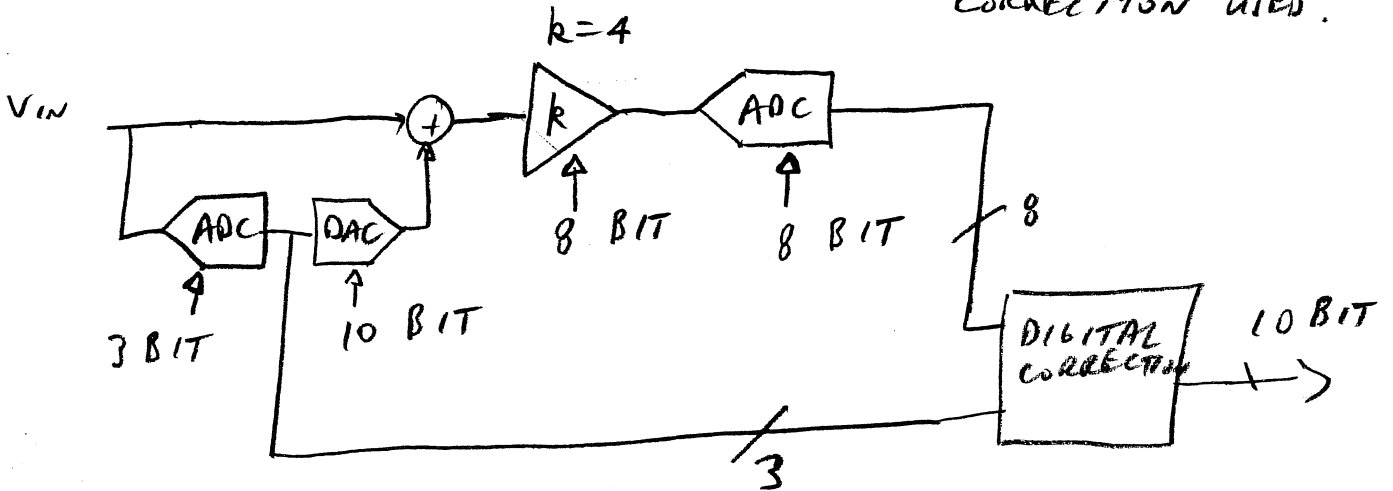a) Draw a block diagram for a 10-bit two-step A/D converter where the first stage determines 3 bits. Indicate the accuracy needed in all blocks. ASSUME DIGITAL ERROR CORRECTION USED.




b) Why is there a speed benefit in using an interpolating A/D converter over a flash A/D converter?

AN INTERPOLATING A/D HAS LESS INPUT CAPACITANCE ON INPUT SIGNAL SINCE FEWER PRE-AMPS ARE USED.

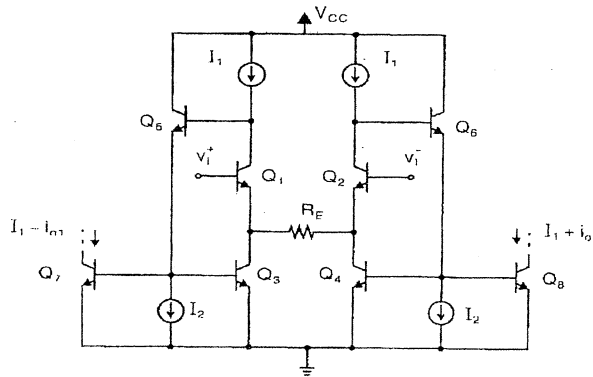c) Why is a thermometer code often used for the top portion of a D/A converter while the bottom portion of the D/A is a binary code?

TO REDUCE GLITCH ENERGY BY USING THERMOMETER PORTION. BINARY PORTION USED TO REDUCE COMPONENTS AND BINARY TO THERMOMETER DECODER SIZE

[6] **Question 5:** Consider the bipolar transconductor shown below where it is desired to have $G_m = 2 \text{ mA/V}$ and all transistors sizes are the same size except for Q_7 and Q_8 which are 4 times larger in BE area.



a) Find the value of R_E .

$$G_m = \frac{4}{R_E} \quad R_E = \frac{4}{2(\text{mA/V})} = \underline{\underline{2 \text{ k}\Omega}}$$

b) Find the value I_1 such that all transistors do not fall below 30 percent of their nominal bias current when the peak value of $v_i = v_i^+ - v_i^- = 500 \text{ mV}$.

$$I_{RE} = \frac{v_i}{R_E} = \frac{0.5}{2 \text{ k}} = 0.25 \text{ mA}$$

$$I_{C3_MIN} = I_1 - I_{RE} \quad I_{C3_NOMINAL} = I_1$$

$$\frac{I_{C3_MIN}}{I_{C3_NOMINAL}} = 0.7 \Rightarrow \frac{I_1 - 0.25 \text{ mA}}{I_1} = 0.7$$

$$0.3 I_1 = 0.25 \text{ mA} \Rightarrow \underline{\underline{I_1 = 0.833 \text{ mA}}}$$

[6] Question 6:

a) If a circuit is measured to have $IIP_3 = 5 \text{ dBm}$ and has a gain of 4 dB , what output-signal level should be used such that the third-order intermodulation products are 60 dB below the fundamental?

$$IIP_3 = 5 \text{ dBm} + \text{GAIN} = 4 \text{ dB} \quad OIP_3 = IIP_3 + \text{GAIN}$$

$$\Rightarrow OIP_3 = 9 \text{ dBm}$$

$$OIP_3 = I_{D1} - \frac{ID_3}{2}$$

$$9 \text{ dBm} = I_{D1} + \left(\frac{60}{2}\right)$$

$$\Rightarrow I_{D1} = 9 - 30 = \underline{\underline{-21 \text{ dBm}}}$$

b) If the noise of the circuit in a) is measured to be -60 dBm , what is the SFDR?

$$SFDR = \left(\frac{2}{3}\right)(OIP_3 - N_0)$$

$$= \left(\frac{2}{3}\right)(9 + 60) = \underline{\underline{46 \text{ dB}}}$$

(page intentionally left blank for rough work)

ECE512

Analog Signal Processing

Equation Sheet

Constants: $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$; $V_T = kT/q \approx 26 \text{ mV}$ at 300° K ;

General: $h(t)$ is impulse response of LTI system; $H(s)$ is the Laplace transform of $h(t)$

$$H(j\omega) = |H(j\omega)| e^{j\phi(\omega)}; T_d(\omega) = -\frac{d\phi(\omega)}{d\omega}; |H(j\omega)|_{\text{dB}} = 20 \log |H(j\omega)|; H(s) = \frac{a_m s^m + \dots + a_0}{s^N + b_{n-1} s + \dots + b_0}; |H(j\omega)|^2 = H(s)H(-s)|_{s=j\omega} = H(j\omega)H(-j\omega);$$

General Lowpass: $|H(j\omega)|^2 = A_0^2 / (1 + F(\omega^2))$;

Butterworth: $F(\omega^2) = \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}$; $A_{\text{max}} = 20 \log \sqrt{1 + \epsilon^2}$; $A_{\text{min}} \leq 10 \log \left[1 + \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}\right]$; Poles lie on circle of radius $\omega_p (1/\epsilon)^{1/N}$ spaced apart by π/N with first angle being $\pi/(2N)$

Chebyshev: (for $\omega_p = 1$); $F(\omega^2) = \epsilon^2 C_M^2(\omega)$; $C_M(\omega) = \cos(N \cos^{-1}(\omega))$ $|\omega| \leq 1$; $C_M(\omega) = \cosh(N \cosh^{-1}(\omega))$ $|\omega| \geq 1$;

$$C_{N+1}(\omega) = 2\omega C_N(\omega) - C_{N-1}(\omega); A_{\text{max}} = 20 \log \sqrt{1 + \epsilon^2}; A_{\text{min}} \leq 10 \log [1 + \epsilon^2 \cosh^2(N \cosh^{-1}(\omega_s/\omega_p))];$$

Second-order polynomial: $s^2 + (\omega_0/Q)s + \omega_0^2$; for $Q > 0.5$; poles complex at radius ω_0 and real part is $-\omega_0/(2Q)$;

Lowpass and highpass: peaking occurs if $Q > 1/\sqrt{2}$ and $\omega_{\text{max}} = \omega_0 \sqrt{1 - 1/2Q^2}$

Bandpass: for complex poles; peak occurs at ω_0 and has 3 dB bandwidth of ω_0/Q

LCR: $\omega_0 = 1/\sqrt{LC}$; $Q = \omega_0 CR$;

KHN Biquad: $RC = 1/\omega_0$; $2((R_1 || R_2)/(R_1 || R_2 + R_3)) = 1/Q$; $2((R_2 || R_3)/((R_2 || R_3) + R_1)) = k$;

Tow-Thomas Biquad: $RC = 1/\omega_0$; damping resistor is QR ; numerator is $-s^2 \left(\frac{C_1}{C}\right) - s \left(\frac{1}{C}\right) \left(\frac{1}{R_1} - \frac{r}{RR_2}\right) - \frac{1}{RR_2 C^2}$;

Noise: noise equivalent bandwidth = $(\pi/2)f_{3\text{dB}}$; $V_R^2(f) = 4kTR$; $I_d^2(f) = 2qI_D$; $r_d = (kT)/(qI_D)$; $V_C^2 = (kT)/C$;

Discrete-Time: $X_s(s) = \sum x_c(nT)e^{-snT}$; $X(z) = \sum x_c(nT)z^{-n}$; $p = (z-1)/(z+1)$; $z = (1+p)/(1-p)$; $\Omega = \tan(\omega/2)$;

Switched-Cap: $R_{\text{eq}} = T/C$; $Q_{\text{CH}} = -WLC_{\text{ox}}(V_{\text{GS}} - V_T)$;

Data Converters: $B_{\text{in}} = b_1 2^{-1} + \dots + b_N 2^{-N}$; $V_{\text{LSB}} = V_{\text{ref}}/2^N$; $V_{\text{out}} = V_{\text{ref}} B_{\text{in}}$; $V_{\text{ref}} B_{\text{out}} = V_{\text{in}} + V_Q$; $|V_Q| \leq 0.5 V_{\text{LSB}}$;

$$V_{Q(\text{rms})} = V_{\text{LSB}}/\sqrt{12}; \text{SNR} = 6.02N + 1.76; E_{\text{off(D/A)}} = V_{\text{out}}/V_{\text{LSB}}|_{0\dots 0}; E_{\text{off(A/D)}} = V_{0\dots 01}/V_{\text{LSB}} - 0.5 V_{\text{LSB}}; \Delta t < 1/(2^N \pi f_{\text{in}});$$

$$E_{\text{gain(D/A)}} = \left(V_{\text{out}}/V_{\text{LSB}}|_{1\dots 1} - V_{\text{out}}/V_{\text{LSB}}|_{0\dots 0} \right) - (2^N - 1); E_{\text{gain(A/D)}} = (V_{1\dots 1}/V_{\text{LSB}} - V_{0\dots 01}/V_{\text{LSB}}) - (2^N - 2);$$

Oversampling: $\text{OSR} = f_s/(2f_0)$; $\text{SNR}_0 = 6.02N + 1.76 + 10 \log(\text{OSR})$; $\text{SNR}_1 = 6.02N + 1.76 - 5.17 + 30 \log(\text{OSR})$;

$$\text{SNR}_2 = 6.02N + 1.76 - 12.9 + 50 \log(\text{OSR}); S_{\text{TF}}(z) = H(z)/(1 + H(z)); N_{\text{TF}}(z) = 1/(1 + H(z))$$

$$T_{\text{avg}}(z) = \frac{1}{M} \sum_{i=0}^{M-1} z^{-i} = \frac{1}{M} \left(\frac{1 - z^{-M}}{1 - z^{-1}} \right); T_{\text{avg}}(e^{j\omega}) = \frac{\text{sinc}(\omega M/2)}{\text{sinc}(\omega/2)}; |N_{\text{TF}}(e^{j\omega})| \leq 1.5 \text{ for 1-bit quantizer stability};$$

Bipolar transistors: $I_C = I_{\text{CS}} e^{V_{\text{BE}}/V_T}$; $g_m = I_C/V_T$; $r_e = \alpha/g_m = V_T/I_E$;

CMOS transistors: $K_n = 0.5 \mu_n C_{\text{ox}}(W/L)$; $I_D = 2K_n((V_{\text{GS}} - V_{\text{th}})V_{\text{DS}} - (V_{\text{DS}}^2/2))$; $r_{\text{ds}} = (2K_n(V_{\text{GS}} - V_{\text{th}}))^{-1}$;

$$I_D = K_n(V_{\text{GS}} - V_{\text{th}})^2; g_m = 2K_n(V_{\text{GS}} - V_{\text{th}}) = (2I_D)/(V_{\text{GS}} - V_{\text{th}}); r_s = 1/g_m;$$

Ideal Transconductor: $i_o = G_m v_i$; **Bipolar Diff Pair:** $I_{C2} = I_1/(1 + e^{v_i/V_T})$;

CMOS Pair: $K_{\text{eq}} = (K_n K_p)/(\sqrt{K_n} + \sqrt{K_p})^2$; $V_{\text{t-eq}} = V_{\text{tn}} - V_{\text{tp}}$;

Dynamic Range: (all in dB or dBm) $ID_3 = ID_3 - ID_1$; $\text{OIP}_3 = ID_1 - ID_3/2$; $\text{SFDR} = (2/3)(\text{OIP}_3 - N_o)$;

$$\text{THD} = 10 \log((V_{h2}^2 + V_{h3}^2 + \dots)/V_f^2);$$