

12.10

Numerator is given by

$$a_7 (s-0) (s^2 + (10^3)^2) (s^2 + (3 \times 10^3)^2) \times (s^2 + (6 \times 10^3)^2)$$

$$= a_7 s (s^2 + 10^6) (s^2 + 9 \times 10^6) (s^2 + 36 \times 10^6)$$


Degree of Numerator  $\triangleq M = 7$

Degree of Denominator  $\triangleq N$

Given that there is one zero at  $\infty$ :

$$N - M = 1 \Rightarrow \underline{N = 8}$$
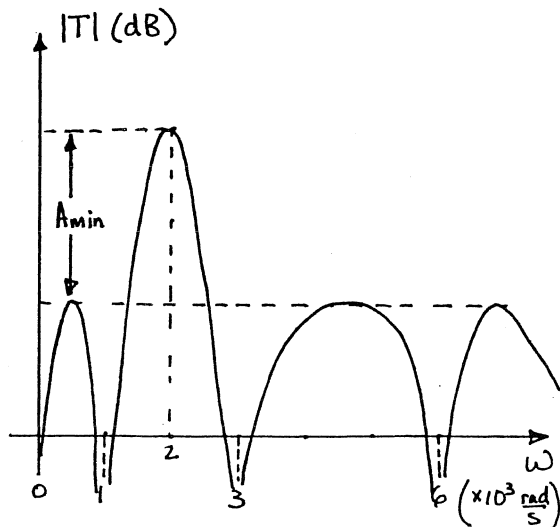
$$\therefore T(s) = \frac{a_7 s (s^2 + 10^6) (s^2 + 9 \times 10^6) (s^2 + 36 \times 10^6)}{s^8 + b_7 s^7 + b_6 s^6 + \dots + b_0}$$



The easiest way to solve the circuit is to use nodal analysis at nodes ①, ②, ③

At node ③  $\sum I = 0$

$$\frac{V_0}{1} + \frac{V_0}{1/s} + \frac{V_0 - V_1}{2s} = 0$$

$$\therefore V_1 = V_0 (2s^2 + 2s + 1) \quad \text{Eq. (a)}$$

At node ②  $\sum I = 0$

$$\frac{V_1 - V_i}{1} + \frac{V_1}{1/s} + \frac{V_1 - V_0}{2s} = 0$$

$$\therefore V_1 (2s^2 + 2s + 1) = V_0 + 2sV_i \quad \text{Eq. (b)}$$

(a)  $\rightarrow$  (b)

$$V_0 (2s^2 + 2s + 1)^2 = V_0 + 2sV_i$$

$$V_0 (4s^4 + s^3(4+4) + s^2(2+4+2) + s(2+2) + 1) = V_0 + 2sV_i$$

$$\frac{V_0(s)}{V_i(s)} \triangleq T(s) = \frac{2s}{4s^4 + 8s^3 + 8s^2 + 4s + 1}$$

$$T(s) = \frac{0.5}{s^3 + 2s^2 + 2s + 1}$$


Poles are given by:

$$s^3 + 2s^2 + 2s + 1 = 0$$

$$(s+1)(s^2 + s + 1) = 0$$

$$\therefore \text{Poles are } s = \underline{\underline{-1}} \text{ and } s = \underline{\underline{-\frac{1}{2} \pm j\sqrt{3}/2}}$$

12.11

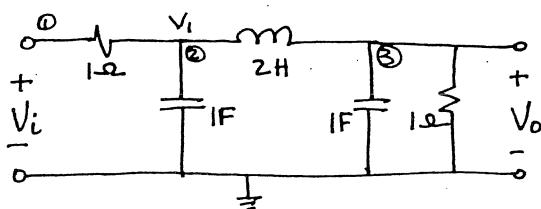

12.12

$$A_{\max} = 1 \text{ dB}, A_{\min} = 20 \text{ dB}, \omega_s/\omega_p = 1.3$$

Using:

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \quad \text{Eq. (12.15)}$$

$$= A_{\min}$$

CONT

$$\epsilon = [10^{A_{min}/10} - 1]^{1/2} = 0.5088$$

$$A_{min} = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]$$

$$10^{A_{min}/10} - 1 = \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N}$$

$$\log(10^{A_{min}/10} - 1) = \log \left( \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right)$$

$$N = \frac{\log \left[ (10^{A_{min}/10} - 1) / \epsilon^2 \right]}{2 \log(\omega_s / \omega_p)}$$

$$= 11.3 \Rightarrow \text{choose } \underline{N=12}$$

The actual value of stopband attenuation can be calculated using the integer value of  $N$ :

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]; N=12$$

$$= \underline{27.35 \text{ dB}} \quad \text{actual attenuation}$$

If the stopband specs are to be met exactly we need to find  $A_{max}$ .

Eq. 12.15 can be rearranged to give

$$\epsilon^2 = \frac{10^{A_{min}/10} - 1}{\left( \omega_s / \omega_p \right)^{2N}} \quad \begin{matrix} A_{min} = 20 \\ N = 12 \end{matrix}$$

$$= 0.1824$$

$$\therefore A_{max} = 10 \log(1 + \epsilon^2)$$

$$= \underline{0.73 \text{ dB}}$$

12.13

$$N=7, A_{max}=3 \text{ dB}$$

We want attenuation at

$$\omega = 1.6 \omega_p \quad \text{or} \quad \frac{\omega}{\omega_p} = 1.6$$

$$\epsilon = \sqrt{10^{A_{max}/10} - 1} = 0.998$$

$$A(\omega) = 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega}{\omega_p} \right)^{2N} \right]$$

$$= 10 \log \left[ 1 + 0.998^2 (1.6)^{14} \right]$$


$$= \underline{28.56 \text{ dB}}$$

12.14

$$\omega_p = 10^3 \text{ rad/s}, N=5$$

$$A_{max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

Find solution graphically

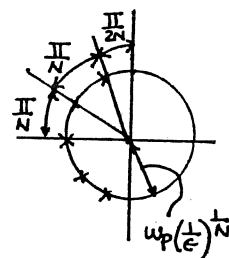

$$P_1 = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} \angle \left( \frac{\pi}{2} + \frac{\pi}{2N} \right)$$

$$= 873.59 \angle \left( \frac{6\pi}{10} \right)$$

$$= 873.59 \left[ \cos \left( \frac{6\pi}{10} \right) + j \sin \left( \frac{6\pi}{10} \right) \right]$$

$$= \underline{-269.96 + j 830.84}$$

$$P_2 = 873.59 \angle \left[ \frac{\pi}{2} + \frac{\pi}{2N} + \frac{\pi}{N} \right]$$

$$= \underline{-706.75 + j 513.49}$$

$$P_3 = 873.59 \angle \pi = \underline{-873.59}$$

12.15

$$f_p = 10 \text{ kHz} \quad \frac{\omega_s}{\omega_p} = 1.5 \quad A_{min} = 15 \text{ dB}$$

$$f_s = 15 \text{ kHz} \quad \omega_p \quad A_{max} = 2 \text{ dB}$$

$$\epsilon^2 = 10^{A_{max}/10} - 1 \Rightarrow \epsilon = 0.76478$$

CONT.

Manipulation Eq. (12.15) we get:

$$N = \frac{\log \left[ (10^{A_{\min}/10} - 1) / \epsilon^2 \right]}{2 \log (\omega_s / \omega_p)} = 4.88$$

$\therefore$  Use  $N = 5$

Finding natural modes graphically:-

$$\text{radius} = \omega_p \left( \frac{1}{\epsilon} \right)^{1/N} \triangleq \omega_0$$

$$\omega_0 = 6.629 \times 10^4$$

$$\begin{aligned} P_1 &= \omega_0 \angle (\pi/2 + \pi/2N) = \omega_0 \angle (6\pi/10) \\ &= \omega_0 \left( \cos\left(\frac{6\pi}{10}\right) \pm j \sin\left(\frac{6\pi}{10}\right) \right) \\ &= \underline{\omega_0 (-0.309 \pm j0.951)} \end{aligned}$$

$$\begin{aligned} P_2 &= \omega_0 \left( \cos\frac{8\pi}{10} \pm j \sin\frac{8\pi}{10} \right) \\ &= \underline{\omega_0 (-0.809 \pm j0.588)} \end{aligned}$$

$$P_3 = \omega_0 (\cos\pi \pm j \sin\pi) = \underline{-\omega_0}$$

Given a natural mode  $-\alpha \pm j\beta$ , the following term results

$$\begin{aligned} &(s + \alpha + j\beta)(s + \alpha - j\beta) \\ &= s^2 + 2\alpha s + \alpha^2 + \beta^2 \\ &= \underline{s^2 + 2\operatorname{Re}[P]s + |P|^2} \end{aligned}$$

Also, note that for a Butterworth, all natural modes have a magnitude of  $\omega_0$ .

$$P_1 \text{ yields: } s^2 + 0.618\omega_0 s + \omega_0^2$$

$$P_2 \text{ yields: } s^2 + 1.618\omega_0 s + \omega_0^2$$

$$P_3 \text{ yields: } s + \omega_0$$

$$\begin{aligned} \therefore T(s) &= \frac{k}{(s + \omega_0)(s^2 + 0.618\omega_0 s + \omega_0^2)} \\ &\times \frac{1}{s^2 + 1.618\omega_0 s + \omega_0^2} \end{aligned}$$

For unity dc gain


$$|T(j0)| = \frac{k}{\omega_0^5} = 1 \Rightarrow k = \omega_0^5$$

$$\begin{aligned} \therefore T(s) &= \frac{\omega_0^5}{(s + \omega_0)(s^2 + 0.618\omega_0 s + \omega_0^2)} \times \\ &\frac{1}{(s^2 + 1.618\omega_0 s + \omega_0^2)} \end{aligned}$$

for attenuation at 20 kHz use Eq. (12.15) with  $\frac{\omega_s}{\omega_p} = \frac{20}{10} = 2$

$$\begin{aligned} A(\omega_s) &= 10 \log \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right] \\ &= \underline{27.8 \text{ dB}} \end{aligned}$$

12.16

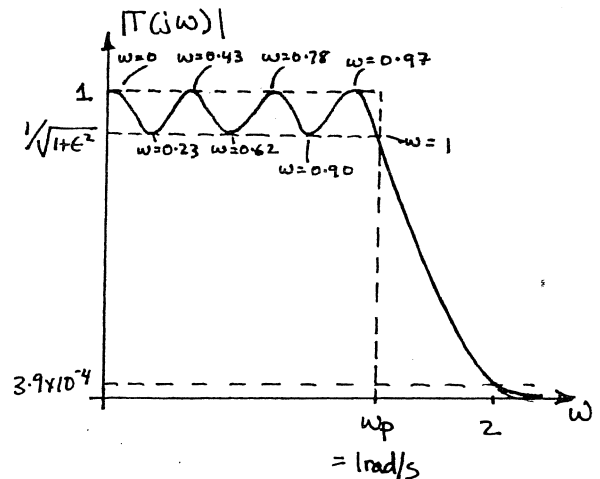

$$\text{Given } A_{\max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

CONT.

Using Eq 12.18

$$|T(j\omega)| = \left[ 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

for  $\omega \leq \omega_p$

If  $|T(j\omega)| = 1$

$$1 = 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \quad \omega_p = 1$$

$$N \cos^{-1} \left( \frac{\omega}{1} \right) = \cos^{-1}(0)$$

$$\cos^{-1}(\omega) = \frac{2i+1}{2N} \pi$$

$\omega$ 's repeat after this value

$$\therefore \omega_i = \cos \left[ \frac{2i+1}{2N} \pi \right] \quad i=0, 1, \dots, \frac{N-1}{2}$$

$\omega_0 = 0.9749$
$\omega_1 = 0.7818$
$\omega_2 = 0.4339$
$\omega_3 = 0$

$\omega$  values at which  $|T|=1$

note  $\omega_4 = -0.4339$   
 $= -\omega_2$

If  $|T| = 1/\sqrt{1+\epsilon^2}$ , then

$$1/\sqrt{1+\epsilon^2} = \left[ 1 + \epsilon^2 \cos^2 \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

$$1 = \cos \left( N \cos^{-1} \left( \frac{\omega}{\omega_p} \right) \right)$$

$$N \cos^{-1}(\omega) = \cos^{-1}(0) = i\pi \quad i=0, 1, 2, \dots$$

$$\omega_i = \cos \left[ \frac{i\pi}{N} \right] \quad i=0, 1, 2, \dots, \frac{N}{2}$$

$\omega_0 = 1.0$
$\omega_1 = 0.9010$
$\omega_2 = 0.6235$
$\omega_3 = 0.2252$

$\omega$  values at which

$$|T| = (1+\epsilon^2)^{-1/2}$$

Note  $\omega_4 = -0.2252$   
 $= -\omega_3$

To find  $|T(j2)|$  use Eq(12.19)  
 since  $\omega > \omega_p$

$$|T(j\omega)| = \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left( \frac{\omega}{\omega_p} \right) \right) \right]^{-1/2}$$

$$= \left[ 1 + 0.5088^2 \cosh^2 \left( 7 \cosh^{-1} 2 \right) \right]^{-1/2}$$

$$= \underline{\underline{3.898 \times 10^{-4} \text{ V/V}}}$$

$$|T|_{dB} = \underline{\underline{-68.2 \text{ dB}}}$$

For roll-off consider

$$T(s) = \frac{k}{s^2 + b_1 s + \dots + b_n}$$

for  $\omega \gg \omega_p \quad T(j\omega) \approx \frac{k}{\omega^2}$

$\therefore$  Roll-off is  $\frac{1}{2^2}$  or  $20 \log(1/2^2)$   
 per octave =  $\underline{\underline{-42 \text{ dB/octave}}}$

12.17


$$\omega_s/\omega_p = 2 \quad A_{max} = 1 \text{ dB} \Rightarrow \epsilon = \sqrt{10^{\frac{A_{max}}{10}} - 1} = 0.5088$$

$$|T_B| = \left[ 1 + \epsilon^2 \left( \frac{\omega_s}{\omega_p} \right)^{2N} \right]^{-1/2}$$

$$|T_C| = \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left[ \frac{\omega_s}{\omega_p} \right] \right) \right]^{-1/2}$$

$$|T_B| = 6.13 \times 10^{-2} \Rightarrow \underline{\underline{-24.3 \text{ dB}}}$$

$$|T_C| = 5.43 \times 10^{-3} \Rightarrow \underline{\underline{-45.3 \text{ dB}}}$$

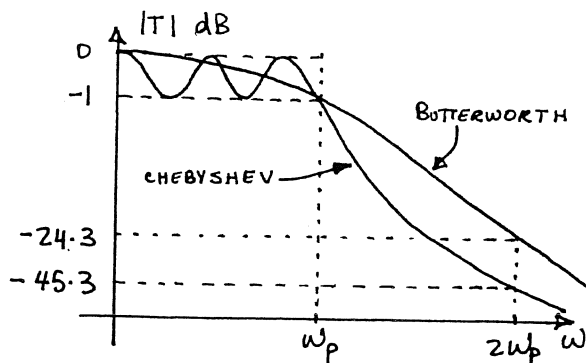



12.18

$$f_p = 3.4 \text{ kHz} \quad A_{\max} = 1 \text{ dB} \Rightarrow \epsilon = 0.5088$$

$$f_s = 4 \text{ kHz} \quad A_{\min} = 35 \text{ dB}$$

$$\omega_s/\omega_p = 1.176$$

Using Eq (12.22) :

$$A(\omega_s) = 10 \log \left[ 1 + \epsilon^2 \cosh^2 \left( N \cosh^{-1} \left( \frac{\omega_s}{\omega_p} \right) \right) \right]$$

§ trying different values for N

N	A(ω <sub>s</sub> )	} ∴ Use <u><u>N=10</u></u>
8	28.8 dB	
9	33.9 dB	
10	38.98 dB	

$$\text{Excess attenuation} = 39 - 35 = \underline{\underline{4 \text{ dB}}}$$

Poles are given by:

$$P_k = -\omega_p \sin \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \sinh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) + j \omega_p \cos \left( \frac{2k-1}{N} \cdot \frac{\pi}{2} \right) \cosh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right)$$

for k = 1, 2, ..., N.

Since  $\epsilon = 0.5088$  and  $N=10$

$$\sinh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) = 0.1433$$

$$\cosh \left( \frac{1}{N} \sinh^{-1} \left( \frac{1}{\epsilon} \right) \right) = 1.010$$

$$\begin{aligned} \therefore P_1 &= \omega_p \left[ -0.1433 \sin \left( \frac{\pi}{20} \right) + j 1.010 \cos \left( \frac{\pi}{20} \right) \right] \\ &= \omega_p (-0.0224 + j 0.9978) \end{aligned}$$

$$P_2 = \omega_p (-0.0650 + j 0.900)$$

$$P_3 = \omega_p (-0.1013 + j 0.7143)$$

$$P_4 = \omega_p (-0.1277 + j 0.4586)$$

$$P_5 = \omega_p (-0.1415 + j 0.1580)$$

Now it should be realized that the remaining poles are complex conjugates of the above.

Pole-pair  $P_1$  &  $P_1^*$  give a factor:

$$\begin{aligned} & s^2 + 2(0.0224)\omega_p s + \omega_p^2 (0.0224^2 + 0.9978^2) \\ &= \underline{\underline{s^2 + 0.0448\omega_p s + 1.023\omega_p^2}} \end{aligned}$$

i.e. this factor is from  $(s-P_1)(s-P_1^*)$

$$P_2 \text{ yields: } \underline{\underline{s^2 + 0.130\omega_p s + 0.902\omega_p^2}}$$

$$P_3 \text{ yields: } \underline{\underline{s^2 + 0.203\omega_p s + 0.721\omega_p^2}}$$

$$P_4 \text{ yields: } \underline{\underline{s^2 + 0.255\omega_p s + 0.476\omega_p^2}}$$

$$P_5 \text{ yields: } \underline{\underline{s^2 + 0.283\omega_p s + 0.212\omega_p^2}}$$

Now  $T(s)$  is given by

$$T(s) = \frac{k \omega_p^{10}}{\epsilon^2 (s-P_1)(s-P_1^*) \dots (s-P_5)(s-P_5^*)}$$


where the second order terms of the denominator are given above.

k is the dc gain

∴ we want the dc gain to be


$$k = \frac{1}{1+\epsilon^2} = \underline{\underline{0.8913}}$$
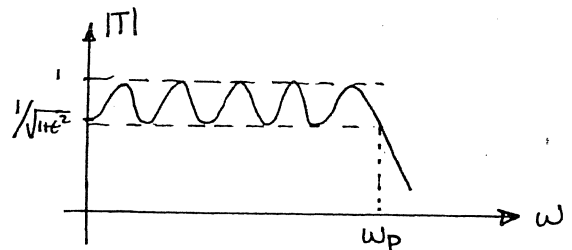
$$\omega_p = \underline{\underline{2\pi \times 3400}}$$



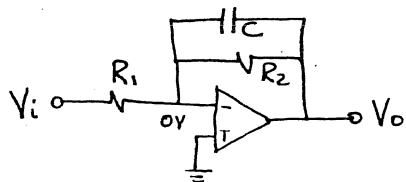12.19

$$f_0 = 10 \text{ kHz} \quad \text{DC gain} = 10 \quad R_{in} = 10 \text{ k}\Omega$$



$$R_{in} = R_1 = \underline{10 \text{ k}\Omega}$$

$$\text{DC gain} = -R_2/R_1 = -10$$

$$R_2 = 10R_1 = \underline{100 \text{ k}\Omega}$$


$$R_2 C = 1/\omega_0$$

$$C = \frac{1}{\omega_0 R_2} = \frac{1}{2\pi \cdot 10^4 \times 100 \times 10^3}$$

$$= \underline{0.159 \text{ nF}}$$

12.20

$$f_0 = 100 \text{ kHz} \quad R_i(\infty) = 100 \text{ k}\Omega \quad |T(\infty)| = 1$$

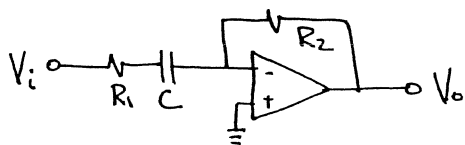

$$R_i(\infty) = R_1 = \underline{100 \text{ k}\Omega}$$

$$|T(\infty)| = R_2/R_1 = 1$$

$$R_2 = R_1 = \underline{100 \text{ k}\Omega}$$


$$C R_1 = 1/\omega_0$$

$$C = \frac{1}{\omega_0 R_1} = \frac{1}{2\pi \cdot 100 \times 10^3 \times 100 \times 10^3}$$

$$= \underline{15.9 \text{ nF}}$$

12.21

Use general first-order circuit:

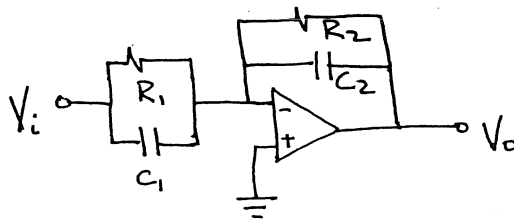

-Zero at 1 kHz ; Pole at 100 kHz  
 $-|T(0)| = 1$  ;  $R_i(0) = 1 \text{ k}\Omega$

$$\text{Thus: } R_i(\text{DC}) = \underline{R_1 = 1 \text{ k}\Omega}$$

$$T(\text{DC}) = -R_2/R_1 = -1$$

$$R_2 = R_1 = \underline{1 \text{ k}\Omega}$$

For a pole at 100 kHz

$$C_2 R_2 = \frac{1}{\omega_0} \Rightarrow C_2 = \frac{1}{2\pi f_0 R_2}$$

$$= \underline{1.59 \text{ nF}}$$

$$\text{For the circuit } T(s) = \frac{a_1 s + a_0}{s + \omega_0}$$

Thus the zero at  $-a_0/a_1 = -2\pi \cdot 10^3$ 


$$C_1 R_1 = a_1/a_0$$

$$C_1 = \frac{1}{2\pi \cdot 10^3 R_1}$$


$$= \underline{159 \text{ nF}}$$

$$\text{High freq gain} = -\frac{C_1}{C_2} = \underline{-100}$$

$$= \underline{40 \text{ dB}}$$

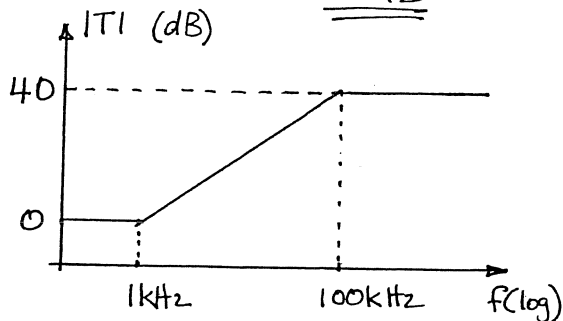

12.22

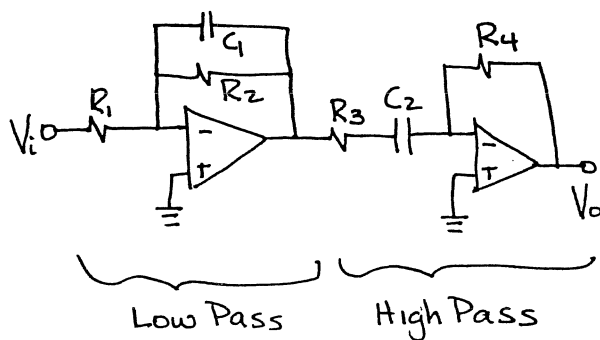

$$\text{gain} = 10^{12/20} = 3.98 \approx 4$$

want  $R_i = R_1$  large  
 $\therefore R_1 = \underline{100k\Omega}$

$$\text{Total gain} = A_{LP} A_{HP} = 4$$

$$A_{LP} = -R_2/R_1 \Rightarrow R_2 = -A_{LP} R_1 \text{ and } R_2 \leq 100k\Omega$$

$$\therefore \text{make } A_{LP} = -1 \quad A_{HP} = -4$$

$$R_2 = \underline{100k\Omega}$$

$$R_2 C_1 = \frac{1}{\omega_{0,LP}}$$

$$C_1 = \frac{1}{2\pi f_{0,LP} R_2} = \frac{1}{2\pi (10 \times 10^3) 100 \times 10^3}$$

$$= \underline{0.159nF}$$

$$A_{HP} = -R_4/R_3 = -4 \quad \left. \begin{array}{l} \text{make } R_4 = 100k\Omega \\ R_4 = 4R_3 \end{array} \right\} R_3 = \underline{25k\Omega}$$


$$\text{Now } R_3 C_2 = 1/\omega_{0,HP}$$

$$C_2 = \frac{1}{2\pi f_{0,HP} R_3}$$

$$= \frac{1}{2\pi (100 \times 10^3) 25 \times 10^3}$$

$$= \underline{63.7nF}$$

12.23

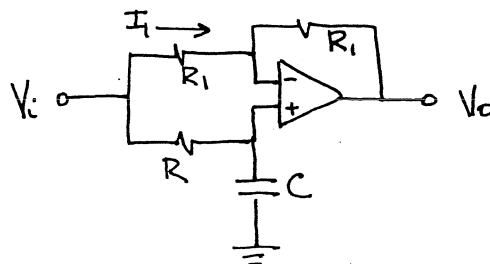

At +ve terminal

$$V_+ = \frac{V_{sc}}{1/s\tau + R_1} V_i$$

$$= \frac{1}{1+s\tau} V_i \quad \tau = RC$$

$V_- = V_+$  due to virtual short between terminals.

$$\therefore I_1 = \left( V_i - \frac{1}{1+s\tau} V_i \right) \frac{1}{R_1}$$

$$V_o = V_- - I_1 R_1$$

$$= \frac{V_i}{1+s\tau} - \left( V_i - \frac{V_i}{1+s\tau} \right) \frac{R_1}{R_1}$$

$$\frac{V_o}{V_i} = \frac{1 - (1+s\tau) + 1}{1+s\tau} = \frac{1-s\tau}{1+s\tau}$$

$$= \frac{\omega_0 - s}{\omega_0 + s} \quad \omega_0 = \frac{1}{\tau}$$

$$= -\frac{s - \omega_0}{s + \omega_0} = T(s)$$

$$T(s) = -\frac{j\omega - \omega_0}{j\omega + \omega_0}$$

$$\phi(\omega) = 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$= 360^\circ - 2\tan^{-1}\left(\frac{\omega}{\omega_0}\right) \quad \begin{array}{l} 0^\circ \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) \\ = 180^\circ - \tan^{-1}\left(\frac{\omega}{\omega_0}\right) \end{array}$$

$$= -2\tan^{-1}(\omega/\omega_0)$$

Now this equation can be rearranged:

$$\frac{\omega}{\omega_0} = \tan(-\phi/2) \Leftrightarrow \omega_0 = \frac{1}{2} = \frac{1}{RC}$$

$$RC\omega = \tan(-\phi/2)$$


CONT.

$$\therefore R = \frac{\tan(-\phi/2)}{C\omega} = 10^4 \tan(-\phi/2)$$

$$\phi = -30^\circ, -60^\circ, -90^\circ, -120^\circ, -150^\circ$$

$$R = 2.68k\Omega, 5.77k\Omega, 10k\Omega, 17.32k\Omega, 37.32k\Omega$$

12.24

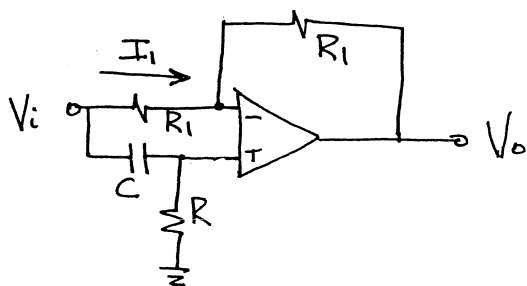

$$V_+ = \frac{R}{R + 1/sC} V_i = \frac{s}{s + \omega_0} V_i$$

$$\text{where } \omega_0 = \frac{1}{RC}$$

$$I_1 = \frac{V_i - (s/s + \omega_0)V_i}{R_1}$$

$$V_o = \frac{s}{s + \omega_0} V_i - I_1 R_1$$

$$= \frac{s}{s + \omega_0} V_i - V_i \left(1 - \frac{s}{s + \omega_0}\right)$$

$$\frac{V_o}{V_i} = \frac{2s - s - \omega_0}{s + \omega_0} = \frac{s - \omega_0}{s + \omega_0}$$

Now:

$$\phi(\omega) = \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$= 180 - \tan^{-1}\left(\frac{\omega}{\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$= 180 - 2 \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\text{Clearly } \phi(0) = 180^\circ \text{ \& } \phi(\omega \rightarrow \infty) = 0^\circ$$

12.25

$$\text{Low Pass } \omega_0 = 10^3 \text{ rad/s}$$

$$Q = 1$$

$$\text{DC gain} = 1$$

$$T(s) = \frac{a_0}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$T(0) = a_0/\omega_0^2 = 1$$

$$a_0 = \omega_0^2 = 10^6$$

$$\therefore T(s) = \frac{10^6}{s^2 + 10^3 s + 10^6}$$

$$\omega_{\max} = \omega_0 \sqrt{1 - 1/2Q^2}$$

$$= \frac{\omega_0}{\sqrt{2}}$$

$$= 0.707 \text{ rad/s}$$

$$|T_{\max}| = \frac{|a_0| Q}{\omega_0^2 \sqrt{1 - 1/4Q^2}} \Leftarrow a_0 = \omega_0^2$$

$$= \frac{1 \omega_0^2}{\omega_0^2 \sqrt{3/4}}$$

$$= 2/\sqrt{3}$$

$$= 1.15 \text{ V/V}$$

$$= 1.21 \text{ dB}$$

12.26


$$\omega_p = 1 \text{ rad/s}$$

$$A_{\max} = 3 \text{ dB}$$

There are many Q-values which may be used

$$Q \leq 1/\sqrt{2} - \text{no peaking}$$

$$Q > 1/\sqrt{2} - \text{peaking}$$

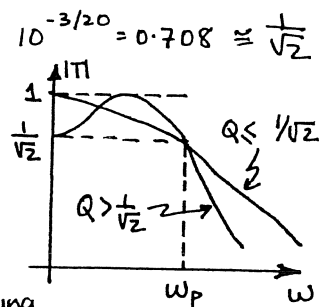

CONT.

Solution 1  $Q \leq 1/\sqrt{2}$

For  $Q = 1/\sqrt{2}$  the response is maximally flat. Because this is desirable, use:  $Q = \frac{1}{\sqrt{2}}$

$$T(s) = \frac{a_0}{s^2 + s\omega_0/\sqrt{2} + \omega_0^2}$$

$$|T(0)| = \frac{a_0}{\omega_0^2} = 1$$

$$\underline{a_0 = \omega_0^2}$$

$$|T(j1)|^2 = \frac{\omega_0^2}{(\omega_0^2 - 1)^2 + 2\omega_0^2} = \left(\frac{1}{\sqrt{2}}\right)^2$$

$$\omega_0 = 1 \text{ rad/s}$$

$$\therefore \underline{T_1(s) = \frac{1}{s^2 + \sqrt{2}s + 1}}$$

Solution 2  $Q > 1/\sqrt{2}$

From the figure:  $|T(0)| = 1/\sqrt{2} = \frac{a_0}{\omega_0^2}$

$$\therefore \underline{a_0 = \omega_0^2/\sqrt{2}}$$

$$\text{Now } |T|_{\max} = \frac{|a_0|Q}{\omega_0^2 \sqrt{1 - 1/4Q^2}} = 1$$

$$\frac{Q}{\sqrt{2} \sqrt{1 - 1/4Q^2}} = 1$$

$$Q = \sqrt{2} \sqrt{1 - 1/4Q^2}$$

$$\therefore Q^2 = 2(1 - \frac{1}{4Q^2})$$

$$= 2 - \frac{1}{2Q^2}$$

$$Q^4 - 2Q^2 + \frac{1}{2} = 0$$

Solving for  $Q^2$  gives:-

$$Q^2 = 1 \pm \sqrt{2}$$

ASIDE:

$$\therefore Q > 1/\sqrt{2}$$

$$Q^2 > 1/2$$

$$4Q^2 > 2$$

$$\frac{1}{4Q^2} < \frac{1}{2}$$

$$\therefore 1 - \frac{1}{4Q^2} > 1/2$$

$$\therefore \left|1 - \frac{1}{4Q^2}\right| = 1 - \frac{1}{4Q^2}$$

$$\Rightarrow Q = 0.5412 \text{ or } 1.3066$$

$$\therefore Q > \frac{1}{\sqrt{2}} \text{ use } \underline{Q = 1.3066}$$

Now at the passband edge

$$|T(j1)| = 1/\sqrt{2}$$

$$|T(j1)|^2 = \frac{(\omega_0^2/\sqrt{2})^2}{(\omega_0^2 - 1)^2 + \frac{\omega_0^2}{Q^2}} = \frac{1}{2}$$

$$\frac{\omega_0^4}{2} = \frac{1}{2} \left[ \omega_0^4 - 2\omega_0^2 + 1 + \frac{\omega_0^2}{Q^2} \right]$$

$$\omega_0^2(2 - 1/Q^2) = 1$$

$$\underline{\omega_0 = 0.841}$$

$$\therefore T_2(s) = \frac{\omega_0^2/\sqrt{2}}{s^2 + \omega_0/Qs + \omega_0^2}$$

$$= \frac{0.5}{s^2 + 0.644s + 0.707}$$

If  $\omega_s = 2$


$$|T_1(j2)| = 0.242 \quad |T_2(j2)| = 0.1414$$

$$\therefore \underline{A_{\min,1} = -12.3\text{dB}} \quad \underline{A_{\min,2} = -17\text{dB}}$$

12.27

$V_2$  lags  $V_1$  by  $120^\circ$

$V_3$  lags  $V_2$  by  $120^\circ$

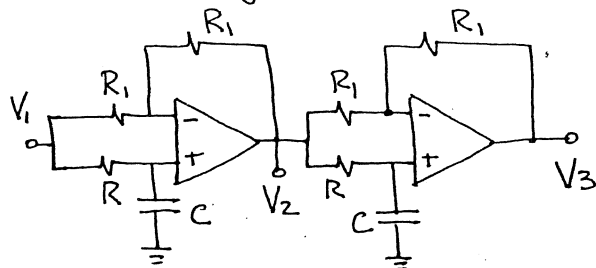

$$\omega = 2\pi 60 \text{ Hz} \quad C = 1 \mu\text{F}$$

$$T(s) = \frac{s - \omega_0}{s + \omega_0} \quad \omega_0 = \frac{1}{RC}$$

CONT.

$$\phi(\omega) = 180^\circ + \tan^{-1}\left(\frac{\omega}{-\omega_0}\right) - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\text{Sub: } \tan\left(\frac{\omega}{-\omega_0}\right) = 180 - \tan^{-1}\left(\frac{\omega}{\omega_0}\right)$$

$$\Rightarrow \phi(\omega) = -2 \tan^{-1}(\omega/\omega_0)$$

$$\text{Now } \phi = -120^\circ \text{ at } \omega = 2\pi 60$$

$$-120 = -2 \tan^{-1}(\omega R C)$$


$$-60 = -\tan^{-1}(2\pi 60 \times R \times 10^{-6})$$

$$\underline{R = 4.59 \text{ k}\Omega}$$

$R_1$  can be arbitrarily chosen

$$\text{use } \underline{R_1 = 10 \text{ k}\Omega}$$

12.28

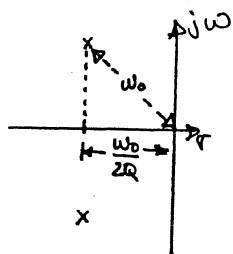

Natural Modes:

$$-\frac{1}{2} \pm j \frac{\sqrt{3}}{2}$$

$$\omega_0 = \sqrt{\left(\frac{1}{2}\right)^2 + \left(\frac{\sqrt{3}}{2}\right)^2}$$

$$= \underline{1.0}$$

$$\frac{\omega_0}{2Q} = \frac{1}{2} \Rightarrow \frac{\omega_0}{Q} = 1$$

$$T(s) = \frac{a_2 s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2} = \frac{a_2 s^2}{s^2 + s + 1}$$

$$|T(j\infty)| = a_2 = 1$$

$$\therefore T(s) = \underline{\underline{\frac{s^2}{s^2 + s + 1}}}$$

12.29

For a 2nd-order bandpass

$$T(s) = \frac{a_1 s}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$T(j\omega) = \frac{j \omega a_1}{(\omega_0^2 - \omega^2) + j \frac{\omega \omega_0}{Q}}$$

$$|T(j\omega)| = \frac{a_1 \omega}{\left[ (\omega_0^2 - \omega^2)^2 + \frac{\omega^2 \omega_0^2}{Q^2} \right]^{1/2}}$$

Part (a):

$$|T(j\omega_1)| = |T(j\omega_2)|$$

$$\frac{a_1 \omega_1}{\sqrt{(\omega_0^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_0}{Q}\right)^2}} = \frac{a_1 \omega_2}{\sqrt{(\omega_0^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_0}{Q}\right)^2}}$$

$$\omega_1^2 \left[ (\omega_0^2 - \omega_2^2)^2 + \left(\frac{\omega_2 \omega_0}{Q}\right)^2 \right] = \omega_2^2 \left[ (\omega_0^2 - \omega_1^2)^2 + \left(\frac{\omega_1 \omega_0}{Q}\right)^2 \right]$$

$$\omega_1^2 (\omega_0^4 - 2\omega_0^2 \omega_2^2 + \omega_2^4) =$$

$$\omega_2^2 (\omega_0^4 - 2\omega_0^2 \omega_1^2 + \omega_1^4)$$

$$\omega_1^2 \omega_0^4 + \omega_1^2 \omega_2^4 = \omega_2^2 \omega_0^4 + \omega_2^2 \omega_1^4$$

$$\omega_0^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^4 - \omega_1^2 \omega_2^4$$

$$\omega_0^4 (\omega_1^2 - \omega_2^2) = \omega_2^2 \omega_1^2 (\omega_1^2 - \omega_2^2)$$

$$\omega_0^4 = \omega_1^2 \omega_2^2$$

$$\underline{\underline{\omega_0^2 = \omega_1 \omega_2 \text{ Q.E.D.}}}$$

CONT.

For Fig. 12.4:  $\omega_{p1} = 8100 \text{ rad/s}$   
 $\omega_{p2} = 10000 \text{ rad/s}$   
 $A_{\max} = 1 \text{ dB}$

$$\omega_0^2 = (8100)(10000)$$

$$\omega_0 = \underline{9000 \text{ rad/s}}$$

$$|T(j\omega_{p1})| = |T(j\omega_{p2})| = 10^{-1/20} = \underline{0.8913}$$

$$|T(j\omega_0)| = \frac{\omega_0 a_1}{\sqrt{(\omega_0^2 - \omega_0^2)^2 + \left(\frac{\omega_0^2}{Q}\right)^2}} = 1$$

$$\Rightarrow \frac{\omega_0 a_1}{\omega_0^2 / Q} = 1$$

$$\therefore \frac{Q a_1}{\omega_0} = 1 \Rightarrow a_1 = \frac{\omega_0}{Q}$$

$$|T(j\omega_{p1})|^2 = |T(j0.9\omega_0)|^2 = 0.8913^2$$

$$\frac{(\omega_0/Q)^2 (0.9\omega_0)^2}{(\omega_0^2 - (0.9\omega_0)^2)^2 + \left(\frac{0.9\omega_0}{Q}\right)^2} = 0.8913^2$$

$$\left(\frac{\omega_0}{Q} (0.9\omega_0)\right)^2 = 0.8913^2 \left[ (\omega_0^2 - (0.9\omega_0)^2)^2 + \left(\frac{0.9\omega_0}{Q}\right)^2 \right]$$

$$\frac{0.81\omega_0^4}{Q^2} = 0.8913^2 \left[ \omega_0^4 (1 - 0.81)^2 + \frac{0.81\omega_0^4}{Q^2} \right]$$

$$\frac{0.81\omega_0^4}{Q^2} (1 - 0.8913^2) = 0.8913^2 \omega_0^4 \times (1 - 0.81)^2$$

SUB  $\omega_0 = 9000$  gives

$$\underline{Q = 2.41}$$

$$\text{Now } a_1 = \frac{\omega_0}{Q} = 0.415 \omega_0$$

$$\therefore T(s) = \frac{0.415 \omega_0 s}{s^2 + 0.415 \omega_0 s + \omega_0^2}$$

$$\text{If } \omega_{s1} = 3000 \text{ rad/s}$$

$$|T(j3000)| = \frac{0.415 \omega_0 (3000)}{\sqrt{(\omega_0^2 - 3000^2)^2 + (\omega_0 3000 \times 0.415)^2}} = 0.1537$$

$$\therefore A_{\min} = -20 \log(0.1537) = \underline{16.3 \text{ dB}}$$

Now  $\omega_{s1}$  and  $\omega_{s2}$  are geometrically symmetrical about  $\omega_0$ :

$$\omega_{s1} \omega_{s2} = \omega_0^2$$

$$\omega_{s2} = \frac{9000^2}{3000}$$

$$= \underline{27000 \text{ rad/s}}$$

12.30

From exercise 12.15

$$Q = \frac{\omega_0}{BW \sqrt{10^{A/10} - 1}} \quad \begin{cases} \omega_0 = 2\pi(60) \\ BW = 2\pi(6) \\ A = 20 \text{ dB} \end{cases}$$

$$= \underline{1.005}$$

$$T(s) = a_2 \frac{s^2 + \omega_0^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$|T(0)| = \frac{a_2 \omega_0^2}{\omega_0^2} = 1 \leftarrow \text{DC Gain}$$

CONT.