

$$\underline{a_2 = 1}$$

$$T(s) = \frac{s^2 + (2\pi 60)^2}{s^2 + s \frac{2\pi 60}{1.005} + (2\pi 60)^2}$$

$$\underline{T(s) = \frac{s + 1.421 \times 10^5}{s^2 + 375.1s + 1.421 \times 10^5}}$$

12.31


FOR ALL PASS:

$$T(s) = a_2 \frac{s^2 - s \omega_0/Q + \omega_0^2}{s^2 + s \omega_0/Q + \omega_0^2}$$

If zero frequency < pole frequency


$$T(s) = a_2 \frac{s^2 - s \omega_n/Q + \omega_n^2}{s^2 + s \omega_0/Q + \omega_0^2} \quad \omega_n < \omega_0$$

At DC: $|T| = a_2 \frac{\omega_n^2}{\omega_0^2}$ where $\frac{\omega_n^2}{\omega_0^2} < 1$

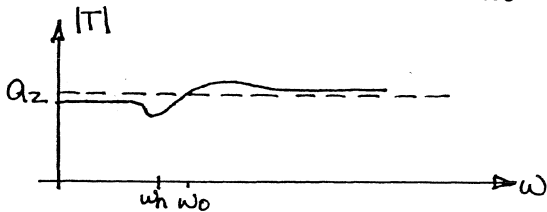

If zero frequency > pole frequency then $\omega_n > \omega_0$

At DC: $|T| = a_2 \omega_n^2 / \omega_0^2$ where $\frac{\omega_n^2}{\omega_0^2} > 1$

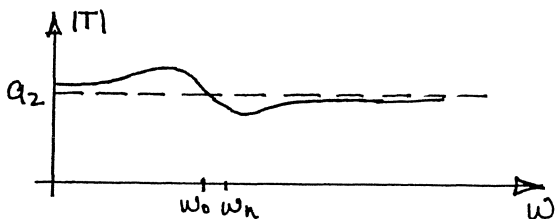

12.32

$$T(s) = \frac{s^2 - s \omega_0/Q' + \omega_0^2}{s^2 + s \omega_0/Q_0 + \omega_0^2} a_2$$


$$\text{Zero } Q < \text{ Pole } Q \Rightarrow Q' < Q_0$$

At $\omega = \omega_0$:

$$|T| = \frac{a_2 \omega_0^2 / Q'}{\omega_0^2 / Q_0} = a_2 \frac{Q_0}{Q'} > a_2$$

If $Q' > Q_0$

$$|T(j\omega_0)| = a_2 \frac{Q_0}{Q'} < a_2$$

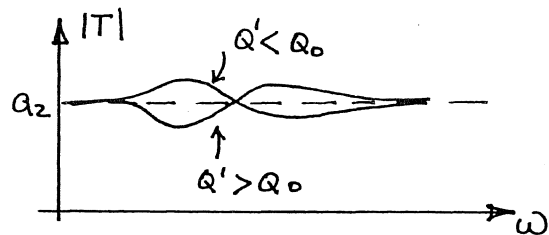

12.33

$$\omega_0 = 10^4 \text{ rad/s}, \quad Q = 2, \quad R = 10 \text{ k}\Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow \omega_0^2 = \frac{1}{LC} \Leftrightarrow L = \frac{R^2 C}{Q^2} = \frac{Q^2}{R^2 C^2}$$

$$C = \frac{Q}{R \omega_0} = \underline{\underline{20 \text{ nF}}}$$

$$L = \frac{1}{C \omega_0^2} = \underline{\underline{500 \text{ mH}}}$$

12.34

$$\omega_0 = \sqrt{LC}$$

If $L' = 1.01L$

$$\omega_0' = (1.01LC)^{-1/2}$$

$$= 0.9950 \frac{1}{\sqrt{LC}}$$

$$= 0.9950 \omega_0$$

$$\therefore \underline{\underline{\Delta\omega_0 = -0.5\%}}$$


If $C' = 1.01C$

$$\omega_0' = 0.9950 \omega_0$$

$$\underline{\underline{\Delta\omega_0' = -0.5\%}}$$

Changing R has no effect on ω_0

12.35

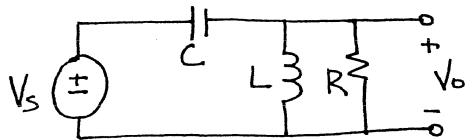

Use voltage divider rule:

$$V_o = \frac{Z_{RL}}{Z_{RL} + Z_C} V_s$$

$$\frac{V_o}{V_s} = \frac{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1}}{\left(\frac{1}{R} + \frac{1}{sL}\right)^{-1} + \frac{1}{sC}}$$

$$= \frac{sC}{\left(\frac{1}{sL} + \frac{1}{R}\right) + sC}$$

$$\therefore \underline{\underline{T(s) = \frac{V_o(s)}{V_s(s)} = \frac{s^2}{s^2 + s/RC + \frac{1}{LC}}}}$$

12.36

Low Pass: $\omega_0 = 10^5$, $C = 0.1 \mu\text{F}$
 $Q = 1/\sqrt{2}$

$$Q = \omega_0 CR$$

$$R = \frac{Q}{\omega_0 C}$$

$$= \frac{1}{\sqrt{2} \times 10^5 \times 0.1 \times 10^{-6}}$$


$$= \underline{\underline{70.7 \Omega}}$$

$$\omega_0 = \sqrt{LC}$$

$$L = \frac{1}{\omega_0^2 C}$$

$$= \underline{\underline{1 \text{ mH}}}$$

12.37

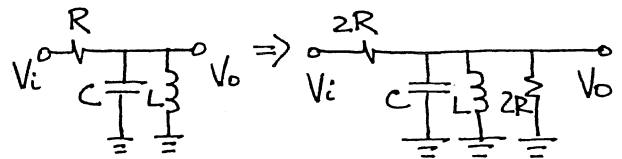

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 CR$$

$$A_{\text{mid}} = 1$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 C (2R \parallel 2R)$$

$$= \omega_0 CR$$

$$A_{\text{mid}} = \frac{2R}{2R+2R} = 1/2$$

12.38

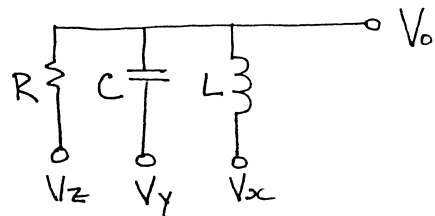

$$\left. \frac{V_o}{V_z} \right|_{V_y = V_x = 0} = T_{\text{BP}}(s)$$

$$\left. \frac{V_o}{V_y} \right|_{V_x = V_z = 0} = T_{\text{HP}}(s)$$

CONT.

$$\left. \frac{V_o}{V_x} \right|_{V_y=V_z=0} = T_{LP}(s)$$

Using superposition

$$\begin{aligned} V_o &= \frac{V_o}{V_x} V_x + \frac{V_o}{V_y} V_y + \frac{V_o}{V_z} V_z \\ &= T_{LP} V_x + T_{HP} V_y + T_{BP} V_z \\ &= \frac{\frac{1}{L_2} V_x + s^2 V_y + \frac{s}{RC} V_z}{s^2 + s/RC + 1/LC} \end{aligned}$$

$$\begin{aligned} \infty V_o &= V_x \frac{1/LC}{s^2 + s/RC + 1/LC} + \\ &V_y \frac{s^2}{s^2 + s/RC + 1/LC} + \\ &V_z \frac{s/RC}{s^2 + s/RC + 1/LC} \end{aligned}$$

but:

$$\begin{aligned} \omega_0^2 &= \frac{1}{(L_1 L_2) C} \quad \text{where } L_1 \parallel L_2 = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}} \\ &= \frac{L_1 + L_2}{L_1 L_2 C} = \frac{L_1 L_2}{L_1 + L_2} \\ &= \frac{L_1 + L_2}{L_2} (0.9 \omega_0)^2 \end{aligned}$$

$$1 = \left(\frac{L_1}{L_2} + 1 \right) 0.9^2$$

$$\therefore L_1/L_2 = \frac{1}{0.9^2} - 1 = \underline{\underline{0.2346}}$$

For $\omega \ll \omega_0$:-


$$|T| \cong \frac{1/L_1 C}{1/(L_1 \parallel L_2) C} = \frac{L_2}{L_1 + L_2}$$

i.e. inductors dominate!

For $\omega \gg \omega_0$ L_1 & L_2 are "open"
C is shorted

$$\underline{\underline{|T| \cong 1}}$$

12.39

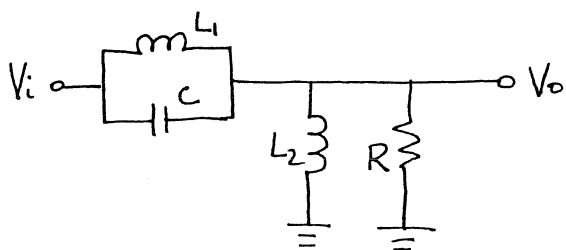

From Eq 12.46

$$T(s) = \frac{s^2 + 1/L_1 C}{s^2 + s(YC R) + \frac{1}{(L_1 \parallel L_2) C}}$$

$$\text{Required notch } \omega_n^2 = \frac{1}{L_1 C} = (0.9 \omega_0)^2$$

12.40

$$L = C_4 R_1 R_3 R_5 / R_2$$

$$\text{Choose } \underline{\underline{R_1 = R_2 = R_3 = R_5 = 10k\Omega}}$$

$$\therefore L = C_4 \times 10^8$$

For:

$$L = 10H = C_4 \times 10^8 \Rightarrow \underline{\underline{C_4 = 100nF}}$$

$$L = 1H \Rightarrow \underline{\underline{C_4 = 10nF}}$$

$$L = 0.1H \Rightarrow \underline{\underline{C_4 = 1nF}}$$

$$T(s) = \frac{0.4508 \omega_p (s^2 + 1.6996 \omega_p^2)}{(s + 0.7294 \omega_p)(s^2 + 0.2786 \omega_p s + 1.0504 \omega_p^2)}$$

$$\text{sub } \omega_p = 10^4 \text{ rad/s}$$

$$T(s) = \frac{4508 (s^2 + 1.6996 \times 10^8)}{(s + 7294)(s^2 + 2786s + 1.0504 \times 10^8)}$$

Part (b)

First decompose $T(s)$ into 1st and 2nd-order sections with unity DC gain!

$$T_1(s) = \frac{k_1}{s + 7294} \quad T_1(0) = \frac{k_1}{7294} = 1$$

$$\Rightarrow k_1 = \underline{\underline{7294}}$$

$$\text{Now } k_1 k_2 = 4508 \Rightarrow k_2 = \underline{\underline{0.6180}}$$

$$\therefore T_2(s) = \frac{0.6180 (s^2 + 1.6996 \times 10^8)}{s^2 + 2786s + 1.0504 \times 10^8}$$

As a check:

$$T_2(0) = \frac{0.6180 (1.6996 \times 10^8)}{1.0504 \times 10^8} = 1.000$$

As EXPECTED!

$$\therefore T(s) = T_1(s) \cdot T_2(s)$$

For first-order section use Fig 12.13(a)

$$\omega_0 = 7294 \text{ rad/s} \quad \text{DC Gain} = 1$$

$$\text{Let } \underline{\underline{C = 10 \text{ nF}}}$$

$$R_1 = R_2 = \frac{1}{\omega_0 C} \Rightarrow \underline{\underline{R_1 = R_2 = 13.71 \text{ k}\Omega}}$$

For second-order section

$$\omega_n^2 = 1.6996 \times 10^8 \Rightarrow \omega_n = 13.037 \times 10^3$$

$$\omega_0^2 = 1.0504 \times 10^8 \Rightarrow \omega_0 = 10.249 \times 10^3$$

$$\frac{\omega_0}{Q} = 2786 \Rightarrow Q = 3.6787$$

For LPN use table 12.1 and Fig 12.22 (e)

Make $R_1 = R_2 = R_3 = R_5 = R$ and

$$C = \underline{\underline{C_4 = C_6 = 10 \text{ nF}}}$$

$$R = \frac{1}{\omega_0 C} = \underline{\underline{9.757 \text{ k}\Omega}} = R_1 = R_2 = R_3 = R_5$$

$$\omega_n^2 = \frac{1}{C R^2 C_{G1}} \Rightarrow \underline{\underline{C_{G1} = 6.18 \text{ nF}}}$$

$$C_{G2} = C - C_{G1}$$

$$= \underline{\underline{3.82 \text{ nF}}}$$

$$Q = R_6 \sqrt{\frac{C_6}{C_4} \frac{R_2}{R_1 R_3 R_5}} = \frac{R_6}{\sqrt{R^2}}$$

$$= \frac{R_6}{R}$$

$$\therefore R_6 = RQ = (9.757 \times 10^3)(3.6787)$$

$$= \underline{\underline{35.89 \text{ k}\Omega}}$$

12.49

$$f_0 = 1 \text{ kHz}$$

The 3dB bandwidth for a 2nd order filter is given by:

$$B = \omega_0 / Q \Rightarrow Q = \frac{2\pi \times 10^3}{2\pi \times 50} = \underline{\underline{20}}$$

Choose $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_0 C} = \underline{\underline{15.92 \text{ k}\Omega}}$$

$$\text{Use } \underline{\underline{R_1 = R_2 = 10 \text{ k}\Omega}}$$

CONT.

$$\frac{R_3}{R_2} = 2Q - 1 = 39$$


choose $R_2 = 10k\Omega$ $R_3 = 390k\Omega$

Now $T(s) = \frac{-k\omega_0 s}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$

$$\Rightarrow |T(j\omega_0)| = \frac{k\omega_0^2}{\omega_0^2/Q} = kQ$$

but $k = 2 - 1/Q = 1.95$

∴ Centre-freq gain = $kQ = 39$

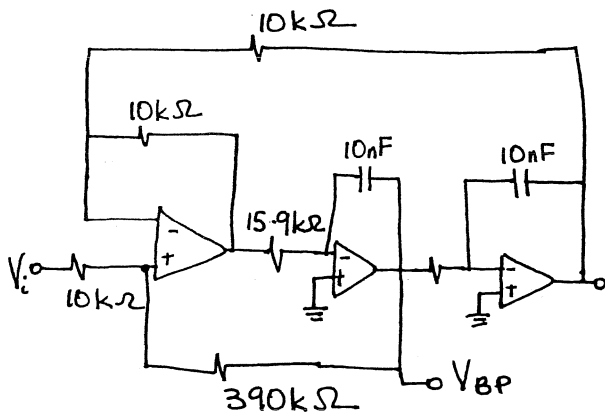

Part (b) - $\omega_0 = 10^4 \text{ rad/s}$ $Q = 2$ Flat Gain = 10

choose $C = 10nF \Rightarrow R = \frac{1}{\omega_0 C} = 10k\Omega$

choose $R_F = R_1 = 10k\Omega$

$$\frac{R_3}{R_2} = 2Q - 1 = 3 \Rightarrow R_2 = 10k\Omega$$

$$R_3 = 30k\Omega$$

Now $k = 2 - 1/Q = 1.5$

∴ Flat Gain = 10 = $(1.5) \frac{R_F}{R_H}$

∴ $\frac{R_H}{R_F} = 0.15$

choose $R_F = 100k\Omega$

$$R_H = R_L = 15k\Omega$$

$$R_B = QR_H = 30k\Omega$$

12.51

Note ω_n does not depend on R or C
From eq. 12.67:

$$\frac{R_H}{R_L} = \left(\frac{\omega_n}{\omega_0}\right)^2$$

∴ $\omega_n = \omega_0 \sqrt{\frac{R_H}{R_L}}$ Nominally $R_H = R_L \pm 1\%$

Thus:

$$\omega_n' = \omega_0 \sqrt{\frac{1.01}{0.99}} \quad \omega_n'' = \omega_0 \sqrt{\frac{0.99}{1.01}}$$

$$= 1.01\omega_0 \quad = 0.99\omega_0$$

∴ ω_n can deviate from ω_0
by $\pm 1\%$

12.50

$$R_L = R_H = R_B/Q \Rightarrow R_B = QR_H$$

$$R_L = R_H$$

Using Eq 12.66:

$$\frac{V_o}{V_i} = -k \frac{\frac{R_F}{R_H} s^2 - s\left(\frac{R_F}{R_B}\right)\omega_0 + \left(\frac{R_F}{R_L}\right)\omega_0^2}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

$$= -k \frac{R_F}{R_H} \frac{s^2 - \frac{\omega_0}{Q}s + \omega_0^2}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

Flat Gain = $-k \frac{R_F}{R_H}$

12.52

Use Tow Thomas to realize a LPN
(Fig 12.26)

$$\omega_0 = 10^4 \quad \omega_n = 1.2\omega_0 \quad Q = 10 \quad \text{DC Gain} = 1$$

$$C = 10 \text{ nF} \quad r = 20 \text{ k}\Omega$$

$$R = \frac{1}{\omega_0 C} = \underline{\underline{10 \text{ k}\Omega}}$$

from Eq. 16(e):

$$\text{DC Gain} = a_2 \frac{\omega_n^2}{\omega_0^2} = 1$$

$$a_2 \frac{1.2^2 \omega_0^2}{\omega_0^2} = 1$$

$$a_2 = \frac{1}{1.2^2} = \text{HF Gain}$$

$$C_1 = C a_2 = \frac{10 \times 10^{-9}}{1.2^2} = \underline{\underline{6.94 \text{ nF}}}$$

$$R_2 = \frac{R (\omega_0 / \omega_n)^2}{\text{HF Gain}} = R \left(\frac{1}{1.2}\right)^2 \times (1.2)^2$$

$$= R = \underline{\underline{10 \text{ k}\Omega}}$$

$$\underline{\underline{R_1 = R_3 = \infty}}$$

$$Q_z = \frac{\sqrt{\frac{1}{C^2 R R_2} \frac{C}{C_1}}}{\frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{R R_3}\right) \left(\frac{C}{C_1}\right)}$$

$$= \frac{1}{\sqrt{R R_2} \left(\frac{1}{R_1} - \frac{r}{R R_3}\right) \sqrt{\frac{C}{C_1}}}$$

For All Pass $R_1 \rightarrow \infty$

To adjust Q_z , trim r or R_3
(independent of ω_z !)

Now $\omega_0 = \frac{1}{CR}$ so do not trim R or C !

Note if we trim R_2 or C_1 to adjust ω_z , this will also affect Q_z . So the options are:

For ω_z : (a) trim R_2 AND (r or R_3) to maintain the value of Q_z

OR

(b) trim C_1 , and r or R_3

Prefer not to trim a capacitor so use (a)!

12.53

For all pass:

$$T(s) = \frac{-s^2 \left(\frac{C_1}{C}\right) + s \frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{R R_3}\right) + \frac{1}{C^2 R R_2}}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_z^2 = \frac{1}{C^2 R R_2} \cdot \frac{C}{C_1} \Rightarrow \omega_z = \frac{1}{C R R_2} \cdot \sqrt{\frac{C}{C_1}}$$

$$Q_z = \frac{\omega_z}{\frac{1}{C} \left(\frac{1}{R_1} - \frac{r}{R R_3}\right) \frac{C}{C_1}}$$

12.54

$$T(s) = \frac{0.4508 (s^2 + 1.6996)}{(s + 0.7294)(s^2 + 0.2786s + 1.0504)}$$

Part (a) Replace s with s/ω_p
 $\omega_p = 10^4$ rad/s.

$$T(s) = \frac{0.4508 \left(\frac{s^2}{\omega_p^2} + 1.6996\right)}{\left(\frac{s}{\omega_p} + 0.7294\right) \left(\frac{s^2}{\omega_p^2} + \frac{0.2786s}{\omega_p} + 1.0504\right)}$$

CONT.

$$T(s) = \frac{0.4508 \omega_p (s^2 + 1.6996 \omega_p^2)}{(s + 0.7294 \omega_p)(s^2 + 0.2786 \omega_p s + 1.0504 \omega_p^2)}$$

$$= \frac{4508 (s^2 + 1.6996 \times 10^8)}{(s + 7294)(s^2 + 2786s + 1.0504 \times 10^8)}$$

For FIRST ORDER SECTION use Fig 12.13(a)

$$\omega_0 = 7294 \quad \text{DC gain} = 1$$

choose $C = 10 \text{ nF}$

$$R_1 = R_2 = \frac{1}{\omega_0 C} \Rightarrow R_1 = R_2 = 13.711 \text{ k}\Omega$$

For SECOND ORDER SECTION - use Fig 12.26

$$\omega_n^2 = 1.6996 \times 10^8 \Rightarrow \omega_n = 13.037 \times 10^3$$

$$\omega_0^2 = 1.0504 \times 10^8 \Rightarrow \omega_0 = 10.249 \times 10^3$$

$$\frac{\omega_0}{Q} = 2786 \Rightarrow Q = 3.6787$$

$$\text{DC gain} = 1$$

For Tow Thomas LPN use table 12.2

choose $C = 10 \text{ nF}$

$$R = \frac{1}{\omega_0 C} = \frac{1}{10.249 \times 10^3 \times 10 \times 10^{-9}}$$

$$= 9.757 \text{ k}\Omega$$

choose $r = 20 \text{ k}\Omega$

Now from Fig 12.16 (e):

$$T(0) = a_2 \frac{\omega_n^2}{\omega_0^2} = 1 \Rightarrow a_2 = \frac{\omega_0^2}{\omega_n^2} = 0.618$$


$$\therefore \text{HF gain} = a_2 = 0.618$$

$$C_1 = C \times \text{HF gain} \Rightarrow C_1 = 6.18 \text{ nF}$$

$$R_2 = R \left(\frac{\omega_0}{\omega_n} \right)^2 / 0.618$$

$$R_2 = R \Rightarrow R_2 = 9.757 \text{ k}\Omega$$
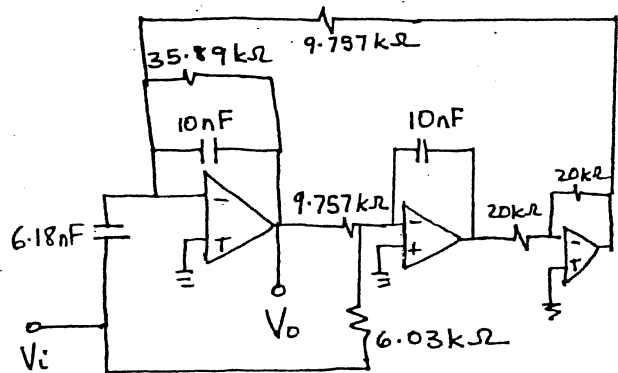
$$R_1 = R_3 = \infty \quad QR = 35.89 \text{ k}\Omega$$



12.55

Make $C_1 = C_2 = 1 \text{ nF} = C$

$$\omega_0 = \frac{1}{\sqrt{C_1 C_2 R_3 R_4}} \quad Q = \left[\frac{\sqrt{C_1 C_2 R_3 R_4}}{R_3} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) \right]^{-1}$$

$$\text{Let } R_3 = R$$

$$R_4 = \frac{R}{m}$$

$$m = 4Q^2$$

$$= 4/2 = 2$$

$$\therefore \omega_0 = \frac{1}{\sqrt{C^2 R^2/2}} = \frac{\sqrt{2}}{RC} = 10^4$$

$$\Rightarrow R = \frac{\sqrt{2}}{10^4 \times 10^{-9}} = 141.42 \text{ k}\Omega$$

$$R_3 = 141.4 \text{ k}\Omega$$

$$R_4 = \frac{R_3}{2} \Rightarrow R_4 = 70.7 \text{ k}\Omega$$