

# University of Toronto

## Term Test 1

Date - Oct 13, 2010

Duration: 1.5 hrs

ECE512 — Analog Signal Processing

Lecturer - D. Johns

**ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY**

1. Both programmable and non-programmable calculators allowed.
  2. Equation sheet on last page of this test.
  3. **Only tests written in pen will be considered for a re-mark.**
  4. Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.
- 

Last Name: SOLUTIONS

First Name: \_\_\_\_\_

Student #: \_\_\_\_\_

Question	Mark
1	
2	
3	
4	
5	
Total	

(max grade = 25)

[5] **Question 1:** Answer the True [T] or False [F] questions below by **circling** the correct answer. Each correct answer is worth 0.5 marks.

- T  F The Laplace transform of the impulse response of a linear time-invariant filter equals the filter's transfer-function.
- T  F A filter realized using only resistors and capacitors will have all its poles and zeros on the real axis.
- T  F The transfer-function order of a filter realized using only inductors, capacitors and resistors equals the total number of inductors and capacitors.
- T  F For a given passband ripple, a Butterworth filter has more stopband attenuation than a Chebyshev filter.
- T  F The units of group delay is seconds.
- T  F A direct-form realization of a filter has poor performance even for a second-order filter.
- T  F When designing a cascade-of-biquads filter, the high-Q poles should be matched with the furthest zeros.
- T  F The Chebyshev polynomial,  $C_3(\omega)$ , can be written as  $4\omega^3 - 3$
- T  F In terms of the phase response, having a zero in the s-plane at  $z_1 = \sigma_1 + j\omega_1$  has the same phase response effect as having a zero at  $-z_1^*$
- T  F For low to moderate frequency filters (0 to 10Mhz), active RC filters are preferred over RLC filters because active RC filters have better linearity performance.

## [5] Question 2:

Consider an 8'th order Butterworth filter with a passband frequency at 10kHz and a passband ripple of 2dB. Find the values of  $\omega_0$  and  $Q$  for the pole pair with the highest  $Q$  only.

$$A_{MAX} = 2 \text{ dB} = 20 \log \sqrt{1 + \epsilon^2}$$

$$10^{0.2} = 1 + \epsilon^2 \Rightarrow \epsilon^2 = 10^{0.2} - 1 = 0.5849$$


$$\epsilon = 0.7648$$

$$\omega_0 = \omega_p \left( \frac{1}{\epsilon} \right)^{\frac{1}{N}}$$

$$\omega_p = 2\pi \times 10 \text{ K}$$

$$N = 8$$
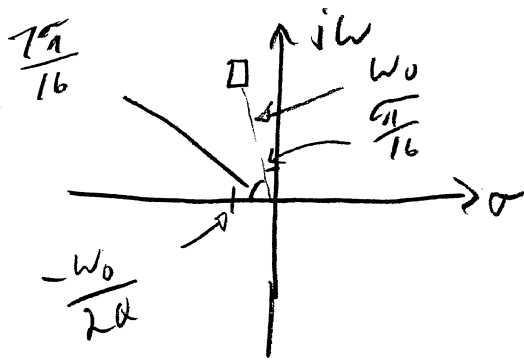
$$\omega_0 = (2\pi \times 10 \text{ K}) \left( \frac{1}{0.7648} \right)^{\frac{1}{8}} = \underline{\underline{6.50 \times 10^4 \text{ RAD/S}}}$$



$$\omega_0 \cos \frac{7\pi}{16} = \frac{\omega_0}{2Q} \Rightarrow Q = \frac{1}{2 \cos \left( \frac{7\pi}{16} \right)}$$

$$\underline{\underline{Q = 2.56}}$$

[5] Question 3:

Given  $H(s) = \frac{1}{(s+1)(s^2+s+1)}$  show that  $|H(j\omega)|^2 = \frac{1}{1+\omega^6}$

$$|H(j\omega)|^2 = H(s)H(-s) \Big|_{s=j\omega}$$

$$H(s)H(-s) = \frac{1}{(s+1)(-s+1)(s^2+s+1)(s^2-s+1)}$$

$$= \frac{1}{(1-s^2)(s^4+s^2+1)}$$

$$= \frac{1}{1-s^6}$$

$$|H(j\omega)|^2 = \frac{1}{1+\omega^6}$$


---




---

[5] Question 4:

It is known that the circuit below realizes the following voltage transfer-function

$$H(s) = \frac{V_o}{V_i} = \frac{2728.4s}{s^2 + 100s + 10^6}$$

which is a bandpass filter.

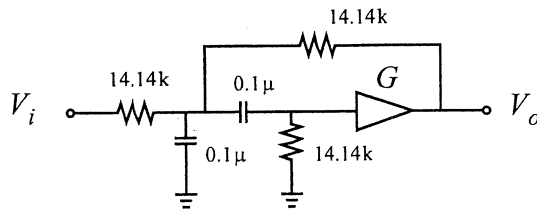


G is an ideal gain of 3.859

a) Apply a frequency scaling to normalize the band center frequency to 1 rad/s. (you will have to determine the center frequency from the transfer-function above).

$H(s)$  IS BANDPASS SO BAND CENTER FREQ =  $\omega_0$

$$\omega_0^2 = 10^6 \text{ SO } \omega_0 = 10^3 \text{ RAD/S}$$

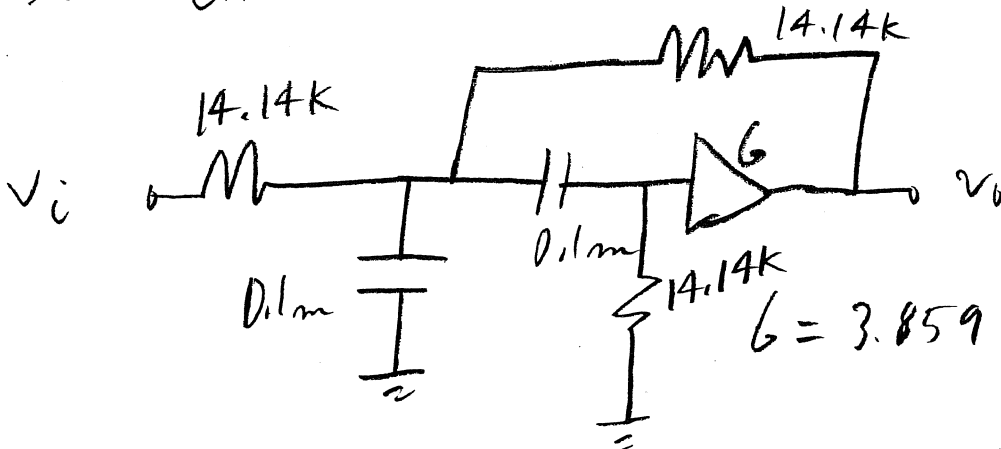
NEED TO FREQ SCALE BY  $10^{-3}$  SO CAPACITORS INCREASED  $10^3$



b) Apply an impedance scaling to the results of a) to normalize the circuit so that both capacitors become 1 F.


WANT  $C = 1\text{ F}$  SO IMPEDANCE  
SCALE BY  $10^{-4}$

$$\Rightarrow R = 1.414 \Omega$$

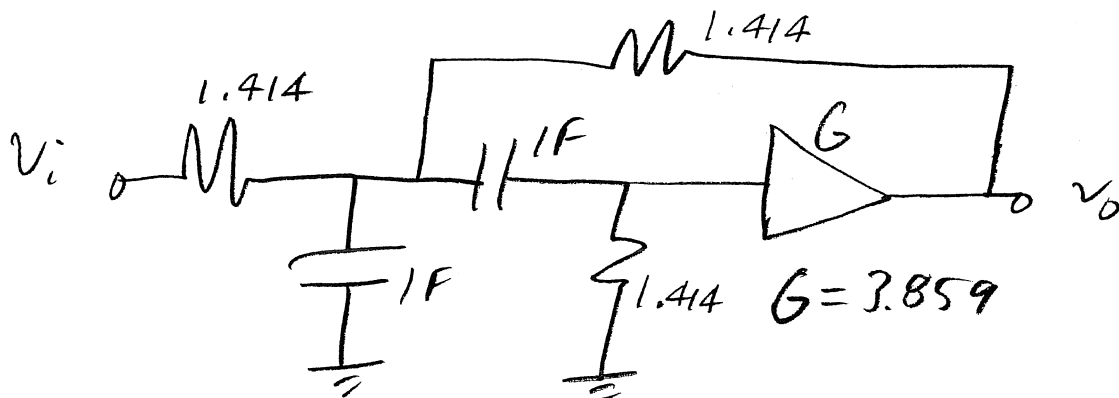

[5] Question 5:

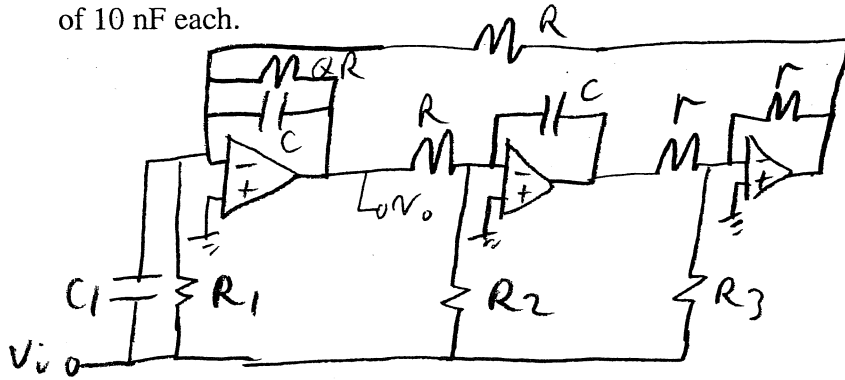Design a Tow-Thomas highpass notch filter with a high frequency gain of -1, a pole frequency of 5kHz, a pole-Q of 5 and a notch frequency at 500Hz. Use integrating capacitors of 10 nF each.



LET  $R = 10k$   
(ARBITRARY)  
(CHOICE)

$$C = 10 \text{ nF} \quad RC = \frac{1}{\omega_0} = \frac{1}{2\pi \times 5k} \Rightarrow \underline{\underline{R = 3.183k}}$$

$$QR = 5 \times R = \underline{\underline{15.92k}}$$

$$R_1 = R_3 = \infty \quad (\text{TO MAKE NOTCH})$$

$$H(s) = \frac{-(s^2(\frac{C1}{C}) + \frac{1}{RR_2C^2})}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2}$$

$$\text{HIGH FREQ GAIN} = -1 \Rightarrow \underline{\underline{C_1 = C = 10 \text{ nF}}}$$

$$K_1 s^2 + K_2 \text{ HAS ZERO AT } s^2 = -\frac{K_2}{K_1}$$

$$\frac{1}{RR_2C^2} = (2\pi \times 500)^2$$

$$R_2 = \frac{1}{RC^2(2\pi \times 500)^2} = \underline{\underline{318.3k}}$$

(blank sheet for scratch calculations)



## ECE512

## Analog Signal Processing

## Equation Sheet

**Constants:**  $k = 1.38 \times 10^{-23} \text{ JK}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$ ;  $V_T = kT/q \approx 26 \text{ mV}$  at  $300^\circ \text{ K}$ ;

**General:**  $h(t)$  is impulse response of LTI system;  $H(s)$  is the Laplace transform of  $h(t)$

$$H(j\omega) = |H(j\omega)|e^{j\phi(\omega)}; T_d(\omega) = -\frac{d\phi(\omega)}{d\omega}; |H(j\omega)|_{\text{dB}} = 20\log|H(j\omega)|; H(s) = \frac{a_m s^m + \dots + a_0}{s^N + b_{n-1}s + \dots + b_0}; |H(j\omega)|^2 = H(s)H(-s)|_{s=j\omega} = H(j\omega)H(-j\omega);$$

**General Lowpass:**  $|H(j\omega)|^2 = A_0^2 / (1 + F(\omega^2))$ ;

**Butterworth:**  $F(\omega^2) = \epsilon^2 \left(\frac{\omega}{\omega_p}\right)^{2N}$ ;  $A_{\text{max}} = 20\log\sqrt{1 + \epsilon^2}$ ;  $A_{\text{min}} \leq 10\log\left[1 + \epsilon^2 \left(\frac{\omega_s}{\omega_p}\right)^{2N}\right]$ ; Poles lie on circle of radius  $\omega_p (1/\epsilon)^{1/N}$  spaced apart by  $\pi/N$  with first angle being  $\pi/(2N)$

**Chebyshev:** (for  $\omega_p = 1$ );  $F(\omega^2) = \epsilon^2 C_N^2(\omega)$ ;  $C_N(\omega) = \cos(N\cos^{-1}(\omega))$   $|\omega| \leq 1$ ;  $C_N(\omega) = \cosh(N\cosh^{-1}(\omega))$   $|\omega| \geq 1$ ;

$$C_{N+1}(\omega) = 2\omega C_N(\omega) - C_{N-1}(\omega); A_{\text{max}} = 20\log\sqrt{1 + \epsilon^2}; A_{\text{min}} \leq 10\log[1 + \epsilon^2 \cosh^2(N\cosh^{-1}(\omega_s/\omega_p))];$$

**Second-order polynomial:**  $s^2 + (\omega_0/Q)s + \omega_0^2$ ; for  $Q > 0.5$ ; poles complex at radius  $\omega_0$  and real part is  $-\omega_0/(2Q)$ ;

**Lowpass and highpass:** peaking occurs if  $Q > 1/\sqrt{2}$  and  $\omega_{\text{max}} = \omega_0\sqrt{1 - 1/2Q^2}$

**Bandpass:** for complex poles; peak occurs at  $\omega_0$  and has 3 dB bandwidth of  $\omega_0/Q$

**LCR:**  $\omega_0 = 1/\sqrt{LC}$ ;  $Q = \omega_0 CR$ ;

**KHN Biquad:**  $RC = 1/\omega_0$ ;  $2((R_1 || R_2) / ((R_1 || R_2) + R_3)) = 1/Q$ ;  $2((R_2 || R_3) / ((R_2 || R_3) + R_1)) = k$ ;

**Tow-Thomas Biquad:**  $RC = 1/\omega_0$ ; damping resistor is  $QR$ ; numerator is  $-s^2\left(\frac{C_1}{C}\right) - s\left(\frac{1}{C}\right)\left(\frac{1}{R_1} - \frac{r}{RR_3}\right) - \frac{1}{RR_2C^2}$ ;

**Noise:** noise equivalent bandwidth  $= (\pi/2)f_{3\text{dB}}$ ;  $V_R^2(f) = 4kTR$ ;  $I_d^2(f) = 2qI_D$ ;  $r_d = (kT)/(qI_D)$ ;  $V_C^2 = (kT)/C$ ;

**Discrete-Time:**  $X_s(s) = \sum_x(nT)e^{-snT}$ ;  $X(z) = \sum_x(nT)z^{-n}$ ;  $p = (z-1)/(z+1)$ ;  $z = (1+p)/(1-p)$ ;  $\Omega = \tan(\omega/2)$ ;

**Switched-Cap:**  $R_{\text{eq}} = T/C$ ;  $Q_{\text{CH}} = -WLC_{\text{ox}}(V_{\text{GS}} - V_T)$ ;

**Data Converters:**  $B_{\text{in}} = b_1 2^{-1} + \dots + b_N 2^{-N}$ ;  $V_{\text{LSB}} = V_{\text{ref}}/2^N$ ;  $V_{\text{out}} = V_{\text{ref}}B_{\text{in}}$ ;  $V_{\text{ref}}B_{\text{out}} = V_{\text{in}} + V_Q$ ;  $|V_Q| \leq 0.5V_{\text{LSB}}$ ;

$$V_{Q(\text{rms})} = V_{\text{LSB}}/\sqrt{12}; \text{SNR} = 6.02N + 1.76; E_{\text{off(D/A)}} = V_{\text{out}}/V_{\text{LSB}}|_{0\dots 0}; E_{\text{off(A/D)}} = V_{0\dots 01}/V_{\text{LSB}} - 0.5\text{LSB}; \Delta t < 1/(2^N \pi f_{\text{in}});$$

$$E_{\text{gain(D/A)}} = \left(V_{\text{out}}/V_{\text{LSB}}|_{1\dots 1} - V_{\text{out}}/V_{\text{LSB}}|_{0\dots 0}\right) - (2^N - 1); E_{\text{gain(A/D)}} = (V_{1\dots 1}/V_{\text{LSB}} - V_{0\dots 01}/V_{\text{LSB}}) - (2^N - 2);$$

**Oversampling:**  $\text{OSR} = f_s/(2f_0)$ ;  $\text{SNR}_0 = 6.02N + 1.76 + 10\log(\text{OSR})$ ;  $\text{SNR}_1 = 6.02N + 1.76 - 5.17 + 30\log(\text{OSR})$ ;

$$\text{SNR}_2 = 6.02N + 1.76 - 12.9 + 50\log(\text{OSR}); S_{\text{TF}}(z) = H(z)/(1 + H(z)); N_{\text{TF}}(z) = 1/(1 + H(z))$$

$$T_{\text{avg}}(z) = \frac{1}{M} \sum_{i=0}^{M-1} z^{-i} = \frac{1}{M} \left(\frac{1 - z^{-M}}{1 - z^{-1}}\right); T_{\text{avg}}(e^{j\omega}) = \frac{\text{sinc}((\omega M)/2)}{\text{sinc}(\omega/2)}; |N_{\text{TF}}(e^{j\omega})| \leq 1.5 \text{ for 1-bit quantizer stability};$$

**Bipolar transistors:**  $I_C = I_{\text{CS}}e^{V_{\text{BE}}/V_T}$ ;  $g_m = I_C/V_T$ ;  $r_e = \alpha/g_m = V_T/I_E$ ;

**CMOS transistors:**  $K_n = 0.5\mu_n C_{\text{ox}}(W/L)$ ;  $I_D = 2K_n((V_{\text{GS}} - V_{\text{tn}})V_{\text{DS}} - (V_{\text{DS}}^2/2))$ ;  $r_{\text{ds}} = (2K_n(V_{\text{GS}} - V_{\text{tn}}))^{-1}$ ;

$$I_D = K_n(V_{\text{GS}} - V_{\text{tn}})^2; g_m = 2K_n(V_{\text{GS}} - V_{\text{tn}}) = (2I_D)/(V_{\text{GS}} - V_{\text{tn}}); r_s = 1/g_m;$$

**Ideal Transconductor:**  $i_o = G_m v_i$ ; **Bipolar Diff Pair:**  $I_{C2} = I_1/(1 + e^{v_i/V_T})$ ;

**CMOS Pair:**  $K_{\text{eq}} = (K_n K_p)/(\sqrt{K_n} + \sqrt{K_p})^2$ ;  $V_{\text{t-eq}} = V_{\text{tn}} - V_{\text{tp}}$ ;

**Dynamic Range:** (all in dB or dBm)  $ID_3 = ID_3 - ID_1$ ;  $\text{OIP}_3 = ID_1 - ID_3/2$ ;  $\text{SFDR} = (2/3)(\text{OIP}_3 - N_0)$ ;

$$\text{THD} = 10\log((V_{h2}^2 + V_{h3}^2 + \dots)/V_f^2);$$