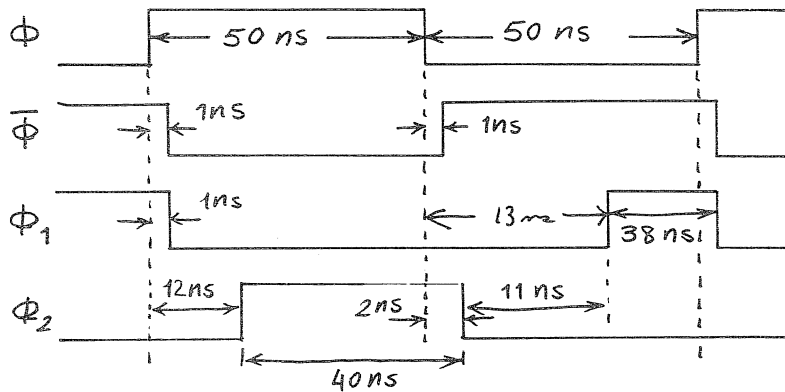


Chapter 10 - Problems

10.1) The clock period is $\frac{1}{10 \text{ MHz}} = 100 \text{ ns}$. Assuming 50% duty cycle, we have the following timing diagram:



(not to scale)

$$10.2) \quad C_2 V_o(n) = C_2 V_o(n-1) - C_1 V_i(n)$$

$$\Rightarrow C_2 V_o(z) = C_2 z^{-1} V_o(z) - C_1 V_i(z) \Rightarrow \frac{V_o(z)}{V_i(z)} = \frac{-C_1/C_2}{1 - z^{-1}}$$


10.3) C_{P2} is always discharged since its voltage is virtually ground.

During ϕ_1 , C_{P1} is charged to $V_i(n) C_{P1}$.

This charge will be transferred

to C_2 during ϕ_2 . Therefore: $C_2 V_o(n) = C_2 V_o(n-1) - C_{P1} V_i(n-1) - C_1 V_i(n)$
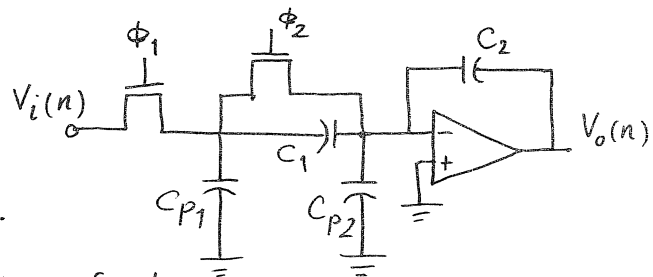
$$\Rightarrow \frac{V_o(z)}{V_i(z)} = - \frac{\frac{C_1}{C_2} + \frac{C_{P1}}{C_2} z^{-1}}{1 - z^{-1}}$$



10.4) A finite gain of A implies the voltage of the inverting terminal is $-\frac{1}{A}V_o(n)$ if the output voltage is $V_o(n)$.

$$C_2 V_o(n) \left[1 + \frac{1}{A}\right] = C_2 V_o(n-1) \left[1 + \frac{1}{A}\right] - C_1 \left[V_i(n-1) + \frac{V_o(n)}{A}\right]$$

Note that at the end of Φ_2 , the voltage across C_1 , which is $V_i(n-1)$, reduces to $-\frac{V_o(n)}{A}$, not ground.

Also, assuming $\frac{1}{A} \ll 1$, we have

$$C_2 V_o(n) = C_2 V_o(n-1) - C_1 \left(V_i(n-1) + \frac{V_o(n)}{A}\right)$$

$$\Rightarrow \frac{V_o(z)}{V_i(z)} = \frac{-C_1/C_2}{z \left(1 + \frac{C_1}{C_2 A}\right) - 1}$$

At dc ($z=1$), this gain is equal to $\frac{-C_1/C_2}{1 + \frac{C_1}{C_2 A}} = -A$

$$Z_p = \frac{1}{1 + \frac{C_1}{C_2 A}} = 1 - \frac{C_1}{C_2 A} \quad \text{assuming } C_1 \ll C_2 A.$$

$$10.5) \quad H(z) = \frac{Kz}{z - 0.53327}$$

$$\text{Setting } H(1) = 1 \Rightarrow H(z) = \frac{0.46673z}{z - 0.53327}$$

Equating $H(z)$ with that of Eq. (10.33) and assuming

$$C_A = 10 \text{ pF} \Rightarrow \underbrace{C_1 = 0} \quad \underbrace{C_2 = -8.752 \text{ pF}} \quad \underbrace{C_3 = 8.752 \text{ pF}}$$

$$\text{The new gain at } 50 \text{ kHz} = \underline{H(-1) = -0.304 = -10.3 \text{ dB}}$$

$$10.6) \quad \omega_{3dB} = \frac{1 \text{ kHz}}{50 \text{ kHz}} \times 2\pi = 0.04\pi \text{ RAD/SAMPLE}$$

Since the zero is at 0 rather than -1, we cannot use a bilinear transform. From example 9.5 in chapter 9, we have

$$\omega_{3dB} = \cos^{-1} \left(2 - \frac{a}{2} - \frac{1}{2a} \right)$$

This example assumed a zero at ∞ which has same magnitude response as a zero at 0.

$$\cos(0.4\pi) = 2 - \frac{a}{2} - \frac{1}{2a} \Rightarrow a = 0.8821$$

$$H(z) = \frac{kz}{z - 0.8821} \quad \text{Forcing } H(1) = 1 \Rightarrow k = 0.1179$$

Equating coeff with (10.33) results in

$$\underline{C_1 = 0}, \quad \underline{-C_2 = C_3 = 6.683 \text{ pF}}$$

$$25 \text{ kHz corresponds to } z = -1 \therefore H(-1) = 0.0626 = \underline{-24.1 \text{ dB}}$$

10.7) The transfer function is given by (10.33). Substituting the given capacitances, we have:


$$\underline{H(z) = \frac{0.1z}{1.1z - 1}}$$

$$\text{At dc: } z=1, \quad \underline{H(1) = 1}, \quad \cancel{H(1) = 0}$$

$$\text{At } f_s/4: z=j, \quad \underline{H(j) = 0.673 \angle -42.27^\circ}$$

$$\text{At } f_s/2: z=-1, \quad \underline{H(-1) = 0.0476 \angle 0^\circ}$$

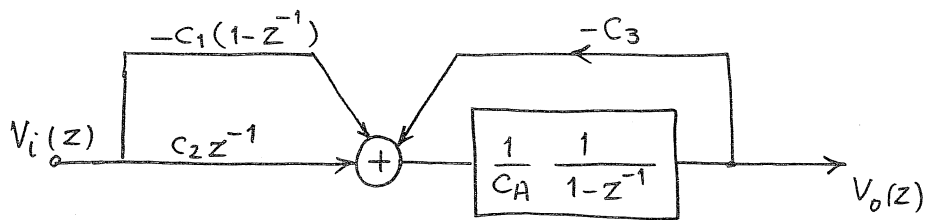10.8) The equivalent signal flow graph is:



$$\{V_i(z)[c_2 z^{-1} - c_1 + c_1 z^{-1}] - c_3 V_o(z)\} \frac{1}{C_A} \frac{1}{1-z^{-1}} = V_o(z)$$

$$\Rightarrow H(z) = \frac{V_o(z)}{V_i(z)} = - \frac{c_1 - (c_1 + c_2) z^{-1}}{(C_A + c_3) - C_A z^{-1}}$$

10.9) The transfer function poles are the zeros of the denominator.

Using (10.49) with $K_6 = 0$, we have

$$z^2 + (K_4 K_5 - 2)z + 1 = 0$$

Since all the coefficients are real numbers, this equation has, in general, two complex conjugate roots, z_1 & z_1^* , with their product equal to the constant term of the equation (i.e. 1).

$$\therefore z_1 z_1^* = 1 \Rightarrow |z_1|^2 = 1 \Rightarrow |z_1| = 1$$

\therefore both z_1 & z_1^* lie on the unit circle.

$$10.10) \omega_0 = \frac{2\pi}{100} = 0.062832 \text{ RAD/SAMPLE} \quad \& \quad Q = 20$$

$$\text{Equivalent } \Omega_0 = \tan\left(\frac{\omega_0}{2}\right) = 0.0314263 \text{ RAD/S}$$

$$\therefore H_a(s) = \frac{\frac{\omega_0}{Q} s}{s^2 + \frac{\omega_0}{Q} s + \omega_0^2} = \frac{0.0015713 s}{s^2 + 0.0015713 s + 0.00098761}$$

Transform using the bilinear transform

$$s = \frac{z-1}{z+1}$$

$$H(z) = \frac{0.001572 z^2 - 0.001572}{1.003145 z^2 - 1.9991875 z + 1}$$

FOR LOW-Q biquad from (10.51) - (10.56)

$$k_3 = -0.001572 \quad k_2 = 0.003144$$

$$k_6 = 0.003145 \quad k_4 = k_5 = 0.06291$$

$$k_1 = 0$$

FOR HIGH-Q biquad from (10.69) - (10.74)

$$H(z) = \frac{0.001567 z^2 - 0.001567}{z^2 - 1.99292 z + 0.99687}$$


$$k_3 = 0.001567 \quad k_1 = 0 \quad k_2 = 0.0499$$

$$k_4 = k_5 = 0.06285 \quad k_6 = 0.0498$$

Ignoring k_3 (since it only sets zero at -1)

CAP ratio for low-Q is 318 while it is 20 for high-Q biquad.

10.11)

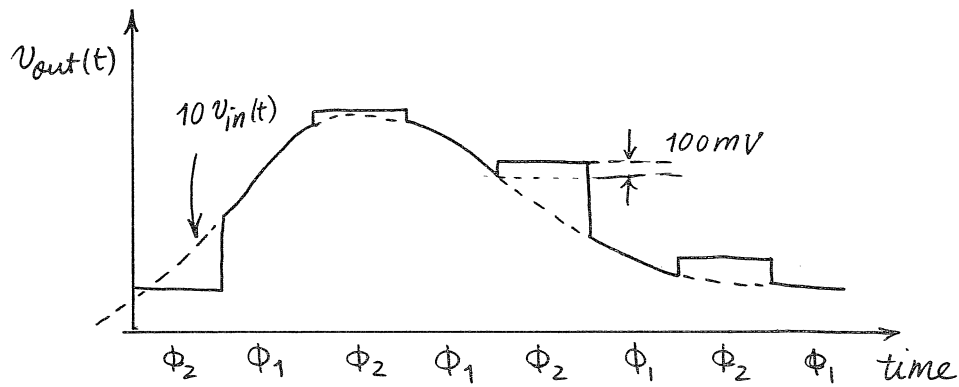10.12) Assuming $V_{out} = -V_{SS}$,

$$\Delta V_x = -K_2 V_{SS} = -K_{in} V_{in}$$

the positive jump of V_x is still $K_1(V_{SS} + V_{DD})$ as before.

$$\Rightarrow T_{osc} = 2 \frac{K_1 (V_{SS} + V_{DD})}{K_2 V_{SS} + K_{in} V_{in}} T$$

Or, equivalently (assuming $V_{SS} = V_{DD}$)

$$f_{osc} = \frac{1}{4} \left(\frac{K_2}{K_1} + \frac{K_{in} V_{in}}{K_1 V_{DD}} \right) f$$