
 



 
# Bulk-Driven Circuits

Michael Gordon, M.A.Sc. Candidate  
University of Toronto  
December 2003


Analog Circuit Design I ECE1392  
Taught by Professor K. Phang



# MOSFET as a 4-terminal device

  

 - Bulk node gives the designer an extra degree of freedom
- But designers don't use the bulk node
- $V_T$  does not scale with  $V_{DD}$  in new submicron processes!






# The Body Effect



- Common bulk effects: “Body Effect”
  - Considered as a “bad” side-effect when  $V_b \neq V_s$
  - Increases  $V_T$  and lowers voltage headroom

$$V_T = V_{T0} \pm \gamma (\sqrt{2 |\phi_F| - V_{BS}} - \sqrt{2 |\phi_F|})$$

 - What if  $V_{BS} > 0$ ?      ←      **Reduce  $V_T$** 
  - Use as a low-voltage technique
  - Might forward bias B-S diode
- Current Driven Bulk (CDB) technique





# Threshold Adjust

 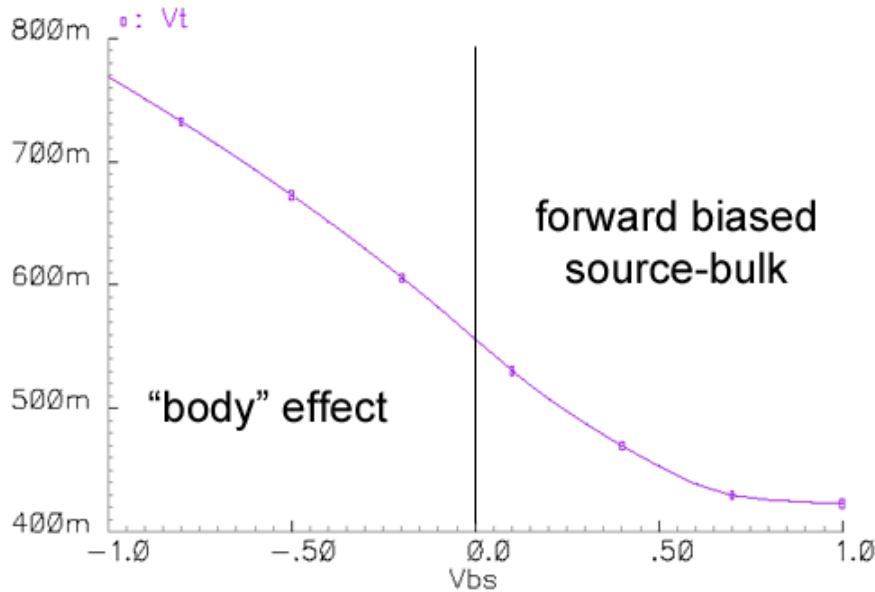


- $V_T$  reduced from 0.55V to 0.45V
- CDB intentionally turns on the BS diode
  - Achieves maximum  $V_{BS} = V_{DIODE} \approx 0.7V$
- Can **AC** signals be applied to the bulk?




# Faster Switching

  

 - Connect VIN to gate AND bulk
  - VIN ↑, V<sub>BS</sub> ↑, V<sub>T</sub> ↓, Turn on faster
  - VIN ↓, V<sub>BS</sub> ↓, V<sub>T</sub> ↑, Turn off faster



 - **Faster switching:** Digital gates, Mixers, etc.




# Bulk Node as AC Input?

- So far used bulk to adjust  $V_T$ , but can we drive actual signals through it?
- We reduced  $V_T$ , but can we get rid of it?
- Gate driven:  $g_m V_{gs}$
- Bulk driven:  $g_{mb} V_{bs}$



$$g_{mb} = \eta g_m$$
 
$$\eta = \frac{\gamma}{2\sqrt{2\phi_F - V_{BS}}} \sim 0.2 \dots 0.4$$






# Linearization

  

Simulation of a differential pair (bulk-input vs. gate-input) [1]

 Main benefits: Linear  $G_m$ , Rail-to-Rail Input, Constant  $G_m$   
**Perfect for building Rail-to-Rail OPAMPs !!! [6,7]**



# The small print


- Gain is reduced  $g_{mb} = \eta g_m$   $\eta \sim 0.2 \dots 0.4$
- Bandwidth is reduced [3]

$$f_{T,bulk-driven} \approx \frac{\eta}{3.8} f_{T,gate-driven}$$

- Higher noise figure (because of lower gm)

$$Noise_{bulk-driven} = \frac{Noise_{gate-driven}}{\eta^2}$$

 - Need separate wells (dual well process)
  - More expensive process
  - Bigger chip area
  - Worst matching








# Latest trends from Intel

“Current performance scaling trends will not continue past the 0.13 - 0.10mm device technologies by using traditional scaling methods.” [2]


“Fundamental limits in  $\text{SiO}_2$  ... are currently being reached” [2]

 - DTMOS switches faster by lowering  $V_T$  during switching
- Circuit topologies are being developed for  $<0.6\text{V}$  supply



Proposed DTMOS –  
Dynamic  $V_T$  MOS Inverter

 **A lot of research in bulk-driven circuits is needed,  
but very few publications exist**



# Summary

---

- Consider the Bulk node as another parameter
  - Static Bulk Voltage – Reduce  $V_T$
  - Dynamic Bulk Voltage – Dynamically Reduce  $V_T$
  - Bulk-Driven Signals – Ignore  $V_T$  completely



# References

---

- [1] E.S. Sinencio, “Bulk Driven Transistors”, ELEN-607 Course notes, Texas A&M University, 2003
- [2] S. Thompson et al, “MOS Scaling: Transistor Challenges for the 21st Century”, Intel Technology Journal, 3<sup>rd</sup> quarter, 1998
- [3] L. Yong, “Complementary Body-driving - A Low-voltage Analog Circuit Technique Realized In 0.35um SOI Process”, M. Sc. Thesis, University of Tennessee, Knoxville, August 2002
- [4] T. Lehmann, M. Cassia, “1-V Power Supply CMOS Cascode Amplifier”, Solid-State Circuits Journal, July 2001
- [5] R. Friend, C.C. Enz, “Bulk driven MOST transconductor with extended linear range”, Electronics Letters, 28 March 1996
- [6] T. Stockstad, H. Yoshizawa, “0.9V, 0.5uA Rail-to-Rail Opamp”, Custom Integrated Circuits Conference, May 2001
- [7] B.J. Blalock et al, “Designing 1-V Op Amps Using Standard Digital CMOS Technology”, Circuits and Systems II: Analog and Digital Signal Processing, July 1998
- [8] H. Huang, J. Lin, “CMOS Bulk Input Technique”, ISCAS, May 2002
- [9] B.J. Blalock, P.E. Allen, “A Low-Voltage, Bulk-Driven MOSFET Current Mirror for CMOS Technology”, ISCAS, May 1995