

**University of Toronto**

**Term Test 1**

Date — Oct 17, 2022: 12:10pm

Duration — 50 min

ECE 331 — Analog Electronics

Lecturer — D. Johns

---

**ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY**

- Equation sheet is on the last page of this test.
- Unless otherwise stated, assume  $g_m r_o \gg 1$
- Notation: 15e3 is equivalent to  $15 \times 10^3$
- Non-programmable calculator is allowed; No other aids are allowed
- Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.

---

**Last Name:** \_\_\_\_\_


**First Name:** \_\_\_\_\_

**Student #:** \_\_\_\_\_

Question	1	2	3	Total
Points:	5	5	5	15
Score:				

## Grading Table


**Q1.** Consider the circuit shown below

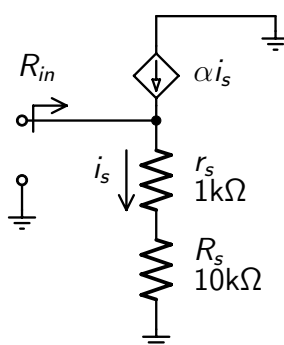

- [3] (a) Find the input impedance,  $R_{in}$ , when  $\alpha = 0.9$ .  
 [1] (b) Find the input impedance,  $R_{in}$ , when  $\alpha = 0.99$ .  
 [1] (c) Find the input impedance,  $R_{in}$ , when  $\alpha = 1$

## Solution

(a)

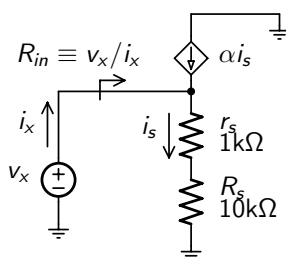

$$i_s = v_x / (r_s + R_s)$$

$$i_x + \alpha i_s = i_s$$

$$i_s = i_x / (1 - \alpha)$$

$$R_{in} \equiv v_x / i_x = (r_s + R_s) / (1 - \alpha)$$

$$R_{in} = (r_s + R_s)/(1 - \alpha) = ((1e3) + (10e3))/(1 - (0.9)) = 110k\Omega$$


(b)

$$R_{in} = (r_s + R_s)/(1 - \alpha) = ((1e3) + (10e3))/(1 - (0.99)) = 1.1M\Omega$$

(c)

$$R_{in} = (r_s + R_s)/(1 - 1) \rightarrow \infty$$

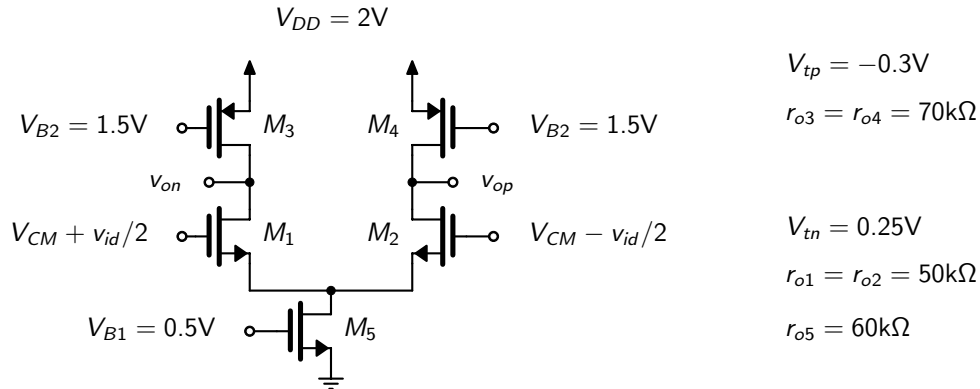**Q2.** Consider the circuit shown below where  $v_o$  is defined to be  $v_{op} - v_{on}$  and all pmos transistors have  $V_{ovp} = 0.2V$  while all nmos transistors have  $V_{ovn} = 0.25V$ . Also,  $V_{CM} = 1V$  and  $I_{D5} = 100\mu A$ .



[3]

(a) Find the small-signal gain  $v_o/v_{id}$ 

[2]

(b) Assuming the small-signal gain is so large that you can ignore the voltage swing on the input differential signal, find the max and minimum output voltage for  $v_{op}$  such that transistors remain in the active region.

## Solution

(a) This is a balanced circuit so we can find the gain of the half circuit  $M_1/M_3$  assuming the source of  $M_1$  is grounded.

In this circuit,  $v_o/v_{id} = -(v_{on}/(v_{id}/2))$  due to the following...

Define  $A_1 = v_{on}/(v_{id}/2)$  ( $A_1$  is a negative gain)

$$v_{on} = A_1(v_{id}/2) \text{ and } v_{op} = A_1(-v_{id}/2)$$

$$v_o = v_{op} - v_{on} = -A_1(v_{id}/2) - A_1(v_{id}/2) = -A_1 v_{id}$$

So  $v_o/v_{id} = -A_1$  where  $A_1$  is the negative gain of the half circuit.

Carrying on, we have

$$I_{D1} = I_{D5}/2 = (100e-6)/2 = 50\mu A$$

$$g_{m1} = (2 * I_{D1})/V_{ovn} = (2 * (50e-6))/(0.25) = 400\mu A/V$$

$$R_o = r_{o1} || r_{o3} = (50e3) || (70e3) = 29.17k\Omega$$

$$v_{on}/(v_{id}/2) = -g_{m1} * R_o = -(400e-6) * (29.17e3) = -11.67V/V$$

$$v_o/v_{id} = -v_{on}/(v_{id}/2) = -(-11.67) = 11.67V/V$$

$$v_o/v_{id} = 11.67\text{V/V}$$

(b) With the assumption of a very large small-signal gain, we can assume the input voltage remains at the common-mode voltage,  $V_{CM}$ .

The maximum voltage for  $v_{op}$  occurs when  $M_4$  is at the edge of triode/active. This occurs when the drain of  $M_4$  is one threshold voltage higher than the gate of  $M_4$  (in other words, higher by  $|V_{tp}|$ ).

$$v_{op,max} = V_{B2} + |V_{tp}| = (1.5) + |(-0.3)| = 1.8\text{V}$$

$$v_{op,max} = 1.8\text{V}$$


(another approach is to look for  $V_{SD}$  of  $M_4$  reaching the overdrive voltage)

The minimum voltage for  $v_{op}$  occurs when  $M_2$  is at the edge of triode/active. This occurs when the drain of  $M_2$  is one threshold voltage below the gate of  $M_2$

$$v_{op,min} = V_{CM} - V_{tn} = (1) - (0.25) = 0.75\text{V}$$

$$v_{op,min} = 0.75\text{V}$$

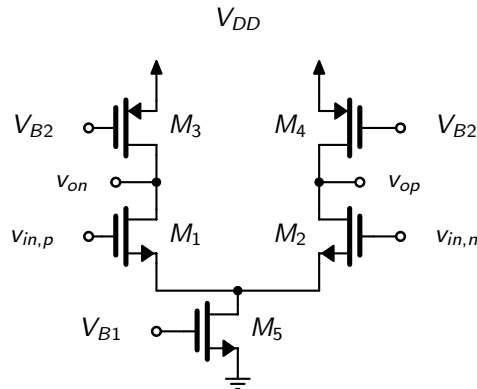- [5] **Q3.** Consider the circuit shown below where all nmos transistors have  $V_{ovn} = 0.15\text{V}$ , all pmos transistors have  $V_{ovp} = 0.3\text{V}$  and  $I_{D5} = 100\mu\text{A}$ . Assume  $M_1/M_2$  are perfectly matched but  $M_3/M_4$  have a  $V_t$  mismatch of  $\Delta V_t = 5\text{mV}$ .



Based on a small-signal analysis approach, find the input offset of the amplifier (the sign of the offset is unimportant).

## Solution

If all transistors are perfectly matched,  $I_{D1} = I_{D2} = I_{D3} = I_{D4} = 50\mu\text{A}$ .

$$g_{m1} = (2 * I_{D1}) / V_{ovn} = (2 * (50e - 6)) / (0.15) = 666.7\mu\text{A/V}$$

$$g_{m3} = (2 * I_{D3}) / V_{ovp} = (2 * (50e - 6)) / (0.3) = 333.3\mu\text{A/V}$$

If there is a  $\Delta V_t$  mismatch between  $M_3/M_4$ , then this is equivalent to  $M_3/M_4$  remaining matched but having a differential voltage of  $\Delta V_t$  being applied between the gates of  $M_3/M_4$ . In this way,  $M_3/M_4$  are a differential pair of transistors with an input differential signal of  $\Delta V_t$ . (Call this input signal 1). So we have

$$v_{o,1} = v_{op} - v_{on} = g_{m3}R_o\Delta V_t$$

$$\text{where } R_o = r_{o1} || r_{o3}$$

The input offset voltage,  $V_{os}$ , is defined to be the input differential voltage applied to the gates of  $M_1/M_2$  that will force  $v_o = 0$ . So this is a second input signal that would result in the output signal being

$$v_{o,2} = v_{op} - v_{on} = g_{m1}R_oV_{os}$$

and we require that

$$v_{o,1} + v_{o,2} = 0$$

which results in

$$g_{m3}R_o\Delta V_t = -g_{m1}R_oV_{os}$$

$$V_{os} = -(g_{m3}/g_{m1})\Delta V_t$$

and ignoring the sign, we have




$$V_{os} = (g_{m3}/g_{m1}) * \Delta V_t = ((333.3e - 6)/(666.7e - 6)) * (5e - 3) = 2.5mV$$

## Equation Sheet

Constants:  $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26 \text{ mV}$  at  $300 \text{ K}$ ;  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ ;  $k_{ox} = 3.9$ ;  $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$ ;  $\omega = 2\pi f$

NMOS:  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{tn} > 0$ ;  $v_{DS} \geq 0$ ;  $V_{ov} = V_{GS} - V_{tn}$   
 (triode)  $v_{DS} \leq V_{ov}$ ;  $v_D < v_G - V_{tn}$ ;  $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{DS} \geq V_{ov}$ ;  $i_D = 0.5k_n V_{ov}^2(1 + \lambda_n v_{DS})$ ;  $v_{DS}' = v_{DS} - V_{ov}$ ;  
 $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_n'|I_D)$

PMOS:  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{tp} < 0$ ;  $v_{SD} \geq 0$ ;  $V_{ov} = V_{SG} - |V_{tp}|$   
 (triode)  $v_{SD} \leq V_{ov}$ ;  $v_D > v_G + |V_{tp}|$ ;  $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{SD} \geq V_{ov}$ ;  $i_D = 0.5k_p V_{ov}^2(1 + |\lambda_p|v_{SD})$ ;  $v_{SD}' = v_{SD} - V_{ov}$   
 $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_p'|I_D)$

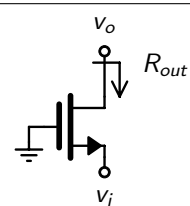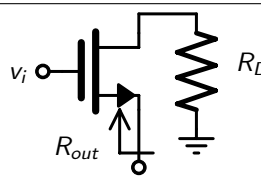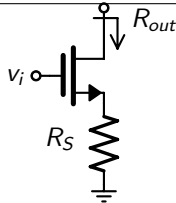

Accurate:  $R_{out} = r_o + (1 + g_m r_o)R_S$   
 $i_{sc} = (-g_m r_o v_i)/(r_o + (1 + g_m r_o)R_S)$   
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (r_o + R_D)/(1 + g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = (g_m r_o v_i)/(1 + g_m r_o)$

$R_{out} = r_o$   
 $i_{sc} = ((1 + g_m r_o)/r_o)v_i$   
 $v_{oc} = (1 + g_m r_o)v_i$

$g_m r_o \gg 1$   $R_{out} = (1 + g_m R_S)r_o$   
 $i_{sc} = -v_i/((1/g_m) + R_S)$   
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (1/g_m) + (R_D/g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = v_i$

$R_{out} = r_o$   
 $i_{sc} = g_m v_i$   
 $v_{oc} = g_m r_o v_i$

Diff Pair:  $A_d = g_m R_D$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$ ;  
 $V_{OS} = \Delta V_t$ ;  $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$ ;  $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$   
 Large signal:  $i_{D1} = (I/2) + (I/V_{ov})(v_{id}/2)(1 - (v_{id}/2V_{ov})^2)^{1/2}$

1st order: step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ ;  
 unity gain freq for  $T(s) = A_M/(1 + (s/\omega_{3dB}))$  for  $A_M \gg 1 \Rightarrow \omega_t \simeq |A_M|\omega_{3dB}$

Freq: for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$

OTC estimate  $\omega_H \simeq 1/(\sum \tau_i)$ ; dominant pole estimate  $\omega_H \simeq 1/(\tau_{max})$

STC estimate  $\omega_L \simeq \sum 1/\tau_i$ ; dominant pole estimate  $\omega_L \simeq 1/(\tau_{min})$

Miller:  $Z_1 = Z/(1 - K)$ ;  $Z_2 = Z/(1 - 1/K)$

Mos caps:  $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$ ;  $C_{gd} = WL_{ov}C_{ox}$ ;  $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$ ;  
 $\omega_t = g_m/(C_{gs} + C_{gd})$ ; for  $C_{gs} \gg C_{gd} \Rightarrow f_t \simeq (3\mu V_{ov})/(4\pi L^2)$

Feedback:  $A_f = A/(1 + A\beta)$ ;  $x_i = (1/(1 + A\beta))x_s$ ;  $dA_f/A_f = (1/(1 + A\beta))dA/A$ ;  $\omega_{Hf} = \omega_H(1 + A\beta)$ ;  $\omega_{Lf} = \omega_L/(1 + A\beta)$ ;  
 Loop Gain  $L \equiv -s_f/s_t$ ;  $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$ ;  $Z_{port} = Z_{p^\circ}((1 + L_s)/(1 + L_o))$ ;  $PM = \angle L(j\omega_t) + 180$ ;  
 $GM = -|L(j\omega_{180})|_{db}$ ;  
 Pole splitting  $\omega_{p1}' \simeq 1/(g_m R_2 C_f R_1)$ ;  $\omega_{p2}' \simeq (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair:  $s^2 + (\omega_o/Q)s + \omega_o^2$ ;  $Q \leq 0.5 \Rightarrow$  real poles;  $Q > 1/\sqrt{2} \Rightarrow$  freq resp peaking

Power Amps: Class A:  $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$ ; Class B:  $\eta = (\pi/4)(\hat{V}_O/V_{CC})$ ;  $P_{DN\_max} = V_{CC}^2/(\pi^2 R_L)$ ;  
 Class AB:  $i_{n1}p = I_Q^2$ ;  $I_Q = (I_S/\alpha)e^{V_{BB}/(2V_T)}$ ;  $i_n^2 - i_L i_n - I_Q^2 = 0$

2-stage opamp:  $\omega_{p1} \simeq (R_1 G_{m2} R_2 C_c)^{-1}$ ;  $\omega_{p2} = G_{m2}/C_2$ ;  $\omega_z = (C_c(1/G_{m2} - R))^{-1}$ ;  
 $SR = I/C_c = \omega_t V_{ov1}$ ; will not SR limit if  $\omega_t \hat{V}_O < SR$