

**University of Toronto**

**Term Test 2**

Date — Nov 21, 2022: 12:10pm

Duration — 50 min

ECE 331 — Analog Electronics

Lecturer — D. Johns

---

**ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY**

- Equation sheet is on the last page of this test.
- Unless otherwise stated, assume  $g_m r_o \gg 1$
- Notation: 15e3 is equivalent to  $15 \times 10^3$
- Non-programmable calculator is allowed; No other aids are allowed
- Grading indicated by [ ]. Attempt all questions since a blank answer will certainly get 0.
- If you need more space, write on the back of pages.

---

**Last Name:** \_\_\_\_\_

**First Name:** \_\_\_\_\_

**Student #:** \_\_\_\_\_

Question	1	2	3	Total
Points:	5	5	5	15
Score:				

### Grading Table

**Q1.** A transfer-function has the equation

$$T(s) = \frac{1e4(1 + s/1.2e5)}{(1 + s/1e2)(1 + s/3e3)}$$

- [3] (a) Estimate the gain (in dB) at  $\omega = 1.2\text{Mrad/s}$ . For this estimate, assume  $\omega = 1.2\text{Mrad/s}$  is much greater than all the pole/zero frequencies.
- [2] (b) Estimate the phase (in degrees) at  $\omega = 1.2\text{Mrad/s}$ . For this estimate, take into account the zero at  $1.2e5$  while assuming  $\omega = 1.2\text{Mrad/s}$  is much greater than the pole frequencies.

### Solution

(a) Since  $\omega = 1.2\text{Mrad/s}$  is much greater than each of  $1.2e5$ ,  $1e2$ ,  $3e3$  so we can ignore the "1" in each term so

$$|T(j\omega)| \approx \frac{|1e4(j\omega/1.2e5)|}{|(j\omega/1e2)(j\omega/3e3)|}$$

$$|T(j\omega)| \approx \frac{|1e4(j1.2e6/1.2e5)|}{|(j1.2e6/1e2)(j1.2e6/3e3)|}$$

$$|T(j\omega)| \approx 2.08e-2$$

and in dB, we have

$$T_{dB} = 20 * \log_{10}(|T(j\omega)|) = -33.6 \text{ dB}$$

(b) Since  $\omega = 1.2\text{Mrad/s}$  is much greater than each of  $1e2$ ,  $3e3$  we can write

$$\angle T(j\omega) = \angle(1e4) + \angle(1 + j\omega/1.2e5) - \angle(1 + j\omega/1e2) - \angle(1 + j\omega/3e3)$$

$$\angle T(j\omega) \approx 0^\circ + \angle(1 + j1.2e6/1.2e5) - 90^\circ - 90^\circ$$


where we have used  $\angle(1 + jk) \approx 90^\circ$  when  $k \gg 1$

$$\angle T(j\omega) \approx \arctan[(1.2e6/1.2e5)/(1)] - 180^\circ$$

$$\angle T(j\omega) \approx 84.29^\circ - 180^\circ$$

$$\angle T(j\omega) \approx -95.71^\circ$$

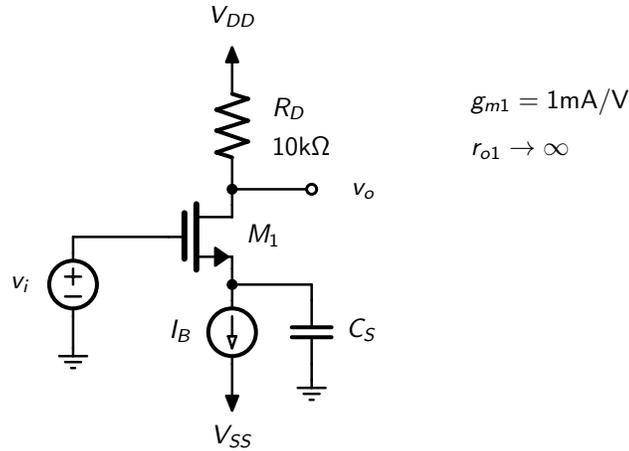**Q2.** Consider the amplifier shown below where the current source  $I_B$  is ideal.



- [4] (a) Find the value for  $C_S$  so that the low frequency cutoff is at 1kHz.  
 [1] (b) Is there a zero in the transfer-function? If so, what is the frequency location for the zero?

## Solution

(a) The pole frequency for  $C_S$  is

$$F_{3dB} = 1/(2\pi C_S R_x)$$

where  $R_x$  is the small-signal resistance seen by  $C_S$ .

Since  $r_{o1} \rightarrow \infty$ , the impedance looking into the source of  $M_1$  is  $1/g_{m1}$  and since the current source  $I_B$  is ideal, we have


$$R_x = 1/g_{m1} = 1/(1e-3) = 1k\Omega$$

Using the  $F_{3dB}$  equation above, we find  $C_S$  as

$$C_S = 1/(2 * \pi * F_{3dB} * R_x) = 1/(2 * (3.142) * (1e3) * (1e3)) = 159.2nF$$

(b) Since the current source is ideal (with infinite output impedance), the gain for this circuit is zero at dc. As a result, there is a zero in the transfer-function and the zero frequency is at 0 Hz.

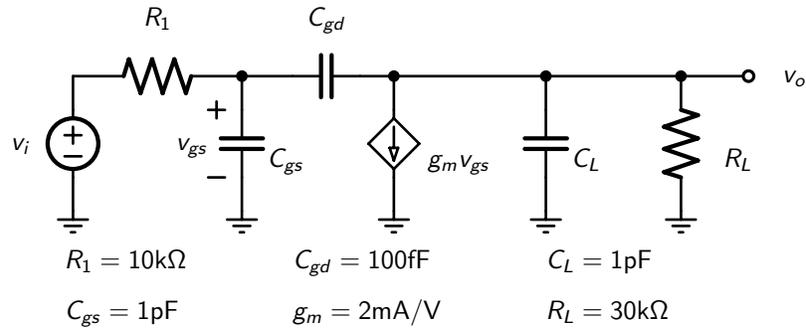**Q3.** The small signal model for a common-source amp is shown below.




- [2] (a) Find the midBand gain  $A_M$
- [3] (b) Use Millers Theorem to find the 2 pole locations,  $F_1$  and  $F_2$  in Hz.
- 

## Solution

(a) For the midband gain, we assume all the capacitors limiting the high freq gain are open circuited (in this case, all the capacitors in this circuit).

$$A_M = -g_m * R_L = -(2e-3) * (30e3) = -60\text{V/V}$$

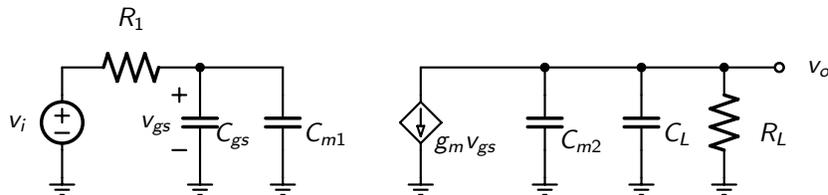(b) Using Millers Theorem, we break  $C_{gd}$  into 2 grounded capacitors,  $C_{m1}/C_{m2}$



$$C_{m1} = C_{gd} * (1 - A_M) = (100e-15) * (1 - (-60)) = 6.1\text{pF}$$

$$C_{m2} = C_{gd} * (1 - (1/A_M)) = (100e-15) * (1 - (1/(-60))) = 101.7\text{fF}$$

So we have 2 poles and the 2 nodes in the circuit resulting in

$$F_1 = 1/(2 * \pi * (C_{gs} + C_{m1}) * R_1) = 1/(2 * (3.142) * ((1e-12) + (6.1e-12)) * (10e3)) = 2.242\text{MHz}$$




$$F_2 = 1/(2 * \pi * (C_{m2} + C_L) * R_L) = 1/(2 * (3.142) * ((101.7e-15) + (1e-12)) * (30e3)) = 4.816\text{MHz}$$

## Equation Sheet

Constants:  $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$ ;  $q = 1.602 \times 10^{-19} \text{ C}$ ;  $V_T = kT/q \approx 26\text{mV}$  at 300 K;  $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$ ;  $k_{ox} = 3.9$ ;  $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$ ;  $\omega = 2\pi f$

NMOS:  $k_n = \mu_n C_{ox}(W/L)$ ;  $V_{tn} > 0$ ;  $v_{DS} \geq 0$ ;  $V_{ov} = V_{GS} - V_{tn}$   
 (triode)  $v_{DS} \leq V_{ov}$ ;  $v_D < v_G - V_{tn}$ ;  $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{DS} \geq V_{ov}$ ;  $i_D = 0.5k_n V_{ov}^2(1 + \lambda_n v_{DS})$ ;  $v_{DS}' = v_{DS} - V_{ov}$ ;  
 $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_n'|I_D)$

PMOS:  $k_p = \mu_p C_{ox}(W/L)$ ;  $V_{tp} < 0$ ;  $v_{SD} \geq 0$ ;  $V_{ov} = V_{SG} - |V_{tp}|$   
 (triode)  $v_{SD} \leq V_{ov}$ ;  $v_D > v_G + |V_{tp}|$ ;  $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$ ;  $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$   
 (active)  $v_{SD} \geq V_{ov}$ ;  $i_D = 0.5k_p V_{ov}^2(1 + |\lambda_p|v_{SD})$ ;  $v_{SD}' = v_{SD} - V_{ov}$   
 $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$ ;  $r_s = 1/g_m$ ;  $r_o = L/(|\lambda_p'|I_D)$

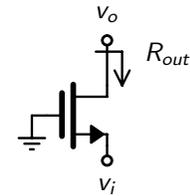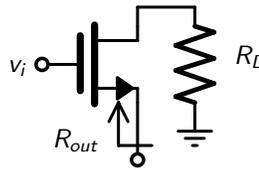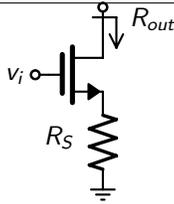

Accurate:  $R_{out} = r_o + (1 + g_m r_o)R_S$   
 $i_{sc} = (-g_m r_o v_i)/(r_o + (1 + g_m r_o)R_S)$   
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (r_o + R_D)/(1 + g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = (g_m r_o v_i)/(1 + g_m r_o)$

$R_{out} = r_o$   
 $i_{sc} = ((1 + g_m r_o)/r_o)v_i$   
 $v_{oc} = (1 + g_m r_o)v_i$

$g_m r_o \gg 1$   $R_{out} = (1 + g_m R_S)r_o$   
 $i_{sc} = -v_i/((1/g_m) + R_S)$   
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (1/g_m) + (R_D/g_m r_o)$   
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$   
 $v_{oc} = v_i$

$R_{out} = r_o$   
 $i_{sc} = g_m v_i$   
 $v_{oc} = g_m r_o v_i$

Diff Pair:  $A_d = g_m R_D$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$ ;  $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$ ;

$V_{OS} = \Delta V_t$ ;  $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$ ;  $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$

Large signal:  $i_{D1} = (I/2) + (I/V_{ov})(v_{id}/2)(1 - (v_{id}/2V_{ov})^2)^{1/2}$

1st order: step response  $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$ ;

unity gain freq for  $T(s) = A_M/(1 + (s/\omega_{3dB}))$  for  $A_M \gg 1 \Rightarrow \omega_t \simeq |A_M|\omega_{3dB}$

Freq: for real axis poles/zeros  $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$

OTC estimate  $\omega_H \simeq 1/(\sum \tau_i)$ ; dominant pole estimate  $\omega_H \simeq 1/(\tau_{max})$

STC estimate  $\omega_L \simeq \sum 1/\tau_i$ ; dominant pole estimate  $\omega_L \simeq 1/(\tau_{min})$

Miller:  $Z_1 = Z/(1 - K)$ ;  $Z_2 = Z/(1 - 1/K)$

Mos caps:  $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$ ;  $C_{gd} = WL_{ov}C_{ox}$ ;  $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$ ;

$\omega_t = g_m/(C_{gs} + C_{gd})$ ; for  $C_{gs} \gg C_{gd} \Rightarrow f_t \simeq (3\mu V_{ov})/(4\pi L^2)$

Feedback:  $A_f = A/(1 + A\beta)$ ;  $x_i = (1/(1 + A\beta))x_s$ ;  $dA_f/A_f = (1/(1 + A\beta))dA/A$ ;  $\omega_{Hf} = \omega_H(1 + A\beta)$ ;  $\omega_{Lf} = \omega_L/(1 + A\beta)$ ;

Loop Gain  $L \equiv -s_f/s_t$ ;  $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$ ;  $Z_{port} = Z_{p^\circ}((1 + L_S)/(1 + L_O))$ ;  $PM = \angle L(j\omega_t) + 180$ ;  
 $GM = -|L(j\omega_{180})|_{db}$ ;

Pole splitting  $\omega_{p1}' \simeq 1/(g_m R_2 C_f R_1)$ ;  $\omega_{p2}' \simeq (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair:  $s^2 + (\omega_o/Q)s + \omega_o^2$ ;  $Q \leq 0.5 \Rightarrow$  real poles;  $Q > 1/\sqrt{2} \Rightarrow$  freq resp peaking

Power Amps: Class A:  $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$ ; Class B:  $\eta = (\pi/4)(\hat{V}_O/V_{CC})$ ;  $P_{DN,max} = V_{CC}^2/(\pi^2 R_L)$ ;

Class AB:  $i_n i_p = I_Q^2$ ;  $I_Q = (I_S/\alpha)e^{V_{BB}/(2V_T)}$ ;  $i_n^2 - i_L i_n - I_Q^2 = 0$

2-stage opamp:  $\omega_{p1} \simeq (R_1 G_{m2} R_2 C_c)^{-1}$ ;  $\omega_{p2} = G_{m2}/C_2$ ;  $\omega_z = (C_c(1/G_{m2} - R))^{-1}$ ;

$SR = I/C_c = \omega_t V_{ov1}$ ; will not SR limit if  $\omega_t \hat{V}_O < SR$