

University of Toronto

Term Test 2

Date — Nov 20, 2023: 4:10pm

Duration — 50 min

ECE 331 — Analog Electronics

Lecturer — D. Johns

ANSWER QUESTIONS ON THESE SHEETS USING BACKS IF NECESSARY

- Equation sheet is on the last page of this test.
- Notation: 15e3 is equivalent to 15×10^3
- Non-programmable calculator is allowed; No other aids are allowed
- Write using a non-erasable ink.
- Grading indicated by []. Attempt all questions since a blank answer will certainly get 0.

Last Name: _____


First Name: _____

Student #: _____

Question	1	2	3	Total
Points:	5	5	5	15
Score:				

Grading Table

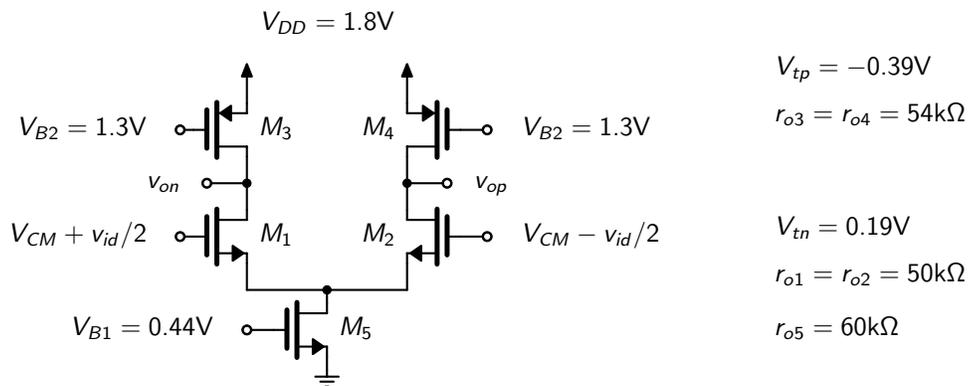Q1. Consider the circuit shown below where v_o is defined to be $v_{op} - v_{on}$ and all pmos transistors have $V_{ovp} = 0.11V$ while all nmos transistors have $V_{ovn} = 0.25V$. Also, $V_{CM} = 0.88V$ and $I_{D5} = 100\mu A$.



- [3] (a) Find the small-signal gain v_o/v_{id}
- [2] (b) Assuming the small-signal gain is so large that you can ignore the voltage swing on the input differential signal, find the max and minimum output voltage for v_{op} such that transistors remain in the active region.

Solution

(a) This is a balanced circuit so we can find the gain of the half circuit M_1/M_3 assuming the source of M_1 is grounded.

In this circuit, $v_o/v_{id} = -(v_{on}/(v_{id}/2))$ due to the following...

Define $A_1 = v_{on}/(v_{id}/2)$ (A_1 is a negative gain)

$$v_{on} = A_1(v_{id}/2) \text{ and } v_{op} = A_1(-v_{id}/2)$$

$$v_o = v_{op} - v_{on} = -A_1(v_{id}/2) - A_1(v_{id}/2) = -A_1 v_{id}$$

So $v_o/v_{id} = -A_1$ where A_1 is the negative gain of the half circuit.

Carrying on, we have

$$I_{D1} = I_{D5}/2 = (100\mu A)/2 = 50\mu A$$

$$g_{m1} = (2 * I_{D1})/V_{ovn} = (2 * (50\mu A))/(0.25) = 400\mu A/V$$

$$R_o = r_{o1} || r_{o3} = (50k\Omega) || (54k\Omega) = 25.96k\Omega$$

$$v_{on}/(v_{id}/2) = -g_{m1} * R_o = -(400e-6) * (25.96e3) = -10.38V/V$$

$$v_o/v_{id} = -v_{on}/(v_{id}/2) = -(-10.38) = 10.38V/V$$

$$v_o/v_{id} = 10.38V/V$$

(b) With the assumption of a very large small-signal gain, we can assume the input voltage remains at the common-mode voltage, V_{CM} .

The maximum voltage for v_{op} occurs when M_4 is at the edge of triode/active. This occurs when the drain of M_4 is one threshold voltage higher than the gate of M_4 (in other words, higher by $|V_{tp}|$).

$$v_{op,max} = V_{B2} + |V_{tp}| = (1.3) + |(-0.39)| = 1.69V$$

$$v_{op,max} = 1.69V$$

(another approach is to look for V_{SD} of M_4 reaching the overdrive voltage)

The minimum voltage for v_{op} occurs when M_2 is at the edge of triode/active. This occurs when the drain of M_2 is one threshold voltage below the gate of M_2

$$v_{op,min} = V_{CM} - V_{tn} = (0.88) - (0.19) = 0.69V$$

$$v_{op,min} = 0.69V$$

Q2. A transfer-function has the equation

$$T(s) = \frac{8.8e3(1 + s/1.19e5)}{(1 + s/8.8e1)(1 + s/2.29e3)}$$

- [3] (a) Estimate the gain (in dB) at $\omega = 1.19\text{Mrad/s}$. For this estimate, assume $\omega = 1.19\text{Mrad/s}$ is much greater than all the pole/zero frequencies.
- [2] (b) Estimate the phase (in degrees) at $\omega = 1.19\text{Mrad/s}$. For this estimate, take into account the zero at $1.19e5$ while assuming $\omega = 1.19\text{Mrad/s}$ is much greater than the pole frequencies.
-

Solution

(a) Since $\omega = 1.19\text{Mrad/s}$ is much greater than each of $1.19e5, 8.8e1, 2.29e3$ so we can ignore the "1" in each term so

$$|T(j\omega)| \approx \frac{|8.8e3(j\omega/1.19e5)|}{|(j\omega/8.8e1)(j\omega/2.29e3)|}$$

$$|T(j\omega)| \approx \frac{|8.8e3(j1.19e6/1.19e5)|}{|(j1.19e6/8.8e1)(j1.19e6/2.29e3)|}$$

$$|T(j\omega)| \approx 1.25e-2$$

and in dB, we have

$$T_{dB} = 20 * \log_{10}(|T(j\omega)|) = -38 \text{ dB}$$

(b) Since $\omega = 1.19\text{Mrad/s}$ is much greater than each of $8.8e1, 2.29e3$ we can write

$$\angle T(j\omega) = \angle(8.8e3) + \angle(1 + j\omega/1.19e5) - \angle(1 + j\omega/8.8e1) - \angle(1 + j\omega/2.29e3)$$

$$\angle T(j\omega) \approx 0^\circ + \angle(1 + j1.19e6/1.19e5) - 90^\circ - 90^\circ$$


where we have used $\angle(1 + jk) \approx 90^\circ$ when $k \gg 1$

$$\angle T(j\omega) \approx \arctan[(1.19e6/1.19e5)/(1)] - 180^\circ$$

$$\angle T(j\omega) \approx 84.29^\circ - 180^\circ$$

$$\angle T(j\omega) \approx -95.71^\circ$$

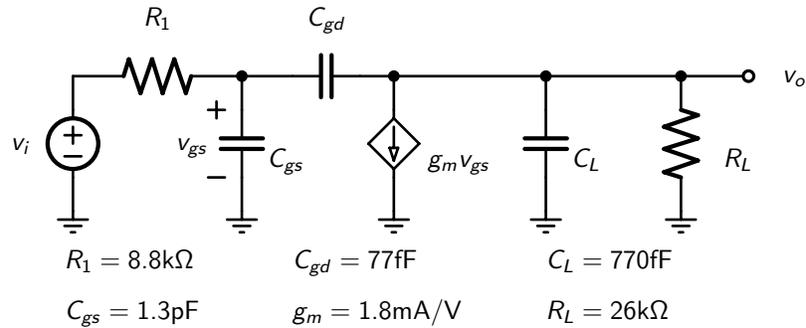Q3. The small signal model for a common-source amp is shown below.




- [2] (a) Find the midBand gain A_M
- [3] (b) Use Millers Theorem to find the 2 pole locations, F_1 and F_2 in Hz.
-

Solution

(a) For the midband gain, we assume all the capacitors limiting the high freq gain are open circuited (in this case, all the capacitors in this circuit).

$$A_M = -g_m * R_L = -(1.8e-3) * (26e3) = -46.8\text{V/V}$$

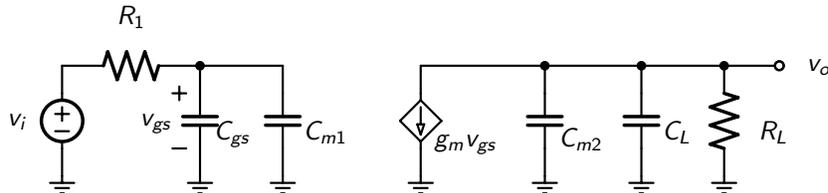(b) Using Millers Theorem, we break C_{gd} into 2 grounded capacitors, C_{m1}/C_{m2}



$$C_{m1} = C_{gd} * (1 - A_M) = (77e-15) * (1 - (-46.8)) = 3.681\text{pF}$$

$$C_{m2} = C_{gd} * (1 - (1/A_M)) = (77e-15) * (1 - (1/(-46.8))) = 78.65\text{fF}$$

So we have 2 poles and the 2 nodes in the circuit resulting in

$$F_1 = 1/(2 * \pi * (C_{gs} + C_{m1}) * R_1) = 1/(2 * (3.142) * ((1.3e-12) + (3.681e-12)) * (8.8e3)) = 3.631\text{MHz}$$




$$F_2 = 1/(2 * \pi * (C_{m2} + C_L) * R_L) = 1/(2 * (3.142) * ((78.65e-15) + (770e-15)) * (26e3)) = 7.213\text{MHz}$$

Equation Sheet

Constants: $k = 1.38 \times 10^{-23} \text{ J K}^{-1}$; $q = 1.602 \times 10^{-19} \text{ C}$; $V_T = kT/q \approx 26 \text{ mV}$ at 300 K; $\epsilon_0 = 8.85 \times 10^{-12} \text{ F m}^{-1}$; $k_{ox} = 3.9$; $C_{ox} = (k_{ox}\epsilon_0)/t_{ox}$; $\omega = 2\pi f$

NMOS: $k_n = \mu_n C_{ox}(W/L)$; $V_{tn} > 0$; $v_{DS} \geq 0$; $V_{ov} = V_{GS} - V_{tn}$
 (triode) $v_{DS} \leq V_{ov}$; $v_D < v_G - V_{tn}$; $i_D = k_n(V_{ov}v_{DS} - (v_{DS}^2/2))$; $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$
 (active) $v_{DS} \geq V_{ov}$; $i_D = 0.5k_n V_{ov}^2(1 + \lambda_n v_{DS})$; $v_{DS} = v_{DS} - V_{ov}$;
 $g_m = k_n V_{ov} = 2I_D/V_{ov} = \sqrt{2k_n I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda_n'|I_D)$

PMOS: $k_p = \mu_p C_{ox}(W/L)$; $V_{tp} < 0$; $v_{SD} \geq 0$; $V_{ov} = V_{SG} - |V_{tp}|$
 (triode) $v_{SD} \leq V_{ov}$; $v_D > v_G + |V_{tp}|$; $i_D = k_p(V_{ov}v_{SD} - (v_{SD}^2/2))$; $r_{ds} = 1/(\mu_p C_{ox}(W/L)V_{ov})$
 (active) $v_{SD} \geq V_{ov}$; $i_D = 0.5k_p V_{ov}^2(1 + |\lambda_p|v_{SD})$; $v_{SD} = v_{SD} - V_{ov}$
 $g_m = k_p V_{ov} = 2I_D/V_{ov} = \sqrt{2k_p I_D}$; $r_s = 1/g_m$; $r_o = L/(|\lambda_p'|I_D)$

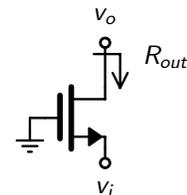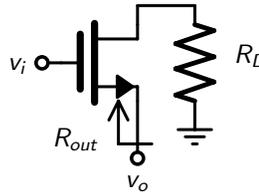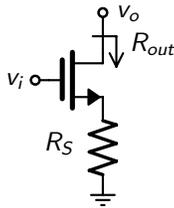

Accurate: $R_{out} = r_o + (1 + g_m r_o)R_S$
 $i_{sc} = (-g_m r_o v_i)/(r_o + (1 + g_m r_o)R_S)$
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (r_o + R_D)/(1 + g_m r_o)$
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$
 $v_{oc} = (g_m r_o v_i)/(1 + g_m r_o)$

$R_{out} = r_o$
 $i_{sc} = ((1 + g_m r_o)/r_o)v_i$
 $v_{oc} = (1 + g_m r_o)v_i$

$g_m r_o \gg 1$ $R_{out} = (1 + g_m R_S)r_o$
 $i_{sc} = -v_i/((1/g_m) + R_S)$
 $v_{oc} = -g_m r_o v_i$

$R_{out} = (1/g_m) + (R_D/g_m r_o)$
 $i_{sc} = (g_m r_o v_i)/(r_o + R_D)$
 $v_{oc} = v_i$

$R_{out} = r_o$
 $i_{sc} = g_m v_i$
 $v_{oc} = g_m r_o v_i$

Diff Pair: $A_d = g_m R_D$; $A_{CM} = -(R_D/(2R_{SS}))(\Delta R_D/R_D)$; $A_{CM} = -(R_D/(2R_{SS}))(\Delta g_m/g_m)$;
 $V_{OS} = \Delta V_t$; $V_{OS} = (V_{OV}/2)(\Delta R_D/R_D)$; $V_{OS} = (V_{OV}/2)(\Delta(W/L)/(W/L))$
 Large signal: $i_{D1} = (I/2) + (I/V_{ov})(v_{id}/2)(1 - (v_{id}/2V_{ov})^2)^{1/2}$

1st order: step response $y(t) = Y_\infty - (Y_\infty - Y_{0+})e^{-t/\tau}$;
 unity gain freq for $T(s) = A_M/(1 + (s/\omega_{3dB}))$ for $A_M \gg 1 \Rightarrow \omega_t \simeq |A_M|\omega_{3dB}$

Freq: for real axis poles/zeros $T(s) = k_{dc} \frac{(1 + s/z_1)(1 + s/z_2) \dots (1 + s/z_m)}{(1 + s/\omega_1)(1 + s/\omega_2) \dots (1 + s/\omega_n)}$

OTC estimate $\omega_H \simeq 1/(\sum \tau_i)$; dominant pole estimate $\omega_H \simeq 1/(\tau_{max})$

STC estimate $\omega_L \simeq \sum 1/\tau_i$; dominant pole estimate $\omega_L \simeq 1/(\tau_{min})$

Miller: $Z_1 = Z/(1 - K)$; $Z_2 = Z/(1 - 1/K)$

Mos caps: $C_{gs} = (2/3)WLC_{ox} + WL_{ov}C_{ox}$; $C_{gd} = WL_{ov}C_{ox}$; $C_{db} = C_{db0}/\sqrt{1 + V_{db}/V_0}$;
 $\omega_t = g_m/(C_{gs} + C_{gd})$; for $C_{gs} \gg C_{gd} \Rightarrow f_t \simeq (3\mu V_{ov})/(4\pi L^2)$

Feedback: $A_f = A/(1 + A\beta)$; $x_i = (1/(1 + A\beta))x_s$; $dA_f/A_f = (1/(1 + A\beta))dA/A$; $\omega_{Hf} = \omega_H(1 + A\beta)$; $\omega_{Lf} = \omega_L/(1 + A\beta)$;
 Loop Gain $L \equiv -s_f/s_t$; $A_f = A_\infty(L/(1 + L)) + d/(1 + L)$; $Z_{port} = Z_{po}((1 + L_S)/(1 + L_O))$; $PM = \angle L(j\omega_t) + 180$;
 $GM = -|L(j\omega_{180})|_{db}$;
 Pole splitting $\omega'_{p1} \simeq 1/(g_m R_2 C_f R_1)$; $\omega'_{p2} \simeq (g_m C_f)/(C_1 C_2 + C_f(C_1 + C_2))$

Pole Pair: $s^2 + (\omega_o/Q)s + \omega_o^2$; $Q \leq 0.5 \Rightarrow$ real poles; $Q > 1/\sqrt{2} \Rightarrow$ freq resp peaking

Power Amps: Class A: $\eta = (1/4)(\hat{V}_O/IR_L)(\hat{V}_O/V_{CC})$; Class B: $\eta = (\pi/4)(\hat{V}_O/V_{CC})$; $P_{DN_max} = V_{CC}^2/(\pi^2 R_L)$;
 Class AB: $i_{n1}i_p = I_Q^2$; $I_Q = (I_S/\alpha)e^{V_{BB}/(2V_T)}$; $i_n^2 - i_L i_n - I_Q^2 = 0$

2-stage opamp: $\omega_{p1} \simeq (R_1 G_{m2} R_2 C_c)^{-1}$; $\omega_{p2} = G_{m2}/C_2$; $\omega_z = (C_c(1/G_{m2} - R))^{-1}$;
 $SR = I/C_c = \omega_t V_{ov1}$; will not SR limit if $\omega_t \hat{V}_O < SR$