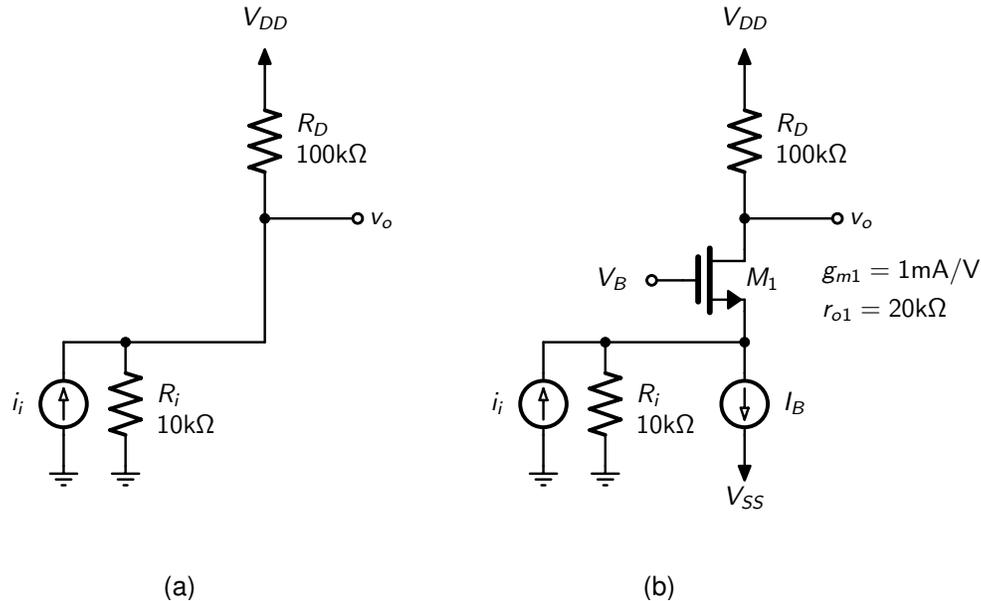


Problem Set 3C - MultiStage

Question 1

It is desired to create a voltage output from a small current source input (say from a photodetector). Shown below, the small current source input and its output impedance is shown as i_i and R_i , respectively. The figure below shows 2 circuits. Circuit (a) does not make use of a transistor while circuit (b) makes use of one transistor. V_B is a dc bias voltage. Also, assume the current source I_B is ideal.




- (a) For circuit (a), find the small-signal gain, v_o/i_i . Next, find the change in v_o when $i_{i,max} = 10\mu\text{A}$.
 (b) For circuit (b), find the small-signal gain, v_o/i_i . Next, find the change in v_o when $i_{i,max} = 10\mu\text{A}$
 (c) What is the small-signal gain improvement for circuit (b) over circuit (a)?

Answer

- (a) $(v_o/i_i)_a = 9.091\text{k}\Omega$; $v_{o,max} = 90.91\text{mV}$ (b) $(v_o/i_i)_b = 63.64\text{k}\Omega$; $v_{o,max} = 0.6364\text{V}$ (c) $k = 7$

Question 2

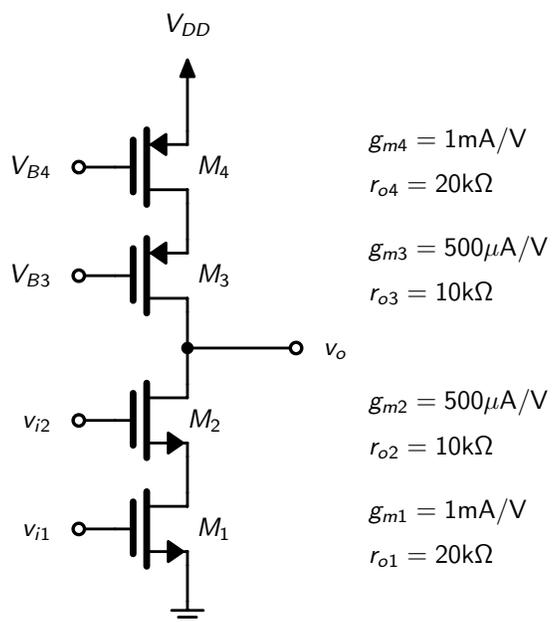

For the circuit above

- (a) Find v_o/v_{i1} assuming v_{i2} is a dc bias voltage.
 (b) Find v_o/v_{i2} assuming v_{i1} is a dc bias voltage.

Answer

- (a) $v_o/v_{i1} = -60\text{V/V}$ (b) $v_o/v_{i2} = -2.5\text{V/V}$