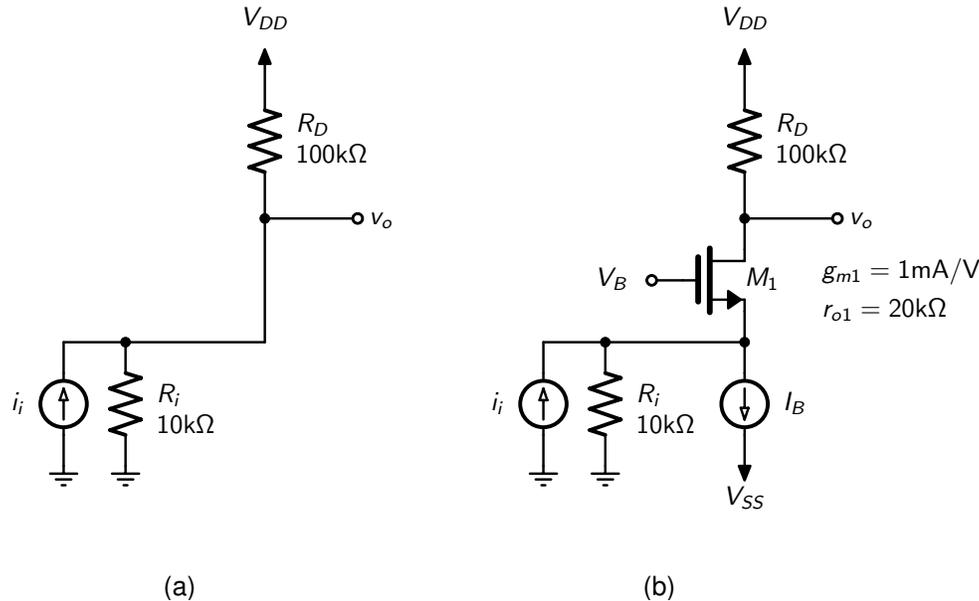


Problem Set 3C - MultiStage

Question 1

It is desired to create a voltage output from a small current source input (say from a photodetector). Shown below, the small current source input and its output impedance is shown as i_i and R_i , respectively. The figure below shows 2 circuits. Circuit (a) does not make use of a transistor while circuit (b) makes use of one transistor. V_B is a dc bias voltage. Also, assume the current source I_B is ideal.



- (a) For circuit (a), find the small-signal gain, v_o/i_i . Next, find the change in v_o when $i_{i,max} = 10\mu\text{A}$.
 (b) For circuit (b), find the small-signal gain, v_o/i_i . Next, find the change in v_o when $i_{i,max} = 10\mu\text{A}$
 (c) What is the small-signal gain improvement for circuit (b) over circuit (a)?

Solution

(a) $R_o = R_i || R_D = (10e3) || (100e3) = 9.091k\Omega$

$i_{sc} = i_i$ and we have $v_o = i_i R_o$ resulting in

$$(v_o/i_i)_a = R_o = (9.091e3) = 9.091k\Omega$$

For $i_{i,max} = 10\mu\text{A}$, we have

$$v_{o,max} = i_{i,max} * ((v_o/i_i)_a) = (10e-6) * ((9.091e3)) = 90.91\text{mV}$$

(b) We can start by finding the output impedance, R_o


Define R_{dx} to be the small signal resistance looking into the drain of M_1

$$R_{dx} = r_{o1} + (1 + g_{m1} * r_{o1}) * R_i = (20e3) + (1 + (1e-3) * (20e3)) * (10e3) = 230k\Omega$$

$$R_o = R_{dx} || R_D = (230e3) || (100e3) = 69.7k\Omega$$

Next, we find the short circuit current, i_{sc}

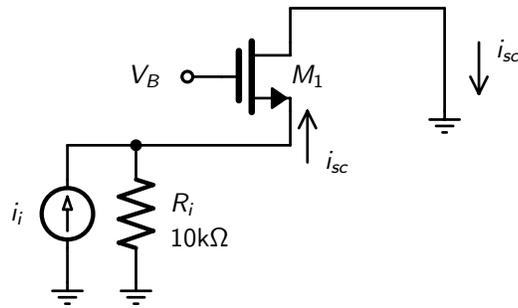We have the following small circuit circuit



Defining R_{sx} to be the impedance looking in to the source of M_1 we have

$$R_{sx} = (1/g_{m1}) || r_{o1} = (1/(1e-3)) || (20e3) = 952.4\Omega$$

and we see a current divider, so we have

$$i_{sc}/i_i = R_i/(R_i + R_{sx}) = (10e3)/((10e3) + (952.4)) = 0.913A/A \text{ leading to}$$


$$(v_o/i_i)_b = i_{sc}/i_i * R_o = (0.913) * (69.7e3) = 63.64k\Omega$$

$$v_{o,max} = i_{i,max} * ((v_o/i_i)_b) = (10e-6) * ((63.64e3)) = 0.6364V$$

(c) The improvement, k , in small-signal gain is

$$k = (v_o/i_i)_b / (v_o/i_i)_a = (63.64e3) / (9.091e3) = 7$$

Question 2

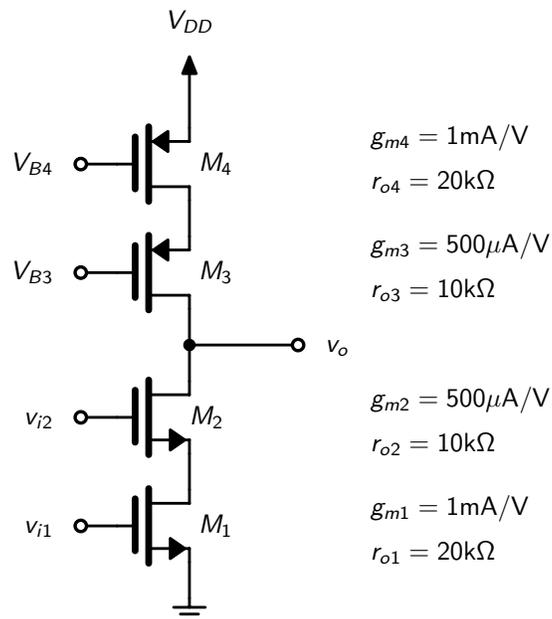

For the circuit above

(a) Find v_o/v_{i1} assuming v_{i2} is a dc bias voltage.

(b) Find v_o/v_{i2} assuming v_{i1} is a dc bias voltage.

Solution

(a) Define R_{op} to be the impedance looking up into the drain of M_3 and define R_{on} to be the impedance looking down into the drain of M_2


$$R_{op} = r_{o3} + (1 + g_{m3} * r_{o3}) * r_{o4} = (10e3) + (1 + (500e-6) * (10e3)) * (20e3) = 130k\Omega$$

$$R_{on} = r_{o2} + (1 + g_{m2} * r_{o2}) * r_{o1} = (10e3) + (1 + (500e-6) * (10e3)) * (20e3) = 130k\Omega$$

Define R_o to be the impedance to ground at node v_o

$$R_o = R_{op} || R_{on} = (130e3) || (130e3) = 65k\Omega$$

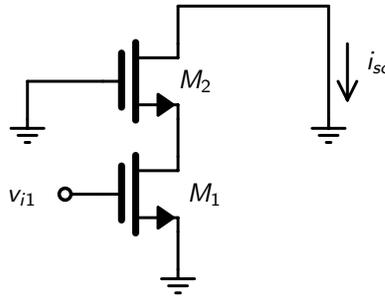For i_{sc} , we have the following circuit



Define R_{S2} to be the impedance looking up into the source of M_2

$$R_{S2} = (1/g_{m2}) || r_{o2} = (1/(500e-6)) || (10e3) = 1.667k\Omega$$

The drain current of M_1 current divides between R_{S2} and r_{o1} resulting in


$$G_{Ma} = -g_{m1} * (r_{o1}) / (r_{o1} + R_{S2}) = -(1e-3) * ((20e3)) / ((20e3) + (1.667e3)) = -923.1e-6$$

and $i_{sc} = G_{Ma} * v_i$. The resulting gain is

$$v_o / v_{i1} = G_{Ma} * R_o = (-923.1e-6) * (65e3) = -60V/V$$

(b) For v_{i2} , we have the same output impedance of $R_o = 65k\Omega$

However, for i_{sc} , we now have

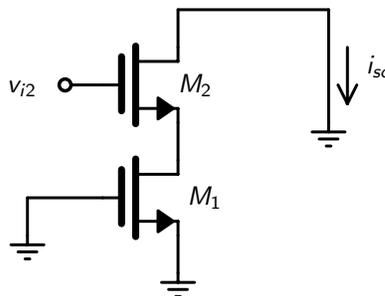

$$G_{Mb} = (-g_{m2} * r_{o2}) / (r_{o2} + (1 + g_{m2} * r_{o2}) * r_{o1}) = -(500e-6) * (10e3) / ((10e3) + (1 + (500e-6) * (10e3)) * (20e3)) = -38.46e-6$$

and $i_{sc} = G_{Mb} * v_i$. The resulting gain is

$$v_o/v_{i2} = G_{Mb} * R_o = (-38.46e-6) * (65e3) = -2.5V/V$$

This result is MUCH smaller than the gain found in (a). This reduction is due to the large resistor value of r_{o1} attached between the source of M_2 and ground and results in a much smaller short circuit current.